

 POLITECNICO DI MILANO



Advanced course on

HIGH RESOLUTION ELECTRONIC MEASUREMENTS
IN NANO-BIO SCIENCE



***Measurements
at a given frequency***
The Lock-in concept



Marco Sampietro




Small bandwidth \Rightarrow Low noise

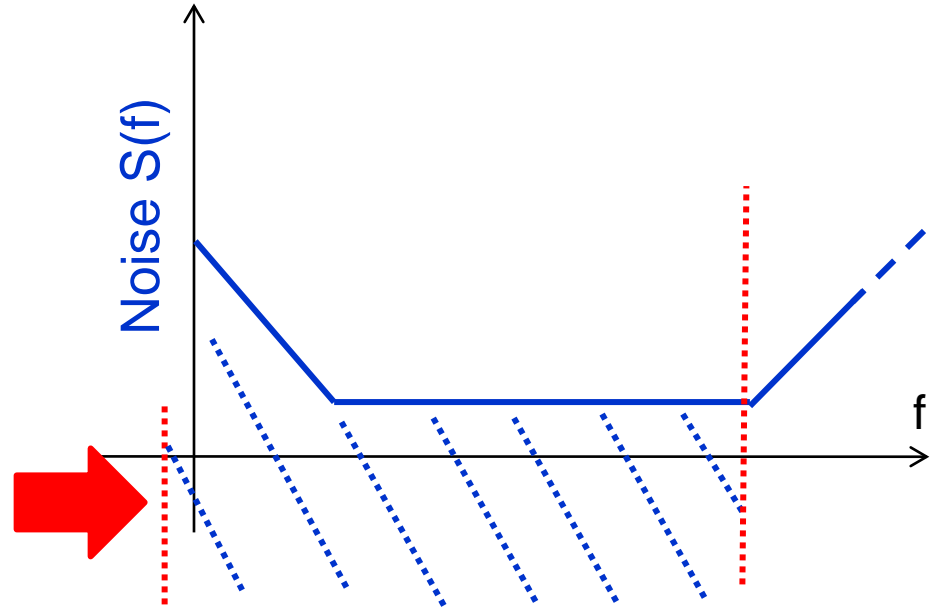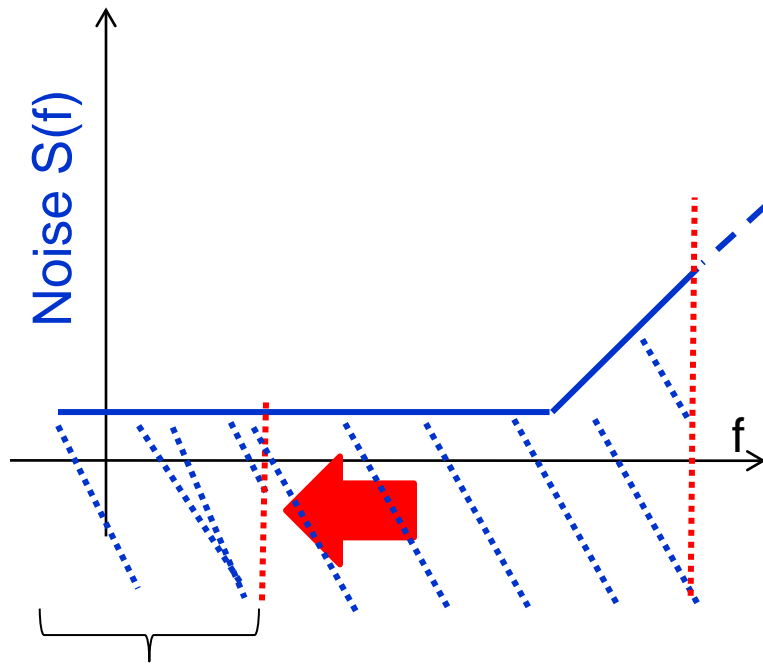


Small BW \Rightarrow small noise



... small bandwidth at high frequency

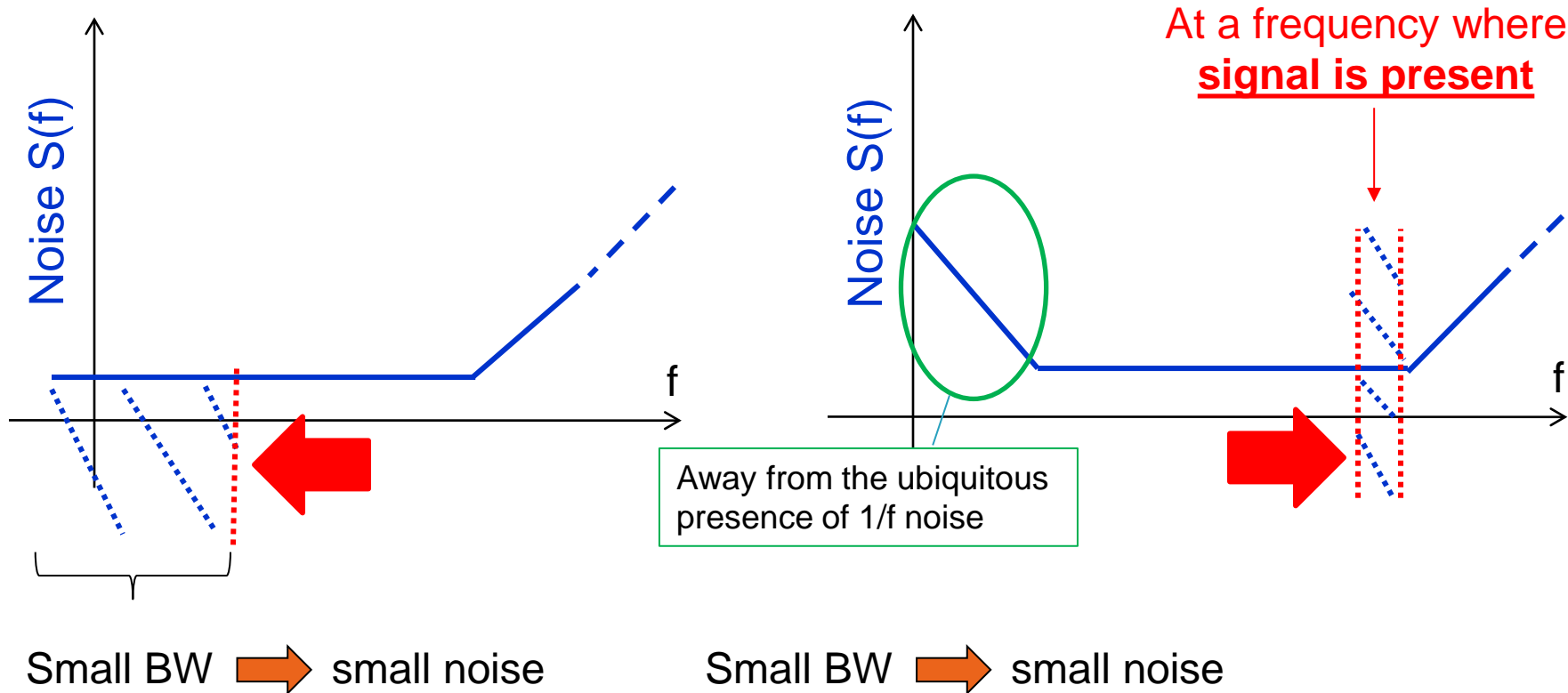


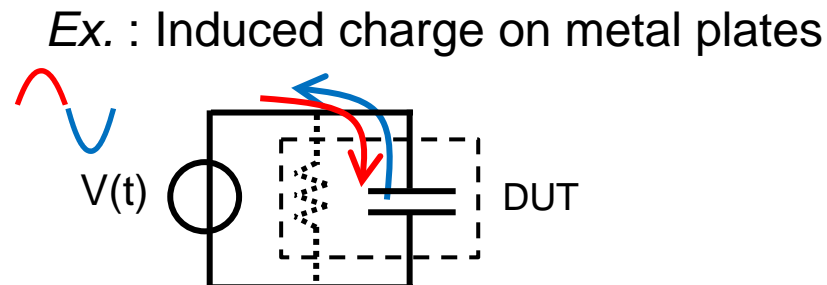A repeated measurement at high frequency needs **"RECHARGEABLE"** events
(AC electronic devices, reversible redox, pump&probe, ...)





Example : measurement of R

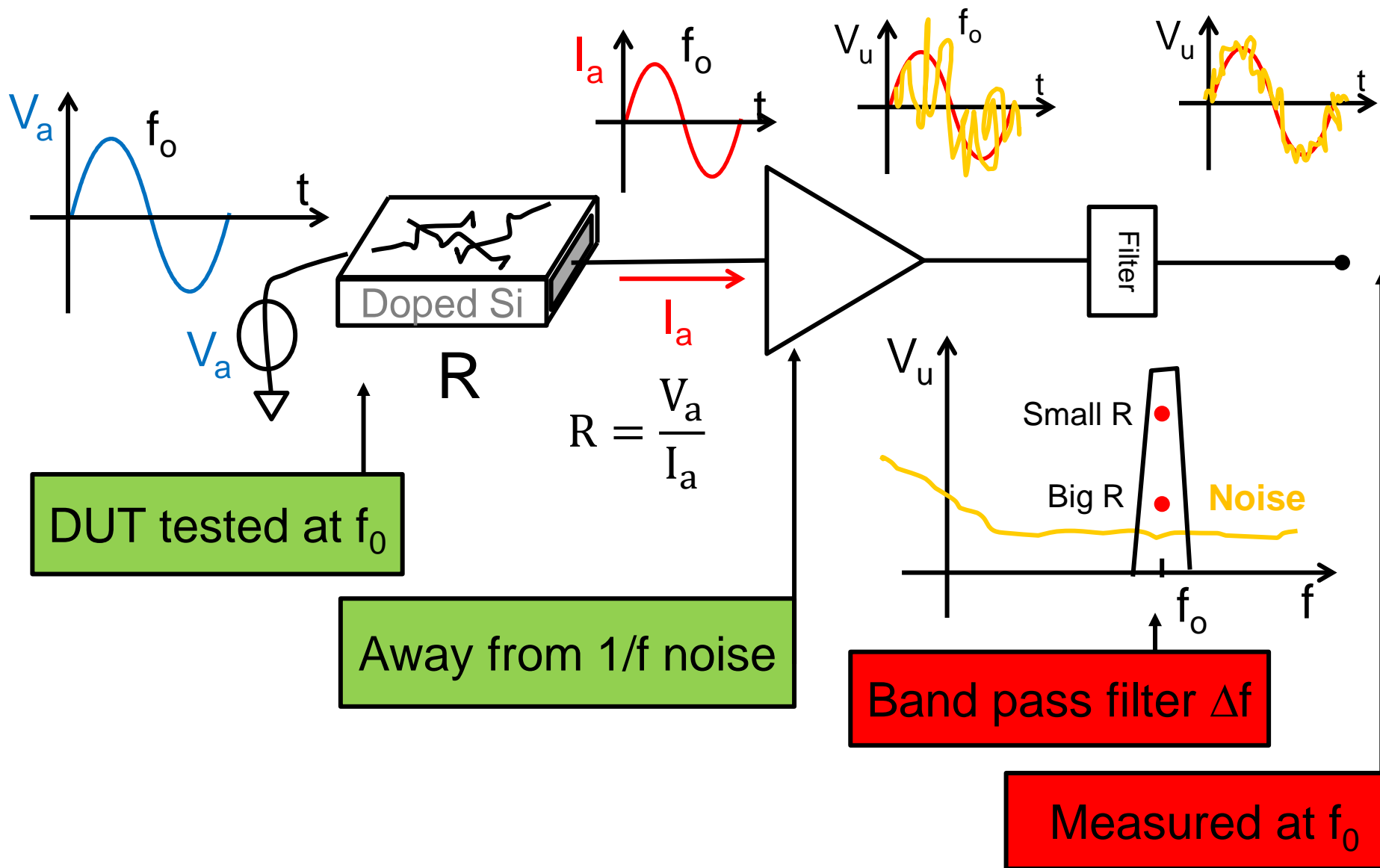




Outline of the lesson

- The Lock-in concept 20 min
- Performance in sensitivity 20 min




The LOCK-IN idea

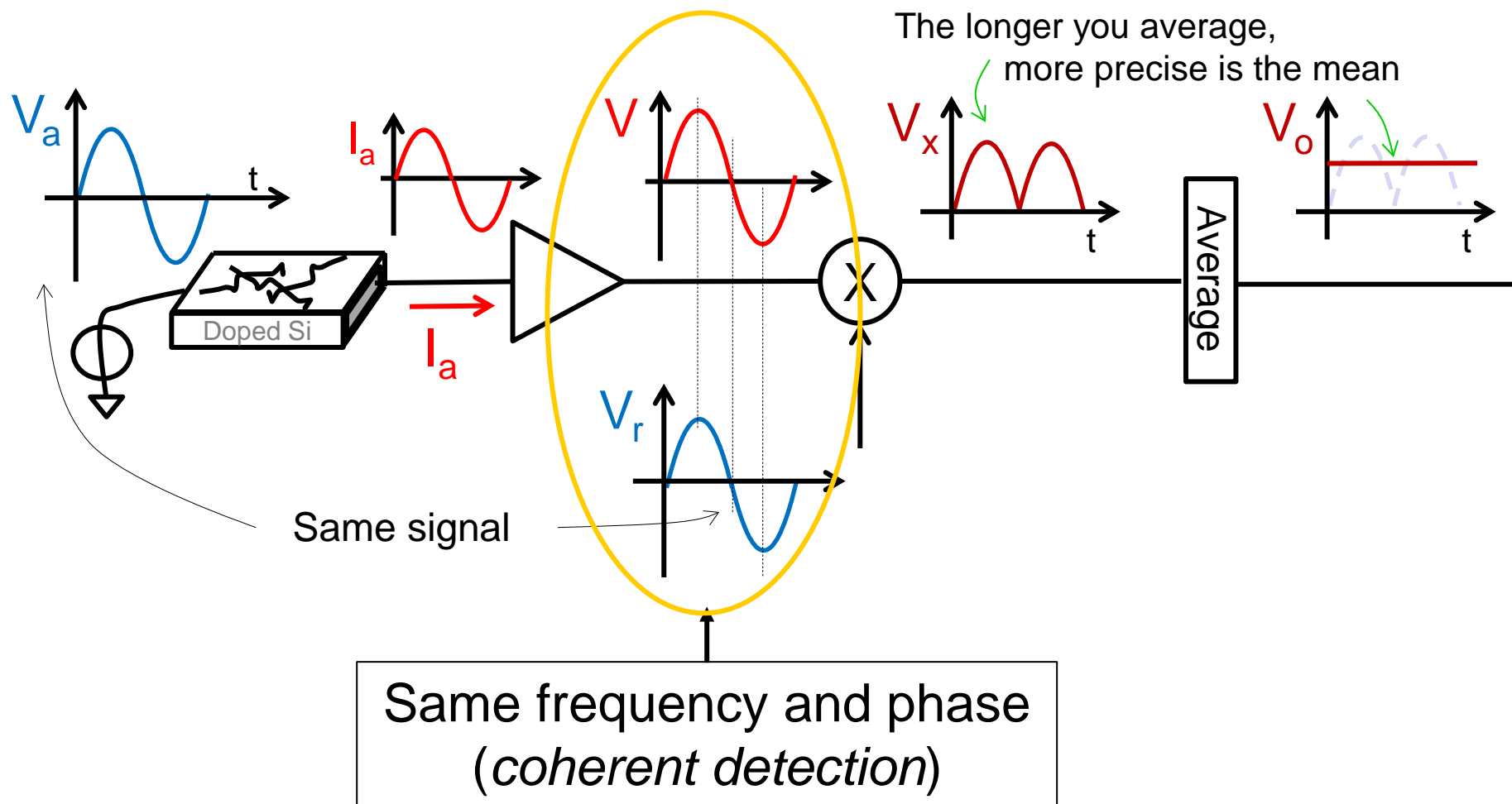




The LOCK-IN idea

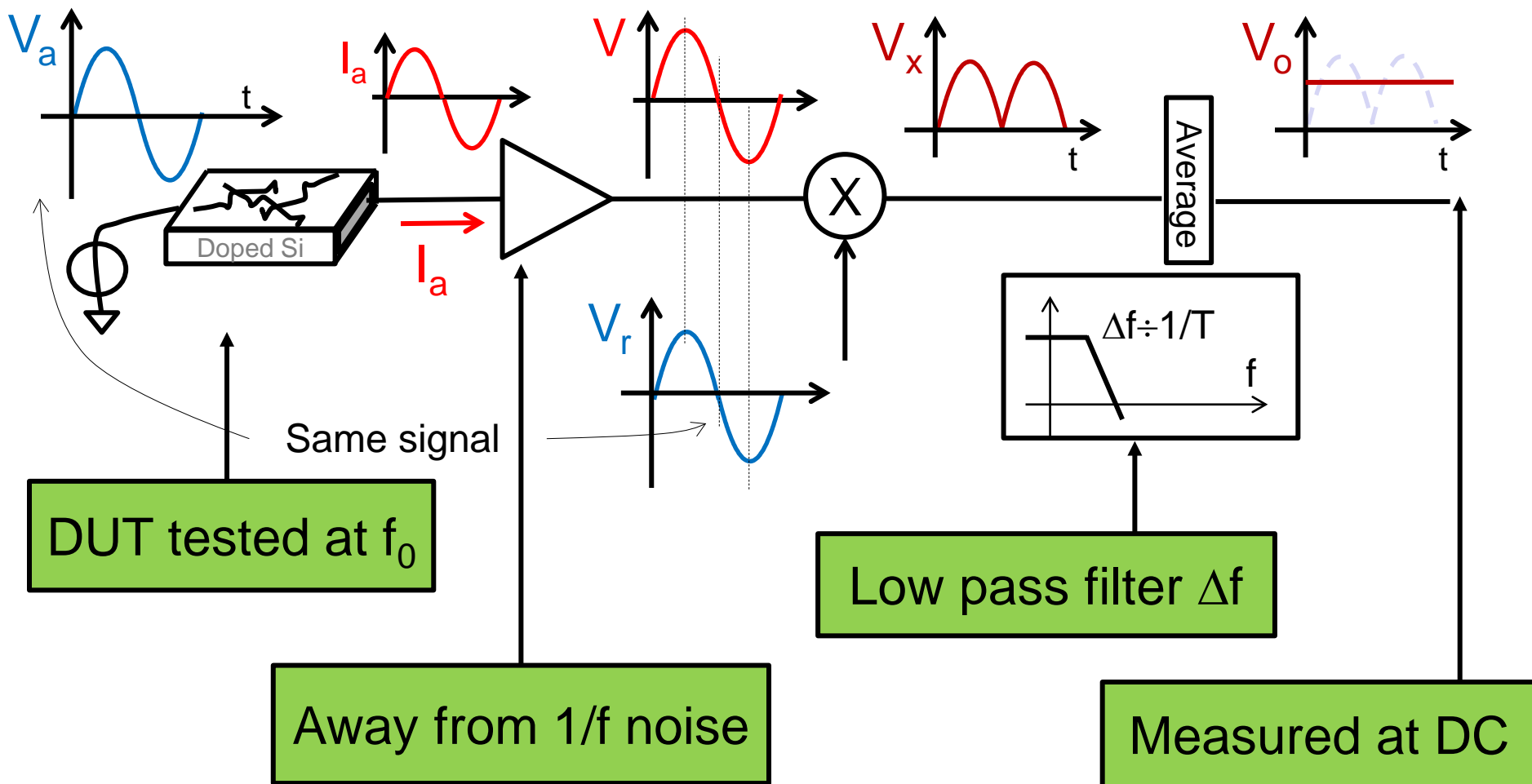

Credited to Robert Dicke, founder of Princeton Applied Research (PAR) in the 1960's.




Tracking sensor with the LOCK-IN

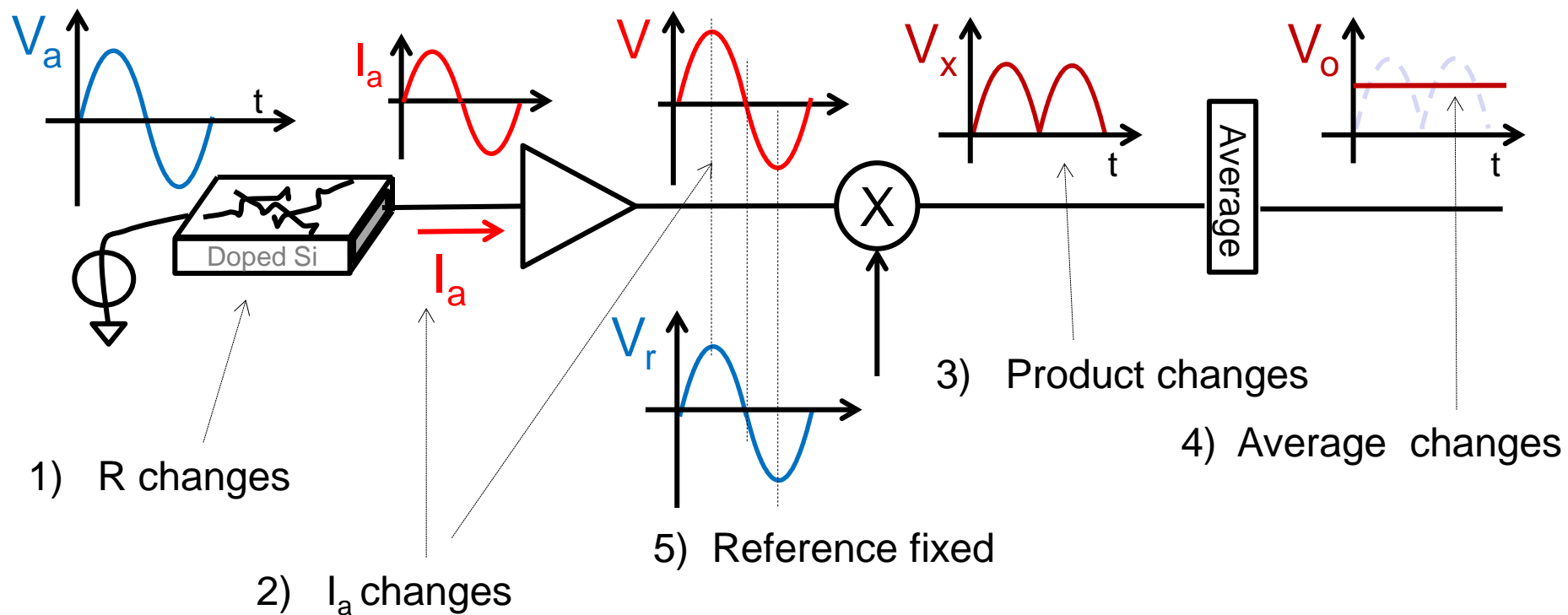

DUT variations can be tracked with time by simply monitoring the level of the output



Phase selectivity of the Lock-in

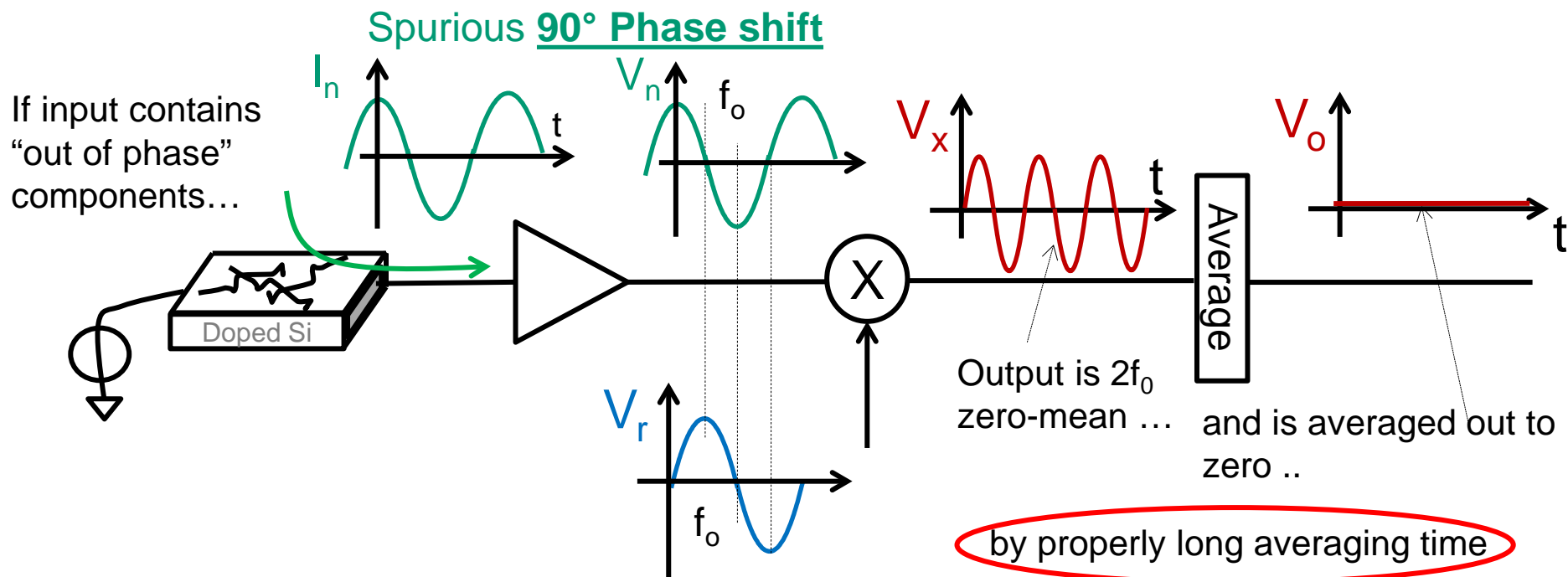

Small bandwidth \rightarrow Long averaging time \rightarrow High rejection of «spurious»


Long measurement time \downarrow Low noise

Signals with 90° ***phase-shift*** to reference are rejected



Frequency selectivity of the Lock-in

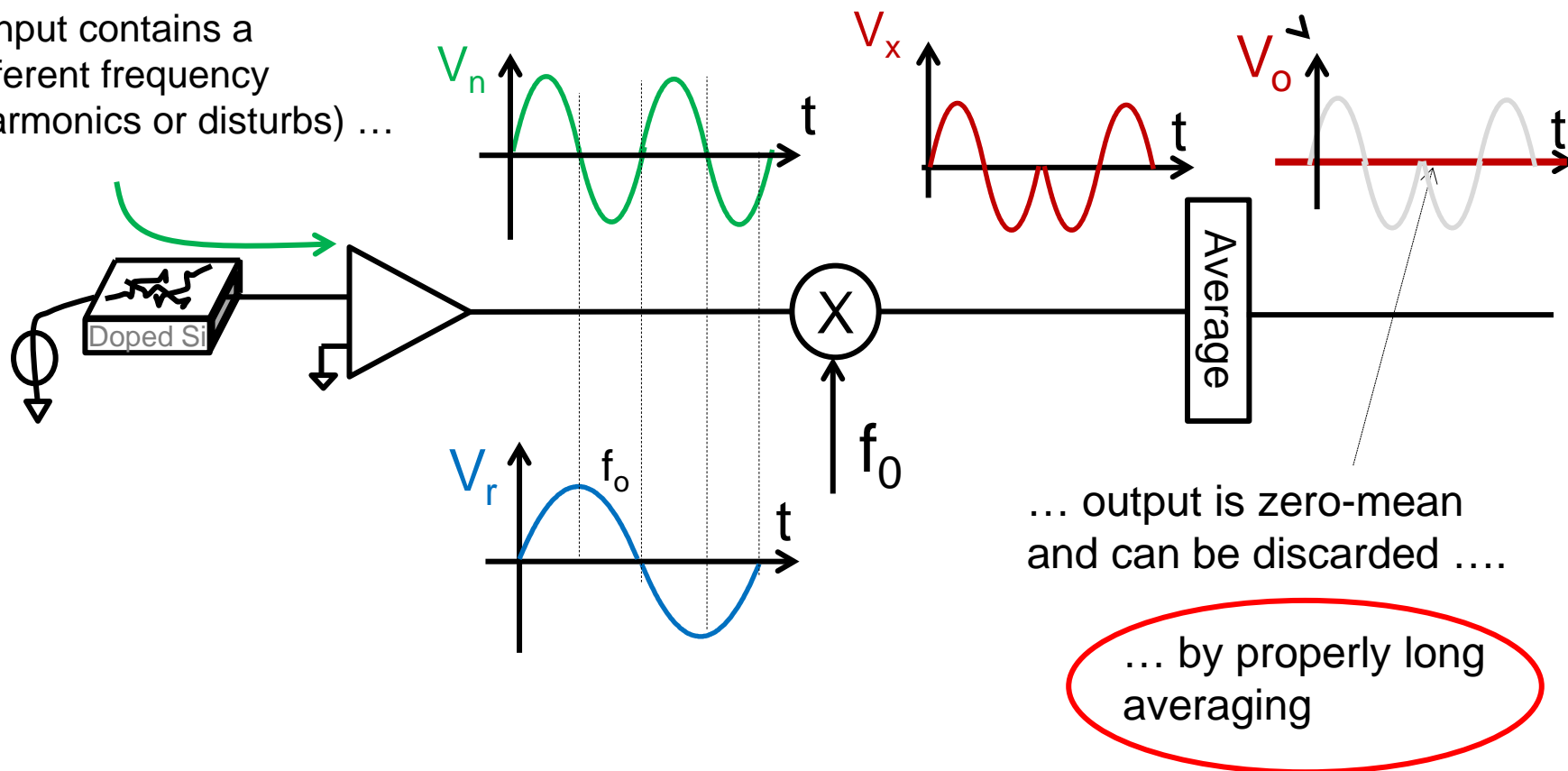If input contains a different frequency (harmonics or disturbs) ...







Signals with different frequency to reference are rejected




Noise suppression

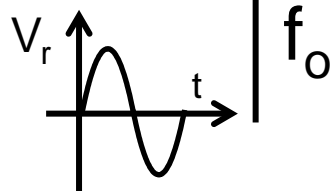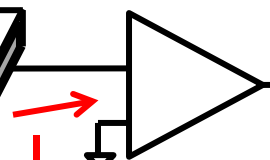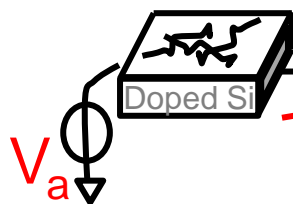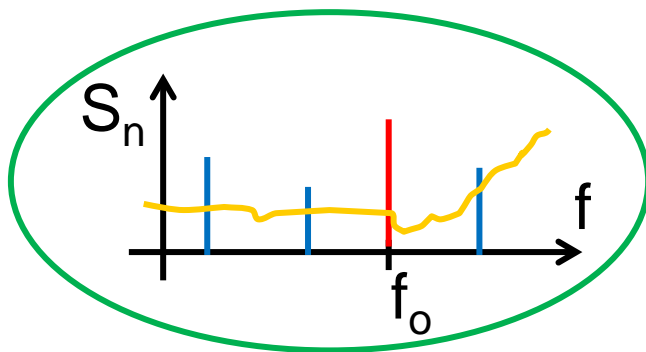
Spectrum of experiment
(*input* + *noise* + *disturbs*)




Reference in phase with *input*

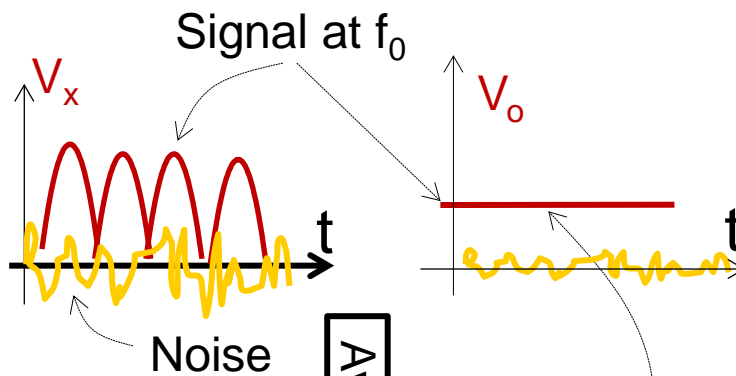

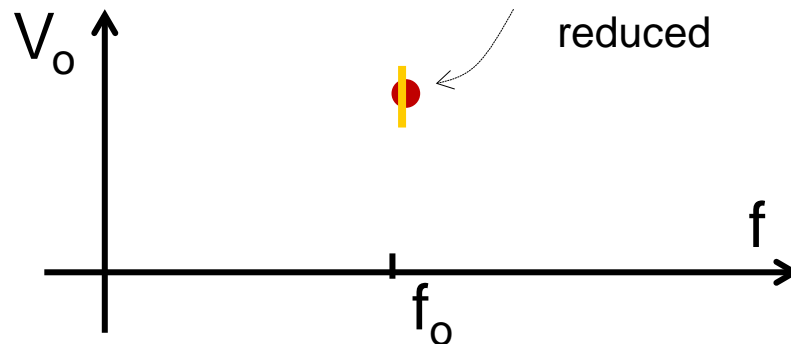f_0 signal is converted
in a DC signal.
All others are
reduced




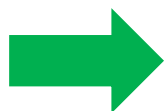NOISE is REDUCED
provided a long time for averaging
SIGNAL is EXTRACTED





Analytical view - Signal

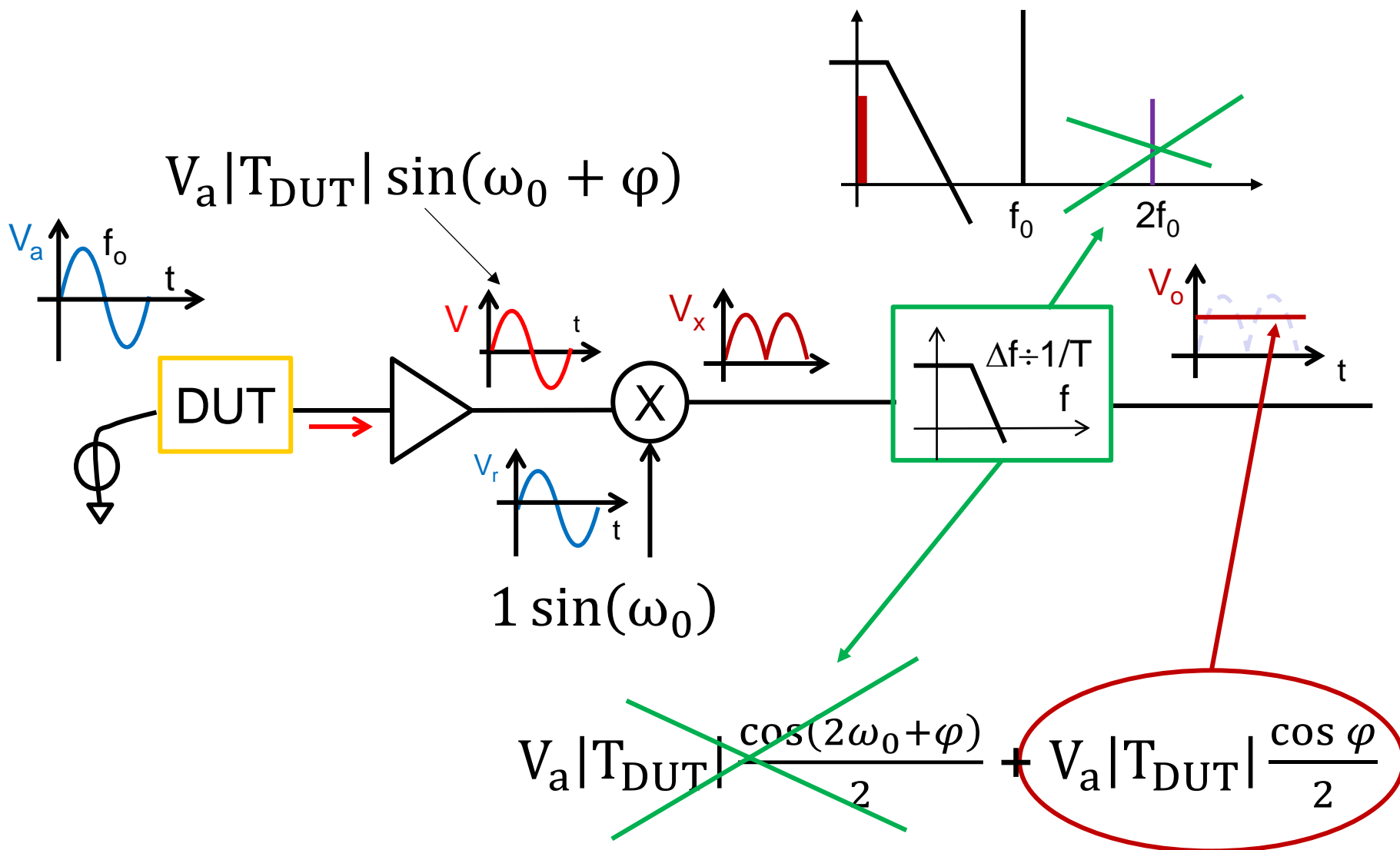




Analytical view - Power

$$P_{in} = \frac{(V_a |T_{DUT}|)^2}{2}$$

$$P_{out} = \left(V_a |T_{DUT}| \frac{\cos \varphi}{2} \right)^2$$

$$V_a |T_{DUT}| \sin(\omega_0 + \varphi)$$

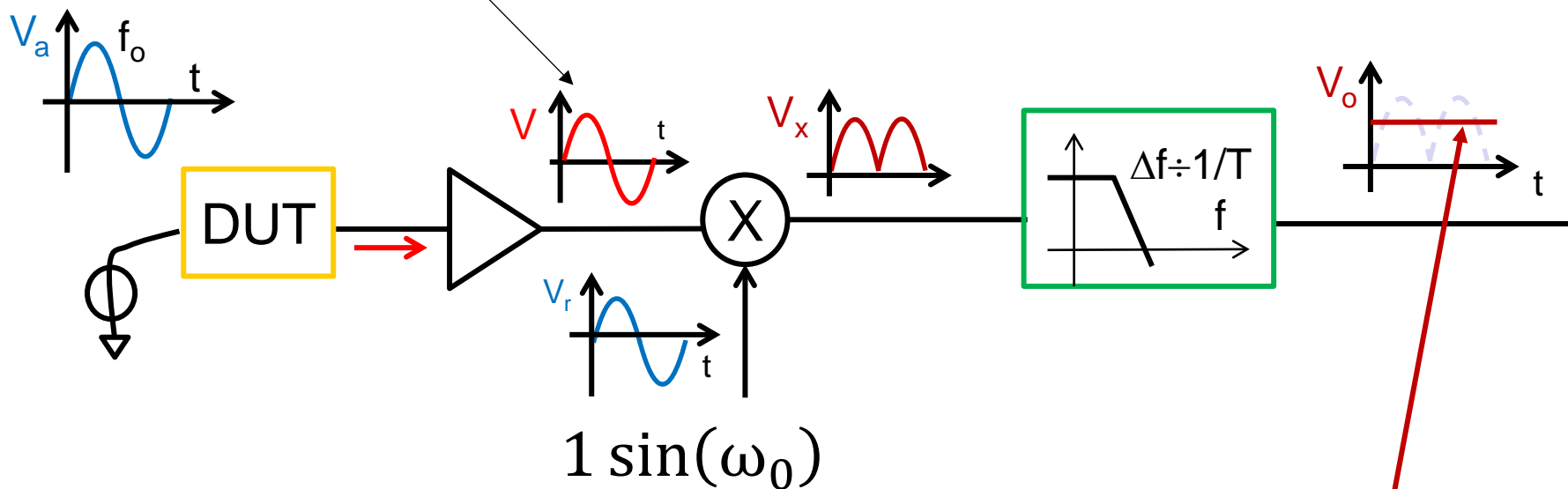


$$V_a |T_{DUT}| \frac{\cos \varphi}{2}$$



Signal to Noise RATIO

$$P_{in|signal} = \frac{(V_a |T_{DUT}|)^2}{2} \quad \boxed{\frac{1}{2}} \quad P_{out|signal} = \left(V_a |T_{DUT}| \frac{\cos \varphi}{2} \right)^2$$

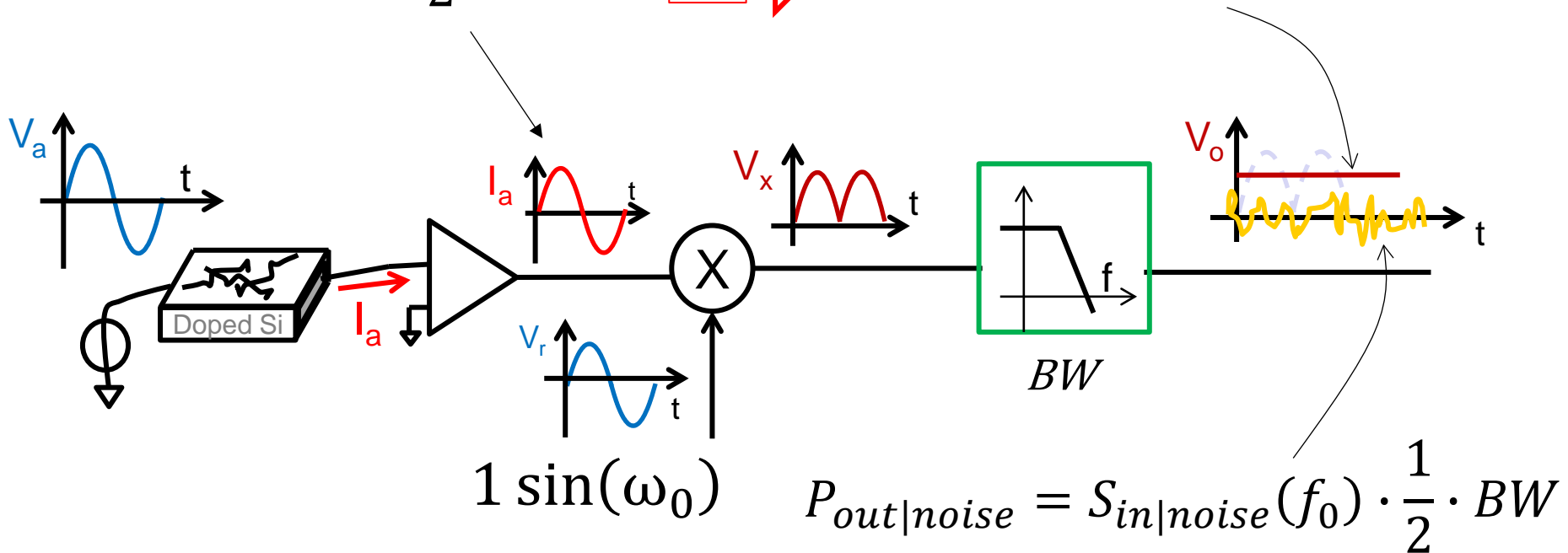

$$\frac{P_{in|signal}}{P_{in|noise}} = \frac{P_{in|signal} \cdot \cancel{\frac{1}{2}}}{S_{in|noise}(f_0) \cdot \cancel{\frac{1}{2}} \cdot BW} = \frac{P_{out|signal}}{P_{out|noise}}$$

same BW of the lock-in around f_0


The Lock-in can be considered an optimal detector of AC signals



Lock-In Noise Filtering

$$\frac{P_{in|signal}}{P_{in|noise}} = \frac{P_{in|signal}}{S_{in|noise}(f_0) \cdot BW}$$

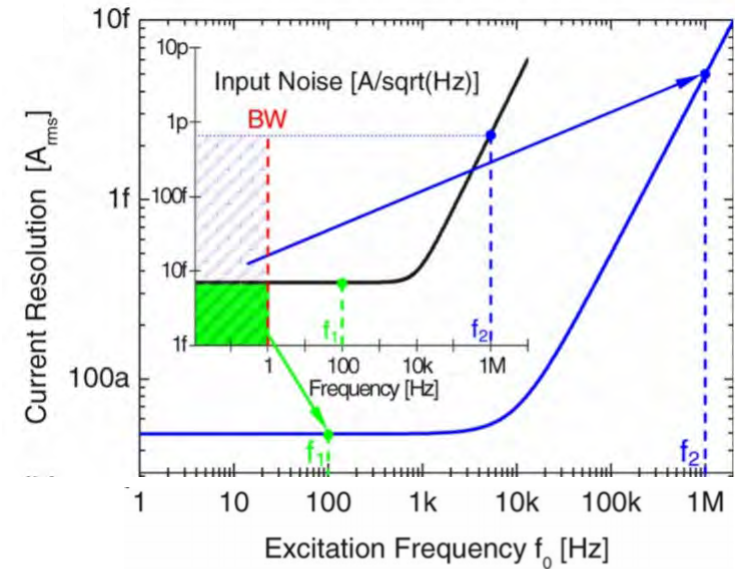- The modulation *whiten* the noise spectrum in base band at the value sampled at f_0
- The order of the filter is not critical for the noise (a first order is ok even with non-white noise)
- The filter has to properly cut the $2f_0$ component






Outline of the lesson

- The Lock-in concept 20 min
- Performance in sensitivity 20 min




Limit of sensitivity : Noise Analysis

A recap of the input noise of the TIA :

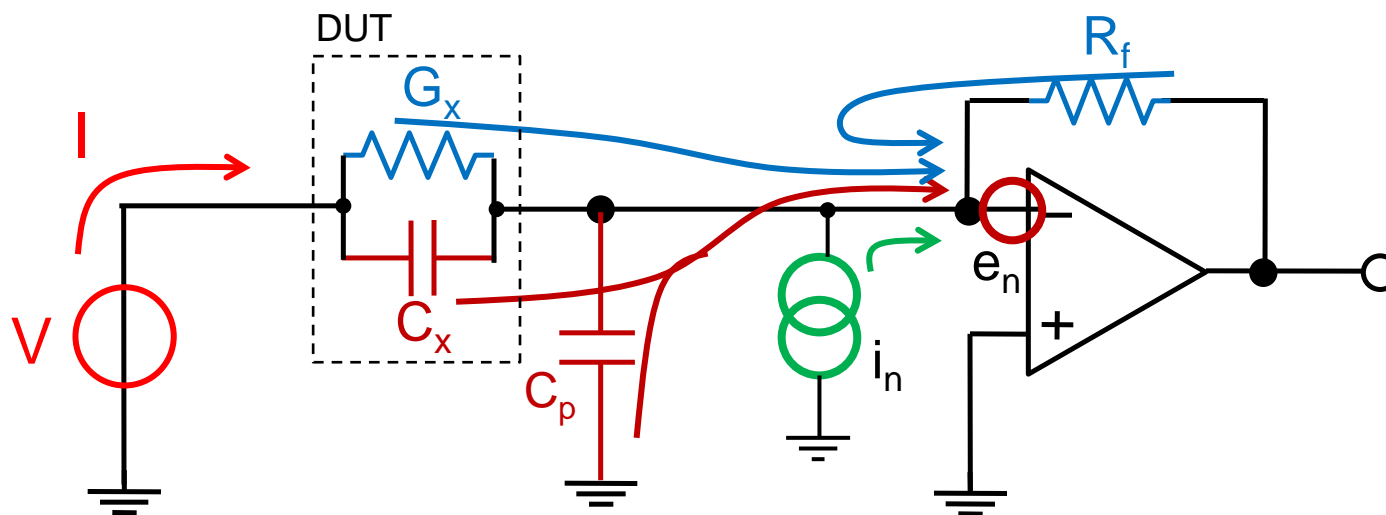


$$S_i = \overline{i_n^2} + 4kT(G_x + G_f) + \overline{e_n^2} \omega^2 (C_x + C_p)^2 + \overline{e_n^2} (G_x + G_f)^2$$

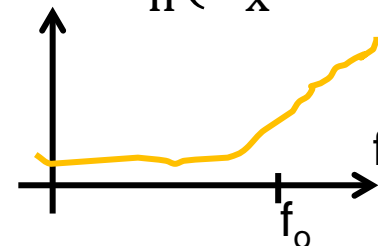To be compared with the **Signal** (V, I)



Limit of sensitivity - for R

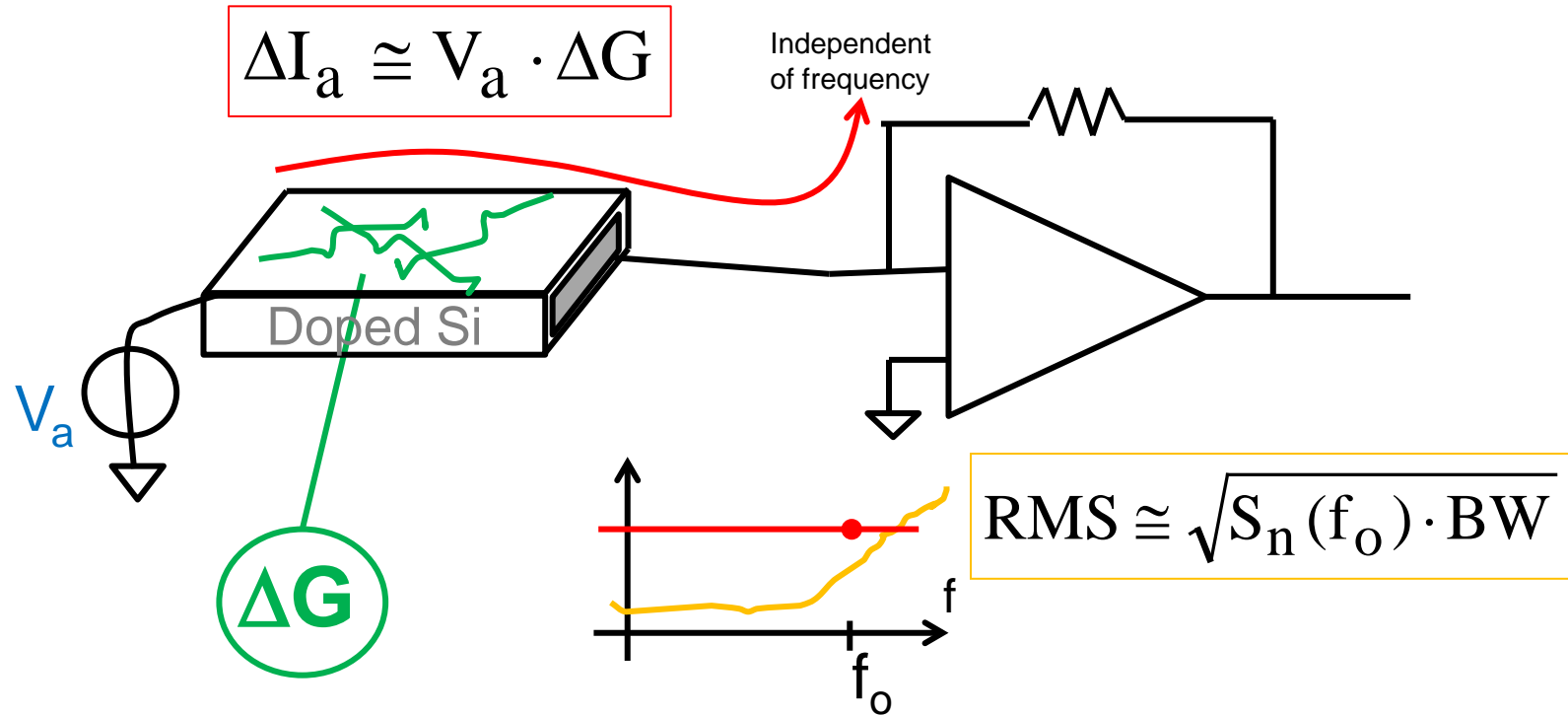


The limit of detection is reached when

$$\Delta I_a \cong \text{RMS}$$



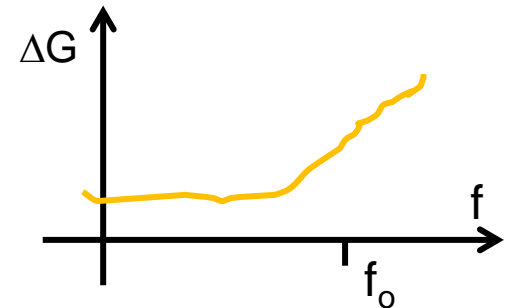
$$\Delta G \cong \frac{\sqrt{S_n(f) \cdot BW}}{V_a}$$




$$e_n = \frac{5nV}{\sqrt{Hz}}, i_n = \frac{10fA}{\sqrt{Hz}}, V_{ac} = 100mV, C_p = 5pF, C_x \ll C_p$$


Good mounting

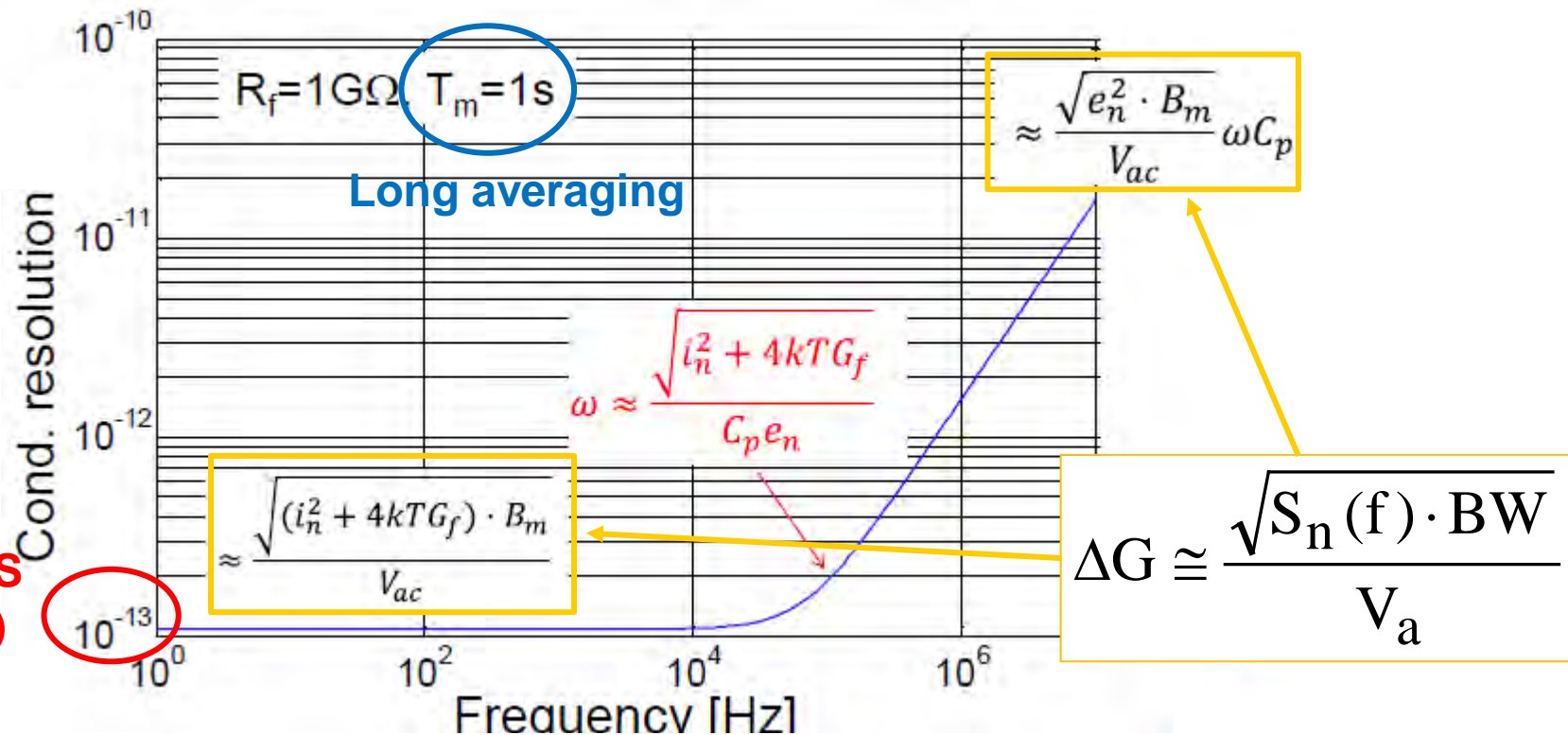


$$S_i = \overline{i_n^2} + 4kT(G_x + G_f) + \overline{e_n^2} \omega^2 (C_x + C_p)^2 + \overline{e_n^2} (G_x + G_f)^2$$



Sinusoidal measurement of C

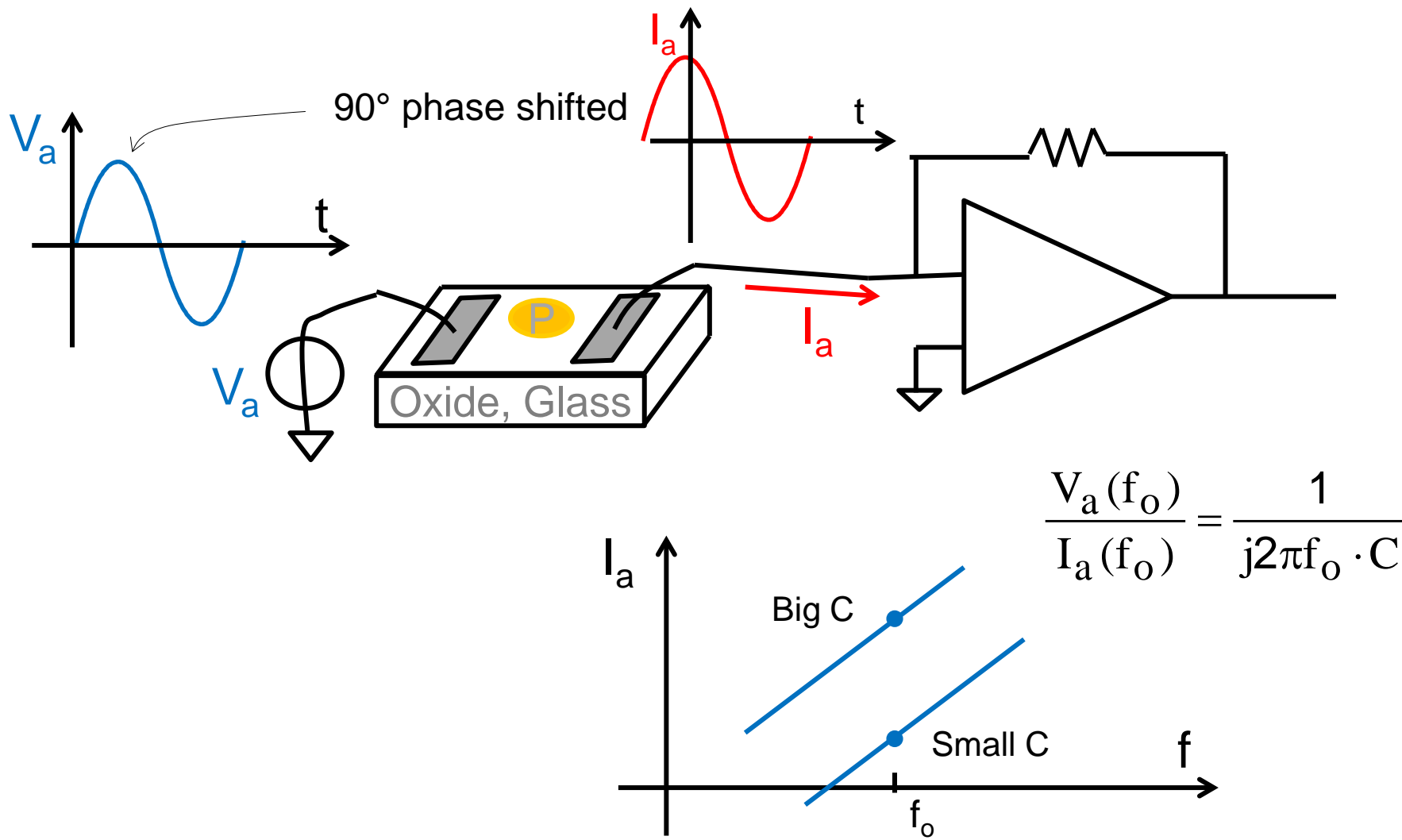

Limit of sensitivity - for C

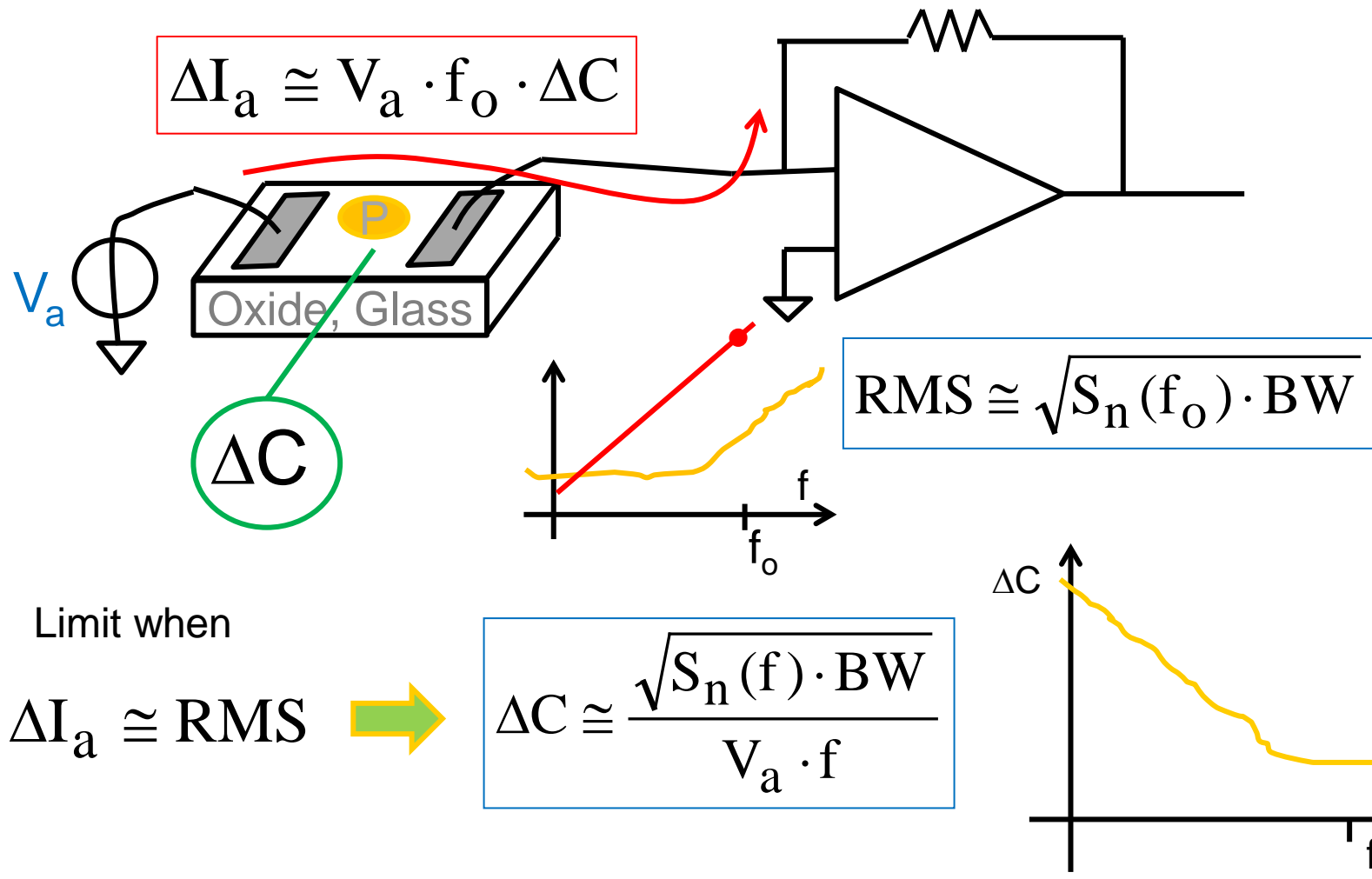




Limit of sensitivity - for C

Still margin of improvement (see next slide) !

$$e_n = \frac{5nV}{\sqrt{Hz}}, i_n = \frac{10fA}{\sqrt{Hz}}, V_{ac} = 100mV, C_p = 5pF, C_x \ll C_p$$




Good electronics

Good mounting

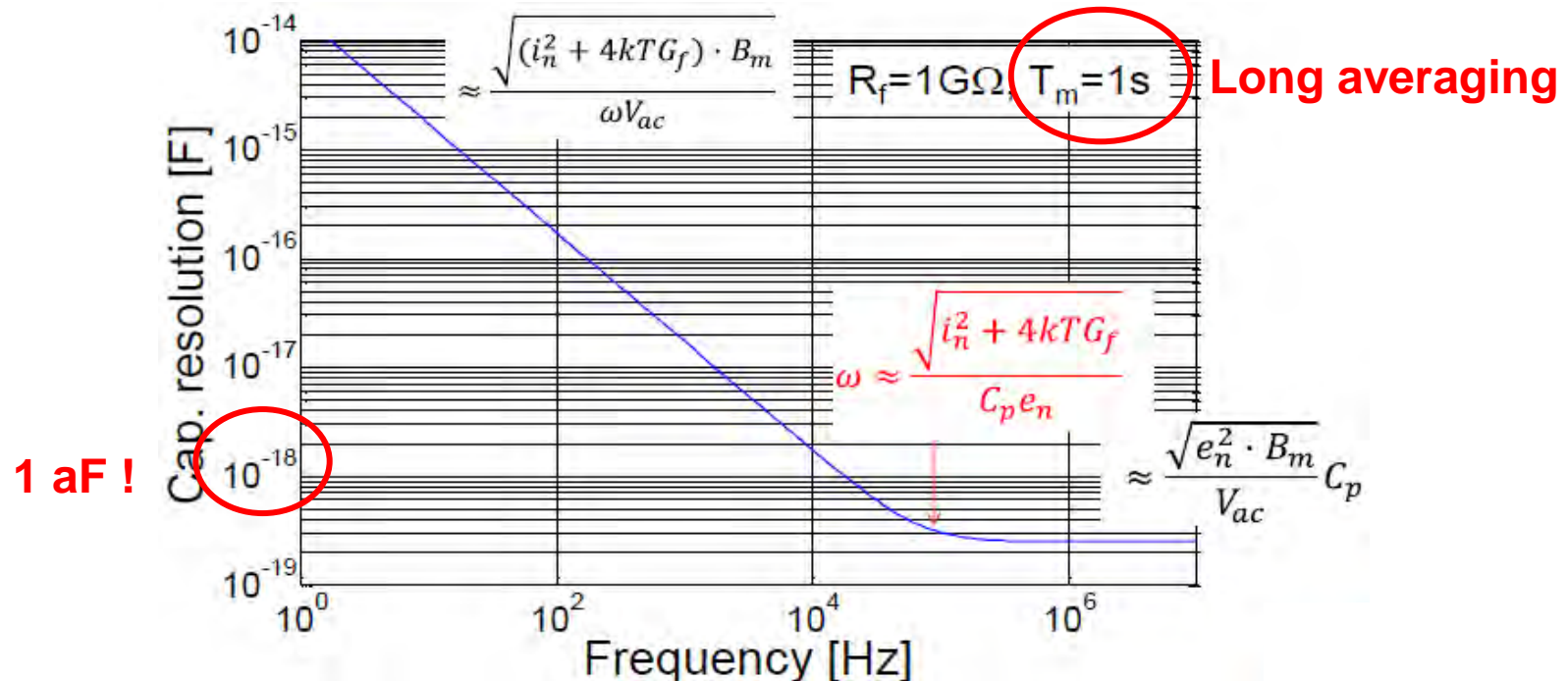





Improvement with Voltage amplitude

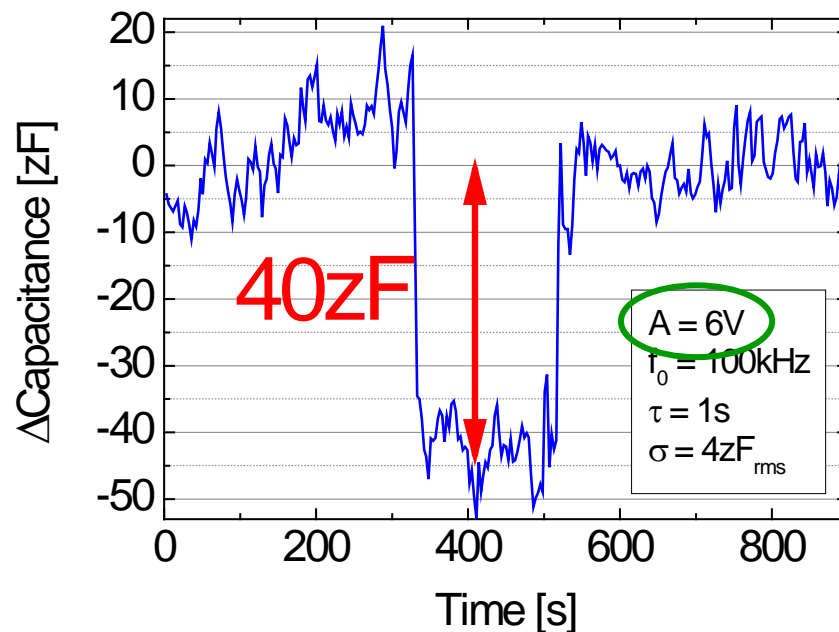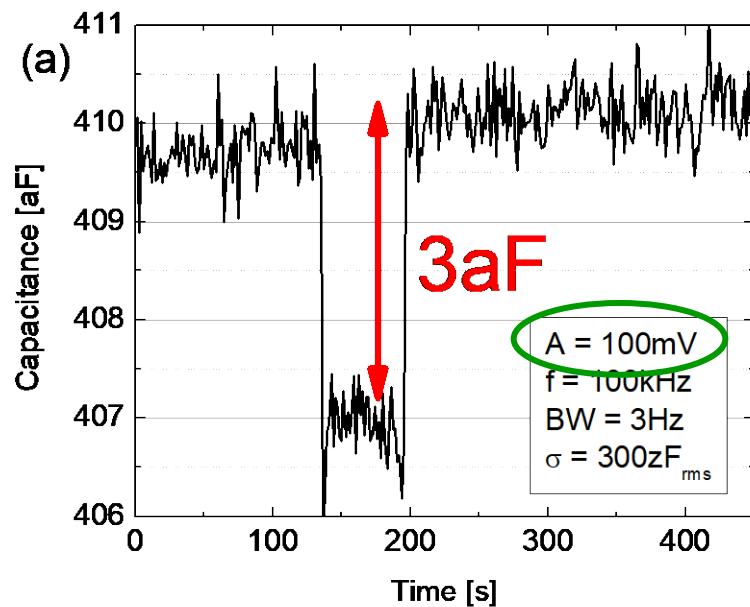
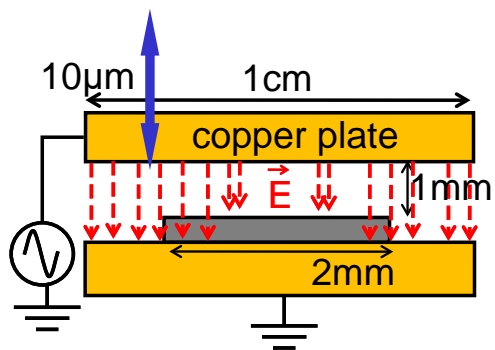




Special TIA for square wave mixer

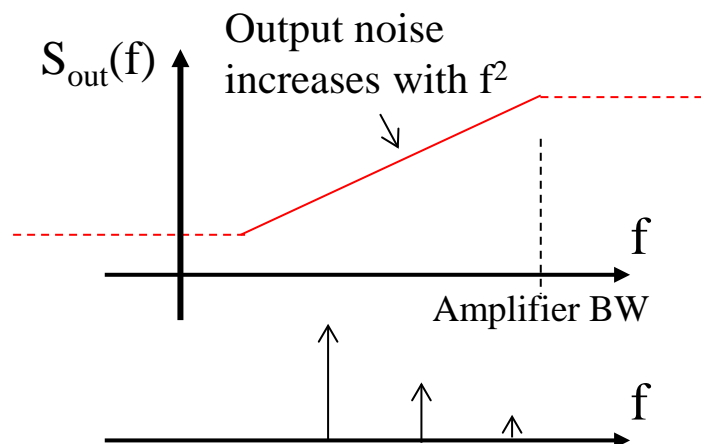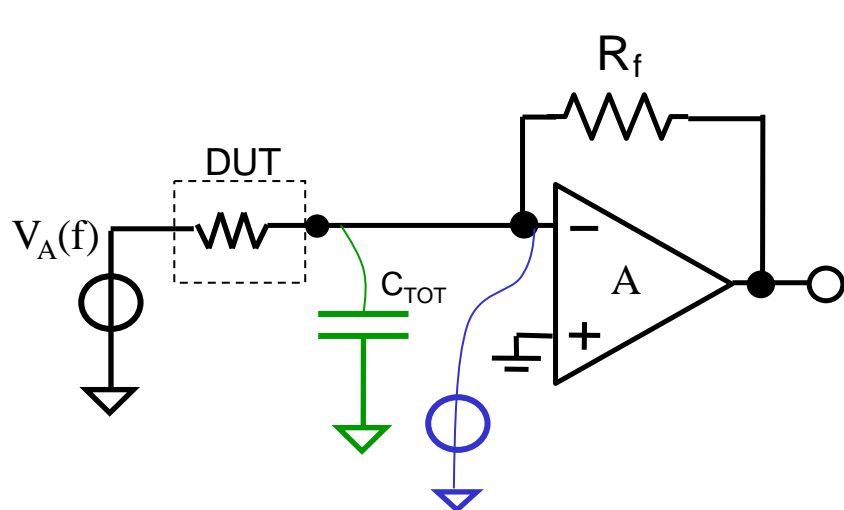

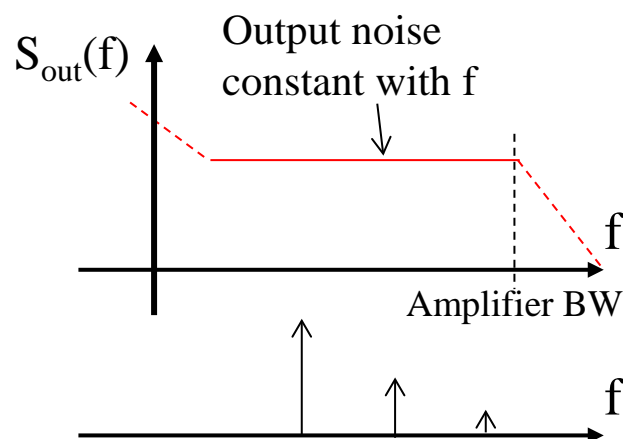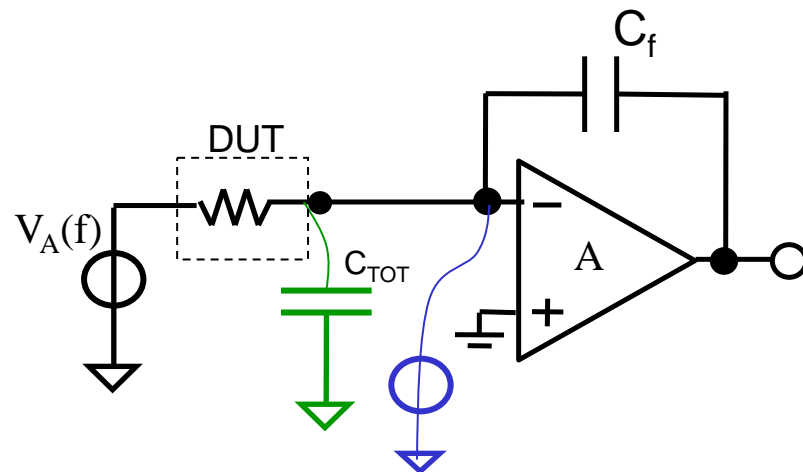If a square wave mixer is used, it introduces harmonics that fold a lot of noise



If a square wave mixer is used, higher harmonics give little noise




In conclusion ...




Things to remember (1)

A Lock-in amplifier is «like» a band-pass filter at f_0

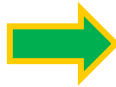Longer averaging  Thinner bandwidth
(around f_0)

$$T_{av}=1s$$


$$BW = \frac{1}{T_{av}} = 1 \text{ Hz}$$

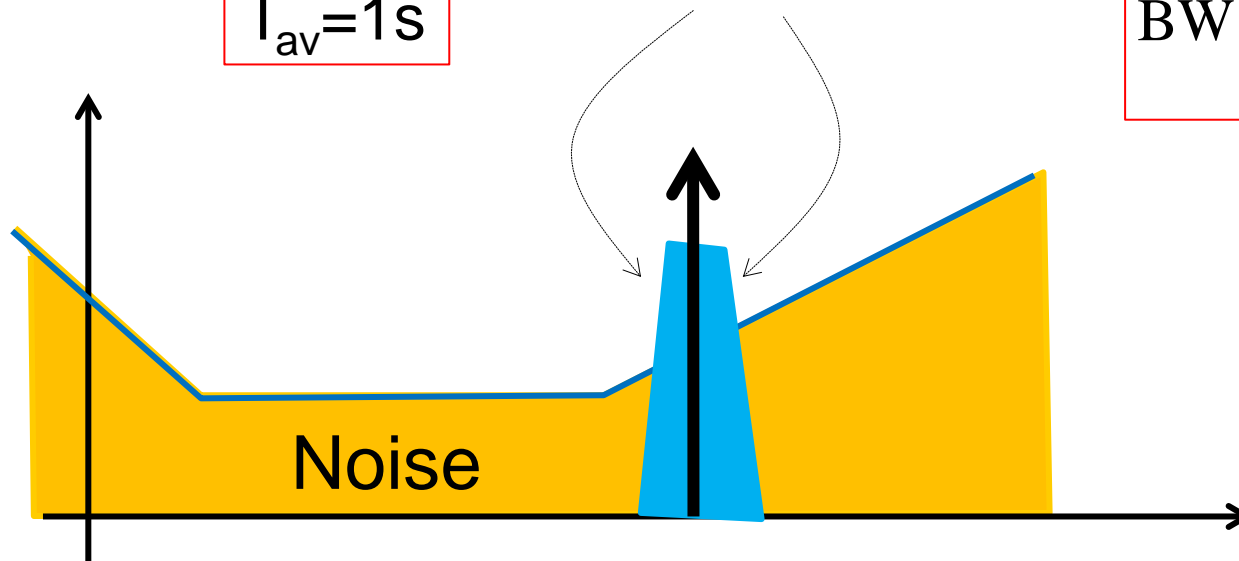

By changing measurement frequency f_0 , you can choose the optimal position



Things to remember (2)

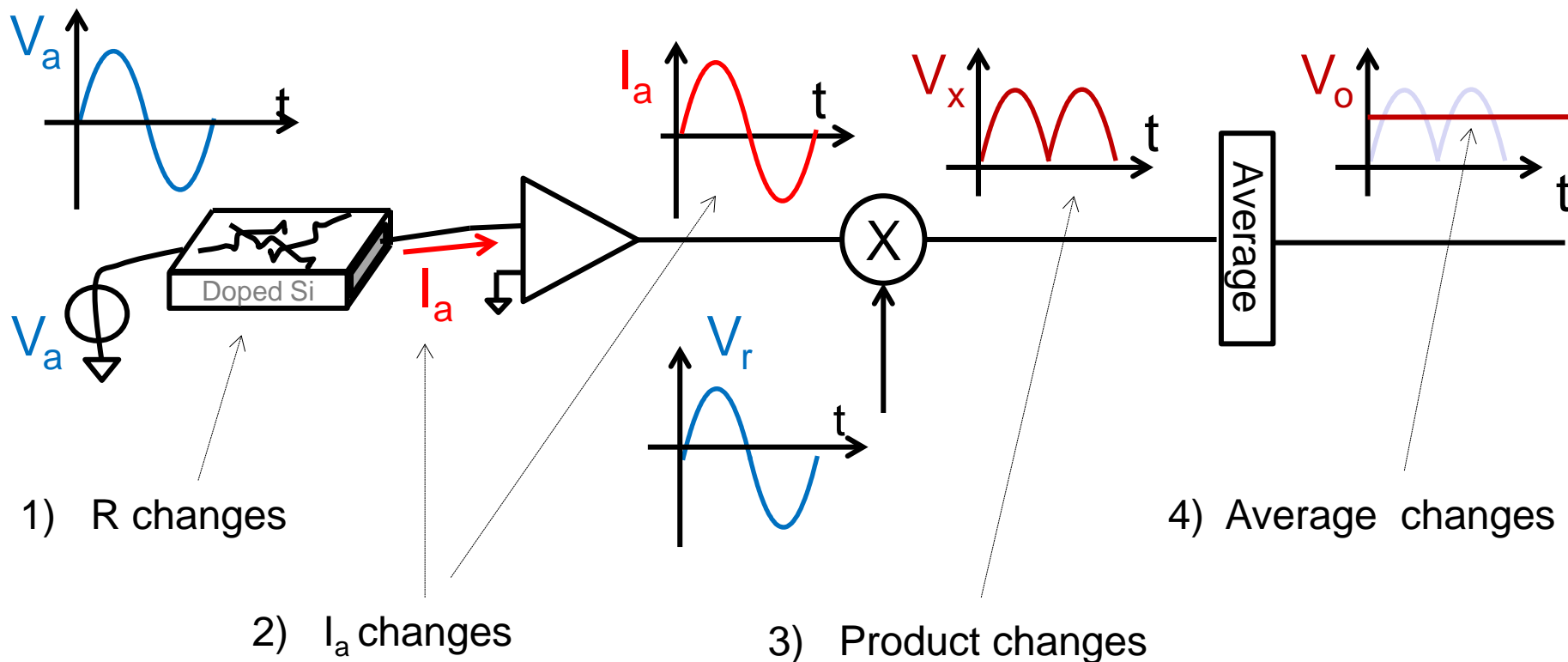

Signal variations can be tracked with time by simply monitoring the level of the output



Things to remember (3)

Extremely high sensitivity can be reached in device characterisation

