



I³N *Innovative
Integrated
Instrumentation
for Nanoscience*



POLITECNICO
MILANO 1863

High Resolution Electronic Measurements in Nano-Bio Science

High-resolution measurements

Sub-ppm measurements using lock-in amplifiers

Giorgio Ferrari

Milano, June, 2025

OUTLOOK of the LESSON



- Introduction to the problem
- Noise sources limiting high-resolution measurements:
 - Additive noise sources
 - Multiplicative noise sources
- Solutions:
 - Ratiometric technique
 - ELIA: Enhanced Lock-In Amplifier
 - Differential approach

Thursday
lesson

Definitions (assuming a linear response for simplicity)

S = quantity to be measured

Sensor + electronics response:

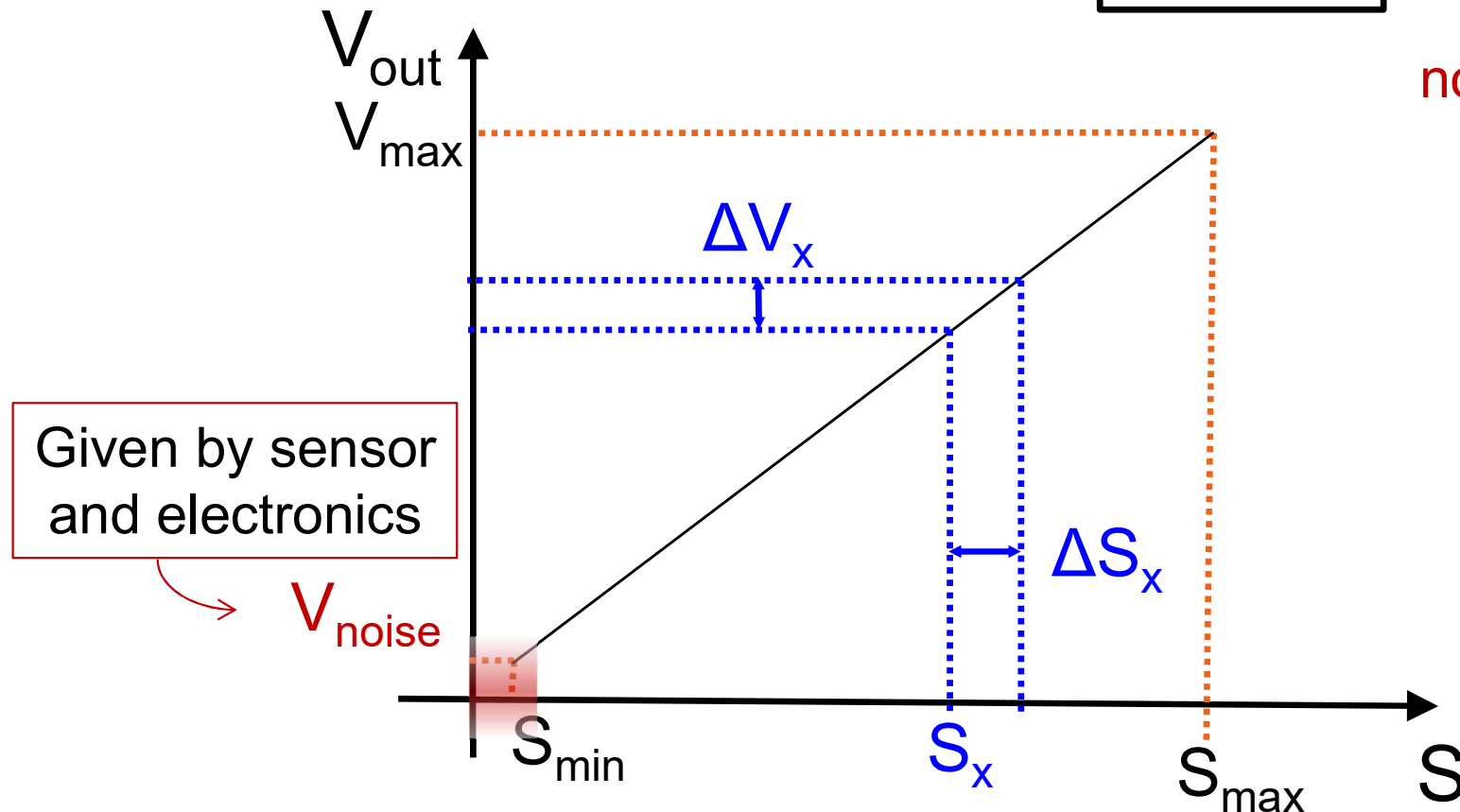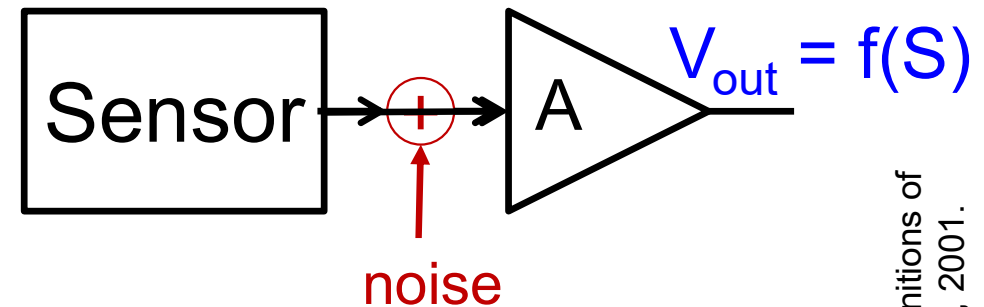

Minimum detectable signal (limit of detection): $S_{\min}$


Resolution: minimum detectable variation ΔS_x

Relative resolution: $\Delta S_x / S_x$ (ppm – parts per million)

Why resolution is important

Marco Sampietro's lesson on impedance:


Impedance at the Nanoscale

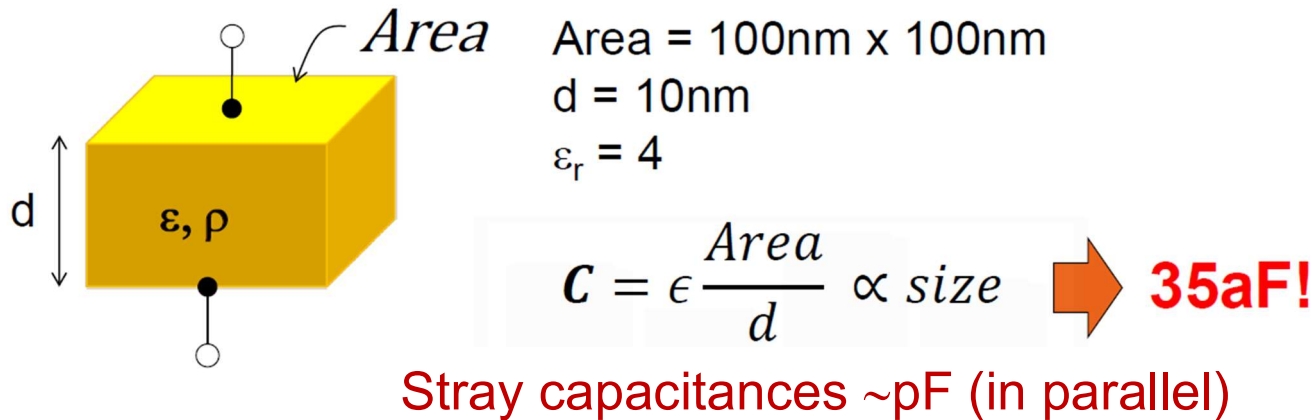

aF variations on
pF baseline
(see Fumagalli's
lessons)

Francesco Zanetto's lesson on transparent detection of light:



CLIPP sensor:

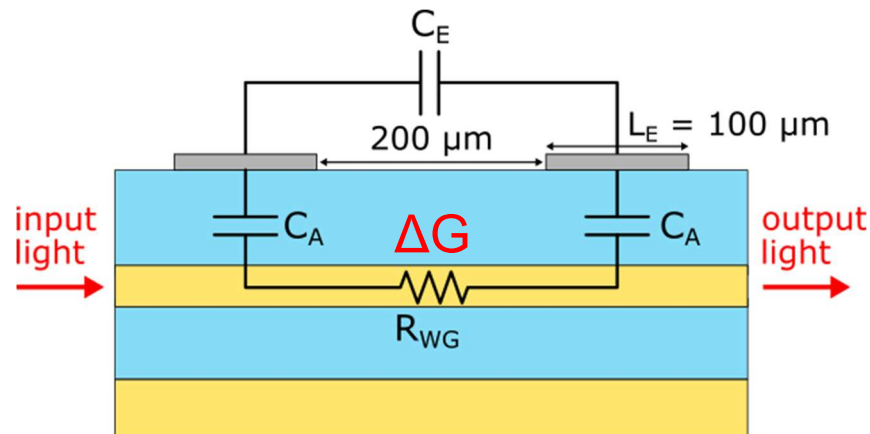

pS variations
on μS baseline

The problem of the lesson

Sensor + electronics response:

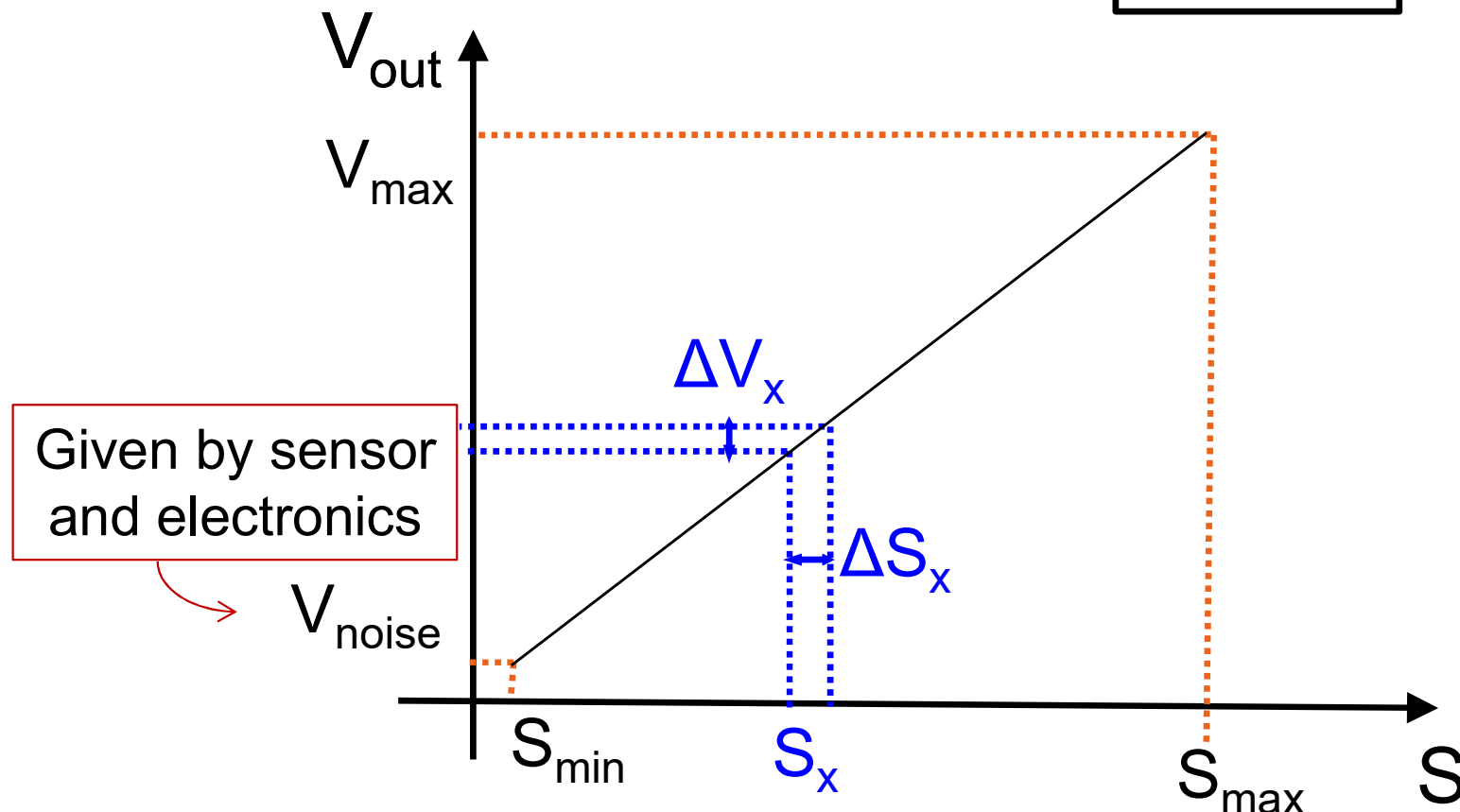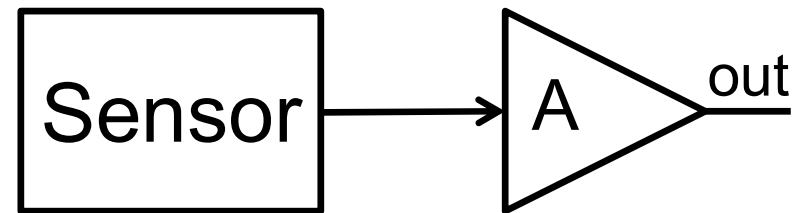


Resolution: minimum detectable variation ΔS_x

What are the limiting factors of the resolution?

Input-referred noise of the electronics


Sensor + electronics response:

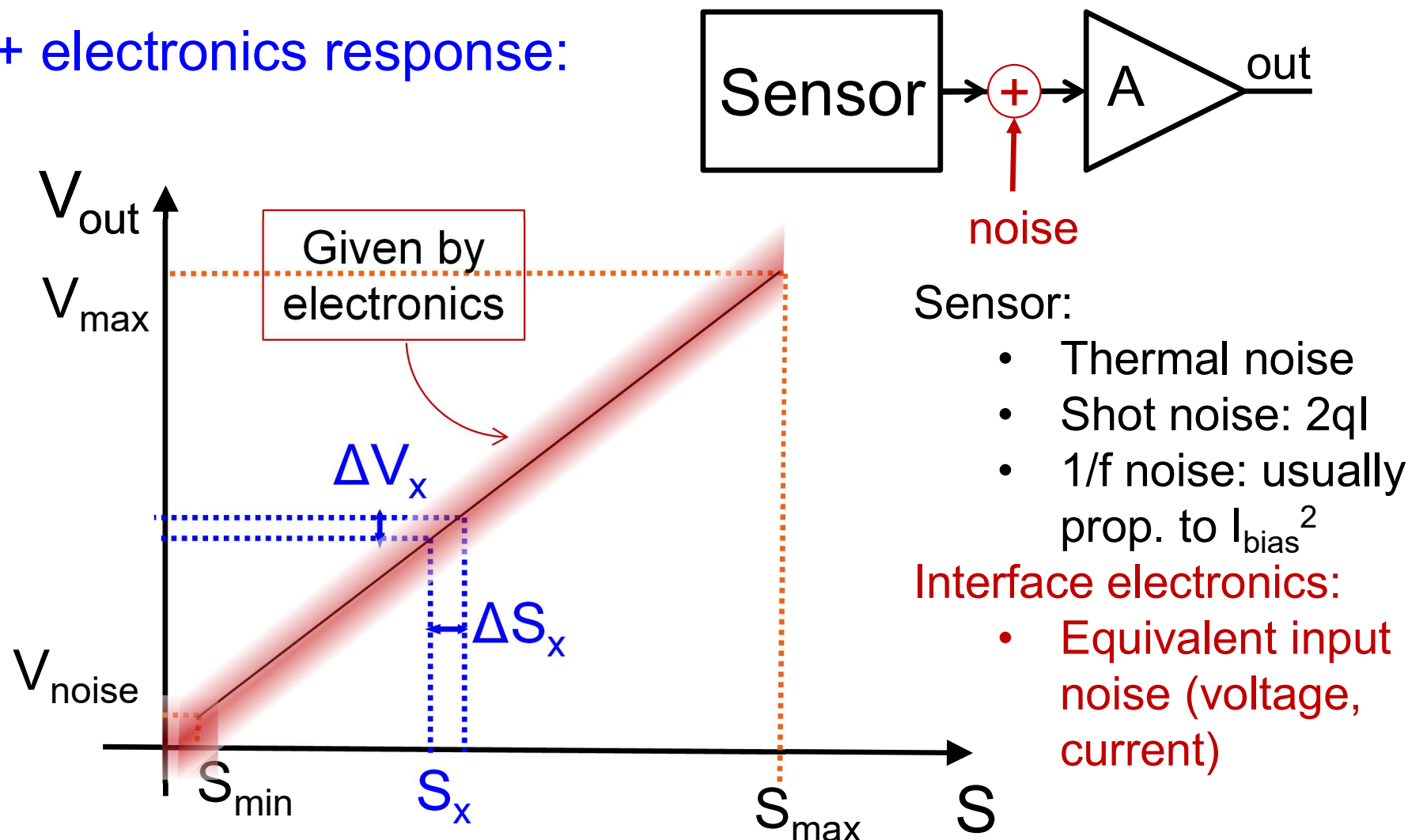

Equivalent input noise of the interface electronics:

- Usually independent from S_x for a fixed gain
- Set the minimum detectable signal and the best resolution

Capacitive sensor: a case study

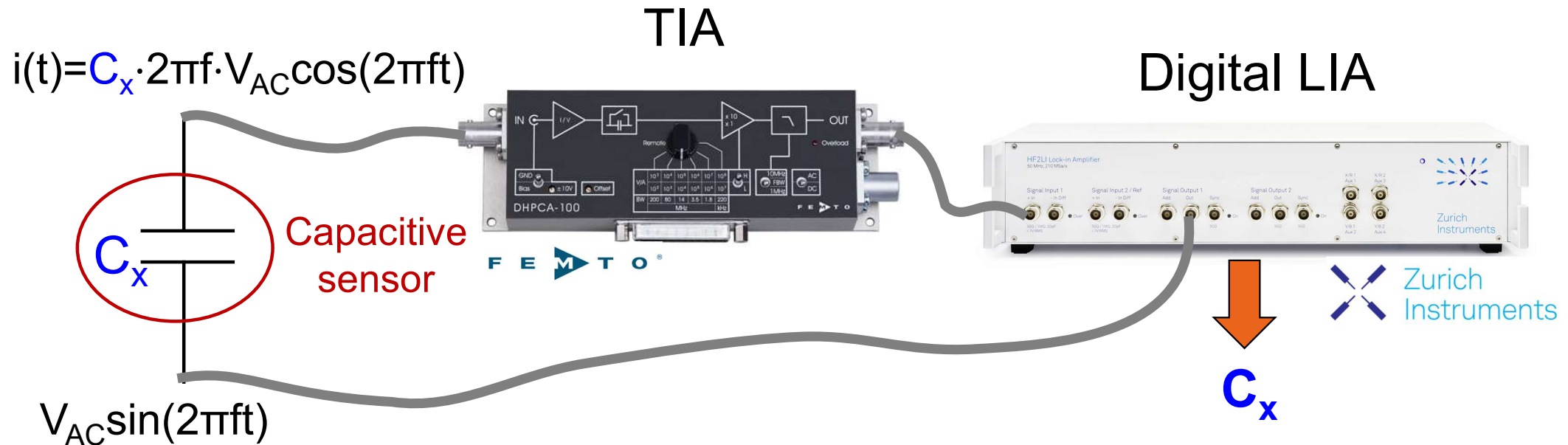

Example:

We choose: LIA: $f = 10\text{kHz}$, $BW_{LIA} = 1\text{Hz}$

Then: TIA: $BW_{TIA} > 100\text{kHz} \rightarrow \text{Gain} = 10^6 \text{ V/A}$,

$$\overline{i_{eq}^2} \cong (140 \text{ fA}/\sqrt{\text{Hz}})^2 \quad (\text{cable length} < 1\text{m})$$

If $C_x = 100 \text{ fF}$, what is the **resolution** ΔC_x ?

$$2\pi f \Delta C_x \cdot V_{AC} > \sqrt{2 \overline{i_{eq}^2} BW_{LIA}}$$





$$\Delta C_{x,min} \approx 3 \text{ aF} / V_{AC}$$

Capacitive sensor: experimental results

$C_x = 100 \text{ fF}$, $f=10\text{kHz}$, $G=10^6 \text{ V/A}$, $BW_{LIA}=1\text{Hz}$, fixed ranges and gains
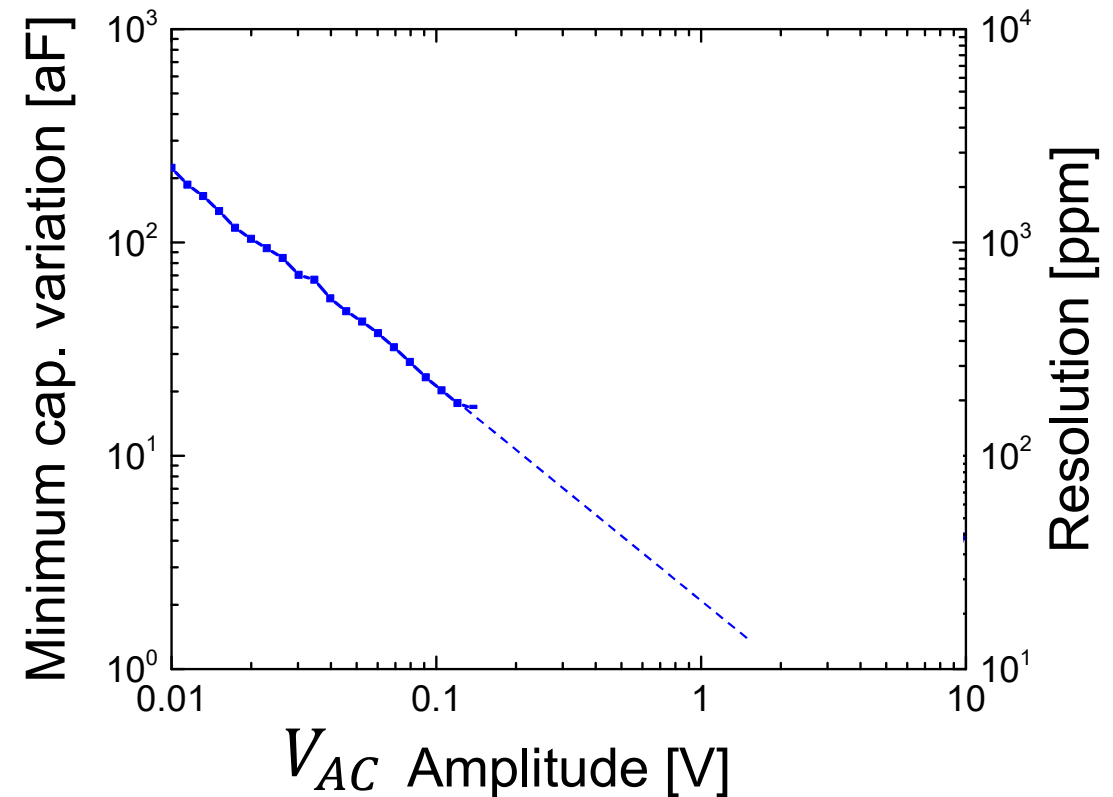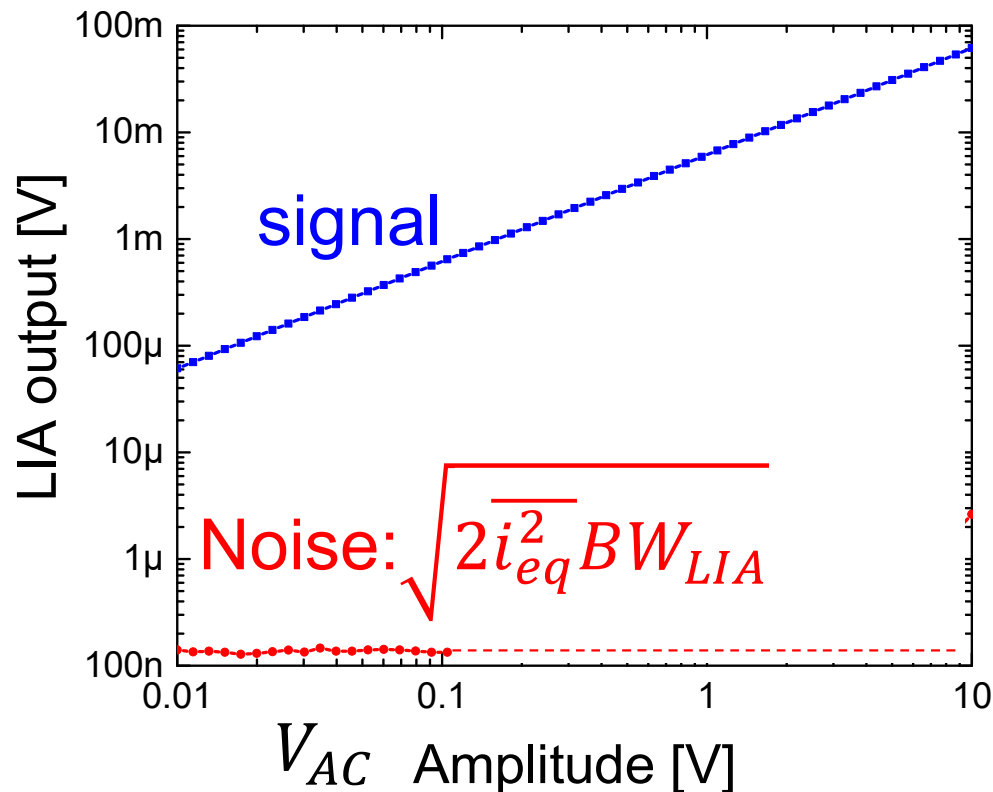
$$LIA_{out} = C_x \cdot 2\pi f \cdot V_{AC}$$




- C_x is «noise-free»
- LIA to avoid the $1/f$ noise

Why is the resolution limited?

High resolution measurements require:

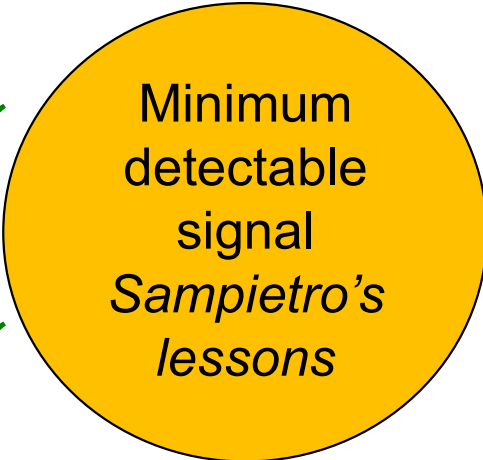- Low-noise, wide-bandwidth circuits ✓
- Shift the signal to the best frequency ✓
- Limit the BW to the minimum ✓
- Low parasitic capacitance & good insulators (low dielectric noise) ✓




Minimum
detectable
signal
*Sampietro's
lessons*



... and a full control of the experimental setup:

- Noise of the stimulus signal
- Temperature effects
- Analog-to-digital and digital-to-analog conversions
- ...


Capacitive sensor + digital LIA

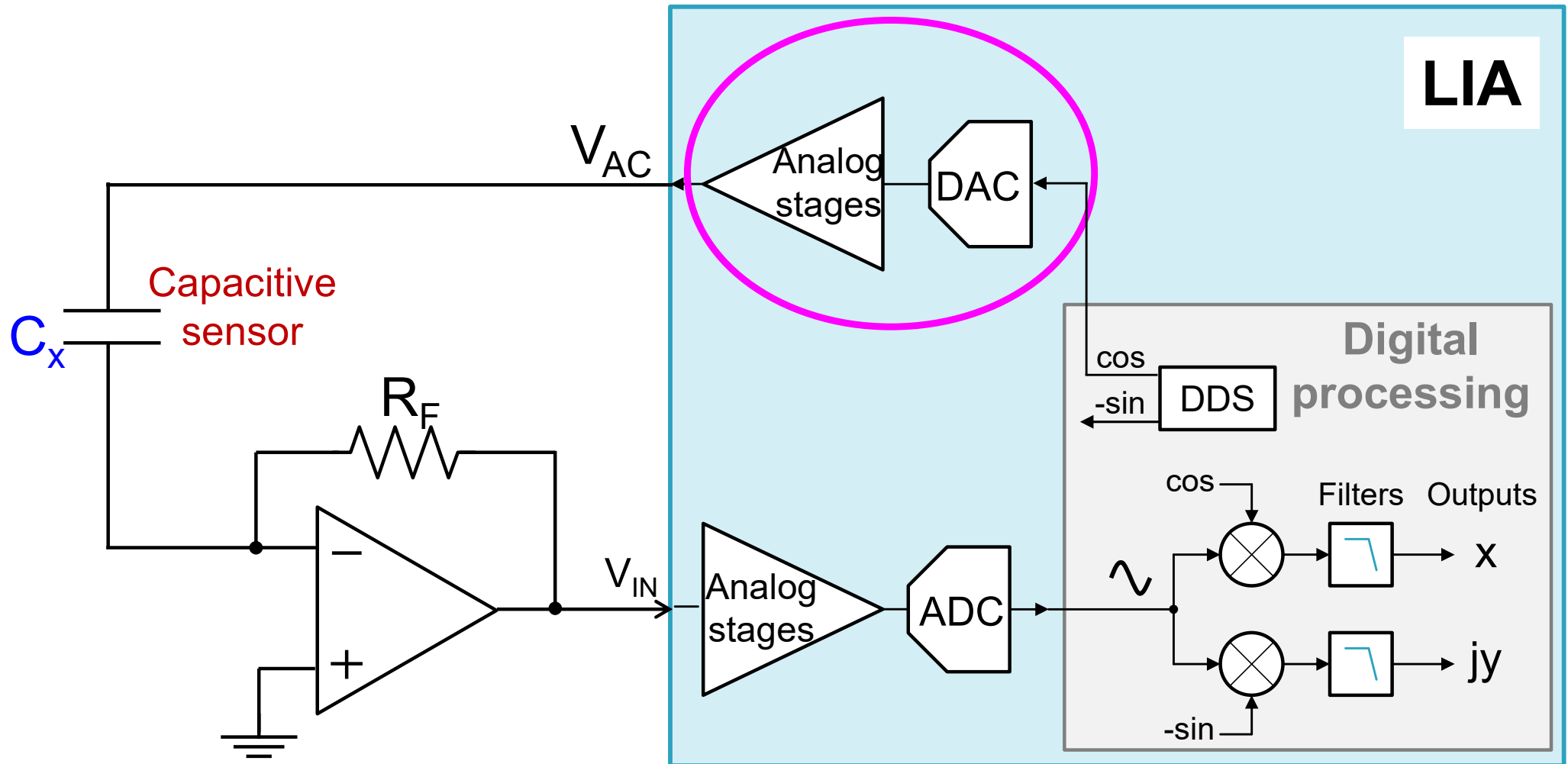

Noise of the stimulus signal

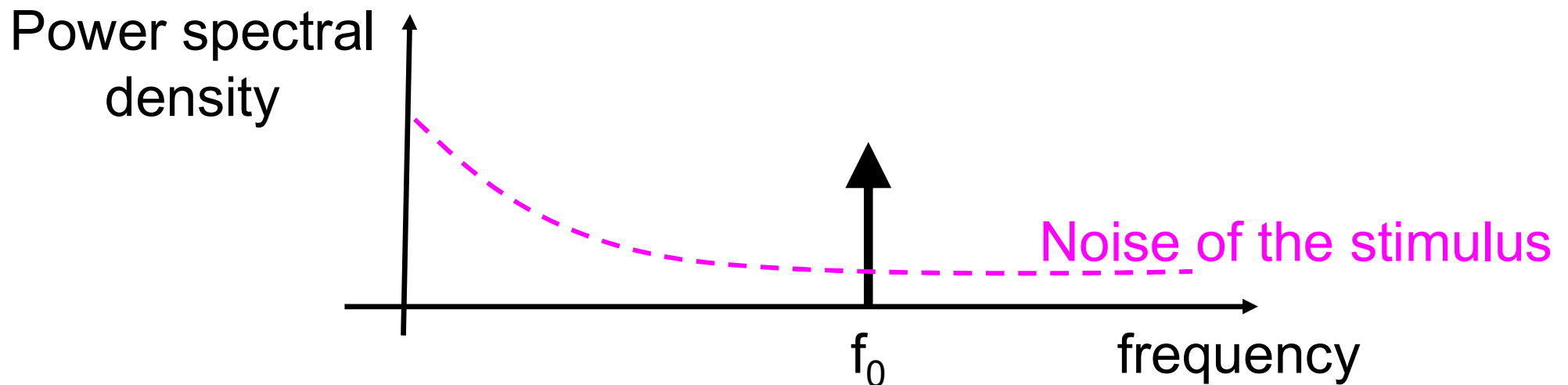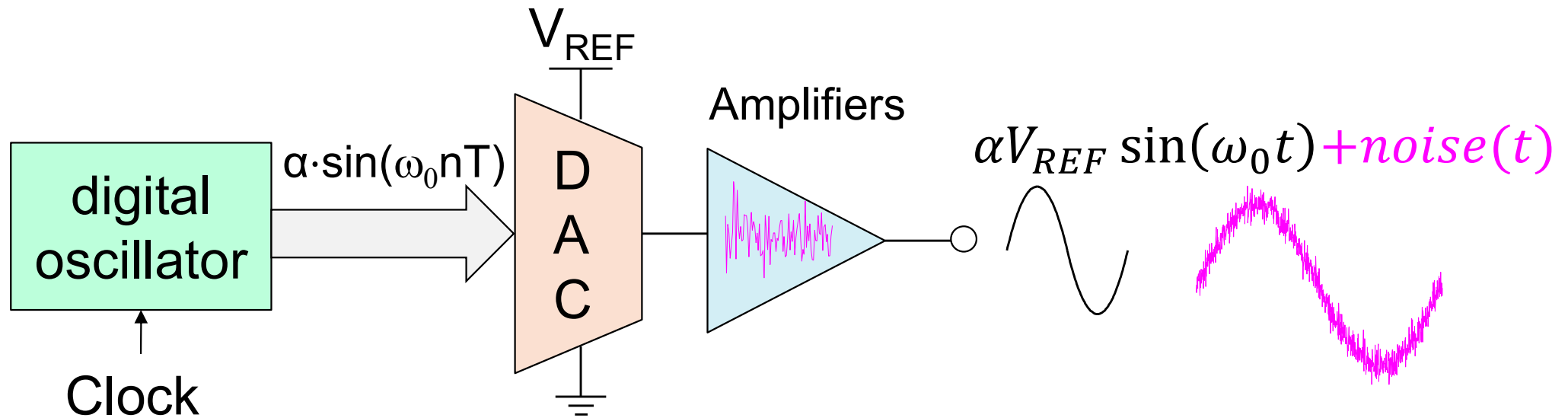

Stimulus: additive noise

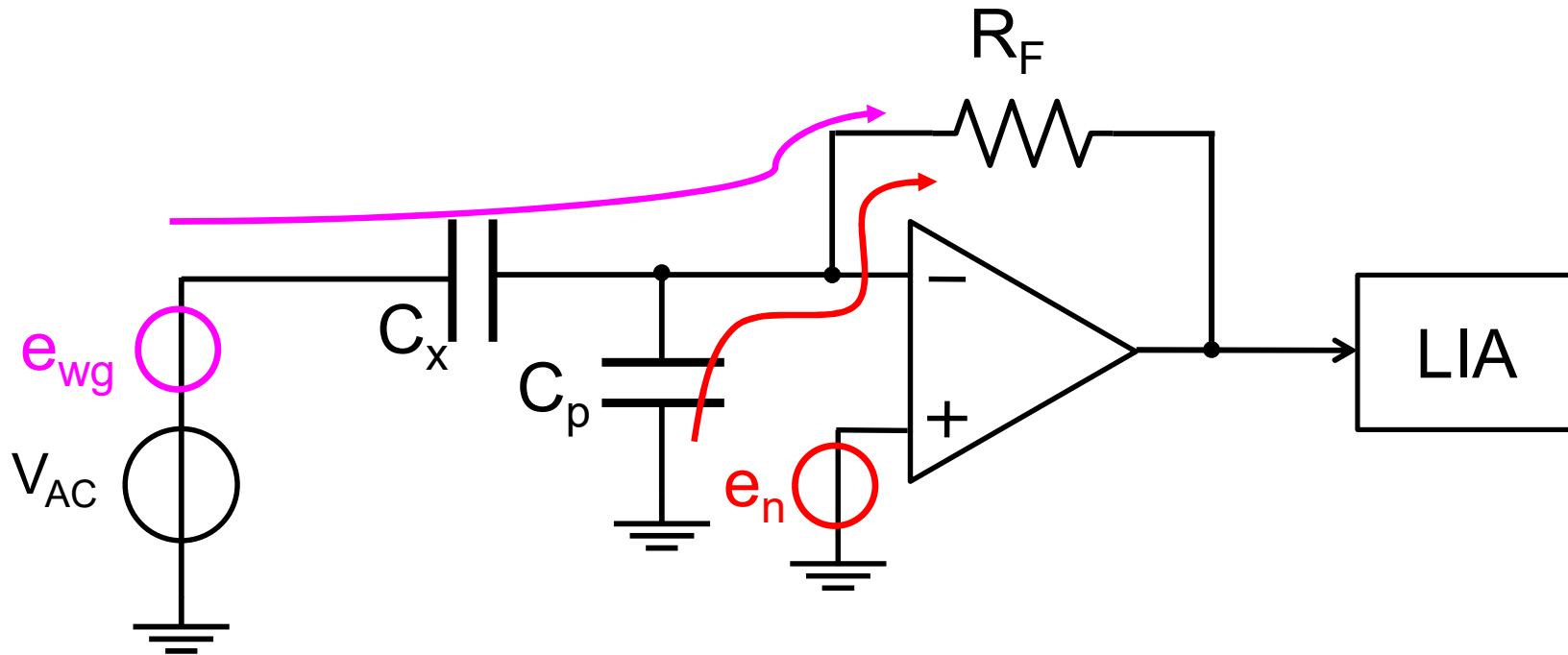


$$\text{Eq. current noise} = \overline{e_n^2} \omega^2 (C_p + C_x)^2 + \overline{e_{wg}^2} \omega^2 C_x^2$$

Signal generators have more noise than good amplifiers:

$$\overline{e_{wg}^2} \approx 25 \text{ nV} / \sqrt{\text{Hz}}, \quad \overline{e_n^2} \approx 5 \text{ nV} / \sqrt{\text{Hz}}$$

However, many nano/micro devices have $C_x \ll C_p$
making the amplifier the primary noise source

Stimulus: additive noise

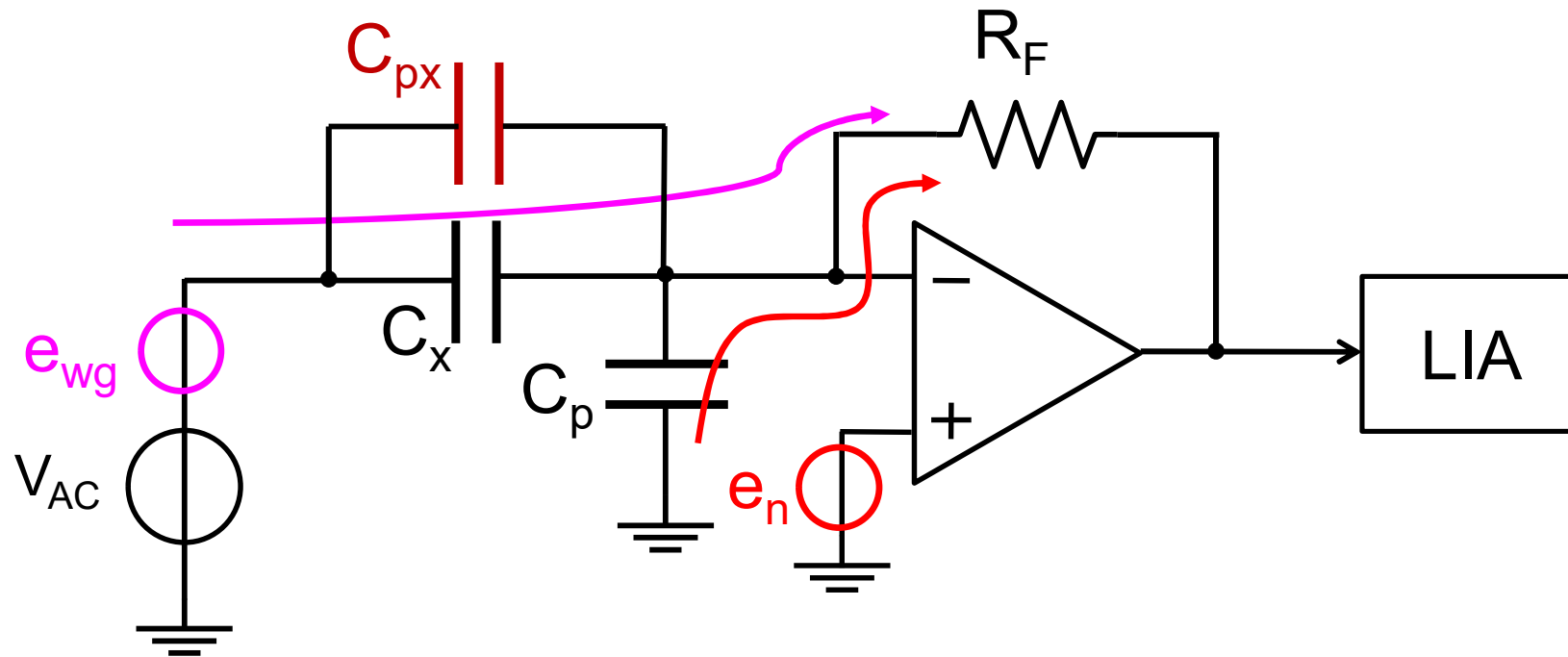


$$\text{Eq. current noise} = \overline{e_n^2} \omega^2 (C_p + C_x + C_{px})^2 + \overline{e_{wg}^2} \omega^2 (C_x + C_{px})^2$$

Signal generators have more noise than good amplifiers:

$$\overline{e_{wg}^2} \approx 25 \text{ nV} / \sqrt{\text{Hz}}, \quad \overline{e_n^2} \approx 5 \text{ nV} / \sqrt{\text{Hz}}$$

However, many nano/micro devices have $C_x \ll C_p$
but as usual, pay attention to stray capacitances! (in parallel to C_x)

Stimulus: additive noise

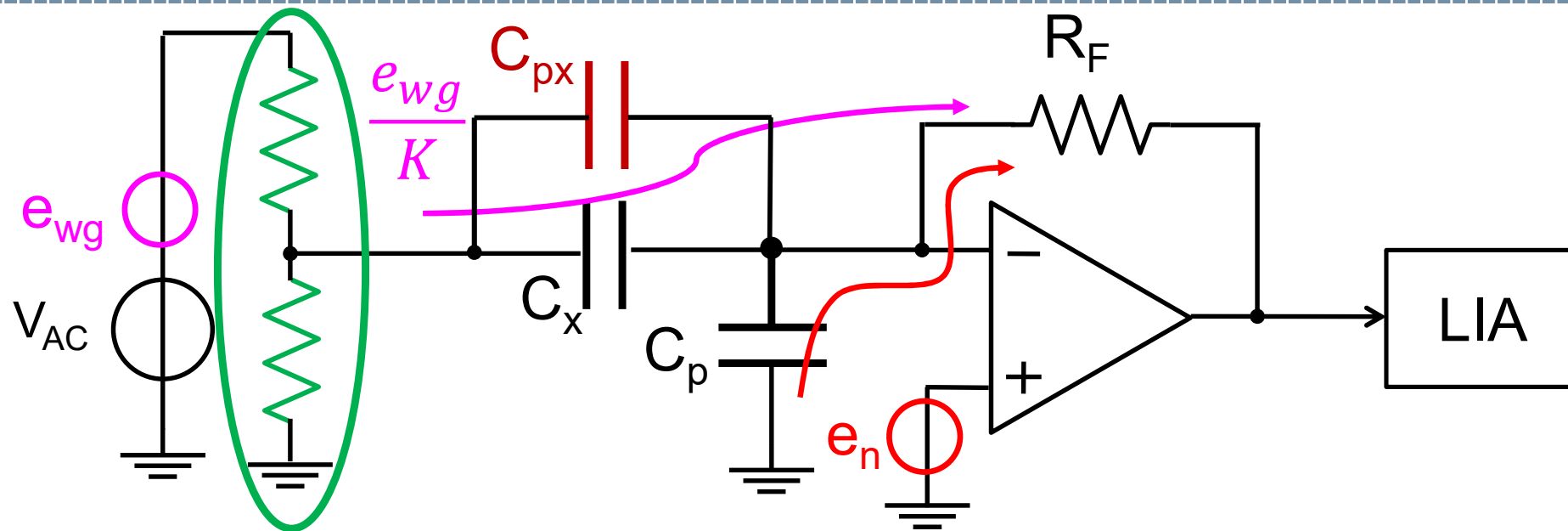



Voltage divider using small value resistors ($\approx 50\Omega$)

A voltage divider can be beneficial if e_{wg} is independent of V_{AC}


$$\text{Equivalent input noise} = \overline{e_n^2} \omega^2 (C_p + C_x + C_{px})^2 + \frac{\overline{e_{wg}^2} \omega^2 (C_x + C_{px})^2}{K^2}$$

- Other techniques: ELIA, differential measurements (see later)

Noise of the stimulus signal

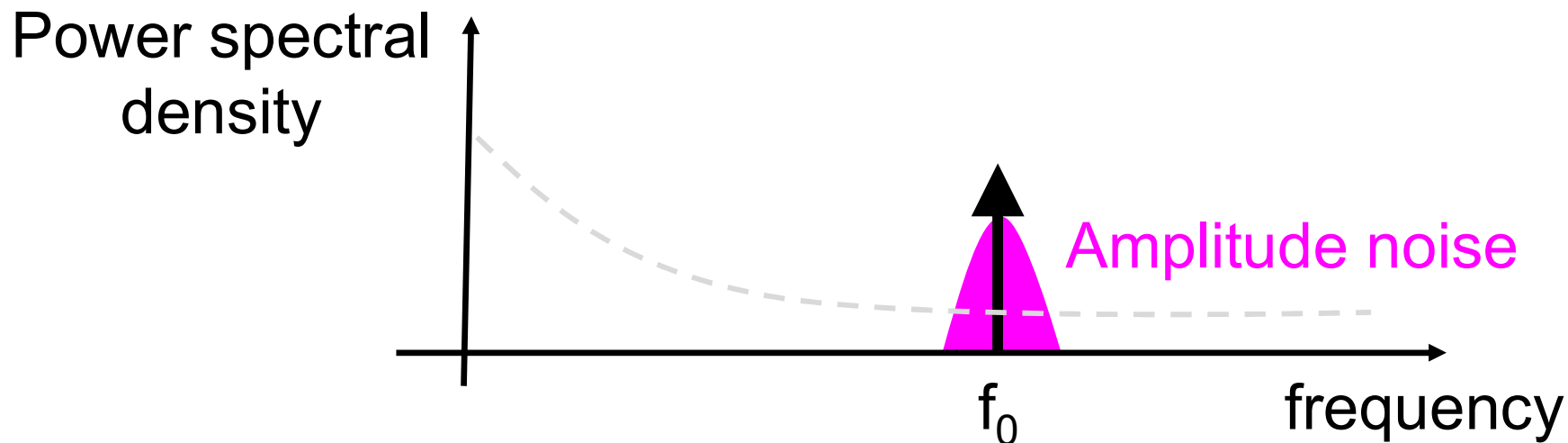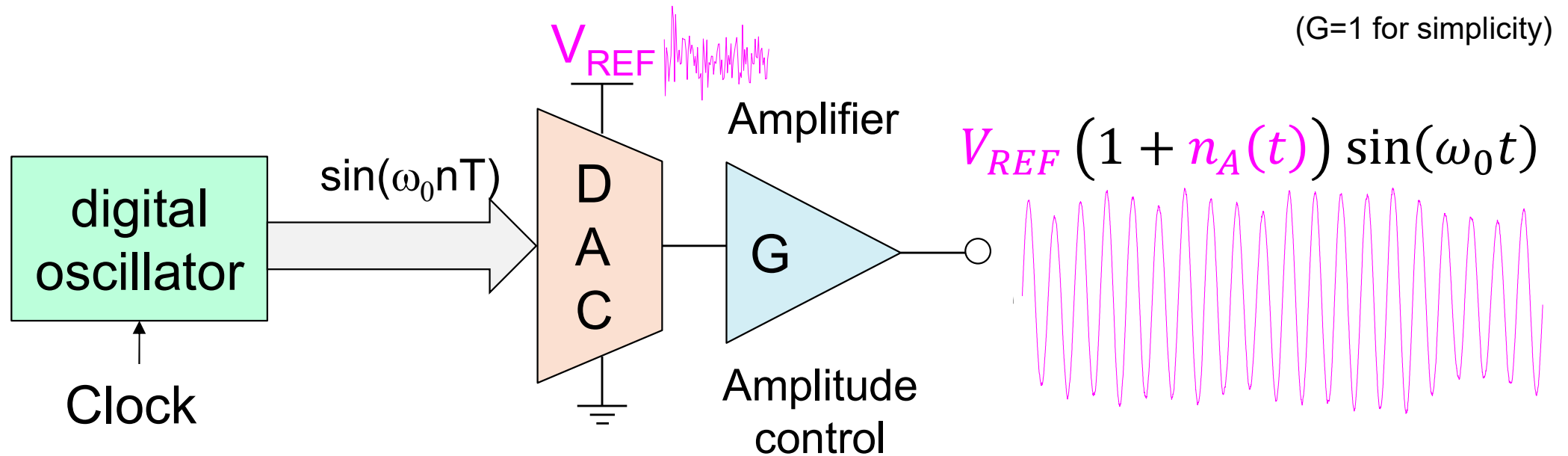


Stimulus: amplitude noise

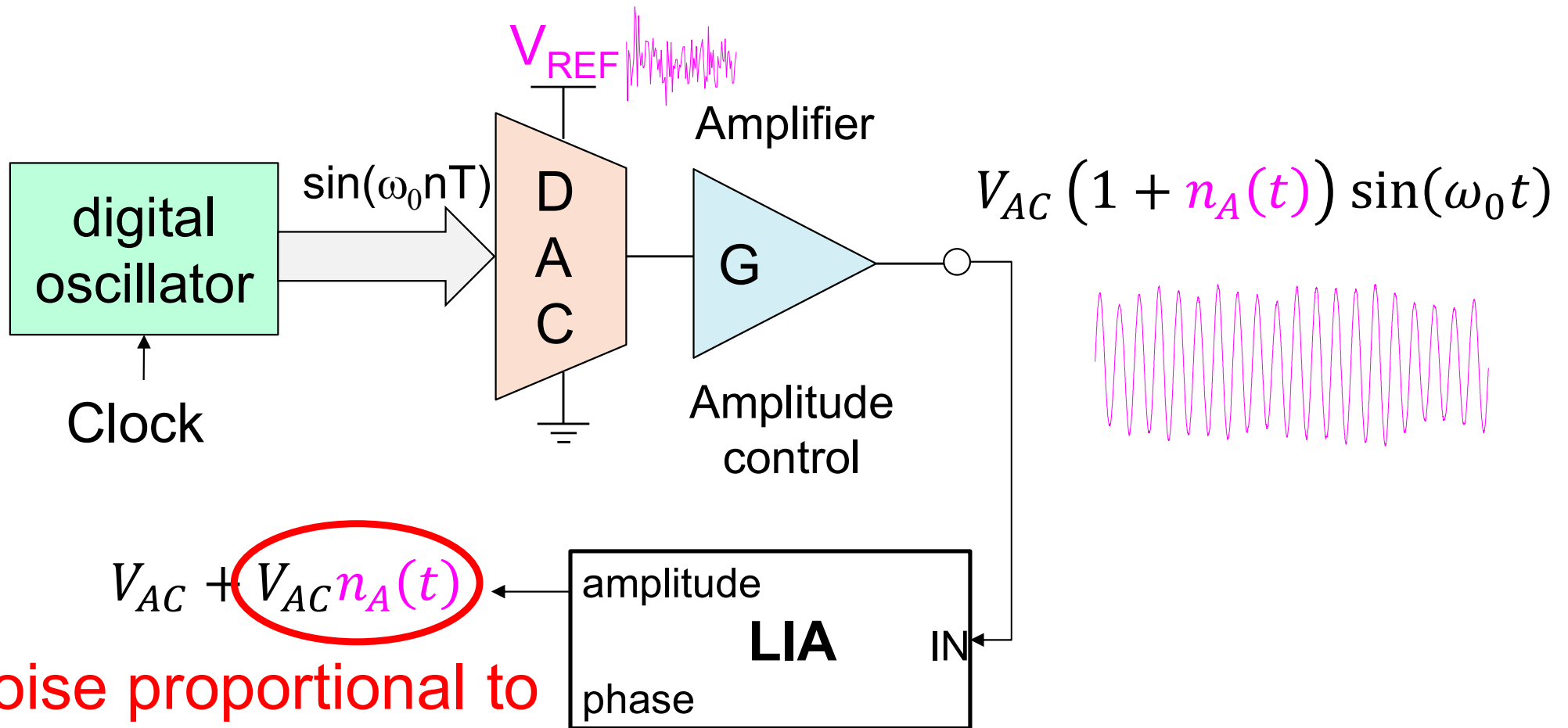


Noise proportional to the signal amplitude

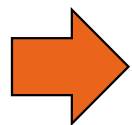The demodulated amplitude has the SAME noise behavior of V_{REF}





1/f noise at the output of the LIA!
(regardless of the frequency of the measurement)

Effect of amplitude noise

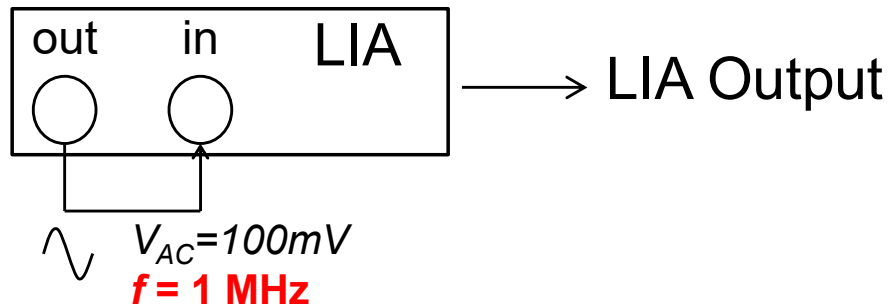


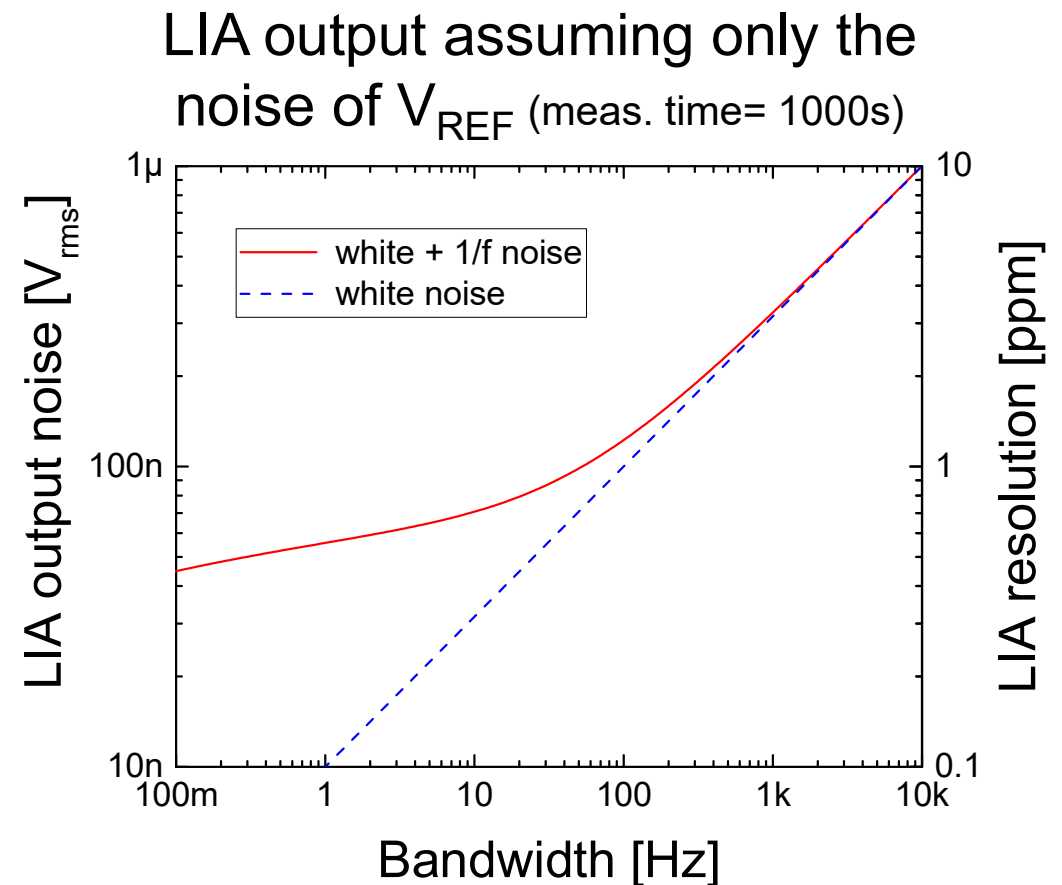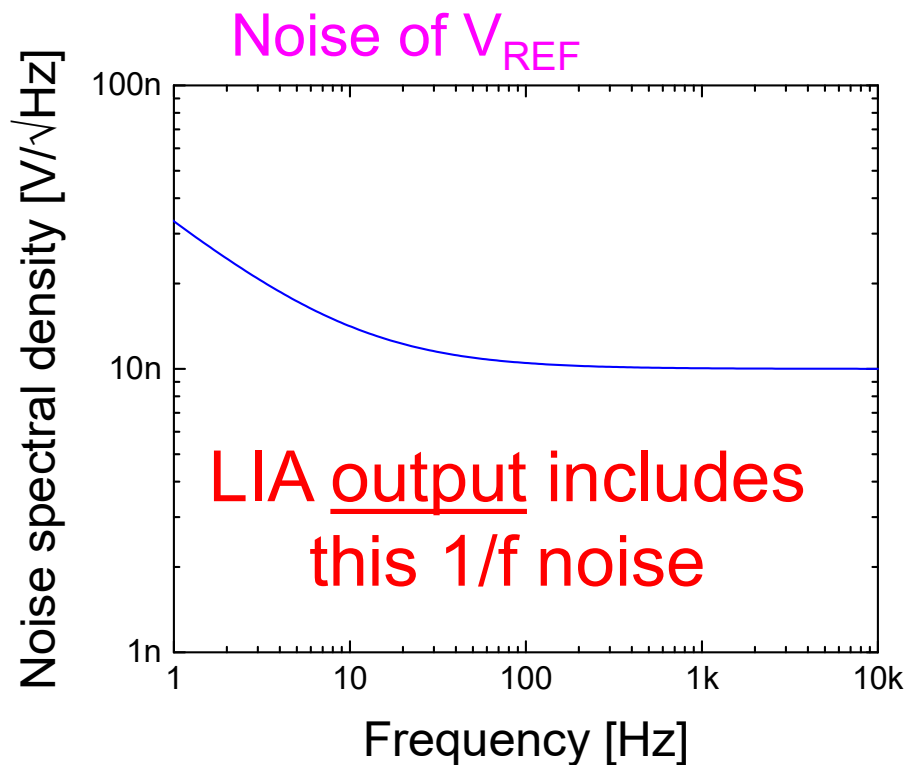Example: amplitude noise of $10\text{nV}/\sqrt{\text{Hz}}$,
1/f corner frequency: 10Hz




High resolution requires narrow BW → 1/f noise of V_{REF} sets a limit!
Noise proportional to the signal: same resolution using $V_{AC} = 1\text{V}$

Capacitive sensor + digital LIA

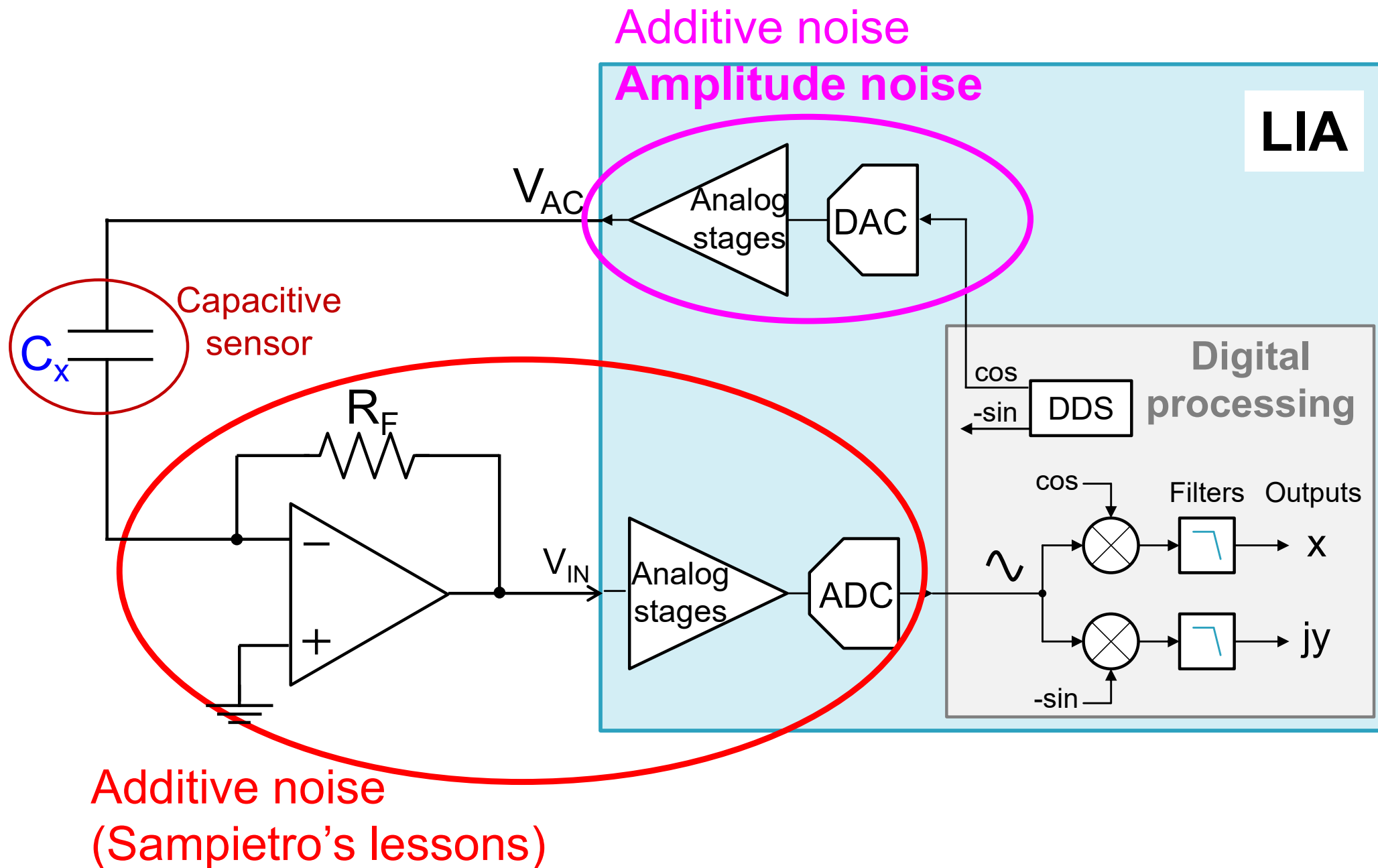

Temperature effects

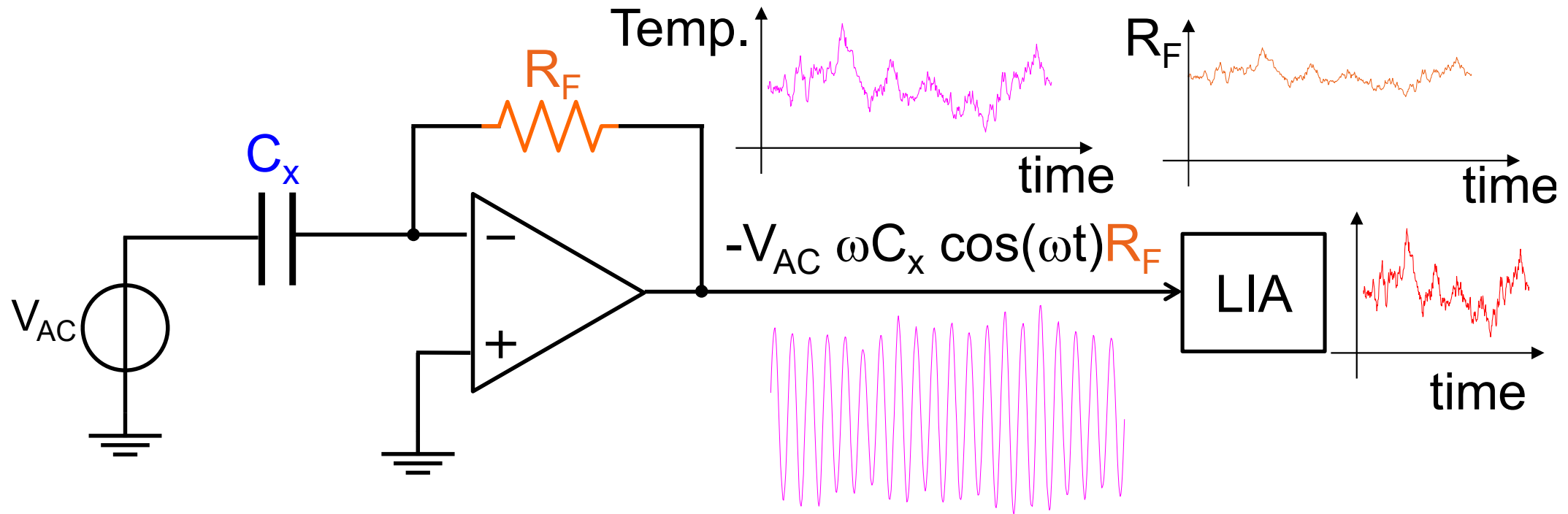


The gain fluctuations are shown in the LIA output (AM)

Temperature coeff. of standard R is 50 ppm/°C (≥ 100 ppm/°C for high value resistors)

➡ 1 ppm requires a temperature stability better than 0.02 °C!

Temperature effects

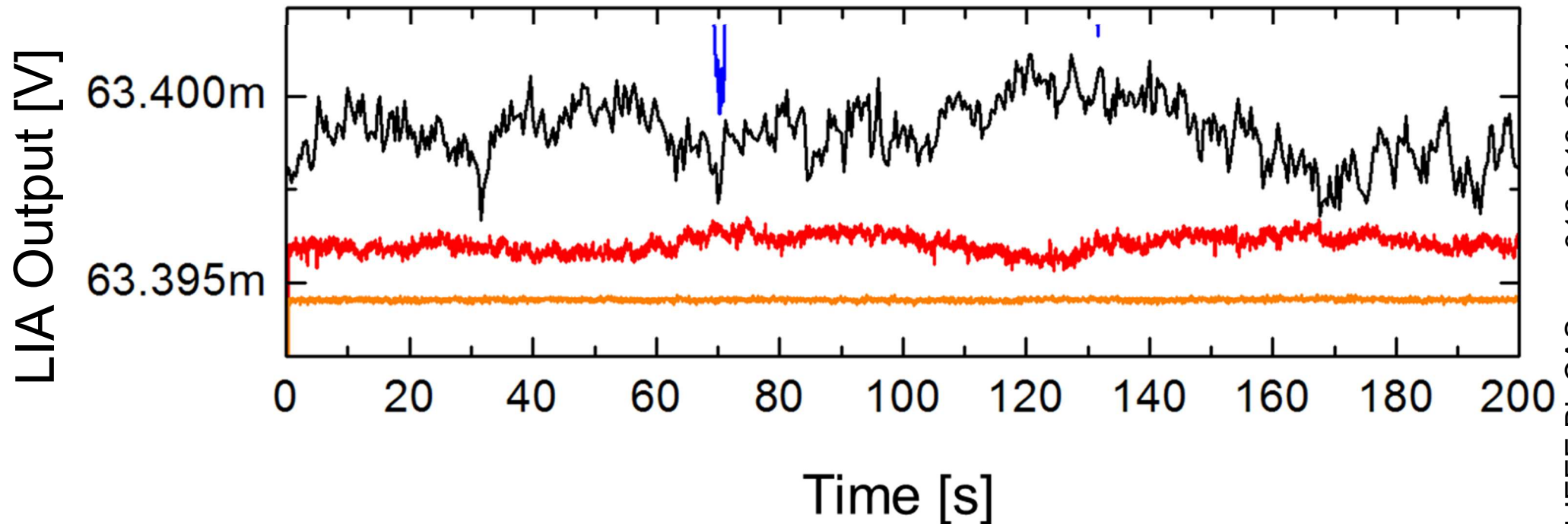

SR830 lock-in: 840nV rms (13 ppm)

Custom lock-in: standard R (50 ppm/°C): 240nV rms (4 ppm)

LTC R (5 ppm/°C): 45 nV rms (0.7 ppm)


**Choose components with a low-temperature coefficient
for the elements setting the gain!**

- (expensive) resistors with low temp. coef. (down to 1 ppm/°C)
- C0G capacitors («0 drift», less than 30 ppm/°C)
- Temperature controller
- Other techniques: see ELIA or differential measurements!

Gain fluctuations (amplitude noise)

Most crucial stage for the additive noise:
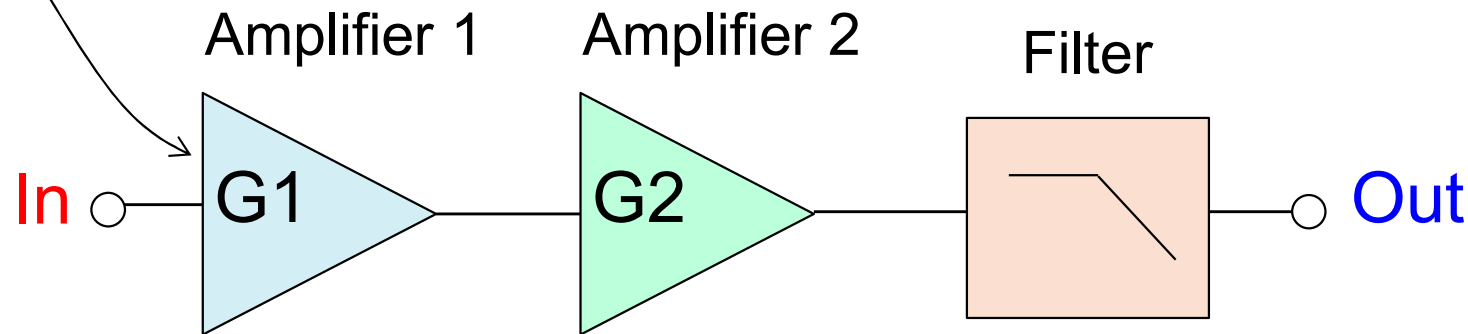
$$\overline{i_{eq}^2} \cong \overline{i_{eq,G1}^2} + \frac{\overline{i_{eq,G2}^2}}{G_1^2} + \frac{\overline{i_{eq,filter}^2}}{G_1^2 G_2^2}$$




$$\text{Out} = G1 \cdot G2 \cdot G_{\text{FILTER}} \cdot \text{In}$$

All stages are equally important for the amplitude noise!


Low temp. coef. components along the entire signal path

Digital lock-in amplifier

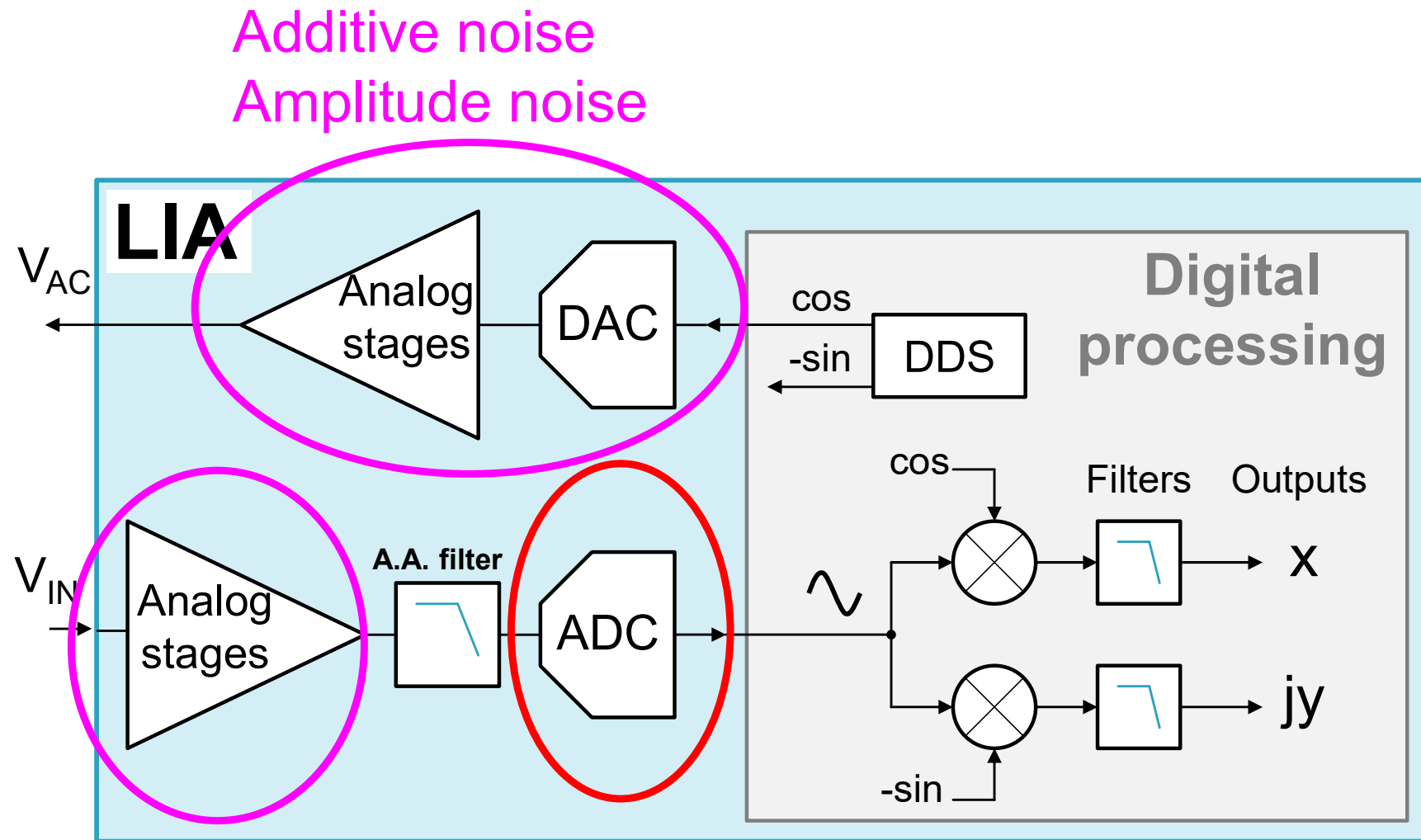


Additive noise
Gain fluctuations

ADC: amplitude noise

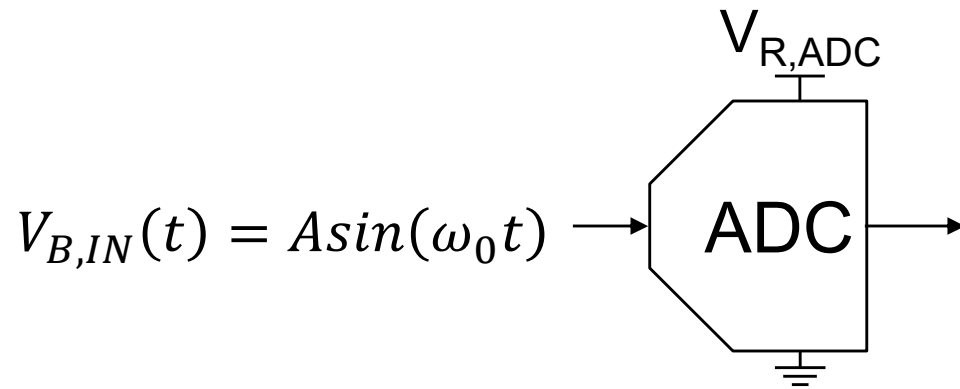


$$V_{dig}(iT_s) \propto \frac{A \sin(\omega_0 iT_s)}{V_{R,ADC}}$$

ADC: amplitude noise




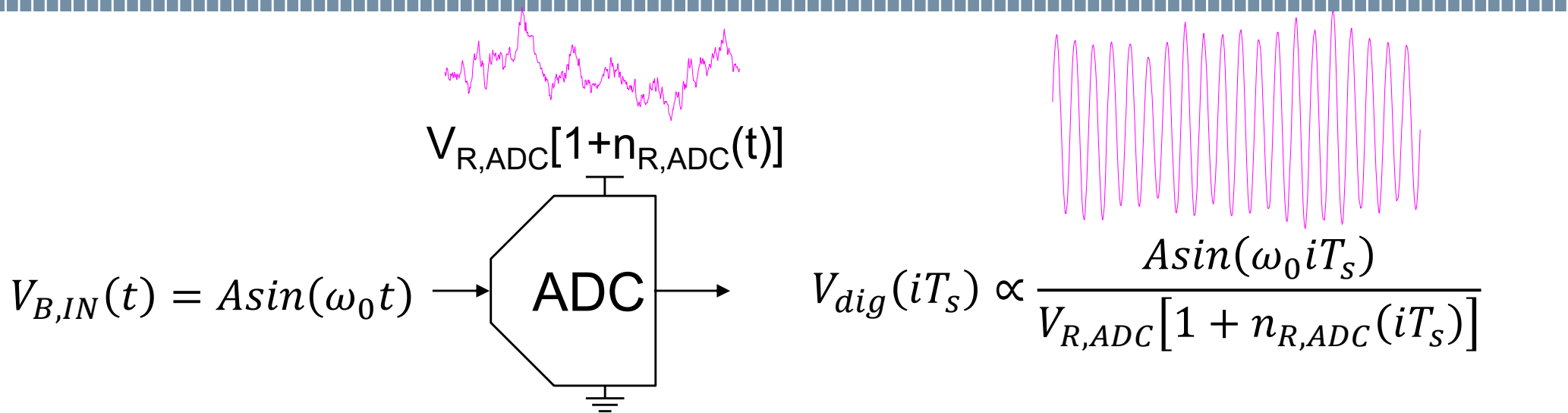


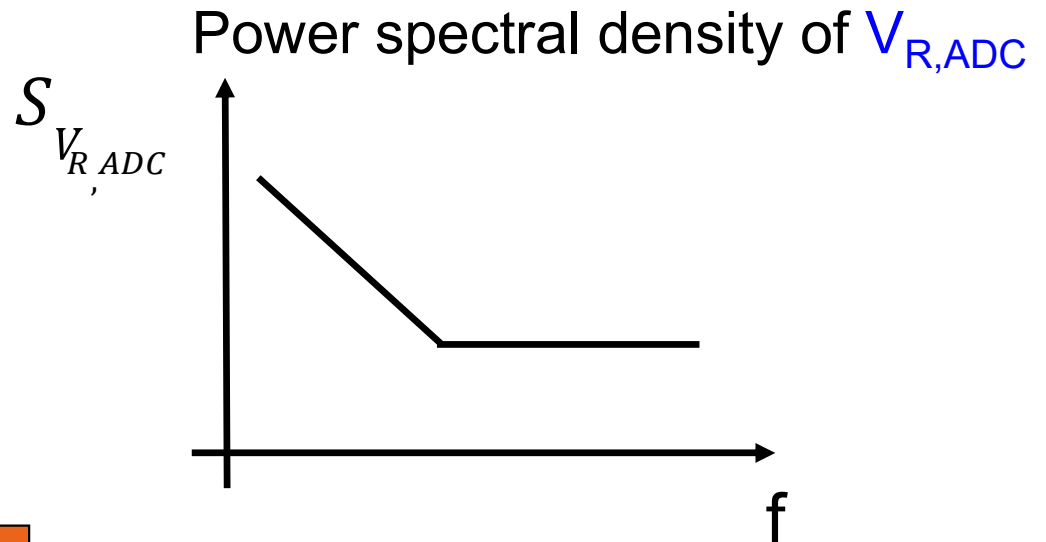Unavoidable slow
fluctuations of the ADC gain
(voltage reference, internal
circuit elements)



Unavoidable fluctuations of the amplitude measured by the LIA!

Quantization error

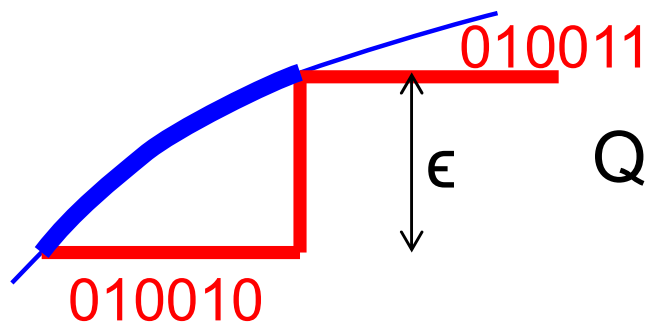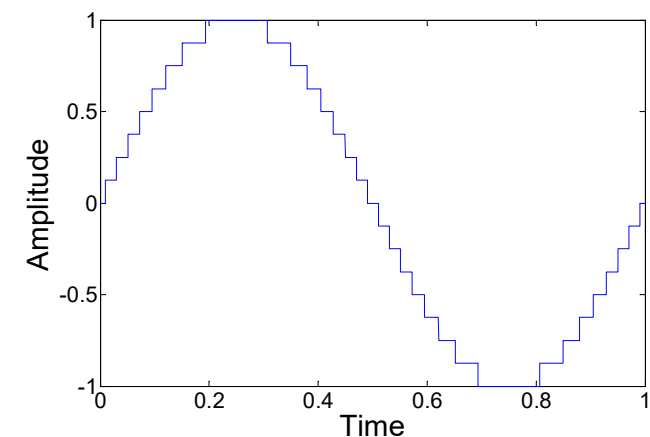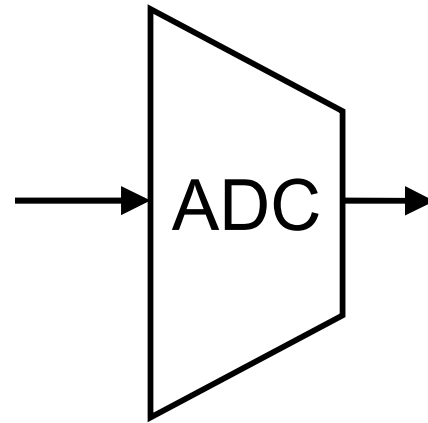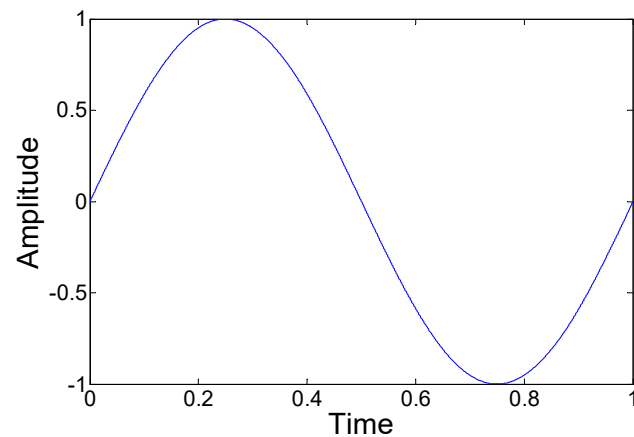

$2^{\text{number of bit}}$ levels $\rightarrow$ quantization error


Quantization error < 1 ppm $\rightarrow >20$ bit

... but 20-bit ADCs are slow ($<10\text{kS/s}$)

no fast high-resolution digital LIA?

We average a large number of samples!

Quantization error

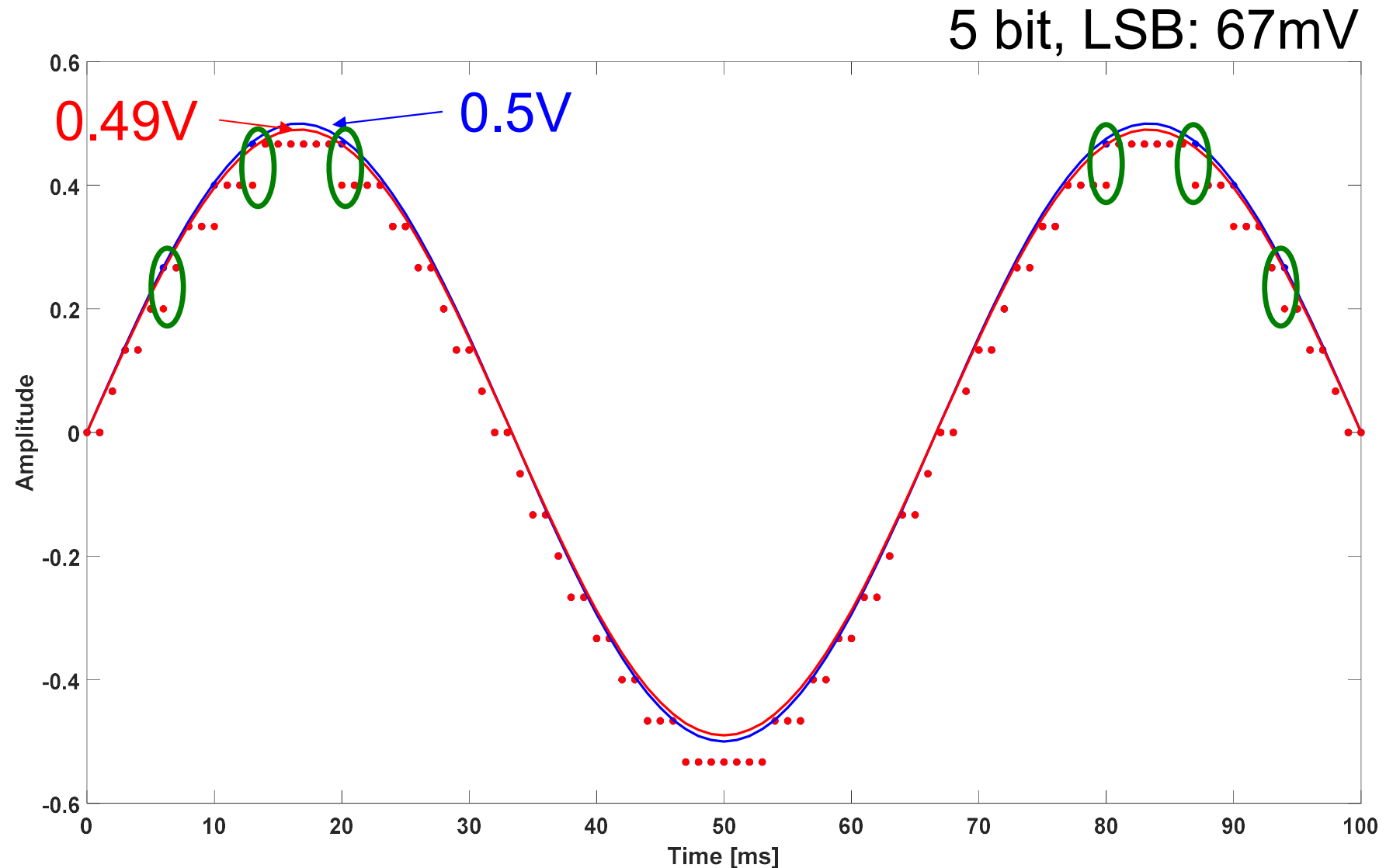


Although the amplitude difference (10mV) is less than the quantization step (67mV), few samples are different

Quantization error

$$V_{AC}=0.5V, f_0=100kHz$$
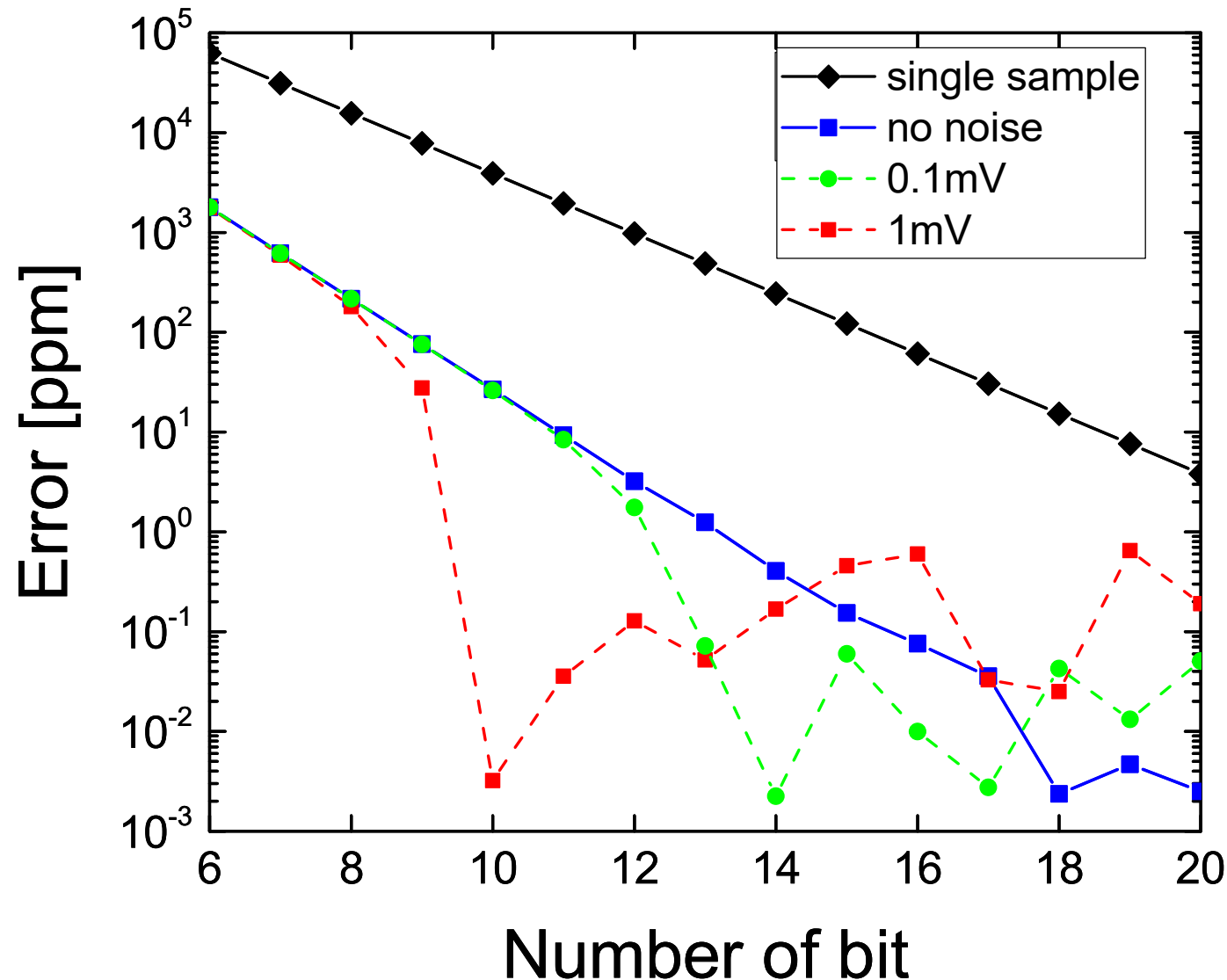
$$V_{REF,ADC}=\pm 1V, f_s=50MS/s, BW_{LIA}\approx 100Hz$$



...the noise further reduces the quantization error!

Things to remember

High-resolution measurements require complete control of the experimental setup:



- Noise of the input amplifier
 - Noise of the sensor
 - Limit the effect of $1/f$ noise! (use LIA if possible)
 - Slow ($1/f$) random fluctuations of the system gain:
 - Signal source (DAC, optical source,...)
 - Temperature dependence of amplifier/filter gains (C, R,...)
 - Gain fluctuation of ADC
 - Quantization error is less critical: high resolution usually requires the average of many samples
 - A standard LIA does NOT solve the problem of gain fluctuations
- } Minimum detectable signal

OUTLOOK of the LESSON

- Introduction to the problem
- Noise sources limiting high-resolution measurements:
 - Additive noise sources
 - Multiplicative noise sources
- **Solutions:**
 - Ratiometric technique
 - ELIA: Enhanced Lock-In Amplifier
 - Differential approach

Thursday
lesson


Resolution limits of LIAs

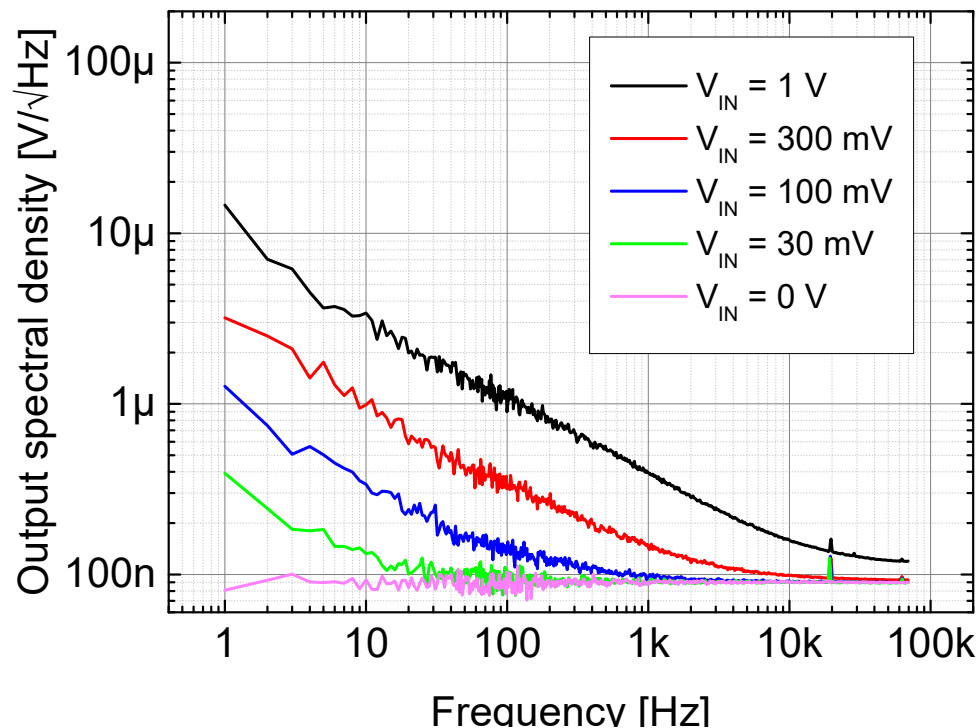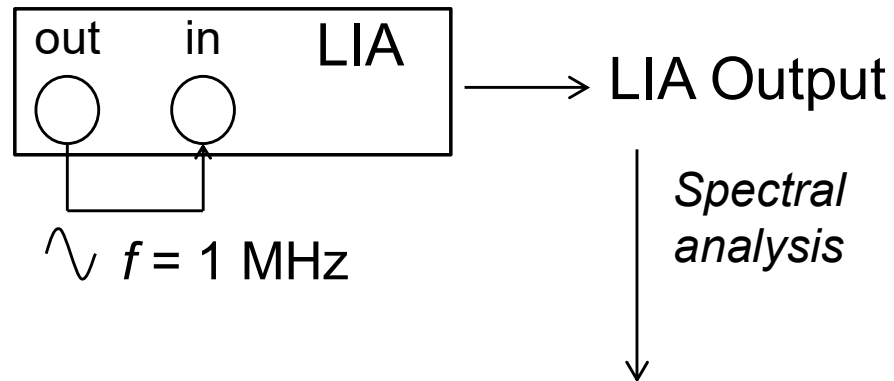

$$\text{Noise} \approx \sqrt{\text{input noise} \cdot BW + kV_{AC}^2}$$

Zurich Instruments, HF2LI

Resolution = Noise / Signal

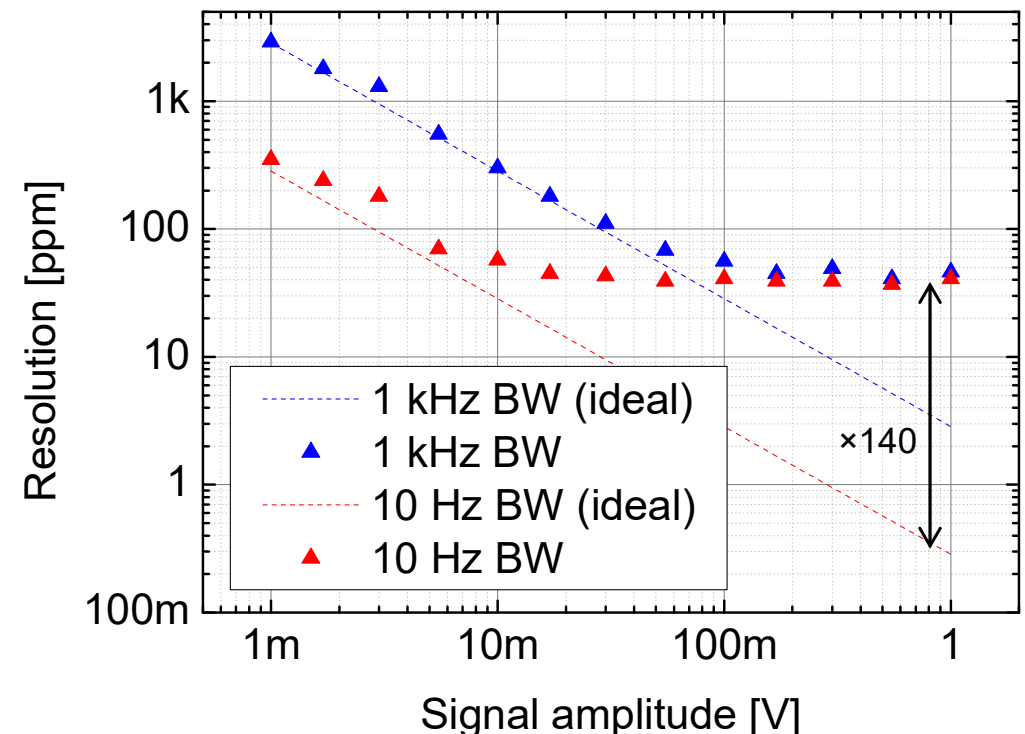

A common limit for high-speed LIA


Model	Maximum frequency [MHz]	Signal amplitude [V]	Measurement frequency [MHz]	Relative resolution [ppm]
Custom LIA [1]	0.1	0.1, 0.3, 1	0.01, 0.05	1
SR830 (Stanford Research Systems)	0.1	0.1, 0.3, 1	0.01, 0.05	12
MCL1-540 (SynkTek)	0.5	1.4	0.1	1.3
SR865 (Stanford Research Systems)	2	0.3	0.5	45
Custom LIA [2]	10	0.03, 0.1, 0.3, 1	0.1, 1	9
HF2LI (Zurich Instruments)	50	0.03, 0.1, 0.3, 1	0.1, 1, 10	39

[1] G. Gervasoni et al., 2014 IEEE BioCAS, pp. 316–319, 2014

[2] M. Carminati et al., 2012 IEEE I2MTC, pp. 264–267, 2012.

The ultimate resolution may be limited by gain fluctuations and NOT by the amplifier noise (< 1 ppm)

How to improve the resolution ?

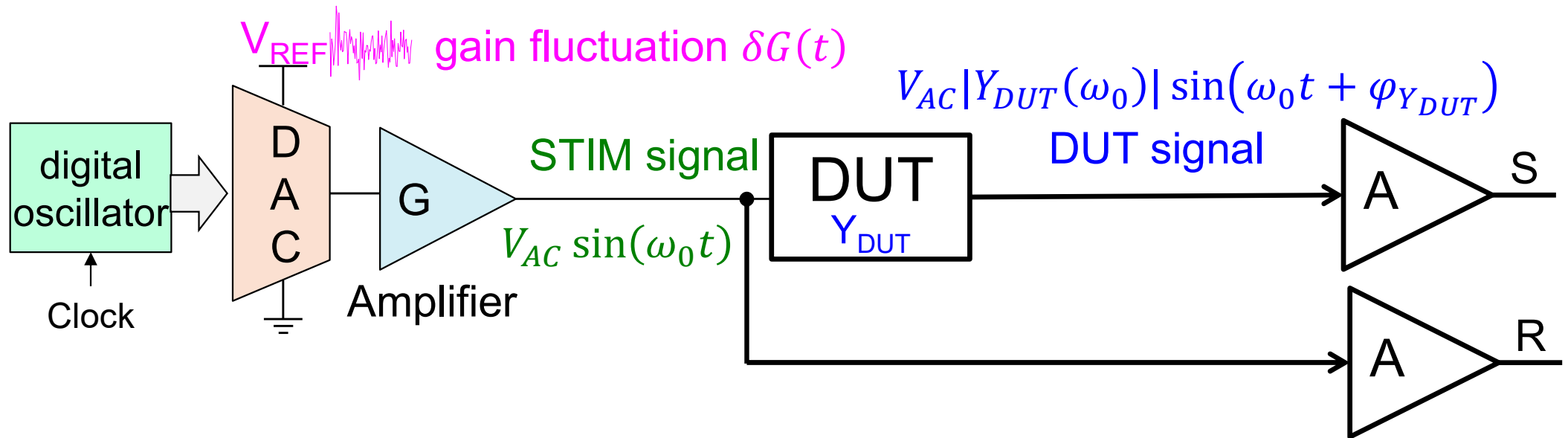

Amplitudes:


$$STIM_{real} = STIM_{id}(1 + \delta G(t)) \quad \Rightarrow \quad S_{DUT,real} = S_{DUT,id} (1 + \delta G(t))$$

Ratiometric approach:

$$\frac{S}{R} = \frac{S_{DUT,real}}{STIM_{real}} = \frac{S_{DUT,id} \cdot \cancel{(1 + \delta G(t))} \cdot A}{STIM_{id} \cdot \cancel{(1 + \delta G(t))} \cdot A} = |Y_{DUT}(\omega_0)| \quad \text{independent of } A, V_{AC} \text{ and } \delta G(t)!$$

No fine-tuning between S and R amplitudes is required


Standard digital LIA

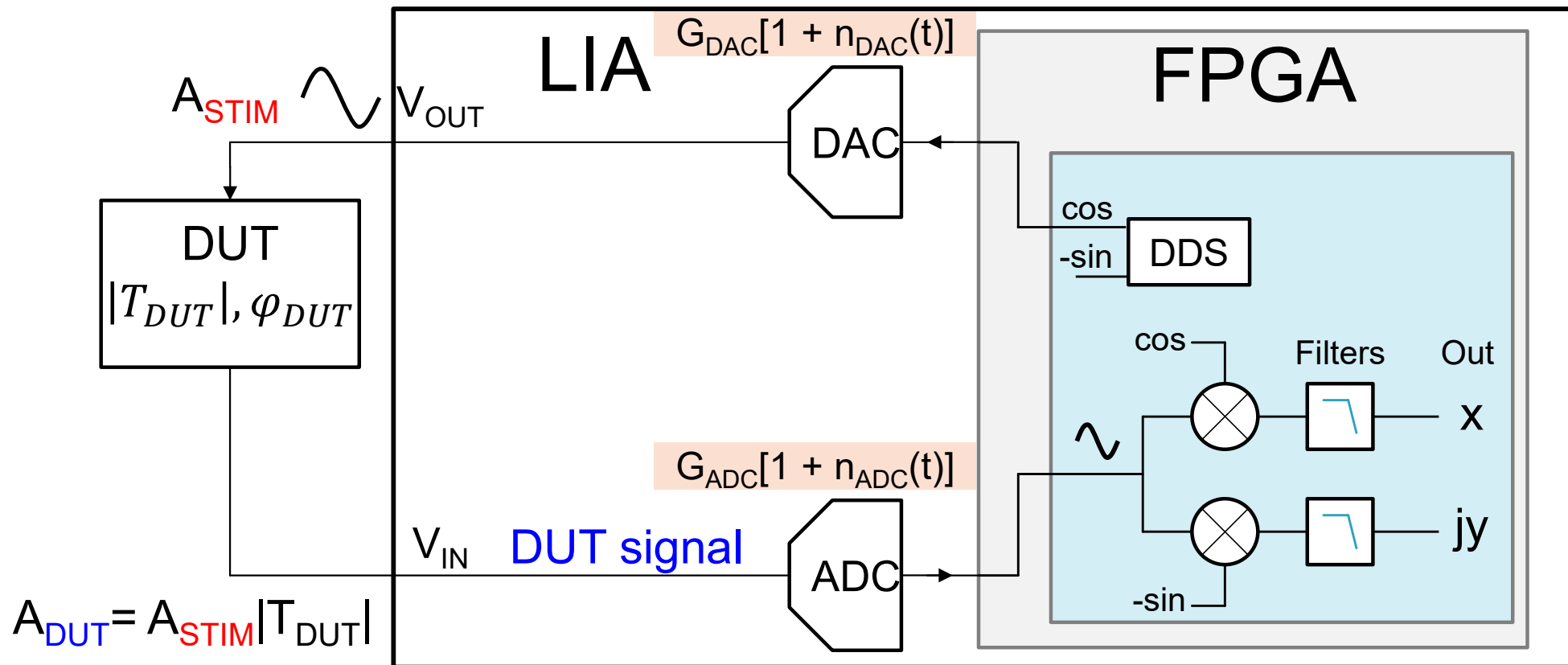

$$\sqrt{x^2 + y^2} = A_{DUT} = A_{STIM} |T_{DUT}| G_{ADC}[1 + n_{ADC}(t)] G_{DAC}[1 + n_{DAC}(t)]$$

(+ any gain fluctuations of the analog stages)


Ratiometric LIA

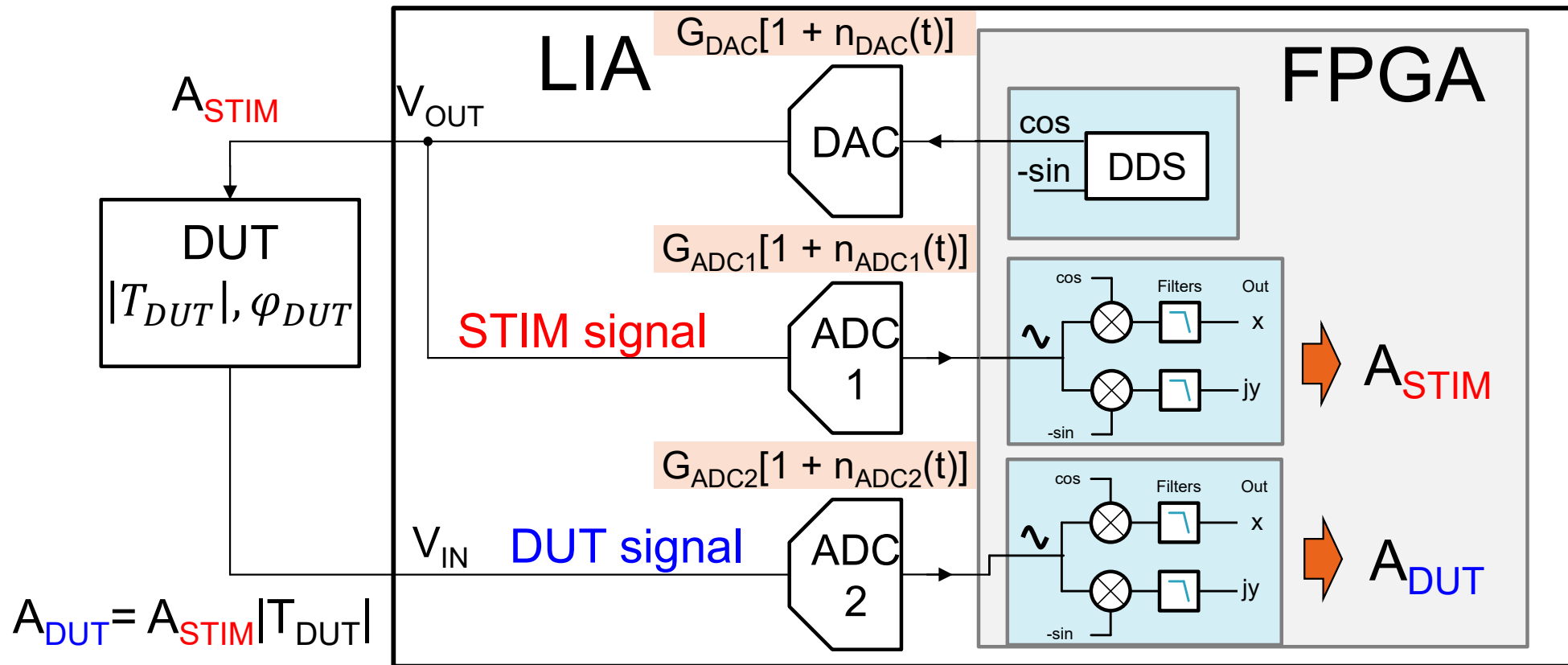

$$\frac{A_{DUT}}{A_{STIM}} = |T_{DUT}| \frac{\cancel{G_{DAC}[1 + n_{DAC}(t)]}}{\cancel{G_{DAC}[1 + n_{DAC}(t)]}} \frac{G_{ADC2}[1 + n_{ADC2}(t)]}{G_{ADC1}[1 + n_{ADC1}(t)]}$$

still amplitude noise!

Enhanced-LIA (ELIA)




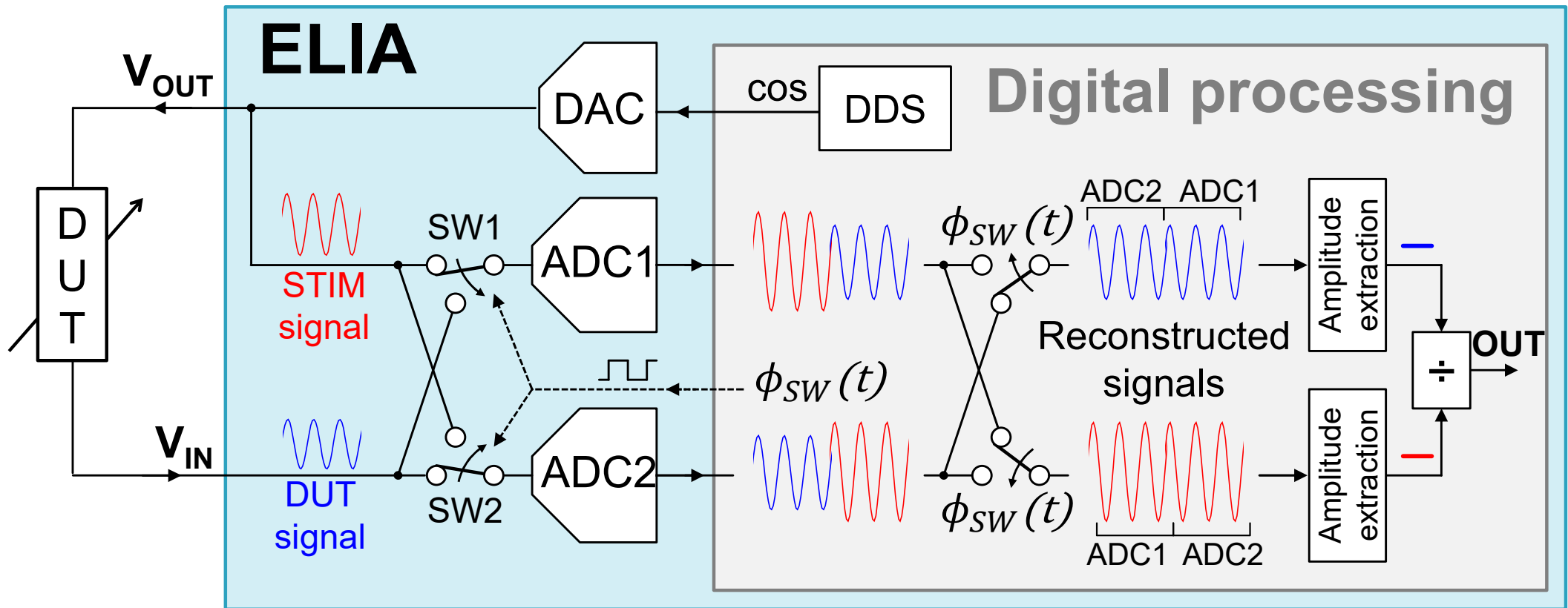


- Digital ratiometric approach
- $\approx$ kHz switching frequency to mix the ADC fluctuations
- Signal reconstruction and LIA demodulation

ELIA: time domain analysis

Gain of the acquired signals


Gain of the reconstructed signals

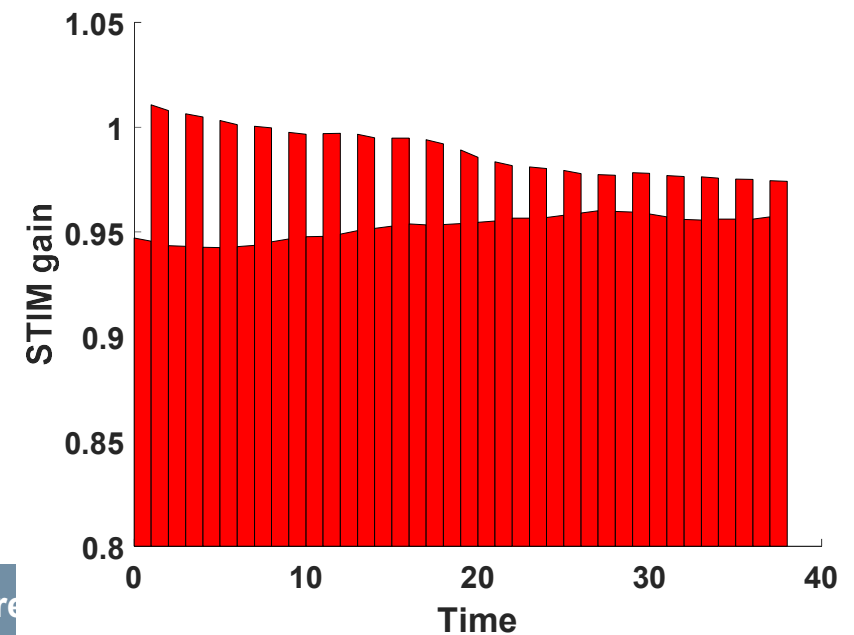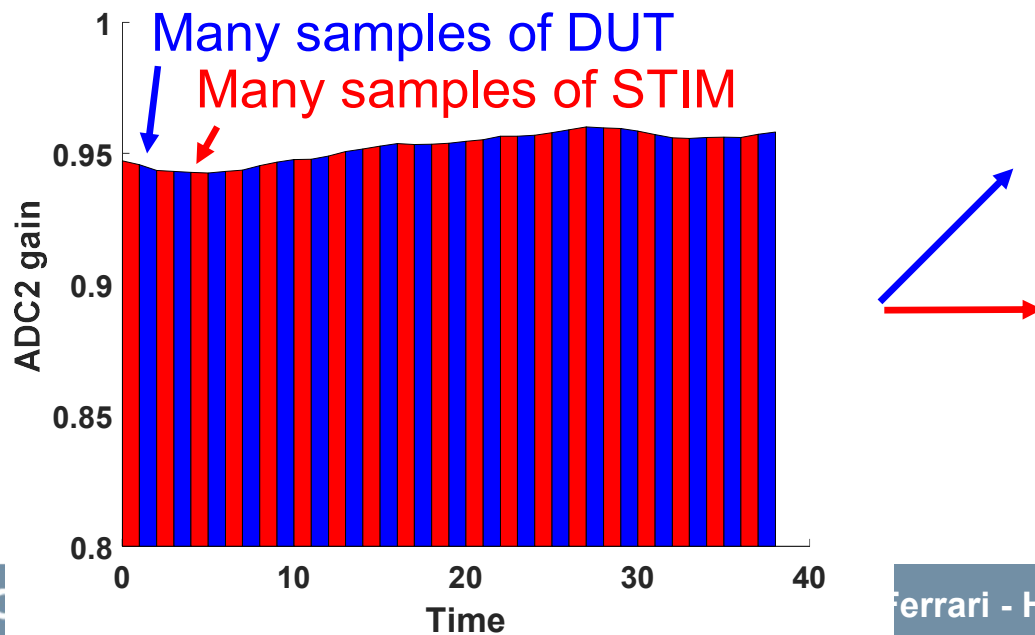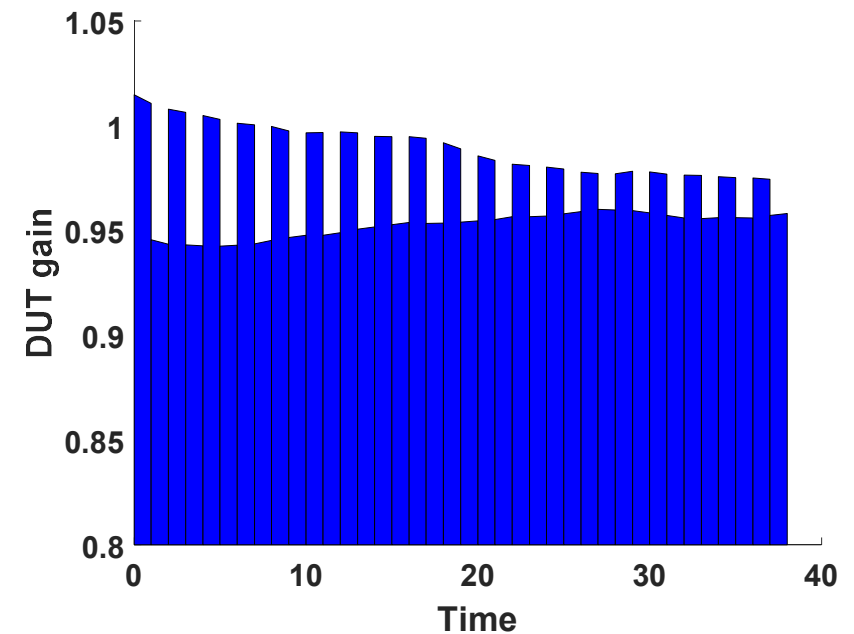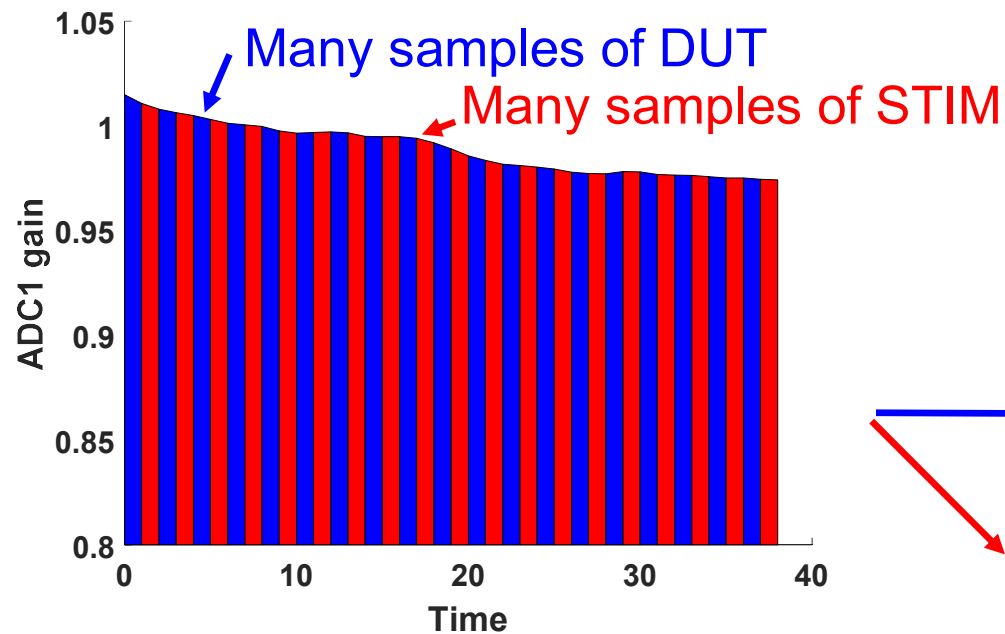

ELIA: time domain analysis




Gain of the acquired signals

Gain of the reconstructed signals

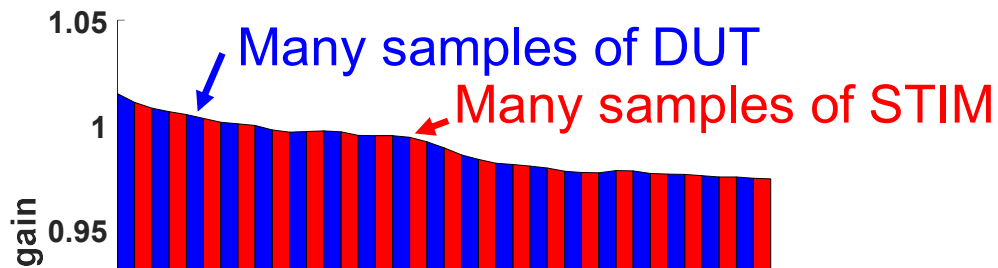


If the switching period is faster than the gain fluctuations
→ same mean gain!

$$\frac{A_{DUT}}{A_{STIM}} \approx |T_{DUT}|$$

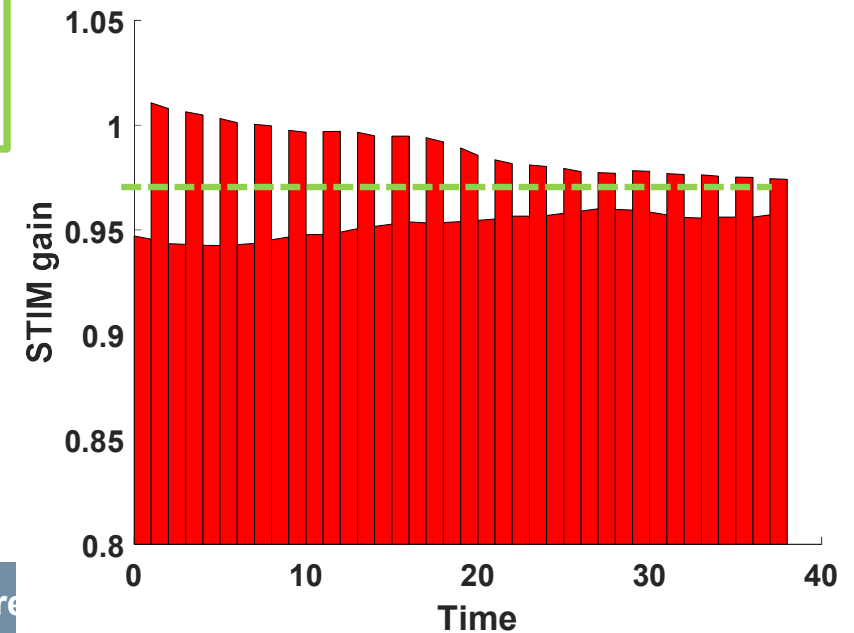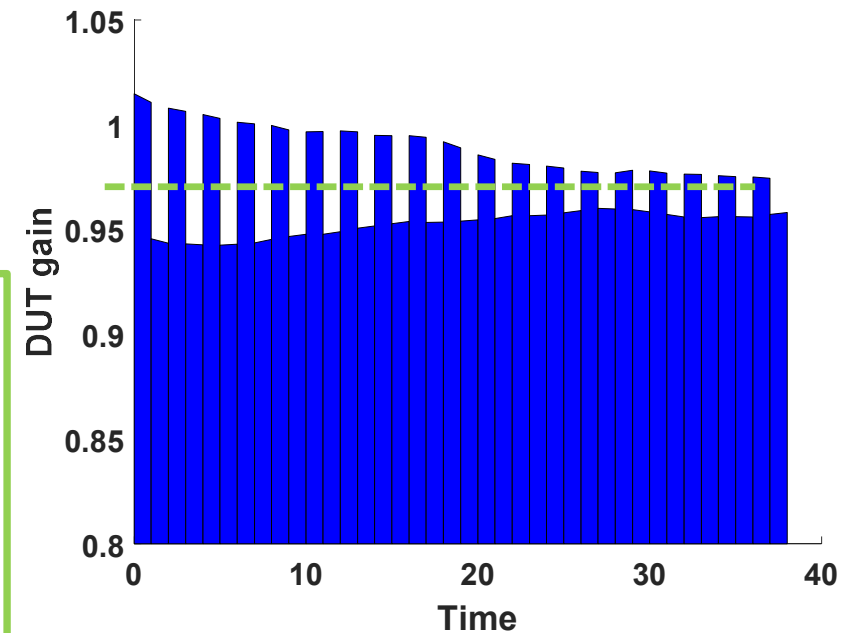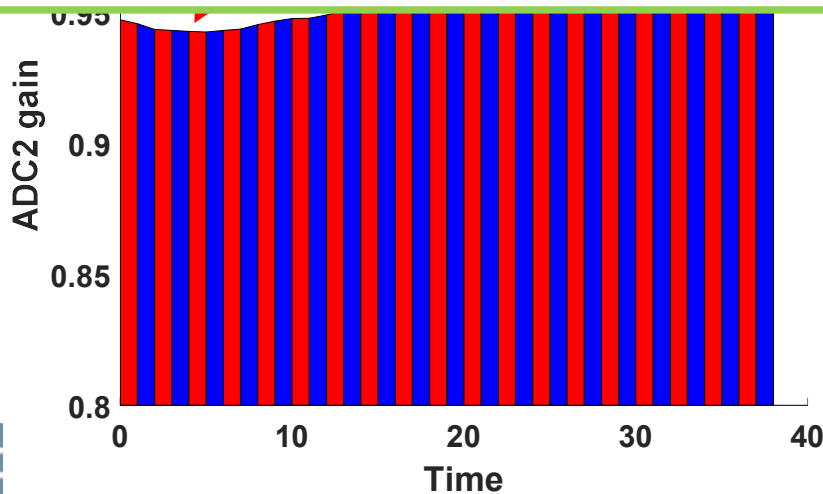

ELIA prototype

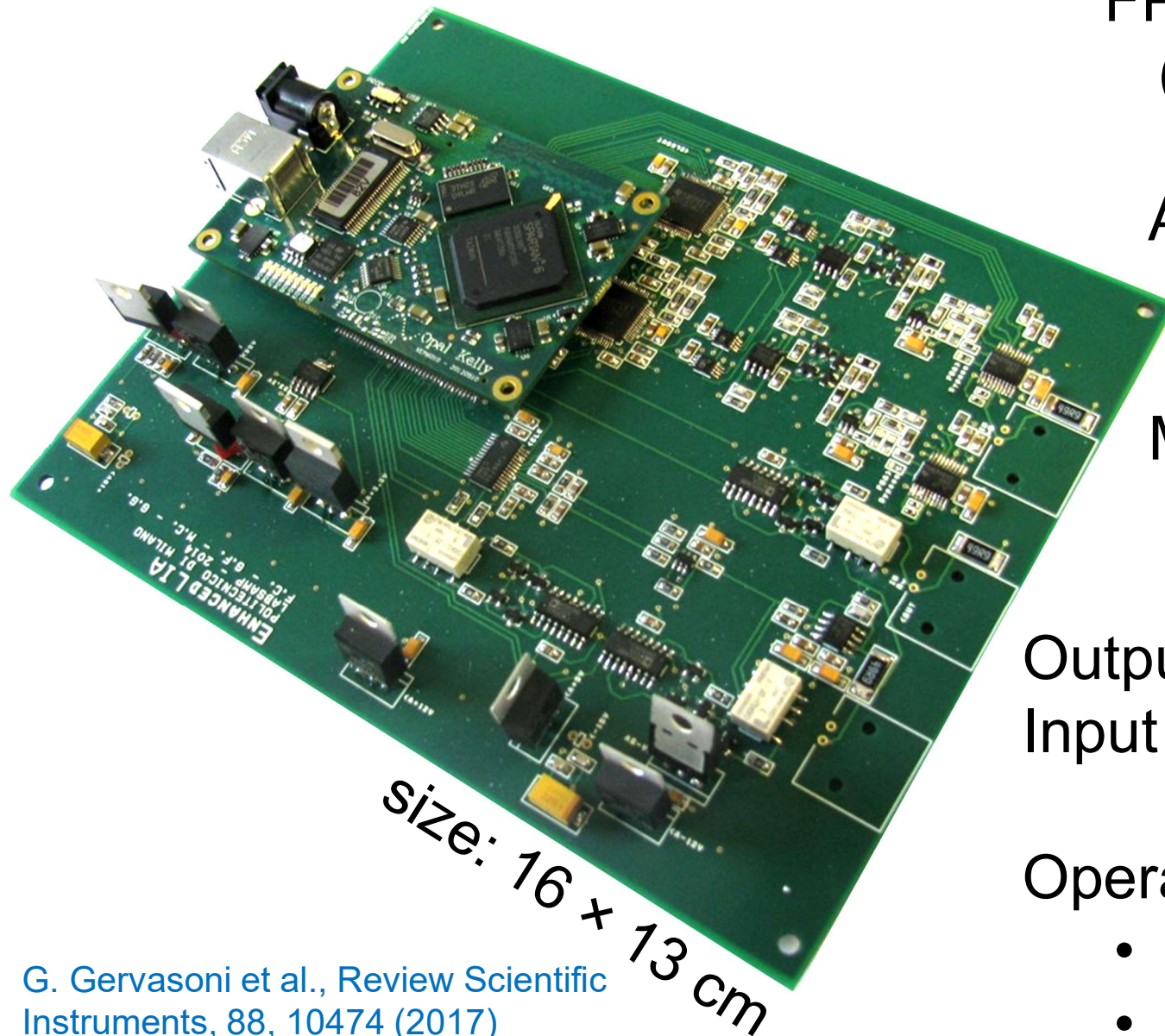

FPGA: Xilinx Spartan 6
(Opal Kelly module)

ADC&DAC: 80MS/s

Maximum AC frequency:
10MHz

Output: 50 μ V – 10V


Input range: ± 100 mV - ± 10 V

Operating modes:

- Two standard LIAs
- ELIA

G. Gervasoni et al., Review Scientific
Instruments, 88, 10474 (2017)

Experimental validation

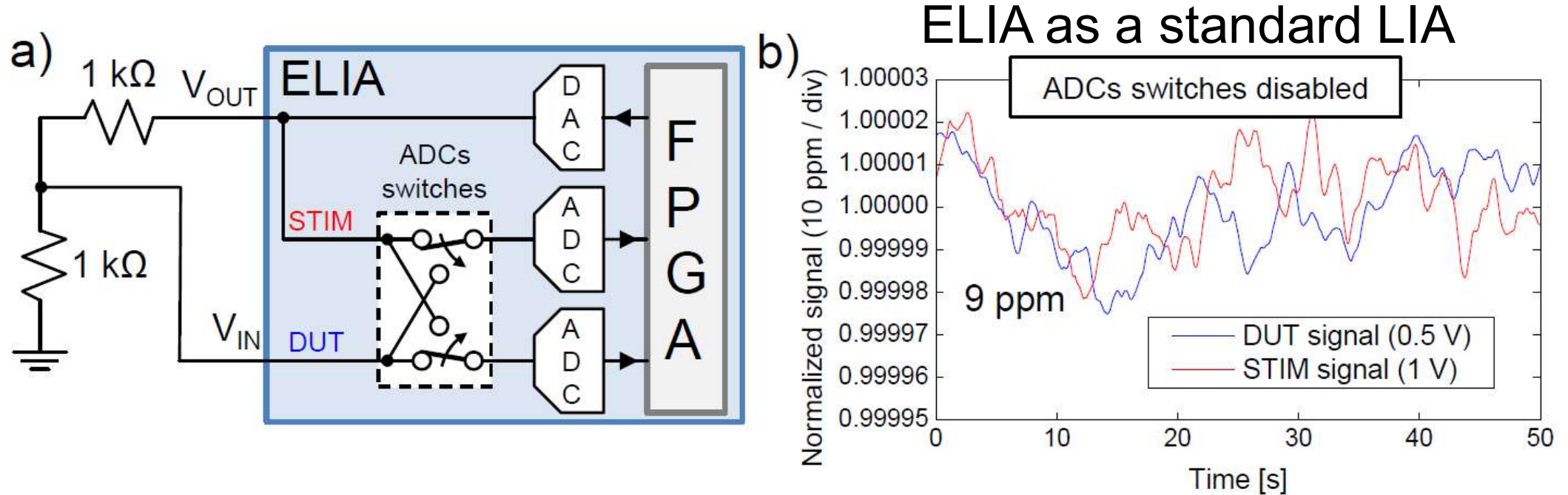


Expected resolution – ideal LIA (no amplitude noise):

- Thermal noise of resistors ($2.8\text{nV}/\sqrt{\text{Hz}}$) + amplifier ($2.2\text{nV}/\sqrt{\text{Hz}}$) + generator ($10\text{nV}/\sqrt{\text{Hz}}$)
- $\text{BW} = 1\text{Hz}$

$$\Delta V_{\text{noise}} \approx \sqrt{2} \sqrt{(2.8\text{nV})^2 + (2.2\text{nV})^2 + (10\text{nV})^2} = 15\text{ nV}$$




Relative resolution: $\frac{\Delta V_{\text{noise}}}{0.5\text{V}} = 0.03\text{ppm} !$

Experimental validation

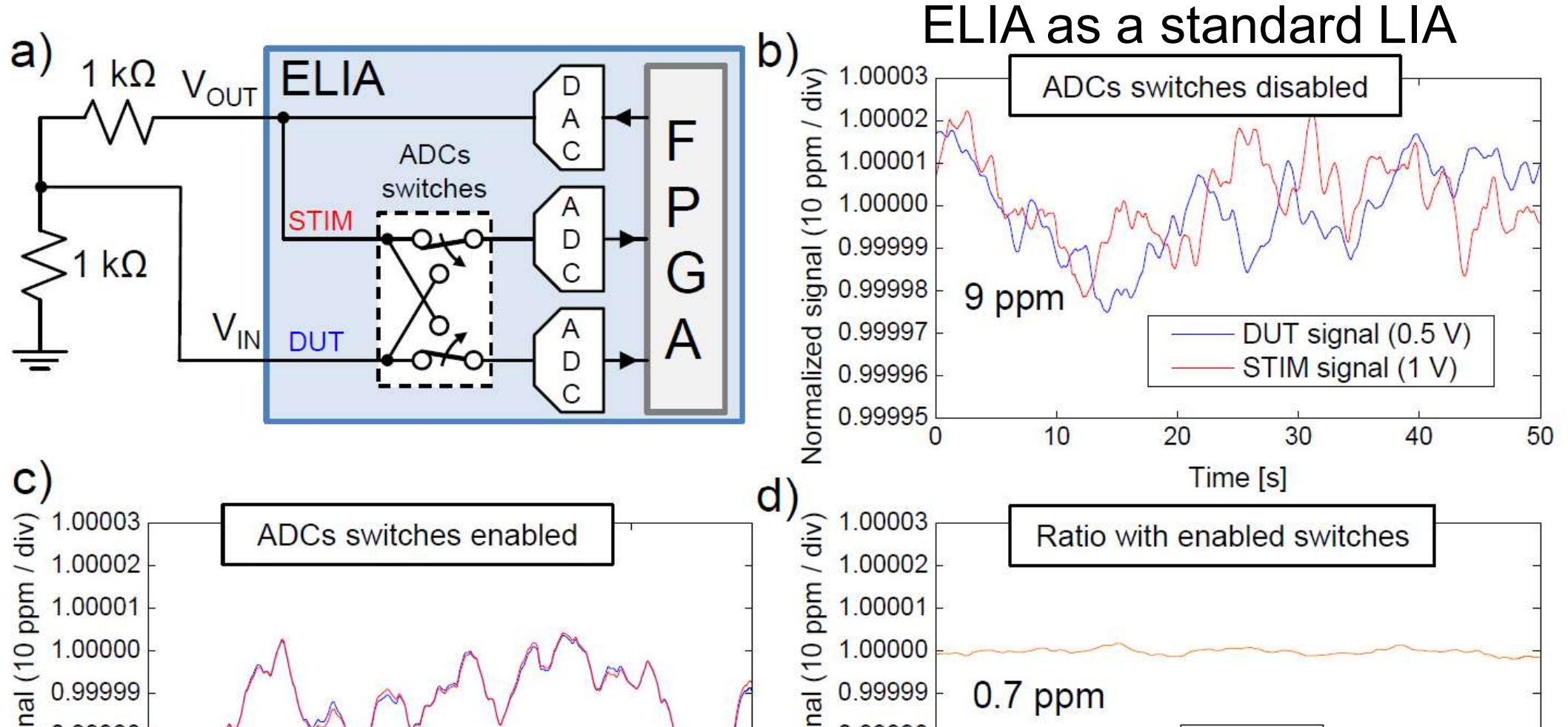

NOTE: the ratiometric approach does NOT improve the SNR if the additive noise is dominant: $\frac{A_{DUT} + noise_{DUT}}{A_{STIM} + noise_{STIM}} \neq |T_{DUT}|$

High resolution spectroscopy

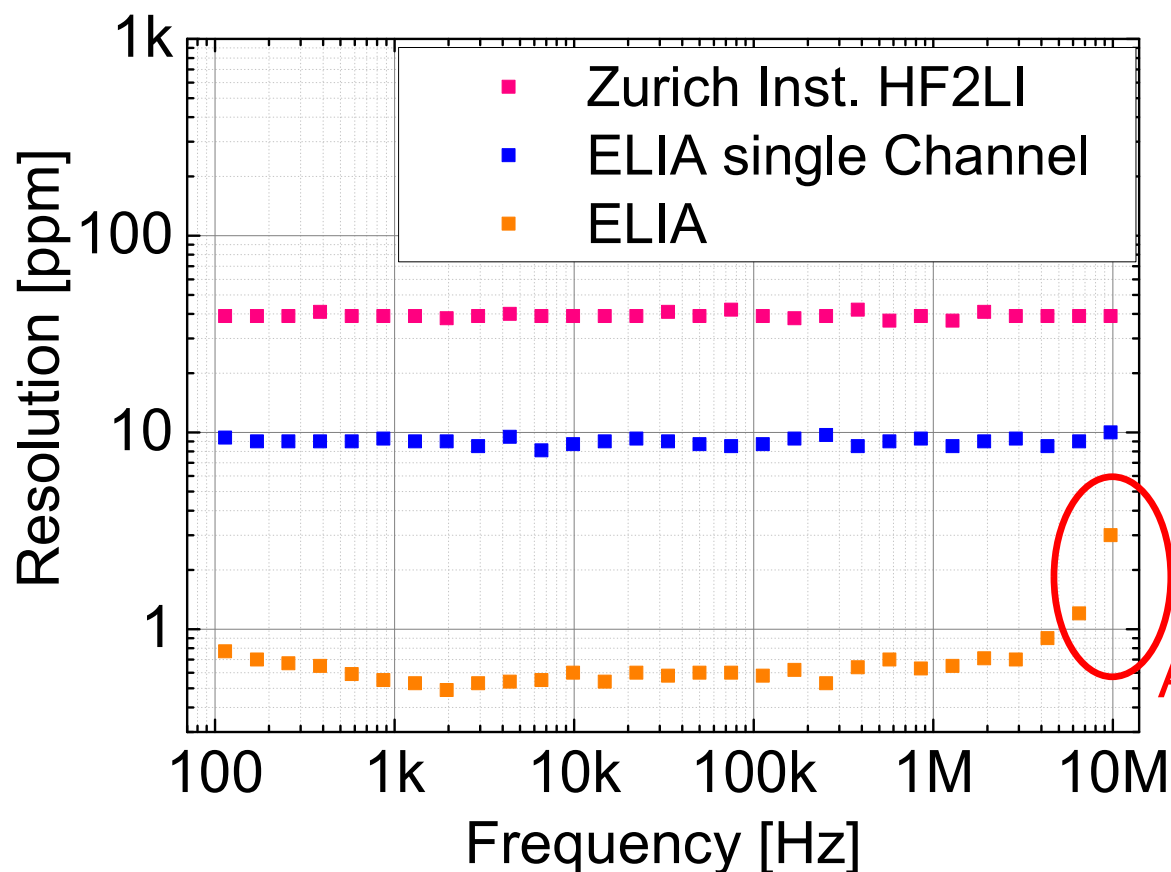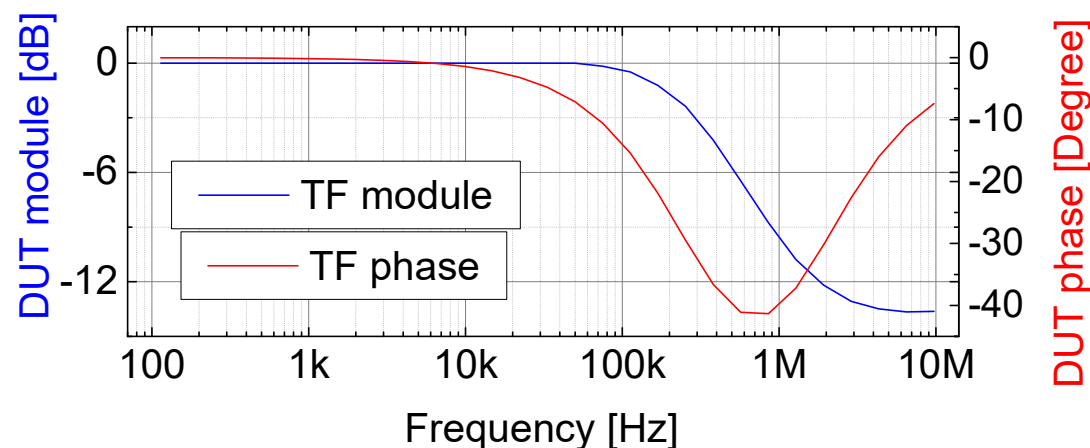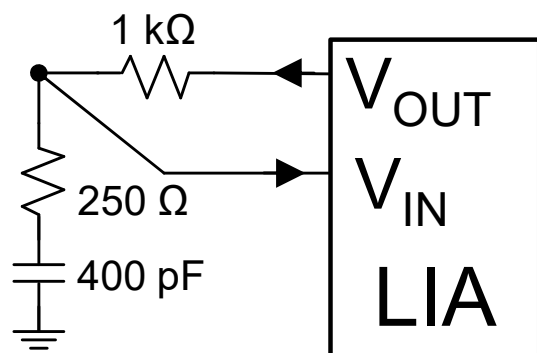

Resolution is insensitive to phase and module of V_{in} !

Antialiasing filter ?

Summary

- Slow ($1/f$) random fluctuations of the system gain:
 - Signal source (DAC, optical source,...)
 - Temperature dependence of amplifier/filter gains (C, R,...)
 - Gain fluctuation of ADC
 - A standard LIA does NOT solve the problem of gain fluctuations
- Ratiometric approach
 - Custom instrument using two ADCs
 - Sub-ppm resolution up to 6MHz
 - No external components
 - No calibration

} “Plug & measure”
- M. Carminati, et al., “Note: Differential configurations for the mitigation of slow fluctuations limiting the resolution of digital lock-in amplifiers,” *Rev. Sci. Instrum.*, vol. 87, no. 2, p. 026102, Feb. 2016.
- G. Gervasoni, et al. “Switched ratiometric lock-in amplifier enabling sub-ppm measurements in a wide frequency range,” *Rev. Sci. Instrum.*, vol. 88, no. 10, p. 104704, Oct. 2017.