



I³N *Innovative
Integrated
Instrumentation
for Nanoscience*



POLITECNICO
MILANO 1863



High Resolution Electronic Measurements in Nano-Bio Science

Measuring quantum devices below 4K

Cryogenic electronics

Giorgio Ferrari

Milano, June 2025

Outline


- Motivation for cryogenic electronics
 - Challenges
 - Design rules
- Examples

Minimum requirements for the physical implementation of a quantum computer

- Robust, reproducible, and scalable qubit technology
- Qubit initialization
- Universal set of gates (single-qubit operations and two-qubit operations)
- Long-coherence time (figure of merit: number of gates before the state is lost for the environmental disruptions)
- Qubit measurement

[DiVincenzo 2000]


Google quantum computer (sycamore)

 

[J. Bardin, ISSSCC 2022]

54 qubits
(transmons)


 
Target for useful applications:
 10^6 physical qubit!!!



Cables connecting qubits ($\ll 4K$) to room temperature electronics are a limiting factor! (≈ 2 coaxial cables /qubit)

How to scale up QCs?

  Today's Quantum Computers (and tomorrow?)



Fabio Sebastiano

© 2025 IEEE

[F. Sebastiano, ISSCC 2025]



Fundamentals of Cryo-CMOS Circuits and
Systems for Quantum Computing




2025 – Silicon-based computers




22 of 82

The role of cryogenic electronics

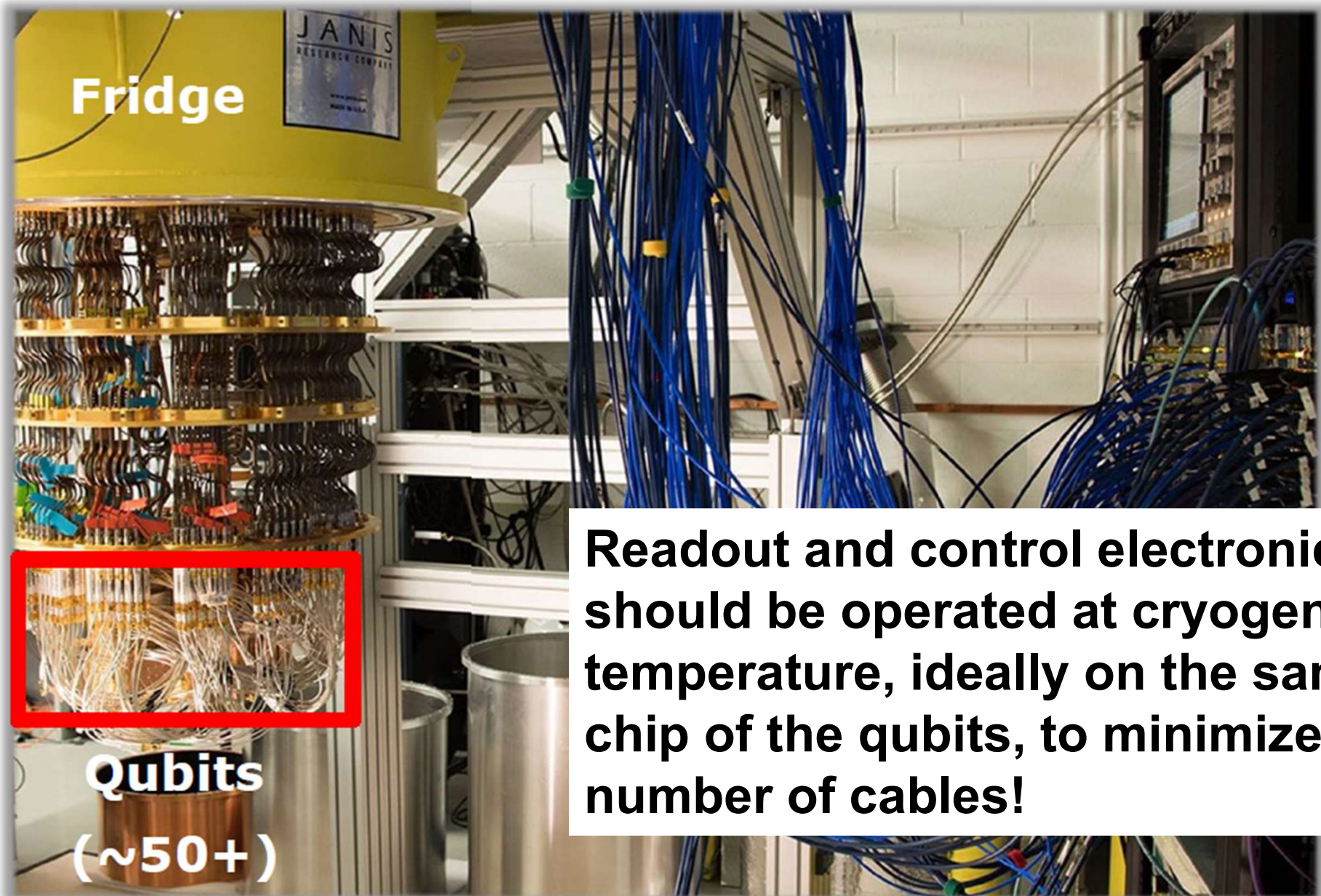

[Bardin, ISSCC 2019]

Cryogenic quantum controller

 

Today

Tomorrow


Future

X. Xue *et al.*, “CMOS-based cryogenic control of silicon quantum circuits,” *Nature*, pp. 205–210, 2021


Outline

- Motivation for cryogenic electronics
 - Challenges
 - Design rules
- Examples

Freeze-out and degenerate semiconductor

 

Electronics below the freeze-out temp.

 

Silicon MOSFETs in standard tech. operate below 40K!


Many GaAs devices operate at cryogenic temperature:
degenerate at 10^{16} cm^{-3}

Limitation: small (and expensive) scale integration

MOSFET operating at 4K

Standard analog CMOS Technology 3.3V, 0.35 μm


PMOS 50 μm / 0.7 μm

 



very similar to the room temperature behavior!

Effects of low temperature


TSMC 40-nm bulk CMOS process

 

  
- substrate Fermi level shifts near to E_c (pMOS) → increase of the threshold voltage
- reduction in electron-phonon scattering → increase in carrier mobility





Problems are tech and size dependent

 

...and no models from the CMOS foundry!

 


AMS 0.35μm

  

Less problems using scaled technologies!


Design rule 1: characterize the technology!

 No simulation models provided by the foundry




Experimental characterization of YOUR technology
is MANDATORY

 For simple circuits 1 nMOS and 1 pMOS is enough
series or parallel combinations of these basic transistors




less conductive MOS

 

more conductive MOS

 Design rule 2: pay attention to mismatch!





K. Das et al. EEE Symposium on
Circuits and Systems, 2010

worsening of mismatch by a factor of 1.5-3 at low temperature compared to room temperature (tech dependent).




Degradation of the offset voltage, linearity of ADC, DAC, bias setting,...

Design rule 3: subthreshold is critical

  

P. A. T'Hart, et al. *IEEE J. Electron Devices Soc.*, pp. 263–273, 2020

 Higher g_m and I_{on}/I_{off} , good!
but...



V_T mismatch of 5mV:

$$I_{out,300K} \approx I_{in} 10^{\frac{5mV}{S_{300K}}} = I_{in} \cdot 1.17$$

$$I_{out,4K} \approx I_{in} 10^{\frac{5mV}{S_{4K}}} = I_{in} \cdot 2.28$$

Design rule 4: limited headroom

LFoondry 180nm: parameters from 300K to 4K

- $V_{T,n}$ from 0.3V to 0.5V
- $V_{T,p}$ from -0.65V to -1.1V
- Power supply: still 1.8V
- no subthreshold


stack up few transistors!

and/or add complexity:

- Back-biasing if SOI tech. [Bohuslavskyi 2018]
- Feed-forward Body Biasing [Overwater 2023]

and

kink effect (old tech.)

 

limit the V_{DS} !

or use more scaled technologies

Noise


Thermal noise: $\overline{e_n^2} = 4kT \frac{\gamma}{g_m}$

$T \searrow$, $g_m \nearrow \rightarrow$ **noise** $\searrow \searrow$
(0.1 nV/ $\sqrt{\text{Hz}}$)

For scaled tech.: white noise can be limited by **shot-noise** (T independent)

Self-heating: MOS channel can be at higher T (reported >40K for $T_{\text{amb}}=4\text{K}$)

 
Flicker noise: increase or independent (tech and size dependent)



350nm AMS

dominant noise up to tens of MHz


28nm FDSOI tech.

 

Outline



- Spin detection using room temperature instrumentation
- Cryogenic electronics
 - Challenges
 - Design rules
- Examples

 Experimental set-up to study quantum devices




Cryogenic transimpedance amplifier

  Noise equivalent to
 $1.7\text{G}\Omega$ @ 300K




CMOS Technology
 3.3V $0.35\mu\text{m}$

 nMos: $50\mu\text{m}/1.4\mu\text{m}$
pMos: $50\mu\text{m}/0.7\mu\text{m}$



(simplified scheme)


Measurements at 4 Kelvin

 


R still linear ($10\text{M}\Omega$
@300K $\rightarrow$ $24\text{M}\Omega$ @ 4.2K)

C is practically unaffected
by temperature

 Gain, linearity and
bandwidth match the
simulations




Measurements at 4 Kelvin

 


- $2.3 \text{ pA}_{\text{RMS}}$ resolution (14 pA)
 - 32 kHz Bandwidth (190 kHz)
- ≈ 30 times better of RT

M. L. V. Tagliaferri et al, *IEEE Trans. Instrum. Meas.*, pp. 1827–1835, Aug. 2016.

Quantum dots with a single ion implanted

 


Single charge state sensing

 


Spin qubit readout: measurement technique

[S. Subramanian, ISSCC 2023]

 


Bulky off-chip components, fast analog-to-digital converter, μ -wave signals

 Fully CMOS-compatible readout operated at $T < 5K$:




Spin qubit readout: measurement technique

[S. Subramanian, ISSCC 2023]

 


Bulky off-chip components, fast analog-to-digital converter, μ -wave signals

 Fully CMOS-compatible readout operated at $T < 5K$:



 
Compact readout based on current measurement




- Fully-integrated 150-nm CMOS technology (NO inductor or μ w comp.)
- Time division multiplexing architecture
- Direct charge-to-digital conversion
- Low power consumption (1 mW/qubit)

[M. CASTRIOTTA et al., IEEE Solid-state Circuits Letters (2023)]

Programmable floating-gate comparator


 


 - V_{th} few mV! Process variations are critical
- Digital-to-Analog Converter (DAC): power consumption, size



- Floating node charged at V_{th}
- Compact and low power
- How do we change the charge?
- How to compensate for the process variations?

  
Floating gate in standard CMOS technology



➤ It requires high voltages to enable tunneling ($\approx 7V$ in our technology)

[M. Castriotta, Solid State Electronics 189 (2022)]

 Floating gate in standard CMOS technology




- Hot electron injection using a p-type MOSFET
- The electrons are removed by tunneling (coarse global resetting of the floating gates)

[M. Castriotta, Solid State Electronics 189 (2022)]


Hot electron injection in p-type FG transistor

 fine-tuning of floating node charge
(i.e. threshold voltage of the FET)



holes collide with sufficient energy ($\approx 3/2 E_{\text{gap}}$)
to liberate additional electron-hole pairs


- $V_{\text{SFG}} > |V_T|$ (ON)
- $V_{\text{SD}} \gg 0V$ (high electric field)
- $V_{\text{SD}} \gg V_{\text{SFG}}$ ($V_{\text{FG}} > V_D$)

 

$$I_{\text{inj}} = C(V_{\text{SD}} - \gamma V_{\text{ov}})^3 I_d e^{-\frac{B}{V_{\text{SD}} - \gamma V_{\text{ov}}}}$$

[M. Castriotta, Solid State Electronics 189 (2022)]

 Characterization of the FG comparator at 4.2 K




Programming accuracy: **300 μ V**

Sigma: **140 μ V**




Calibration time: **225 ms**

Fall/rise time: **2 ns**

 

- Self-programmable threshold voltage
- Internal permanent FG memory
- "Zero" power dissipated by the memory
- Easy implementation of a TDM architecture

Characterization of the readout at 4.2 K

   

Validation @ 4.2K

[M. CASTRIOTTA et al., IEEE Solid-state circuits letters (2023)]

Threshold current: **1.1 nA**

6 Sigma: **250 pA**

Readout time: **500 ns**

Power consumption: **1.2 mW**

Active area: **0.04 mm²** (8 FGs)

Summary

- Cryogenic CMOS circuits are feasible
 - Disadvantages:
 - higher threshold voltage
 - worse mismatch
 - poor simulation models
 - Advantages:
 - higher mobility
 - less thermal noise
 - less stray capacitances (faster devices)
- Transimpedance amplifiers (BW=30kHz, noise= 2.3pA_{RMS})
- RF and baseband spin qubit readout
- ... and also complex system-on-chip: see prototype of quantum controller by Intel (X. Xue et al., Nature, 2021)

Thank you for you attention!

