



POLITECNICO DI MILANO

Piazza Leonardo da Vinci, 32 - 20133 Milano
Tel. +39.02.2399.1 - <http://www.polimi.it>



Advanced course on

**HIGH RESOLUTION ELECTRONIC MEASUREMENTS
IN NANO-BIO SCIENCE**



**ADVANCED TIAs
Reaching aA resolution**

Marco Sampietro



How to :

1 - Extend Bandwidth → reach MHz

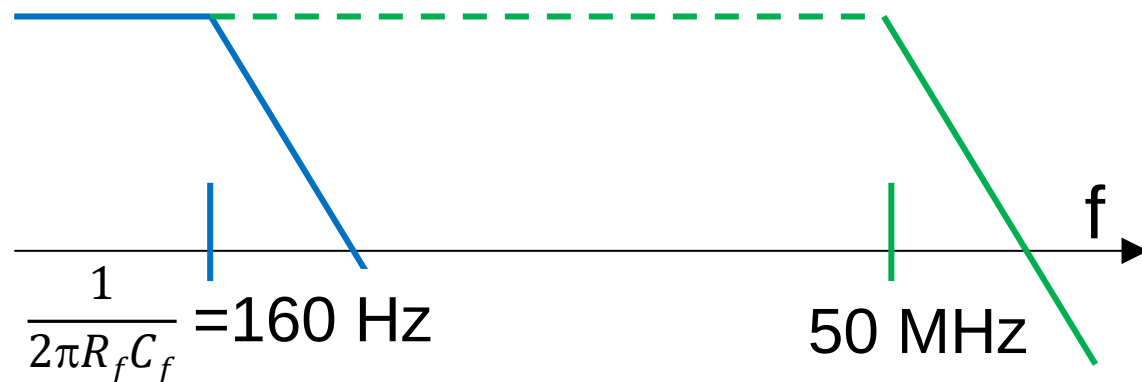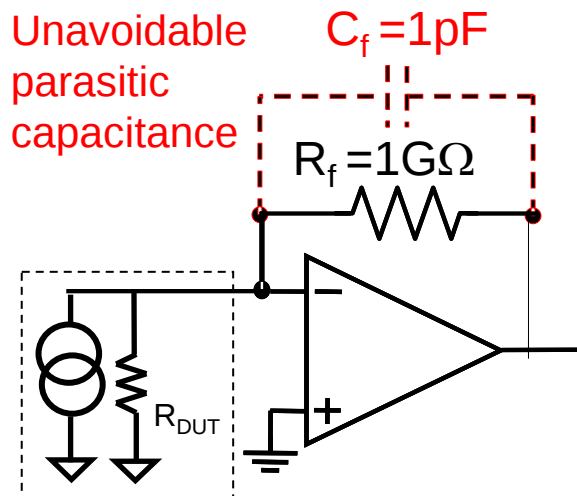


2 - Extend Sensitivity → reach attoAmpère (10^{-18}A)




Why working at higher frequencies ?

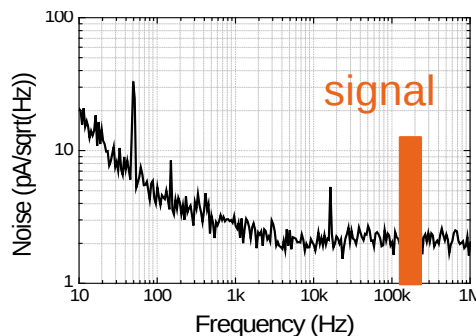
Go away from $1/f$ noise of many sensors/devices



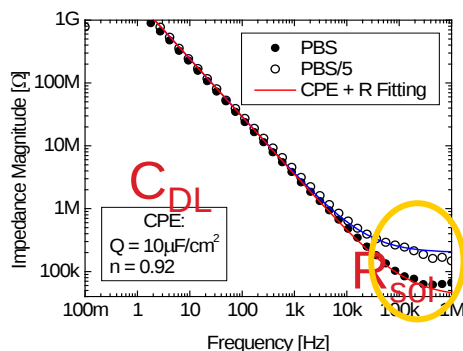Track interesting physics that may be there



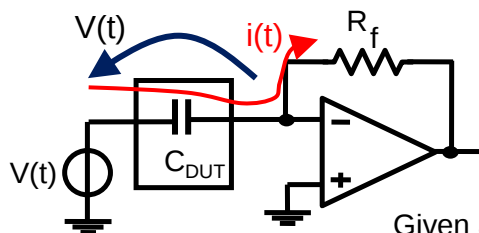Investigate capacitive behaviour in nanodevices



$$i(\omega) = \frac{v(\omega)}{1/j\omega C} = v(\omega) \cdot j\omega C$$

Given a current resolution...


at higher frequency ... smaller C can be measured



How to extend BW ? A guide for circuit designer


T – network

Compensated Transimpedance Amplifier

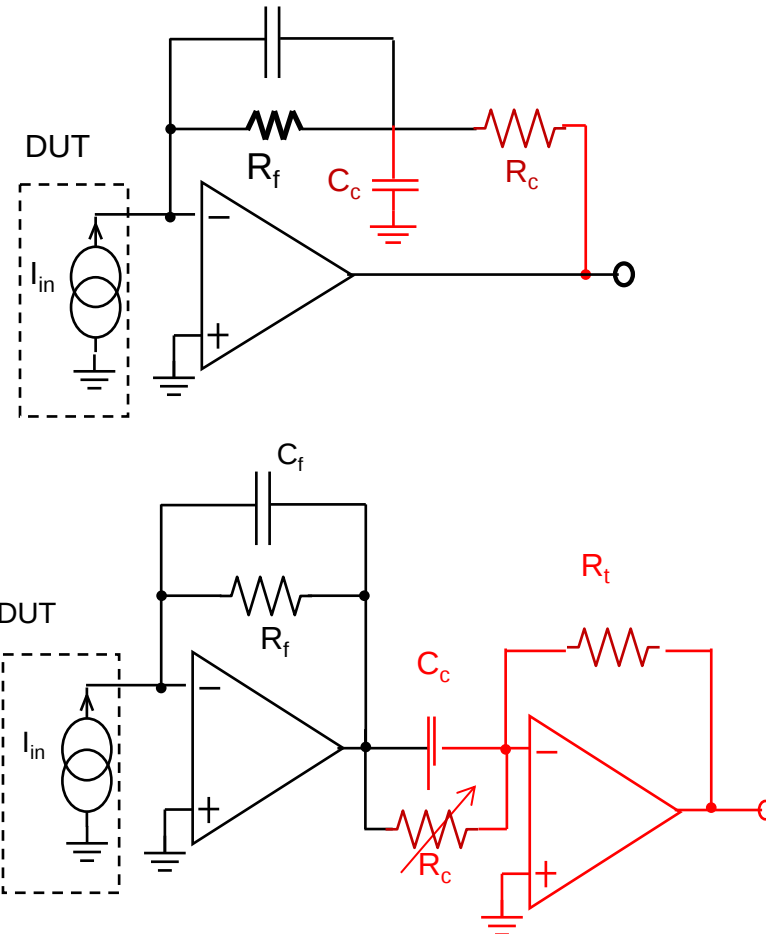



T – network: transfer function

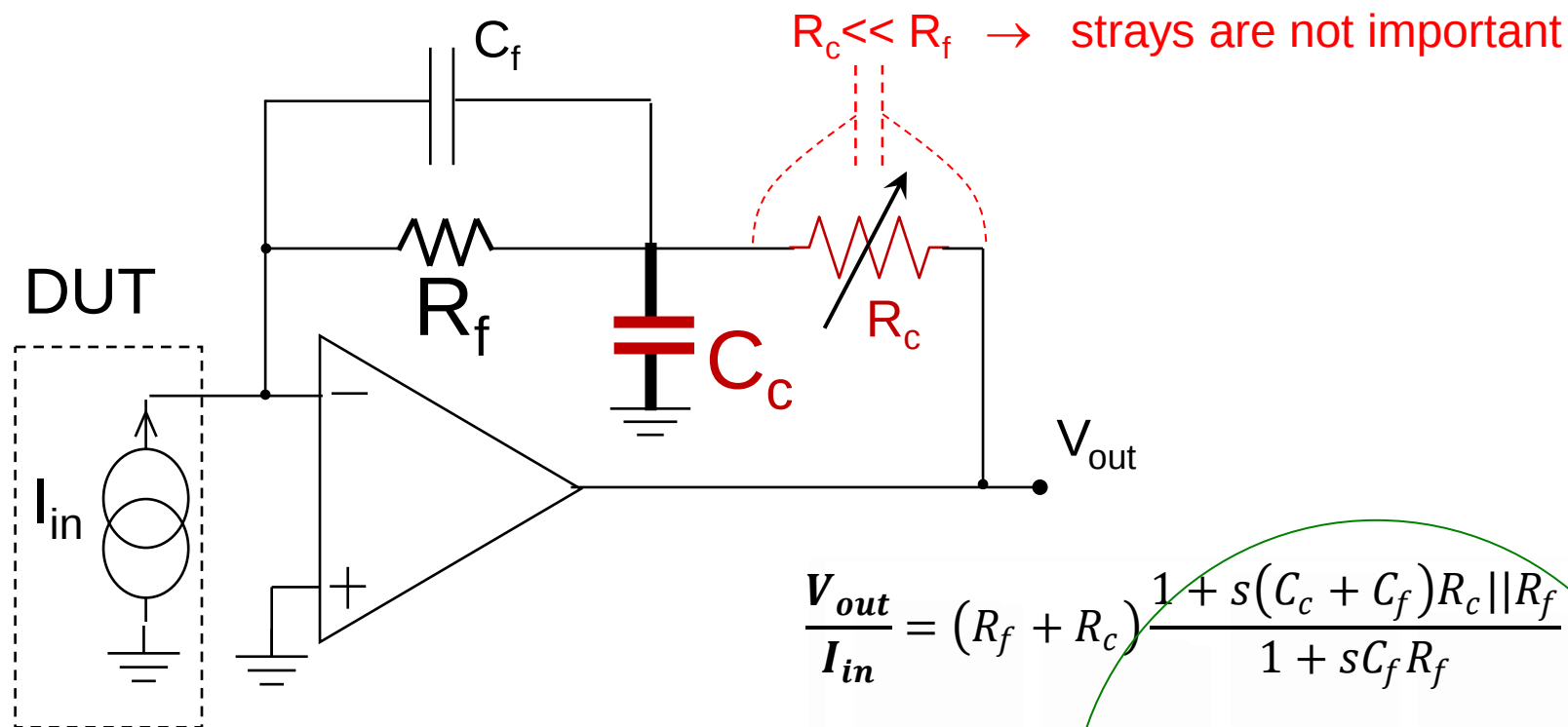

$$\frac{V_{out}}{I_{in}} = (R_f + R_c) \frac{1 + s(C_c + C_f)R_c || R_f}{1 + sC_f R_f}$$

$$\frac{V_{out}}{I_{in}} = (R_f + R_c) \quad \leftarrow$$

Bandwidth limited by OpAmp !


R_c calibrated to obtain
 $(C_c + C_f) R_c || R_f = R_f C_f$



$$C_c R_c \approx R_f C_f$$




T network – low frequencies

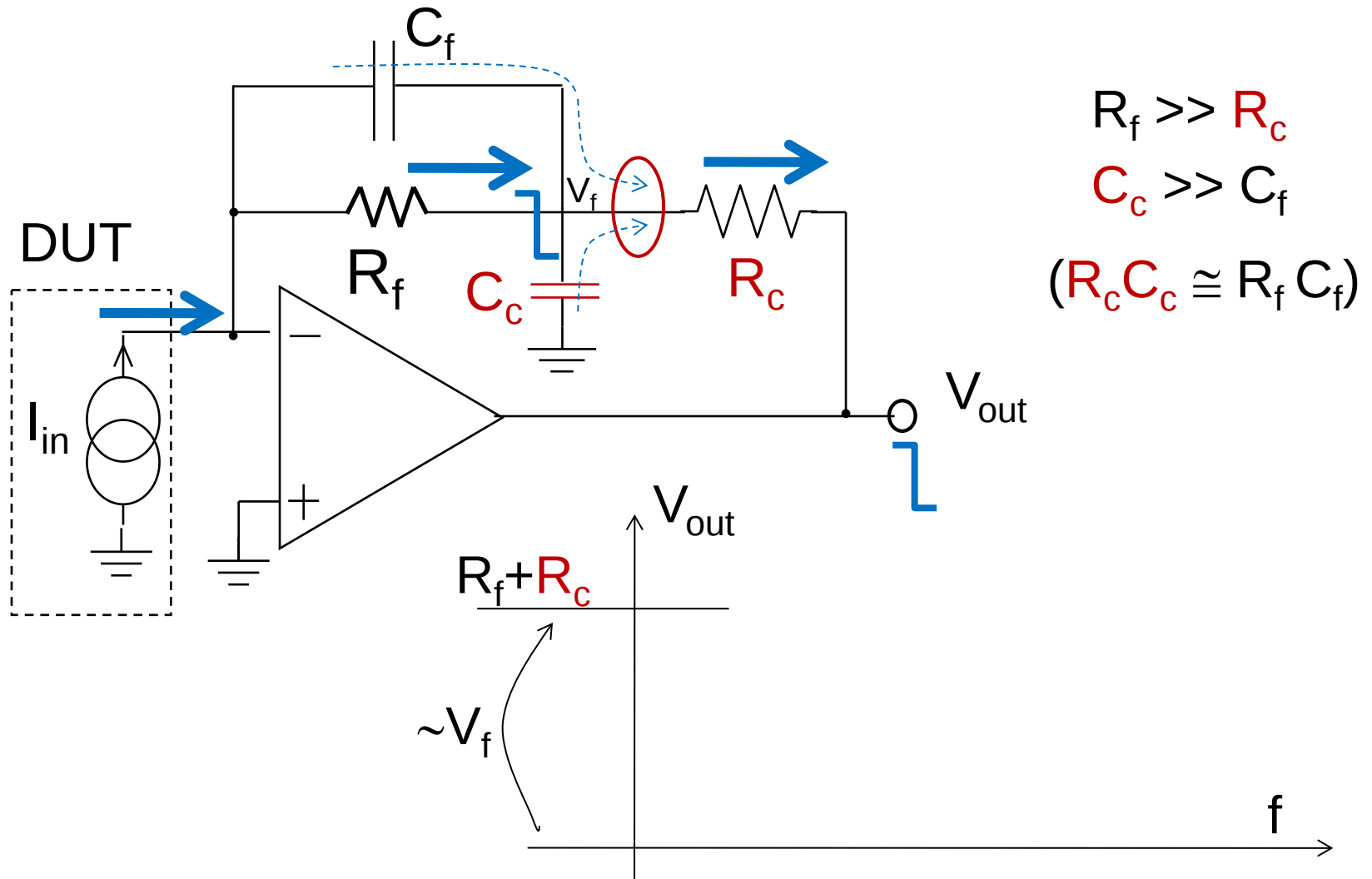




T network - medium frequencies

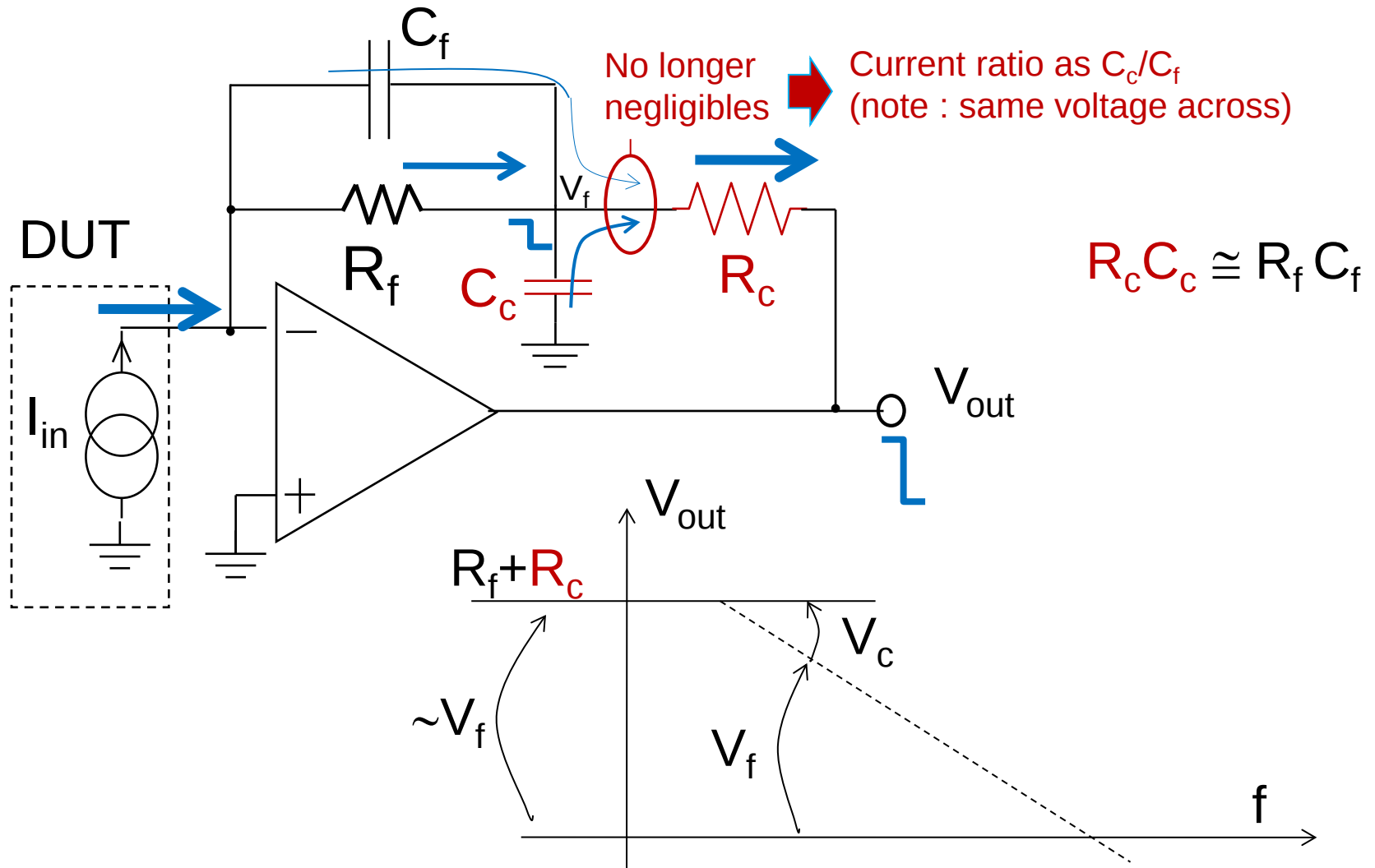




T network - high frequencies

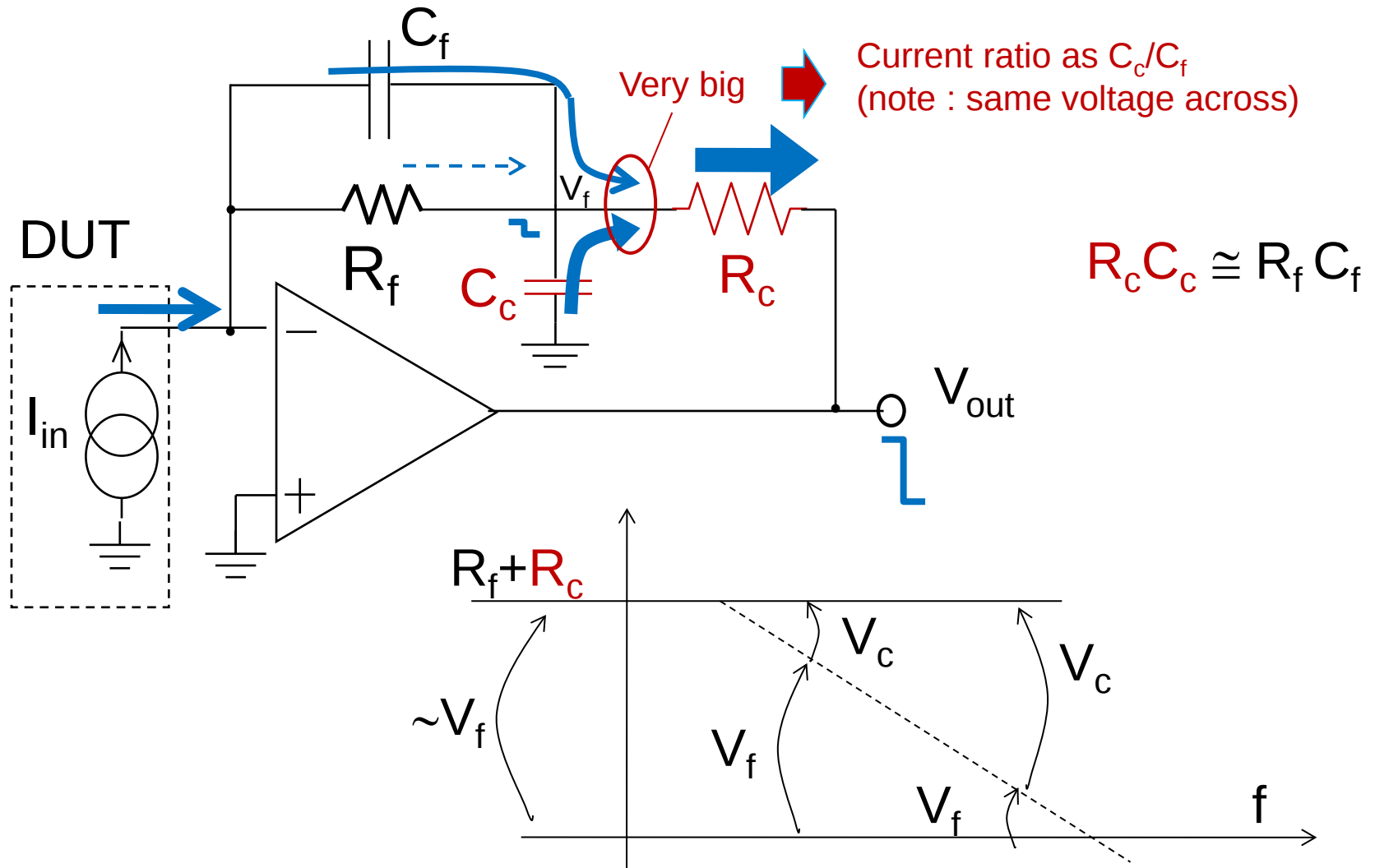




T – network: stability

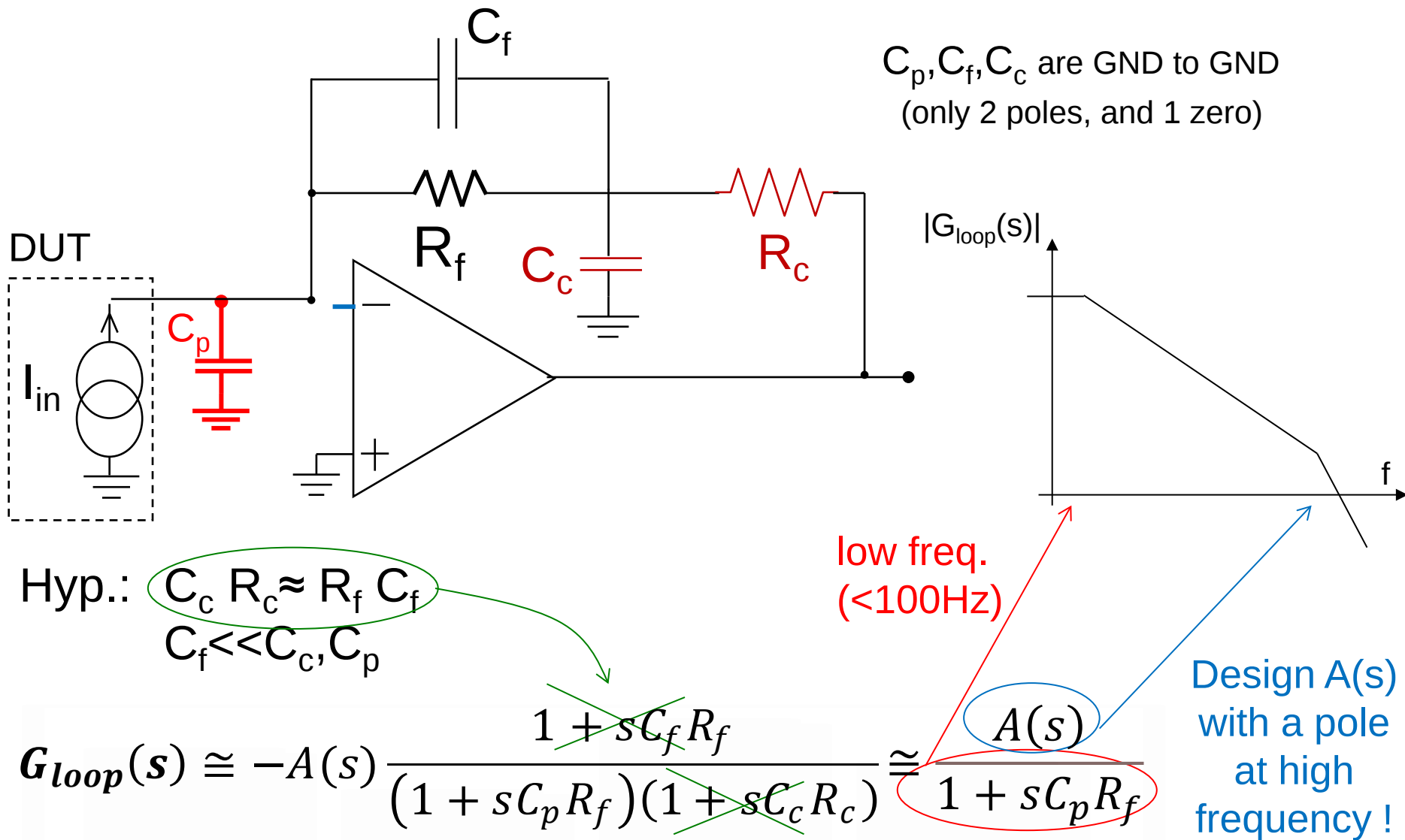



T – network: noise of the added section

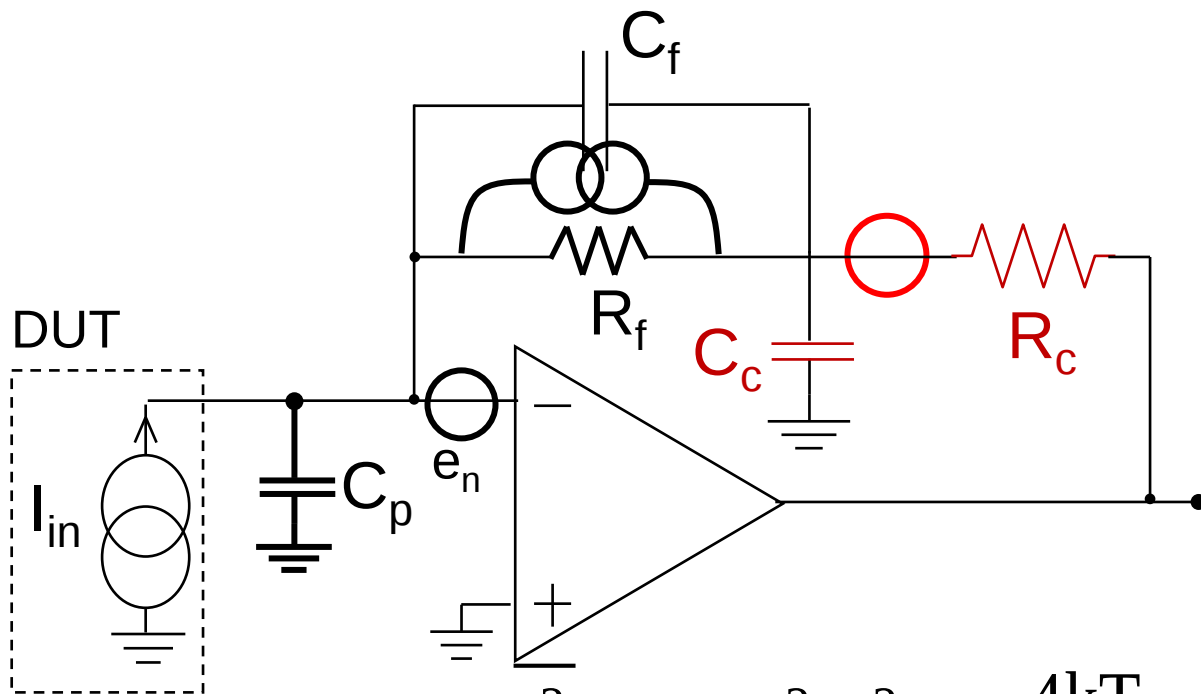

$$i_n^2 = \underbrace{e_n^2 \omega^2 C_p^2 + \frac{4kT}{R_f}}_{\text{LIKE A STANDARD AMP.}} + \frac{4kT \cdot R_C}{(R_f + R_C)^2}$$

NEGLIGIBLE



Howard, RSI, 70, p.1860 (1999): BW=17kHz, $i_{eq} \approx 1.3\text{fA}/\sqrt{\text{Hz}}$ up to 100Hz



How to extend BW ? A guide for circuit designer


T – network

**Compensated
Transimpedance
Amplifier**

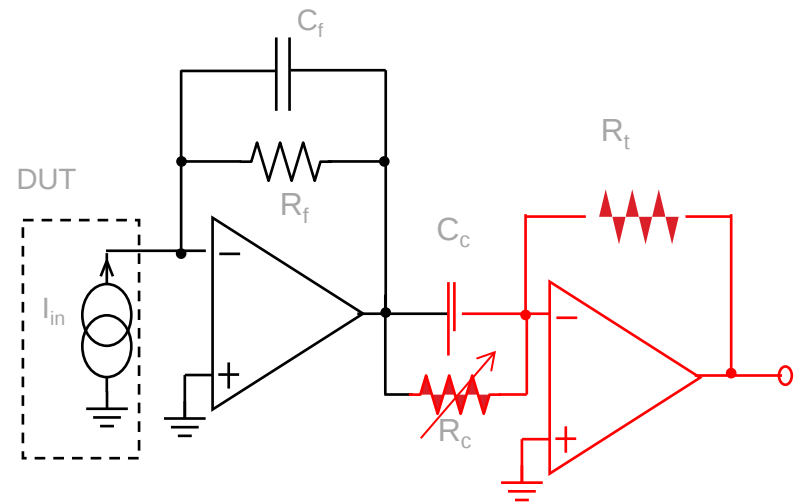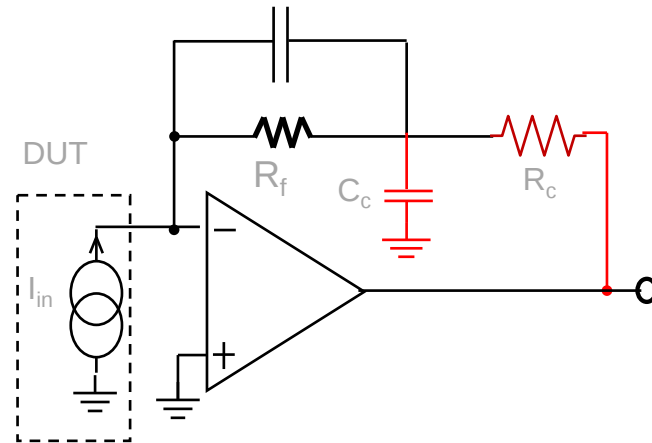



Compensated Transimpedance Ampl.

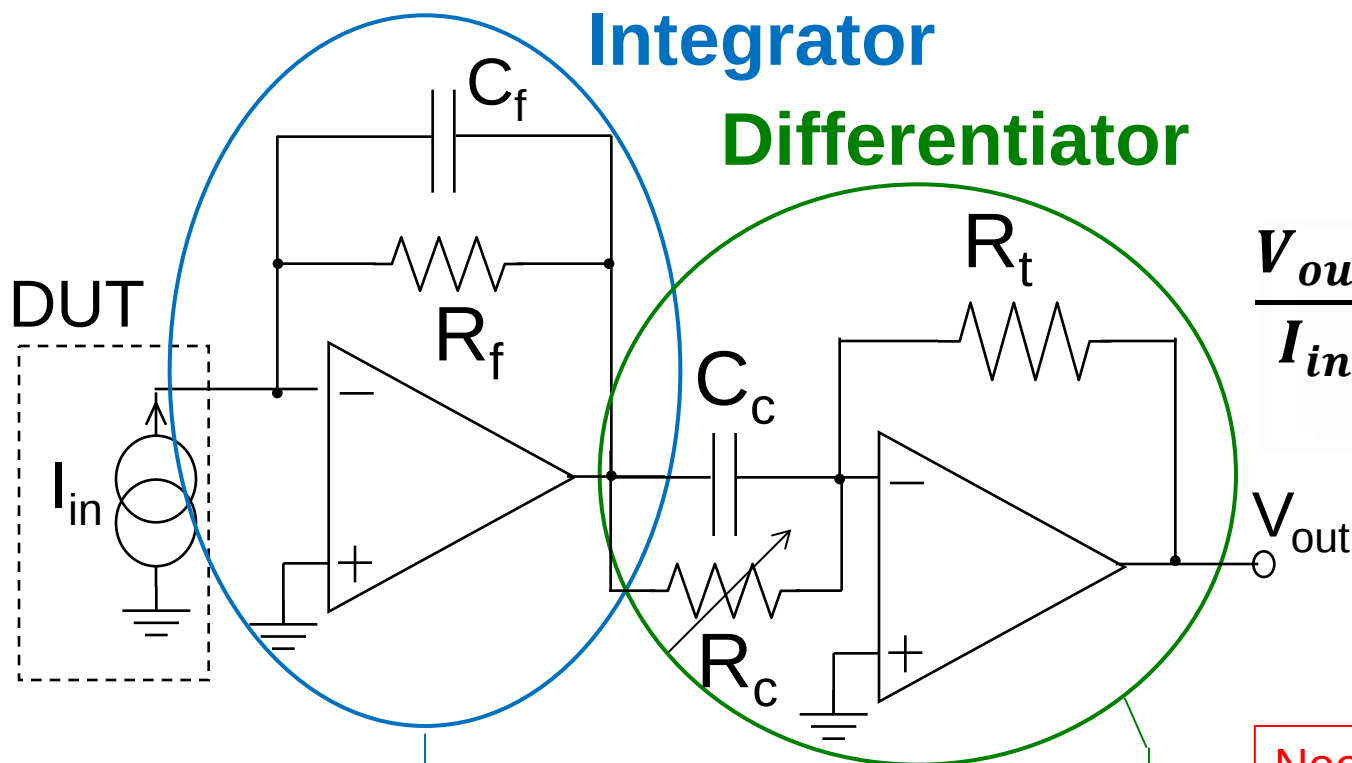


$$\frac{V_{out}}{I_{in}} = R_t \frac{R_f}{R_c} \frac{1 + sC_c R_c}{1 + sC_f R_f}$$



$$C_c R_c = C_f R_f$$

Needs careful tuning of R_c

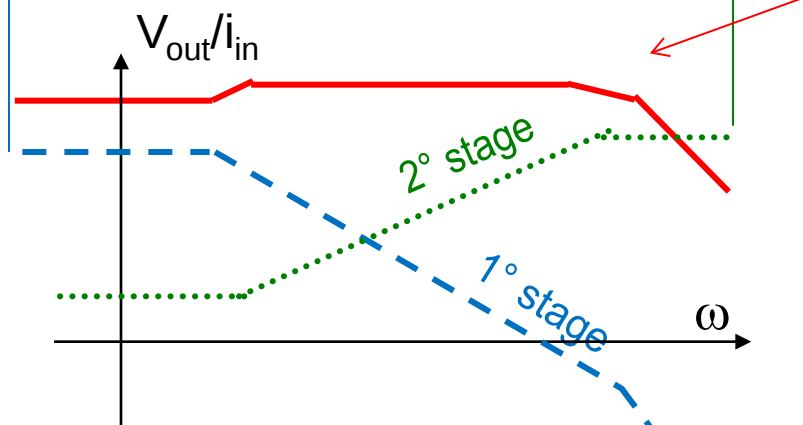


$$\frac{V_{out}}{I_{in}} = R_t \frac{R_f}{R_c}$$


Carlà, RSI, 75, p.497 (2004),
Ciofi, IEEE Instr.&Meas. 55, p.814 (2006)
Carminati, Analog IC Sig. Process (2013)



Compensated Transimpedance Ampl.

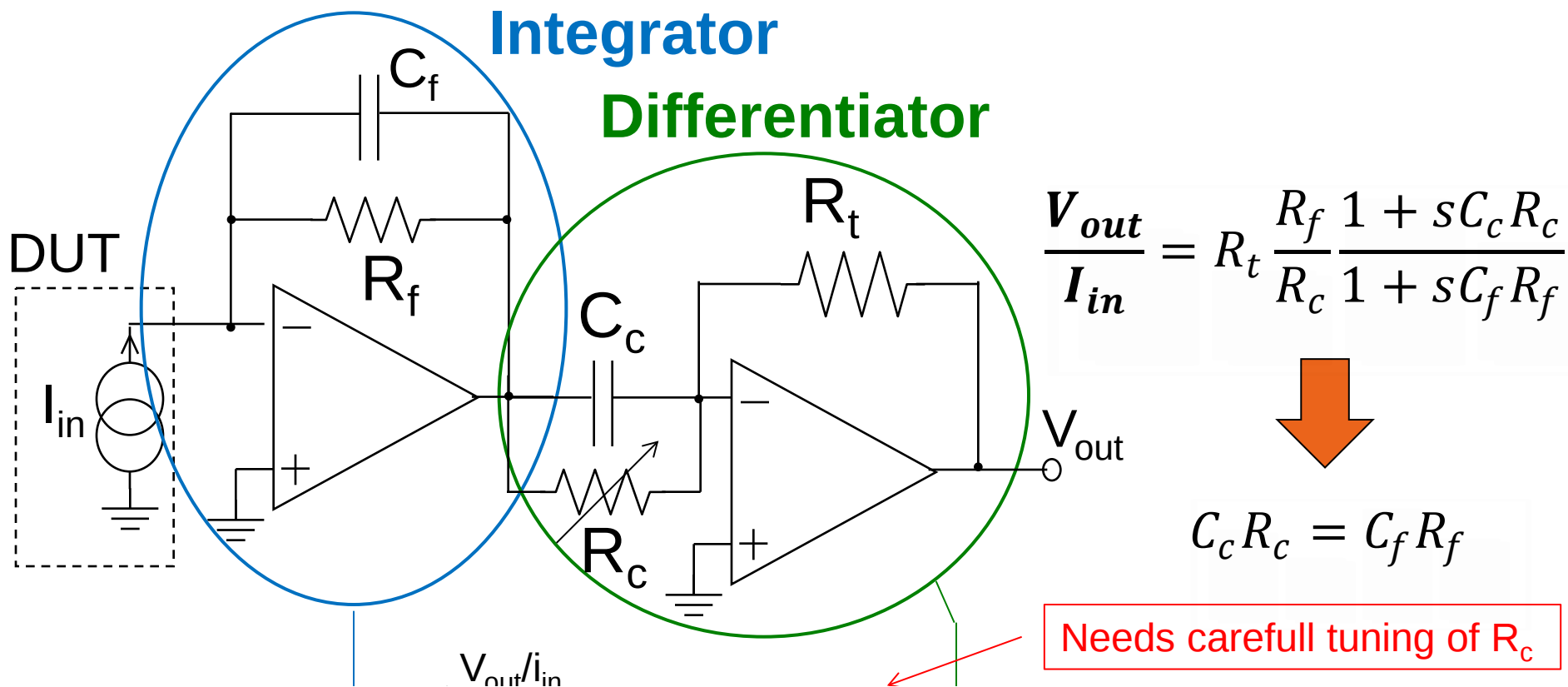


Why keeping R_f and R_c ?

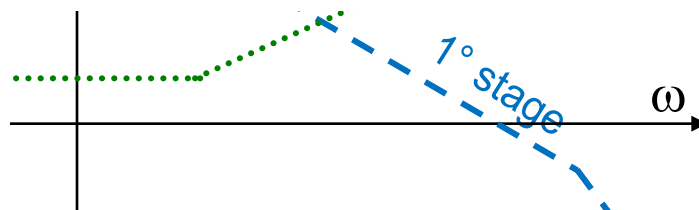

Carlà, RSI, 75, p.497 (2004),
Ciofi, IEEE Instr.&Meas. 55, p.814 (2006)
Carminati, Analog IC Sig. Process (2013)





NO R_f and R_C - SIGNAL OK

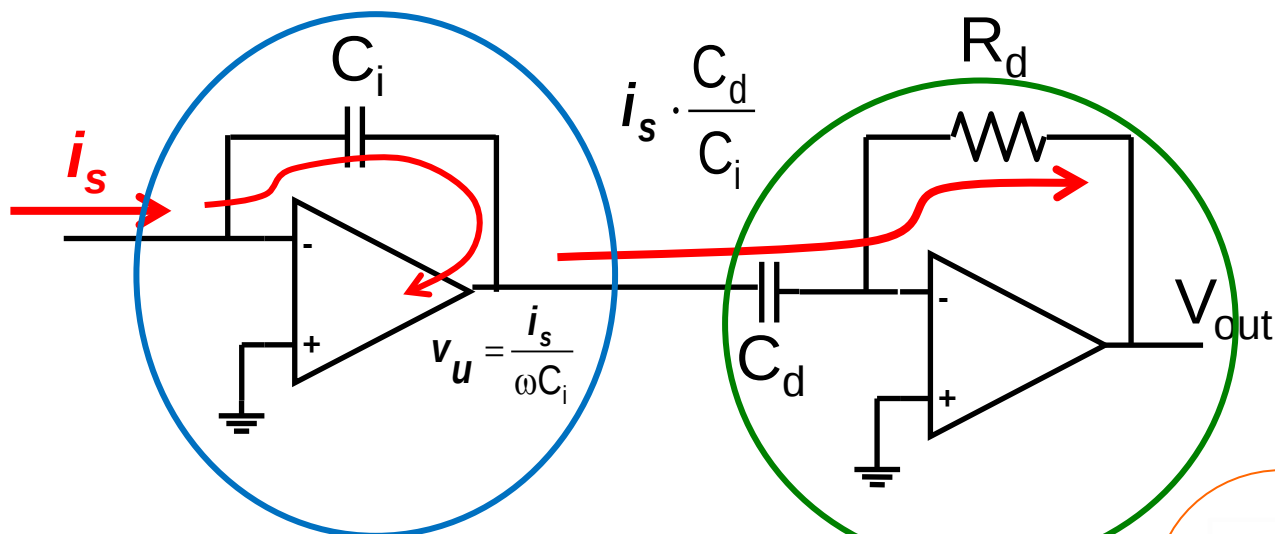

Integrator





Differentiator

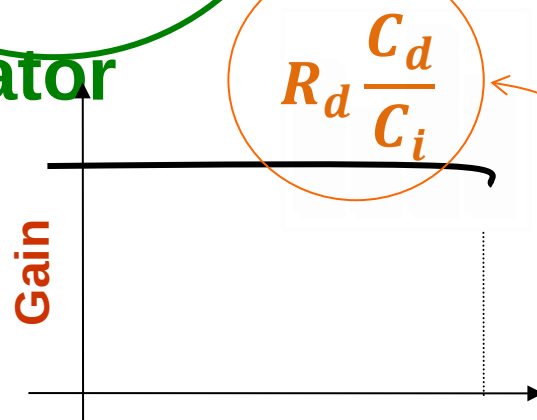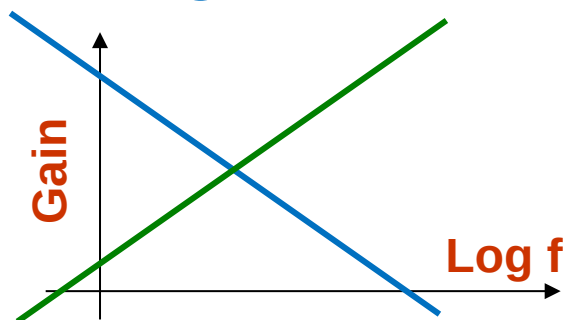

Stable, easy to be set,
linear, no calibration



NO R_f and R_C - BANDWIDTH OK

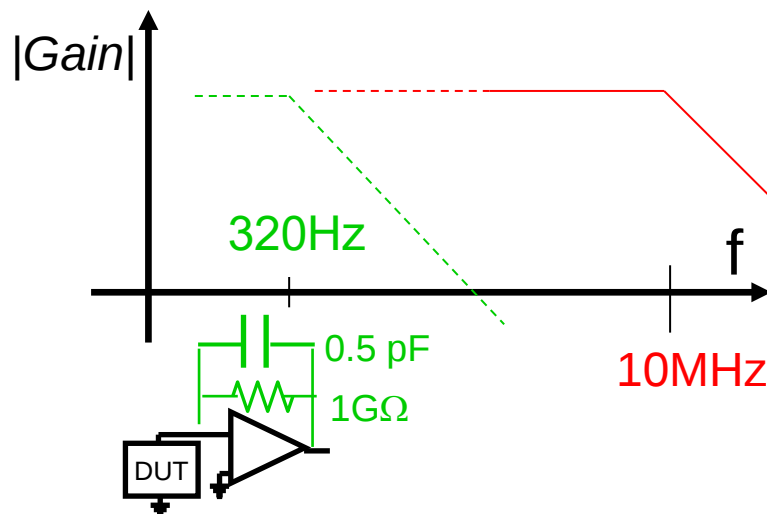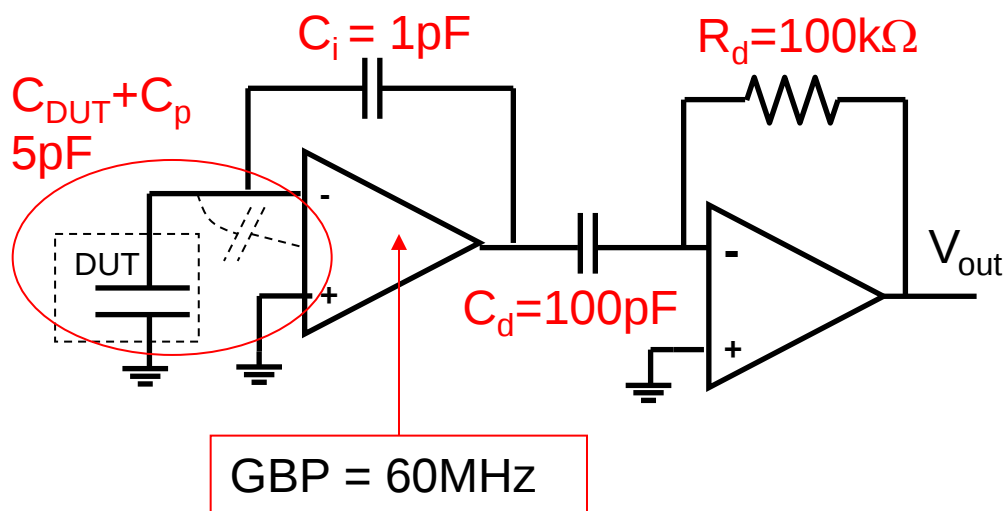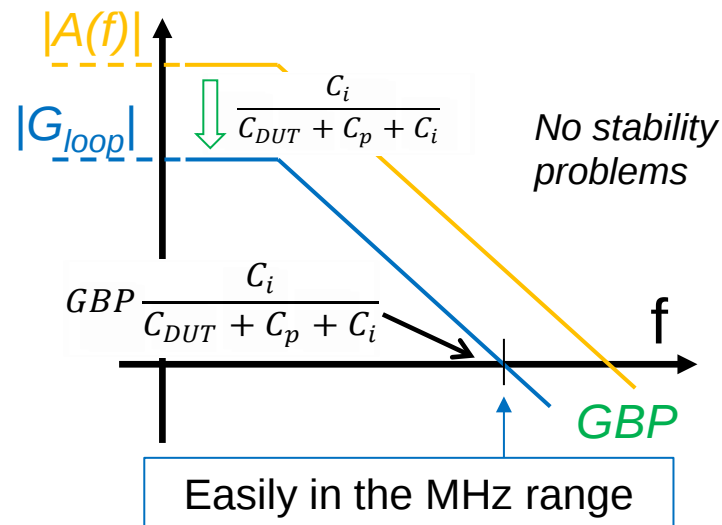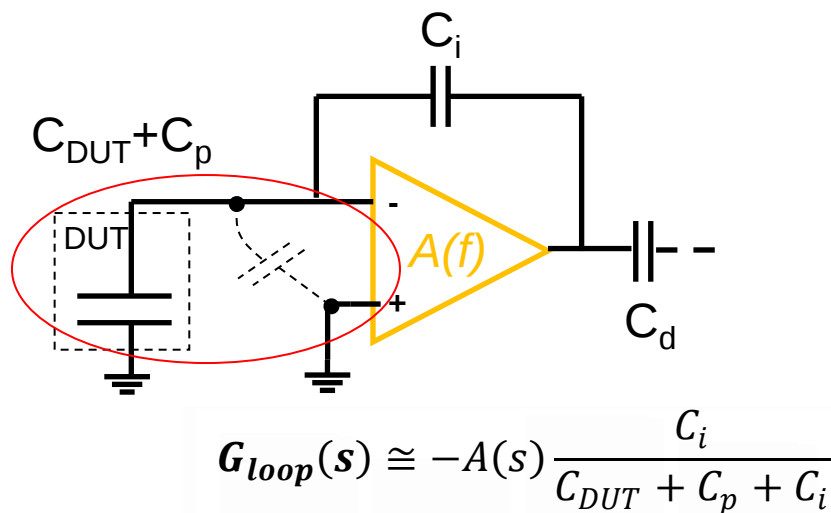





NO R_f and R_C - NOISE OK

Minimum possible
Noise !

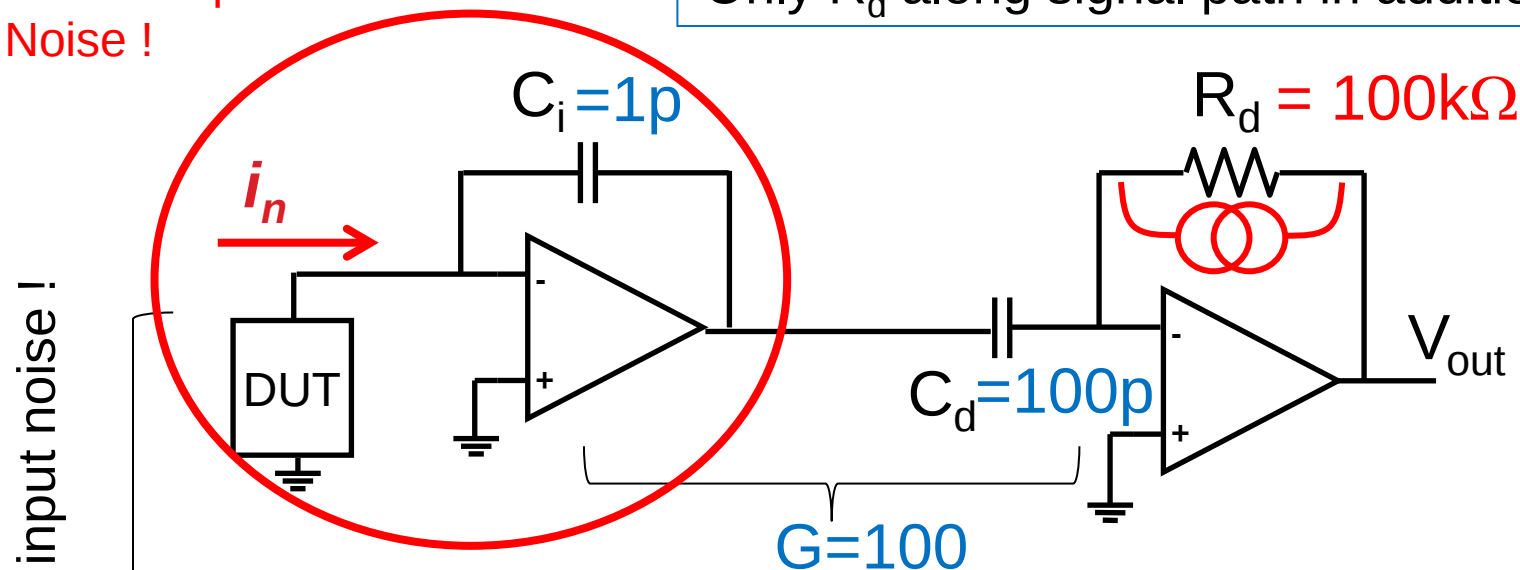Only R_d along signal path in addition to OpAmps



Same equivalent input noise !

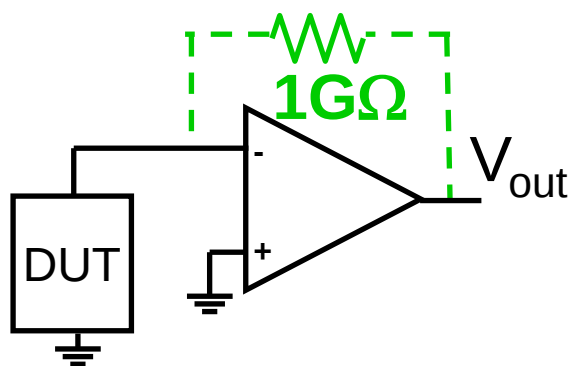


$$S_i = \frac{4kT}{R_d} \left(\frac{C_i}{C_d} \right)^2$$




Equivalent to $1G\Omega$



NO R_f and R_C - OpAmp SATURATION

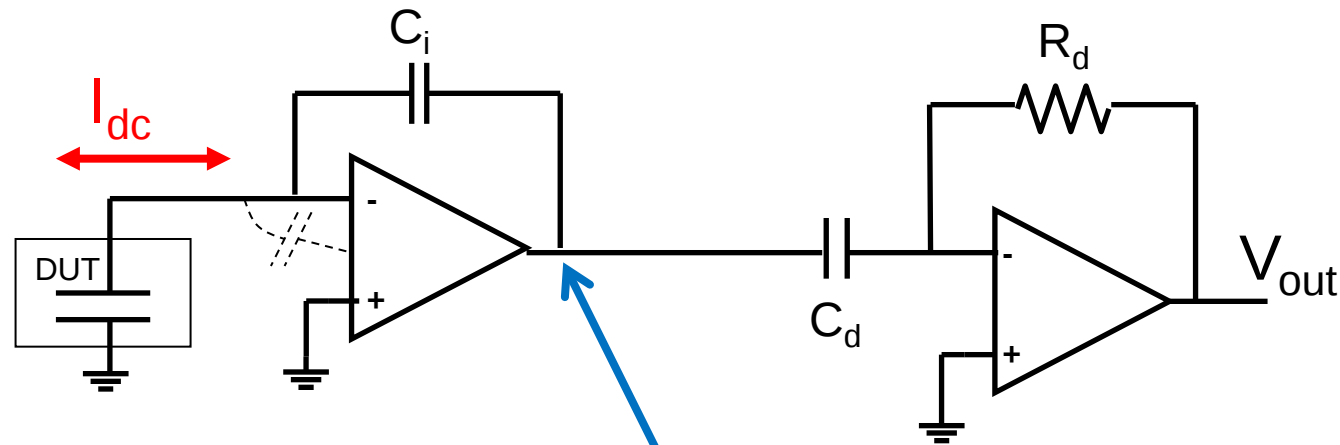
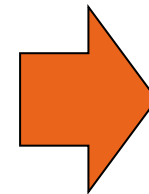
$$V_{out}(t) = \frac{1}{C_i} \int I_{dc} dt = \frac{I_{dc}}{C_i} t$$




We need to reset !


Unavoidable OpAmp saturation !



Pulsed reset

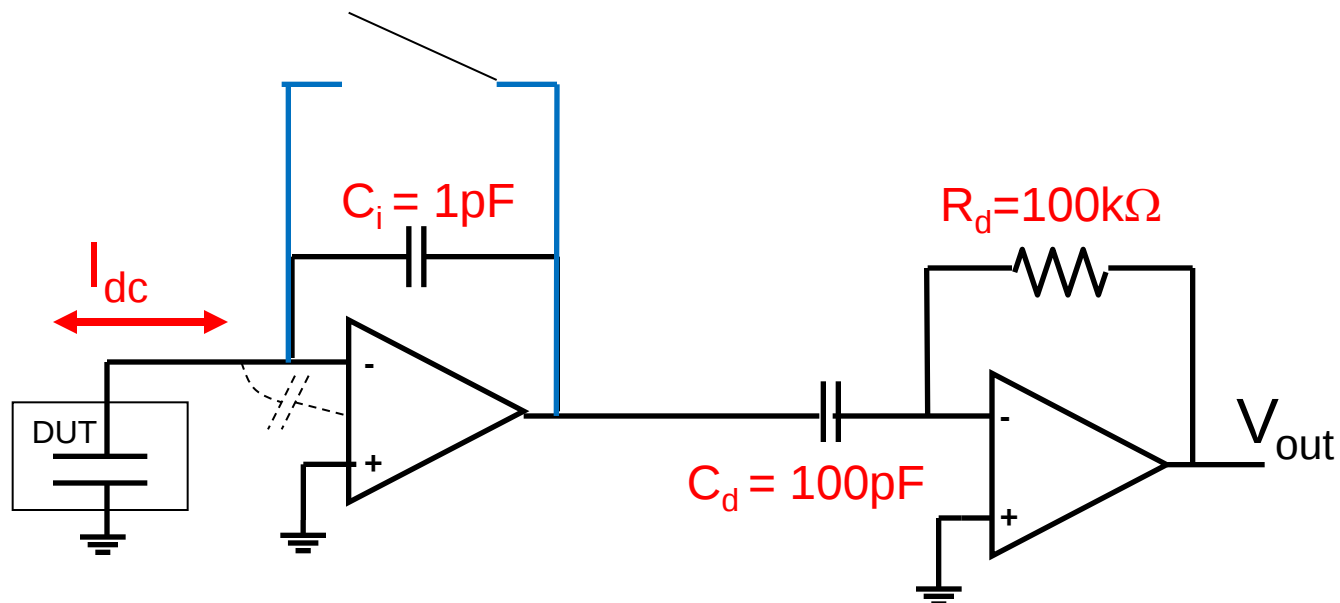

Limited time for measurement :

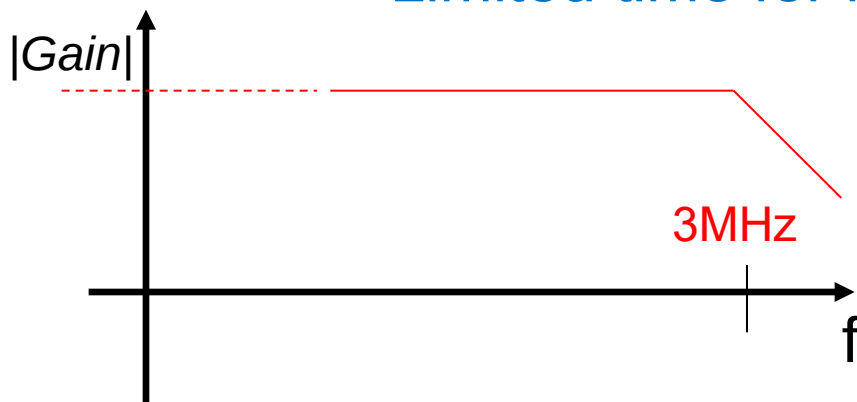

If $I_{dc} = 10\text{nA}$, $V_{max} = 10\text{V}$




$T_m = 1\text{ms}$

Axopatch 200B




DC current reset

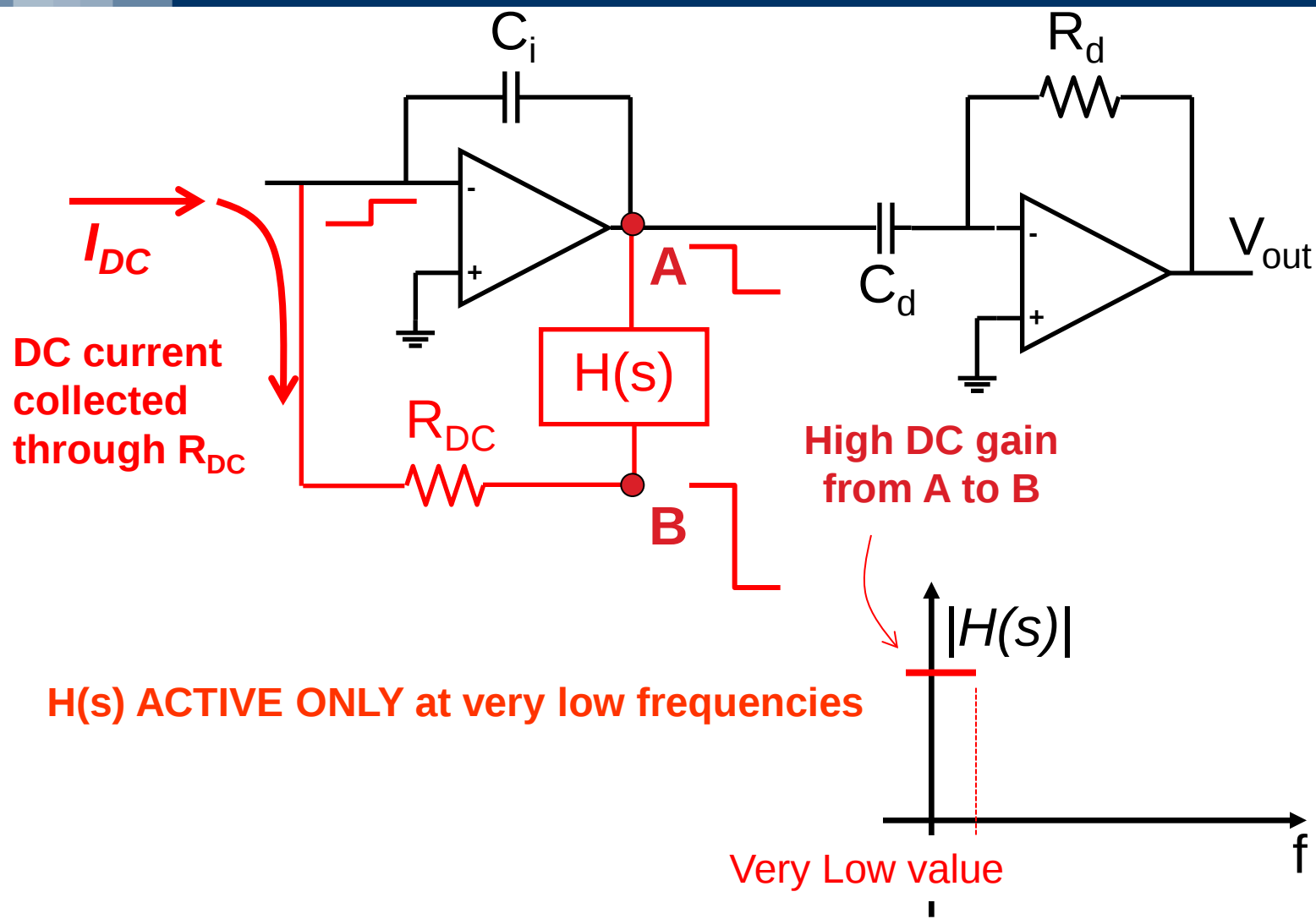


G.Ferrari et al., Rev.Sci.Instr., 78, p. 094703 (2007)



DC current reset : signal path

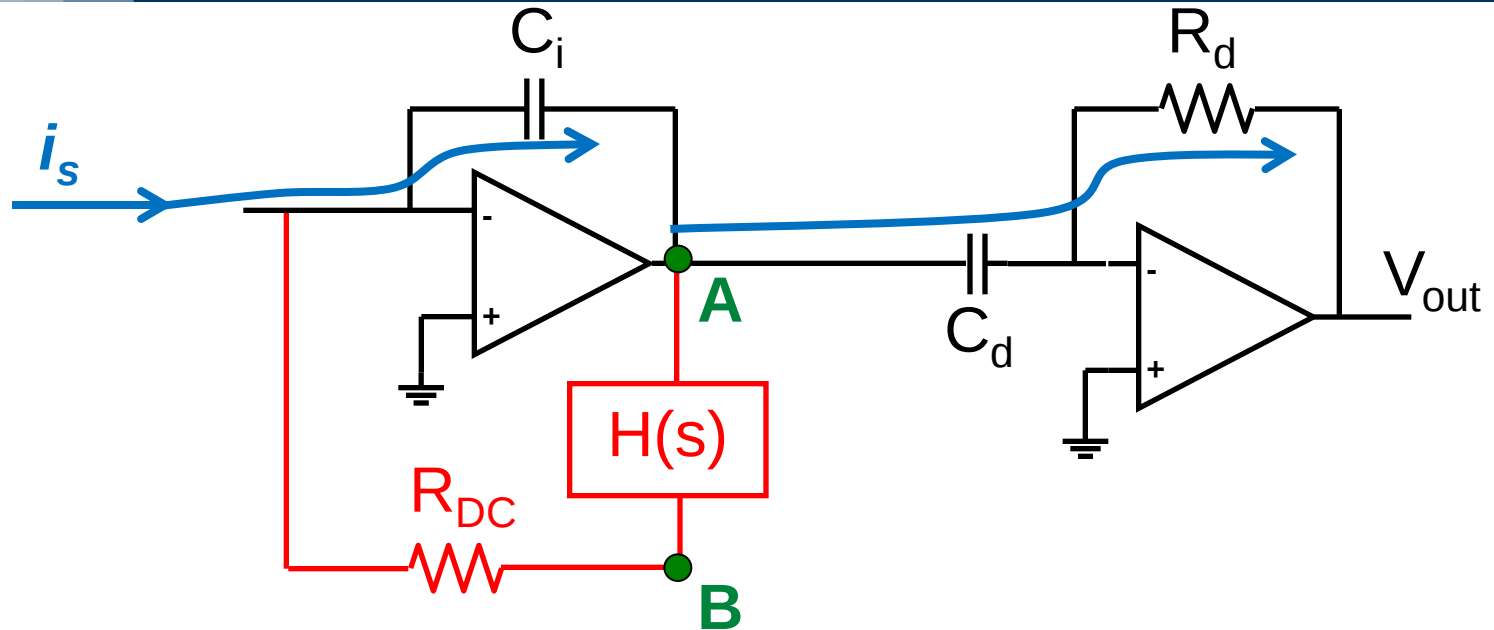



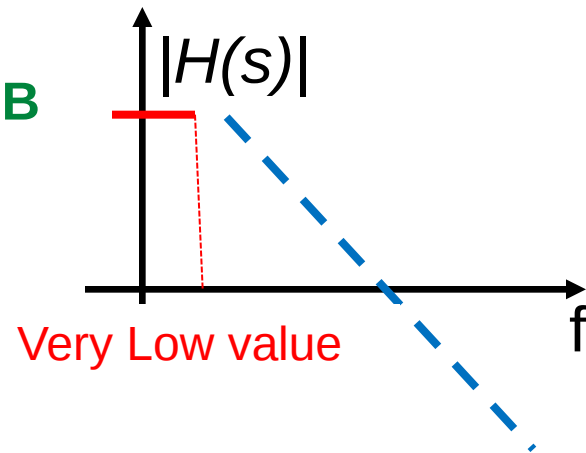
Zero gain of $H(s)$ from A to B
at signal frequencies




$H(s)$ NOT active when signal is present





DC current reset : stability remarks

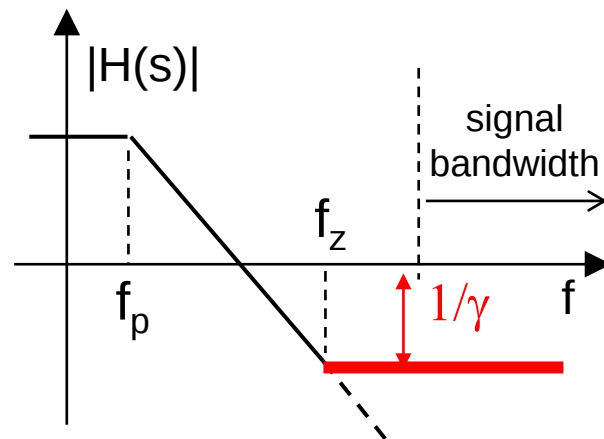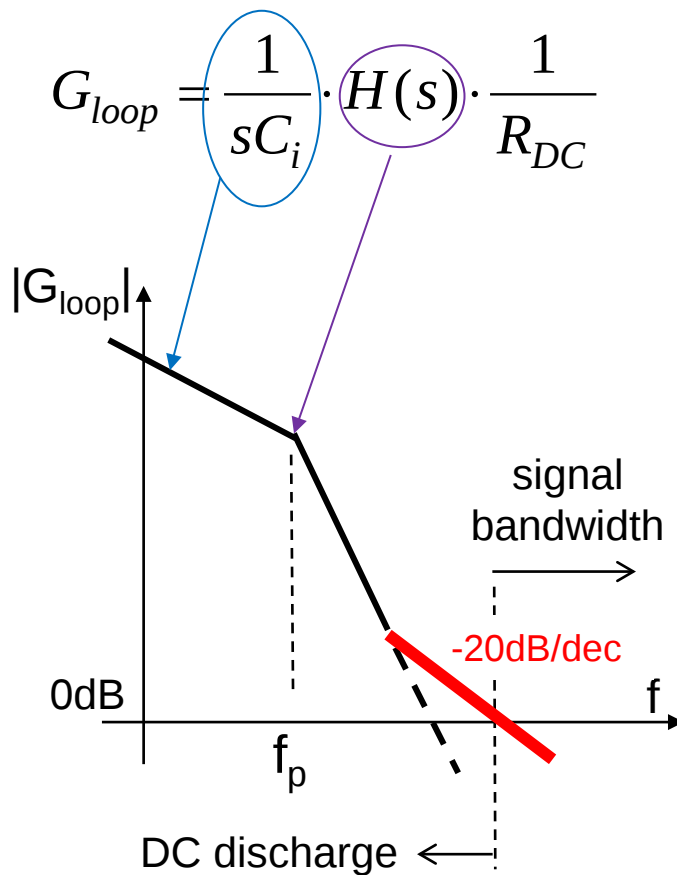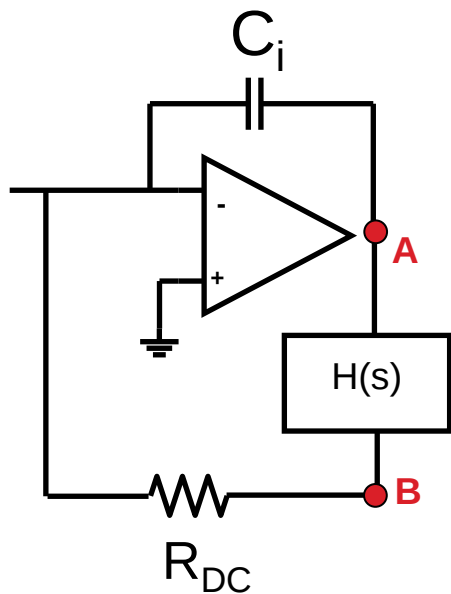

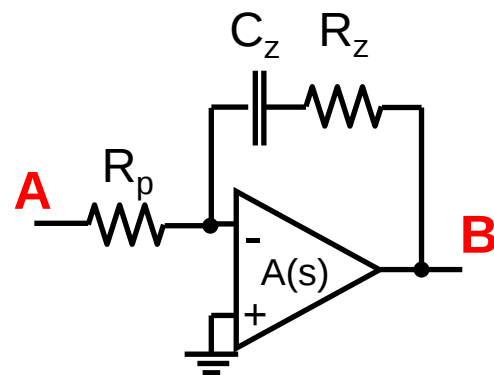STABILITY imposes the same number of poles and zeros in $H(s)$



DC current reset : noise

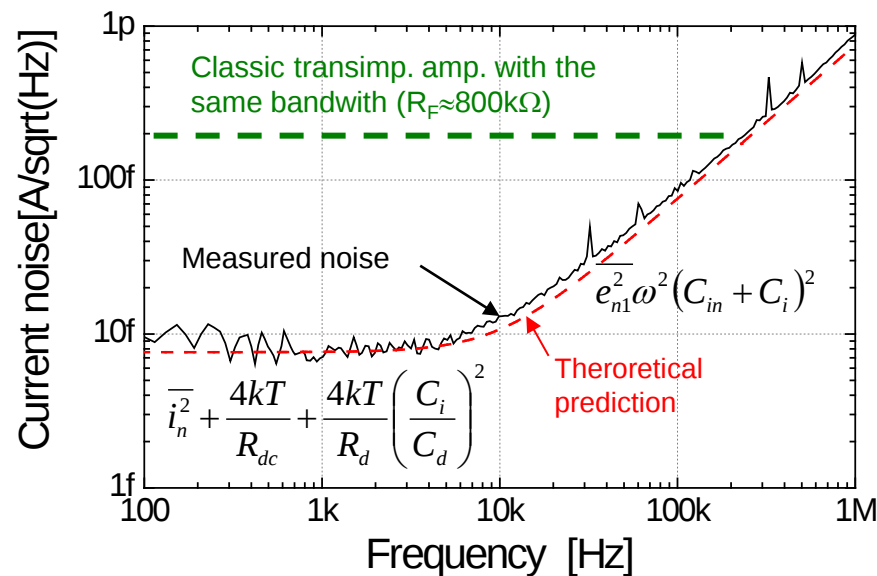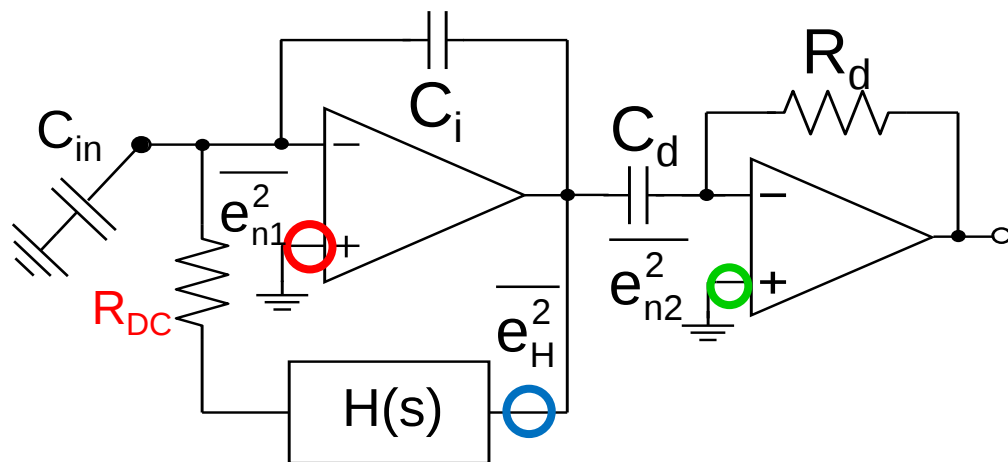

Input equivalent noise: R_{DC} big

$$\overline{i_{eq}^2} \approx \underbrace{\overline{i_n^2} + \overline{e_{n1}^2} \omega^2 (C_{in} + C_i)^2}_{\text{Same as a classical TIA}} + \underbrace{\frac{4kT}{R_{dc}} - \frac{\overline{e_H^2}}{R_{dc}^2}}_{\text{negligible for } R_{dc} > 100k\Omega} + \underbrace{\overline{e_{n2}^2} \omega^2 C_i^2 + \frac{\overline{e_{n2}^2}}{R_d^2} \left(\frac{C_i}{C_d} \right)^2 + \frac{4kT}{R_d} \left(\frac{C_i}{C_d} \right)^2}_{\text{Reduced by the gain } C_d/C_i}$$


Same as a classical TIA

negligible for
 $R_{dc} > 100k\Omega$

Reduced by the gain C_d/C_i




DC current reset : I_{leak} monitor

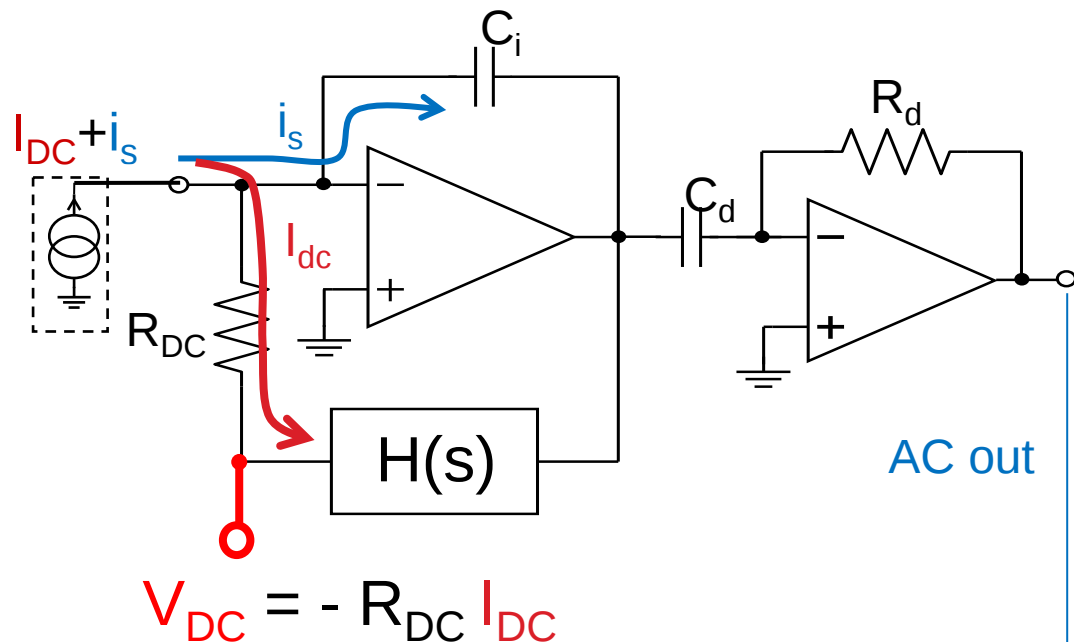

R_{DC} as BIG as possible
 $\Rightarrow$ low noise

R_{DC} not too big
 $\Rightarrow$ large dynamic of I_{DC}



R_{DC} doesn't affect BW
Very good !

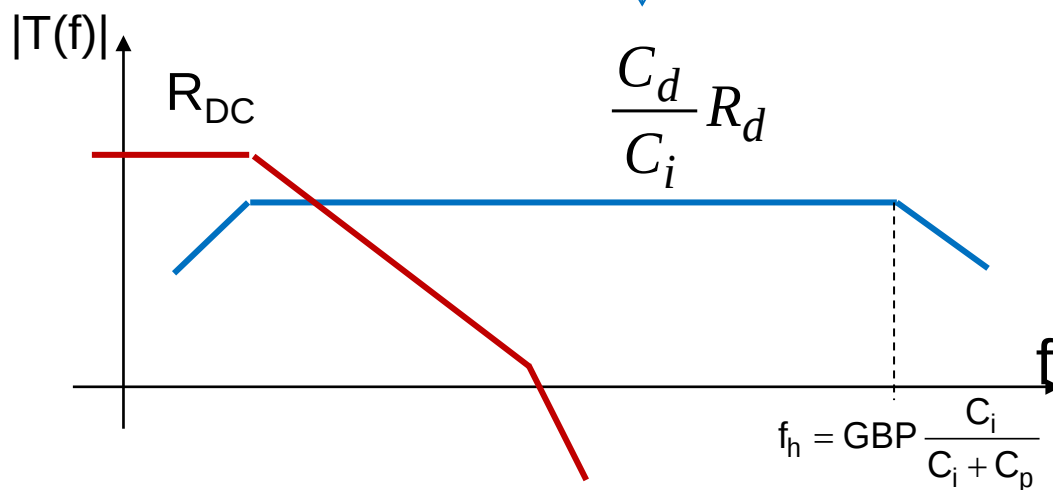





DC current reset : examples

Components on a board

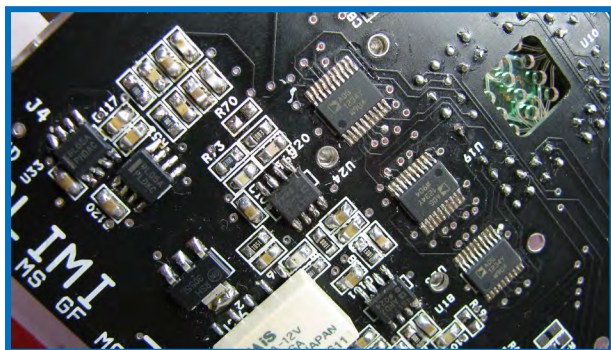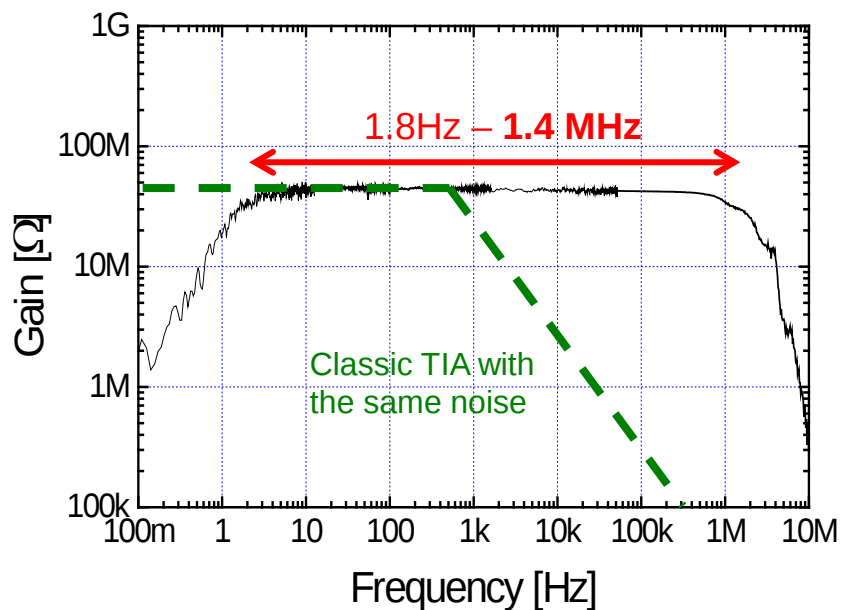


Integrated Circuit (ASIC)

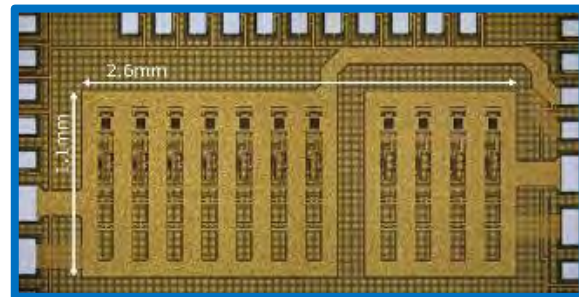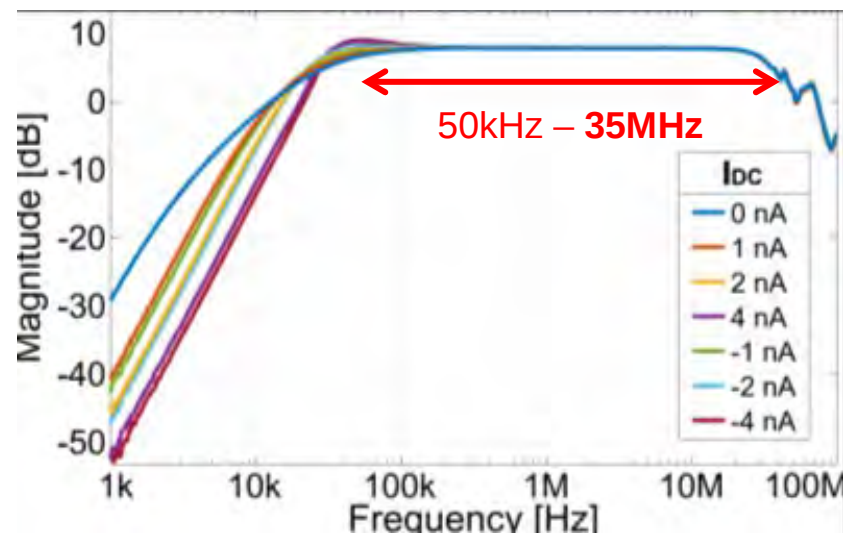




DC current reset : Integrated circuit

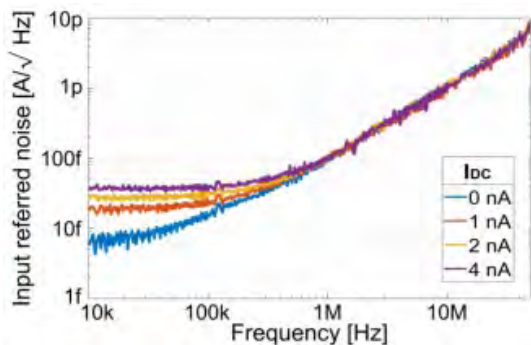


Adaptive
Pseudo-resistor
 $R_{pr} \cong 25mV/I_{DC}$

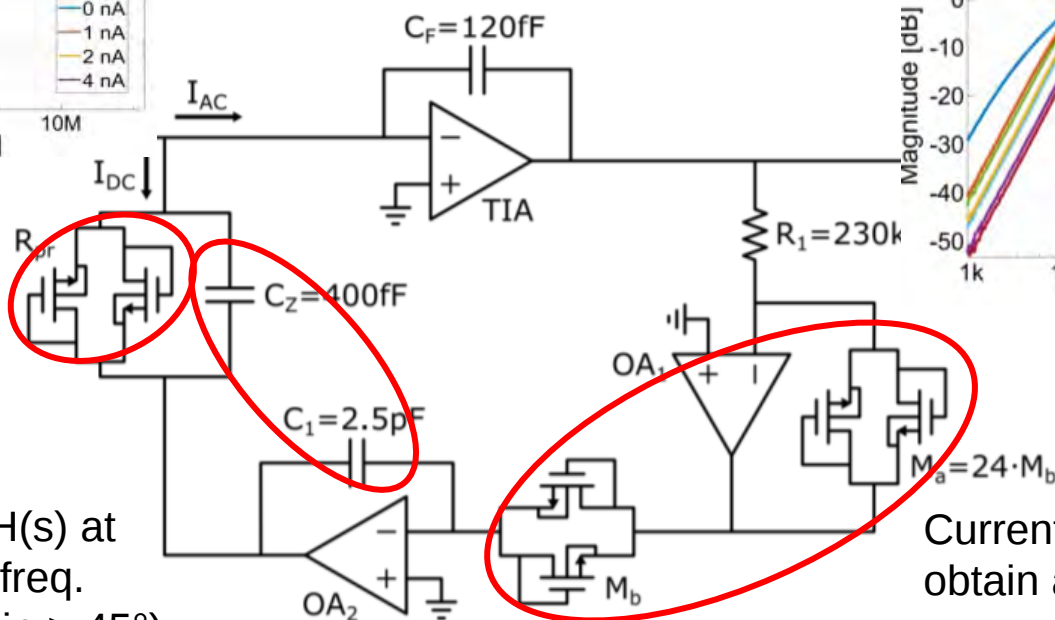Constant $H(s)$ at
medium freq.
(Phase margin $> 45^\circ$)



Signal 50kHz – 35MHz

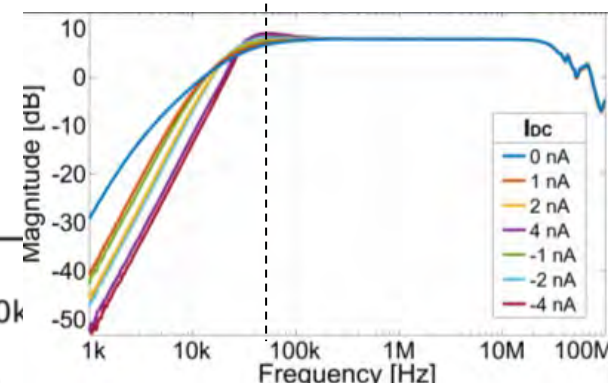


Current reducer (x24) to
obtain a large resistor ($6M\Omega$)

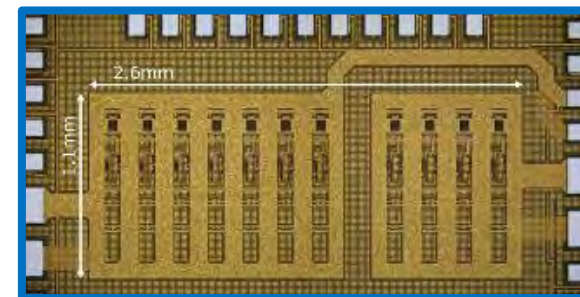E. Guglielmi et al., "High-Value Tunable Pseudo-Resistors Design," in IEEE Journal of Solid-State Circuits, vol. 55, no. 8, pp. 2094-2105, 2020

STm BCD8sP 0.18- μm
Supply voltage : 1.8 V
11 parallel channels
Current cons. : 5 mA/ch



F.Zanetto et al. "Wide Dynamic Range Multichannel Lock-In Amplifier ...", IEEE SOLID-STATE CIRCUITS LETTERS, VOL. 3, 246-249, 2020



Tunneling current reset

When $V=0V$
no tunneling
NO noise

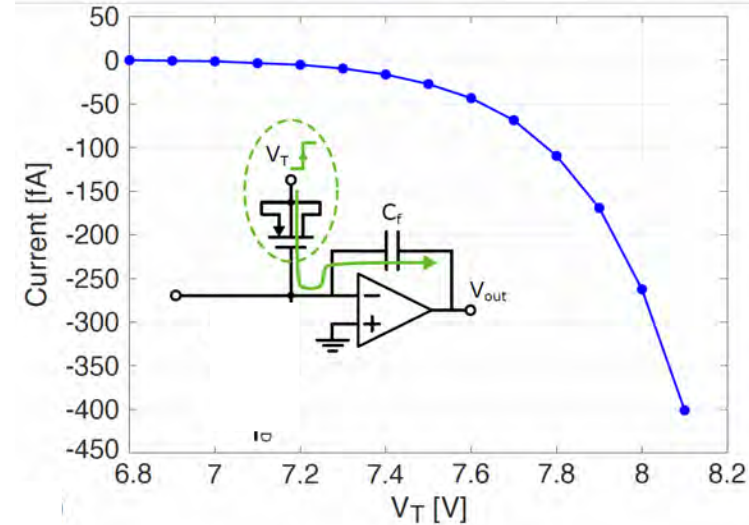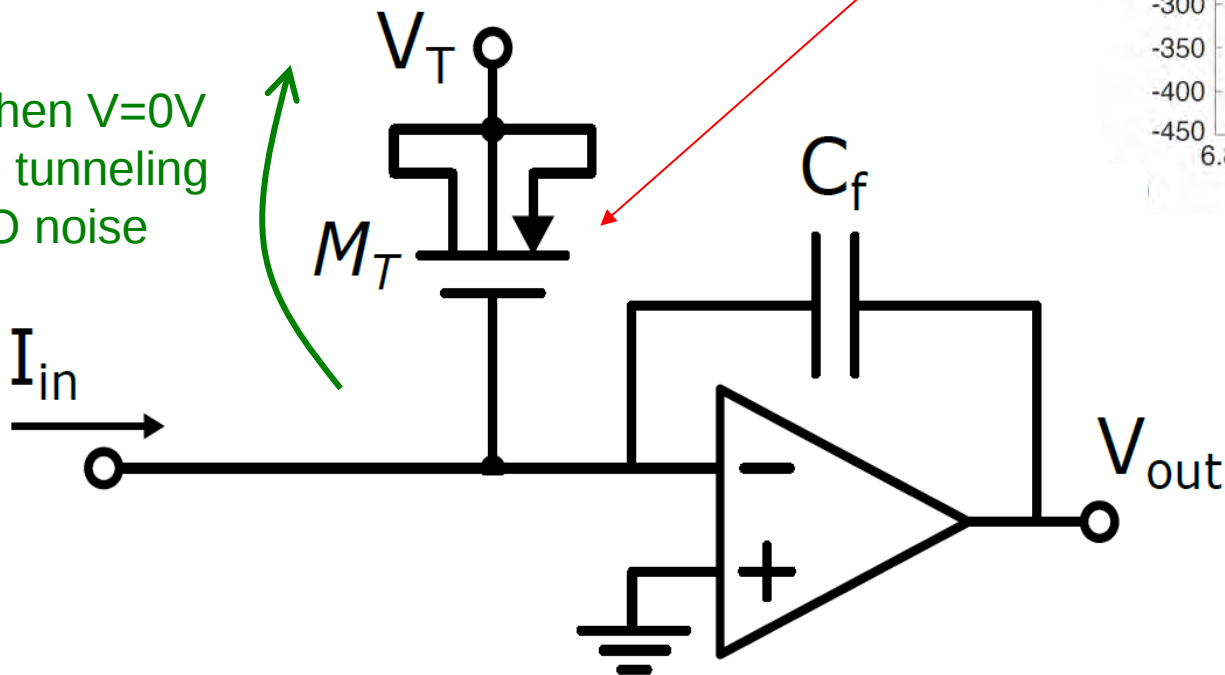
Use tunneling through the MOSFET oxide to reset





Tunneling current reset : sensitivity OK


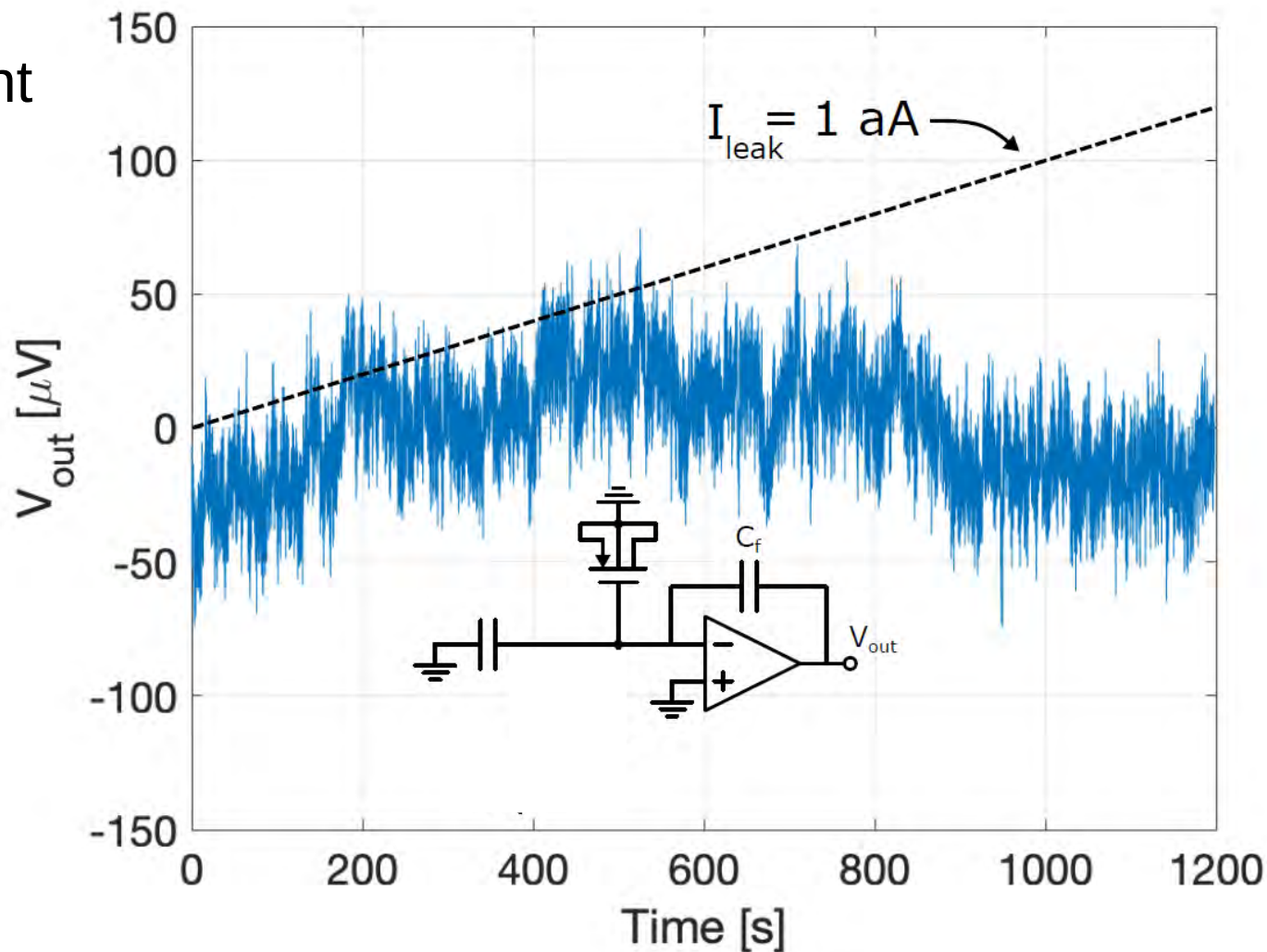
Leakage current in a IC is much less than 1aA





Tunneling current reset : sensitivity OK

Ideal minimum noise

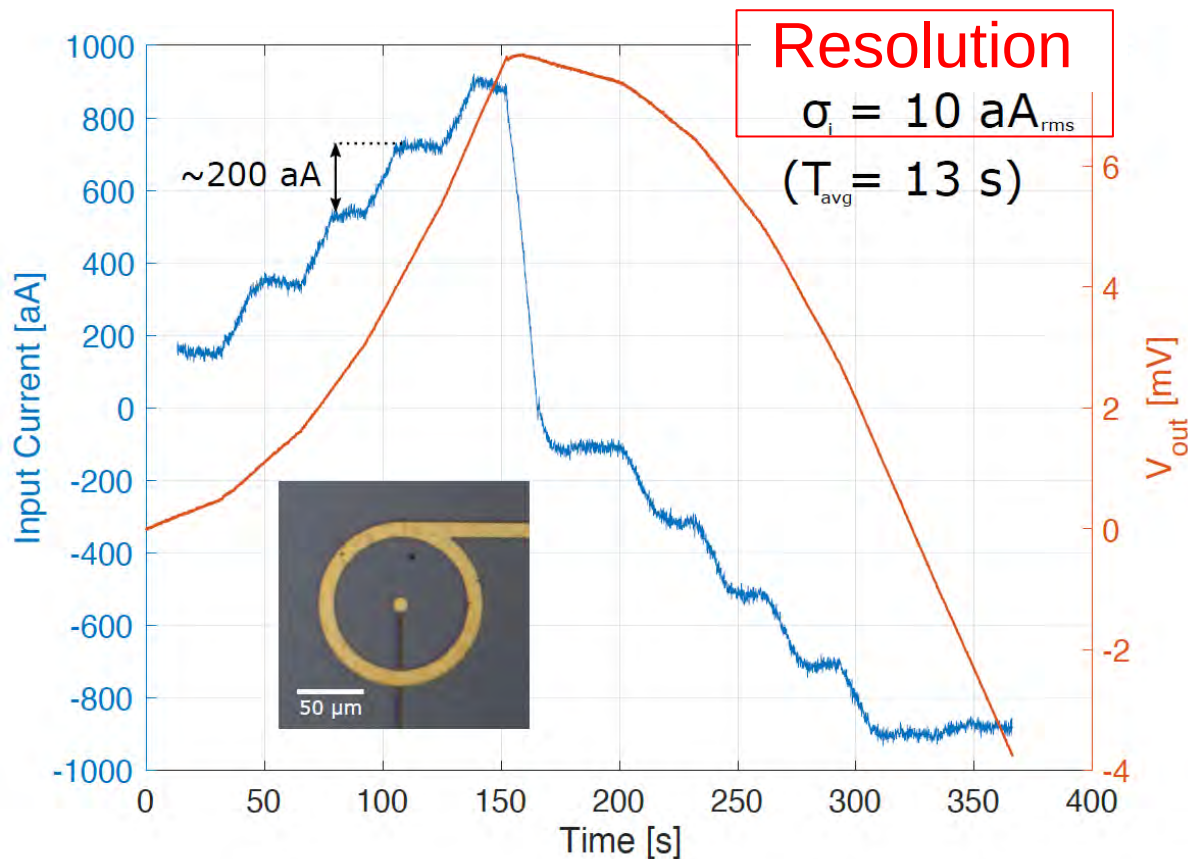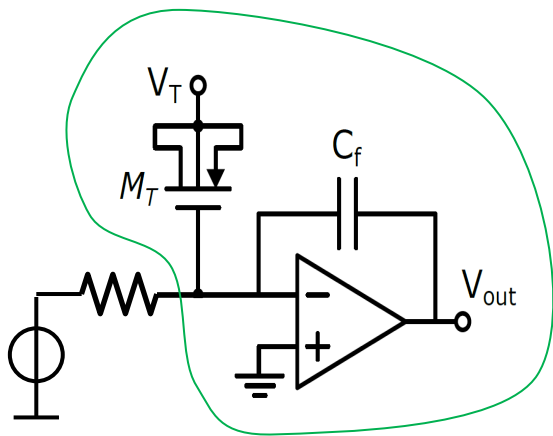

Response is obtained by applying a voltage between metal ring and input electrode (see inset figure). Voltage is decreased from -0.1V to -0.5V and then increased from 0.1V to 0.5V in steps of 0.1V , producing current steps of approximately 200 aA .





Additional material





The challenge of high value resistors

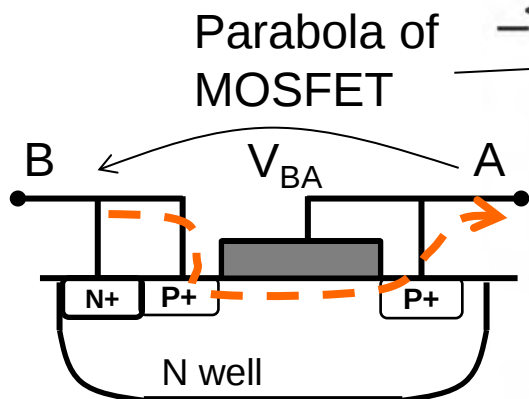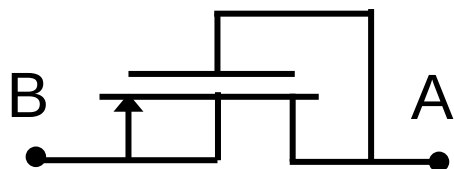single MOSFET connected in transdiode configuration



Parabola of MOSFET

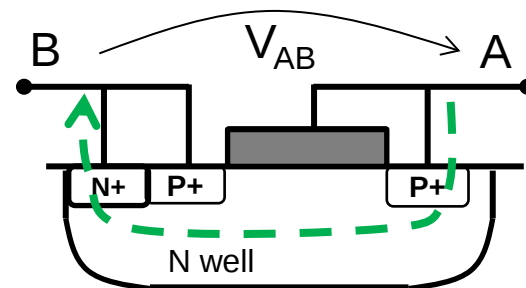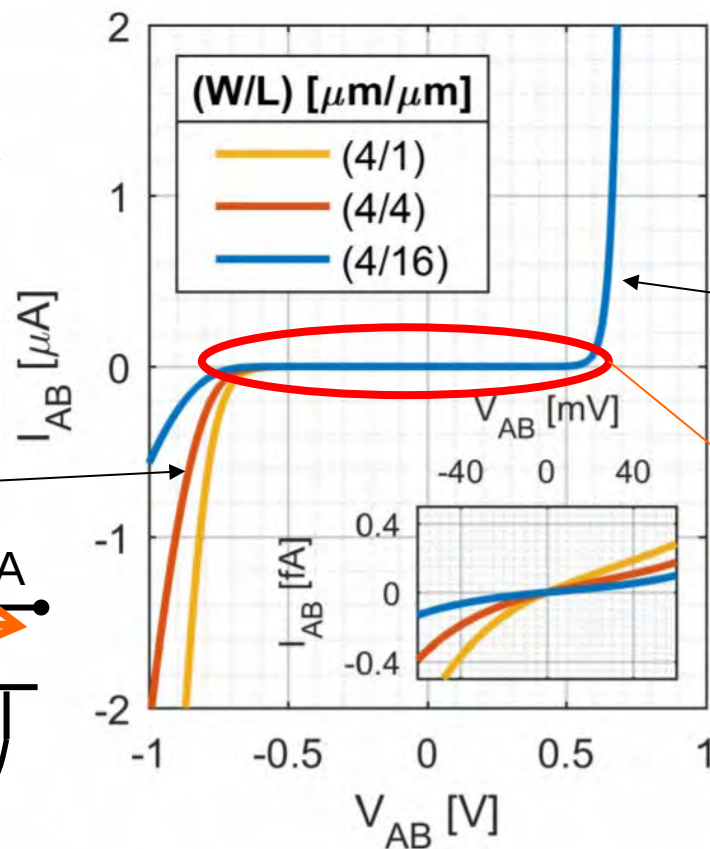

Exponential of PN junction

High equivalent resistance


$$r_{eq} \cong 25\text{mV} / I_{DC}$$



Toward Integrated Circuit - ASIC


Parallel back-to-back

to obtain symmetric response

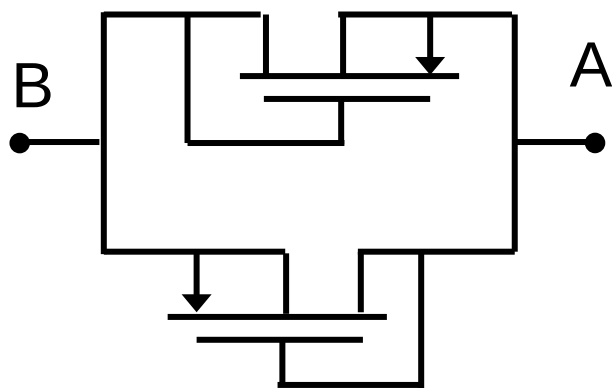

Ratiometric topology

to compensate for non-linearities

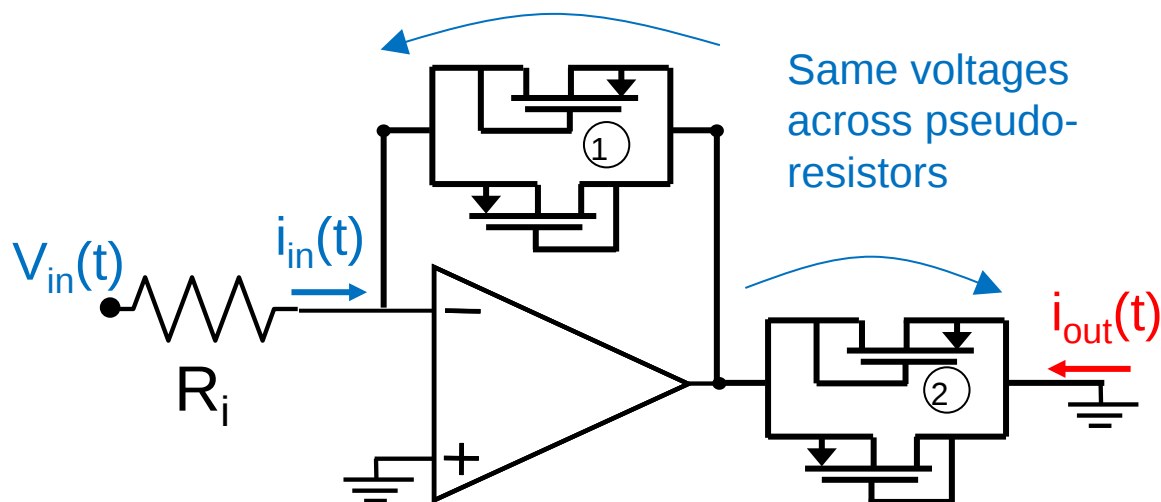



$$\text{If } W_1 = 100 \times W_2 \Rightarrow i_{\text{out}}(t) = \frac{i_{\text{in}}(t)}{100}$$

$$R_{\text{TOT}} = \frac{V_{\text{in}}(t)}{i_{\text{out}}(t)} = 100 \times R_i$$

High value resistor :
small current $i_{\text{out}}(t)$
with large voltage $V_{\text{in}}(t)$



How to make the Differentiator

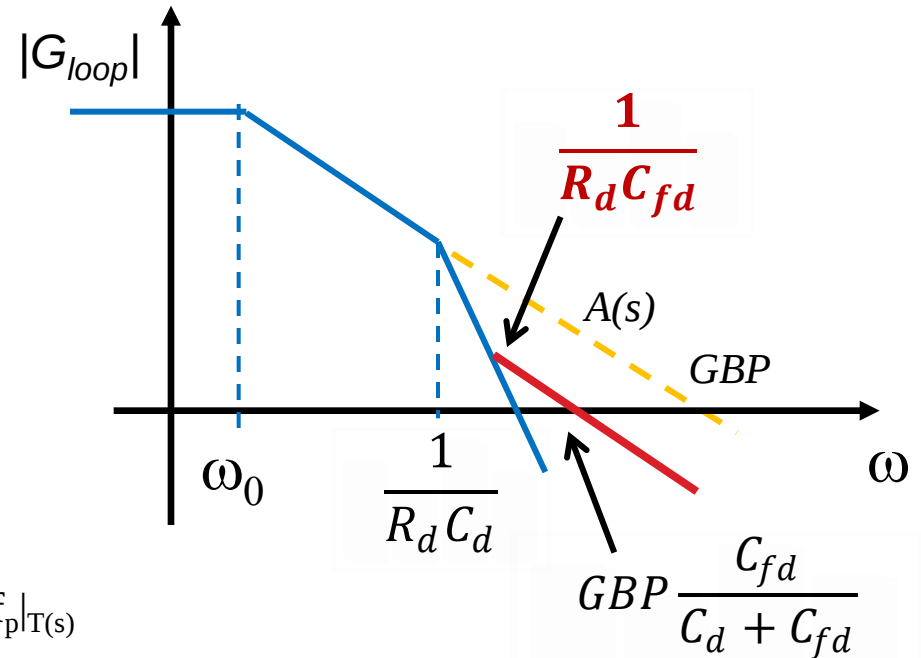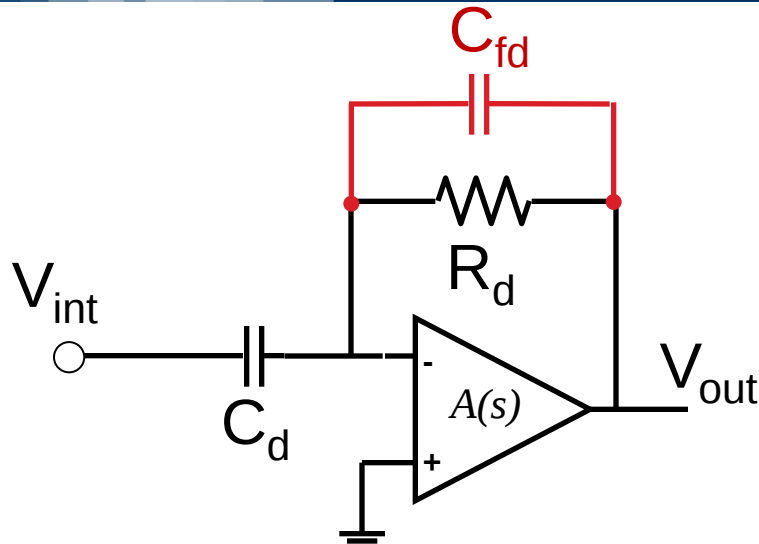

Constraints:

$$\left\{ \begin{array}{l} \frac{1}{2\pi R_d C_{fd}} = BW \cong f_{z|Gloop} \cong f_{p|T(s)} \\ R_d \left(\frac{C_d}{C_i} \right)^2 = R_{eq \text{ noise}} \\ GBP \frac{C_{fd}}{C_d + C_{fd}} > \frac{1}{2\pi R_d C_{fd}} \end{array} \right. \Rightarrow GBP > 2\pi B^2 C_i \sqrt{R_{eq \text{ noise}} R_d}$$

Example:

Chose : $C_i = 1.5 \text{ pF}$
 $C_d = 220 \text{ pF}$

Request : $R_{eq|noise} = 1 \text{ G}\Omega$
 $BW = 2 \text{ MHz}$

$R_d = 47 \text{ k}\Omega$
 $C_{fd} = 2 \text{ pF}$
 $GBP|_{OpAmp} > 260 \text{ MHz}$