

ELECTRONIC SYSTEMS and TECHNOLOGIES


Master in Management Engineering

Prof. Marco Sampietro

GROUND CONCEPTS ON ELECTRONICS

The idea of FEEDBACK

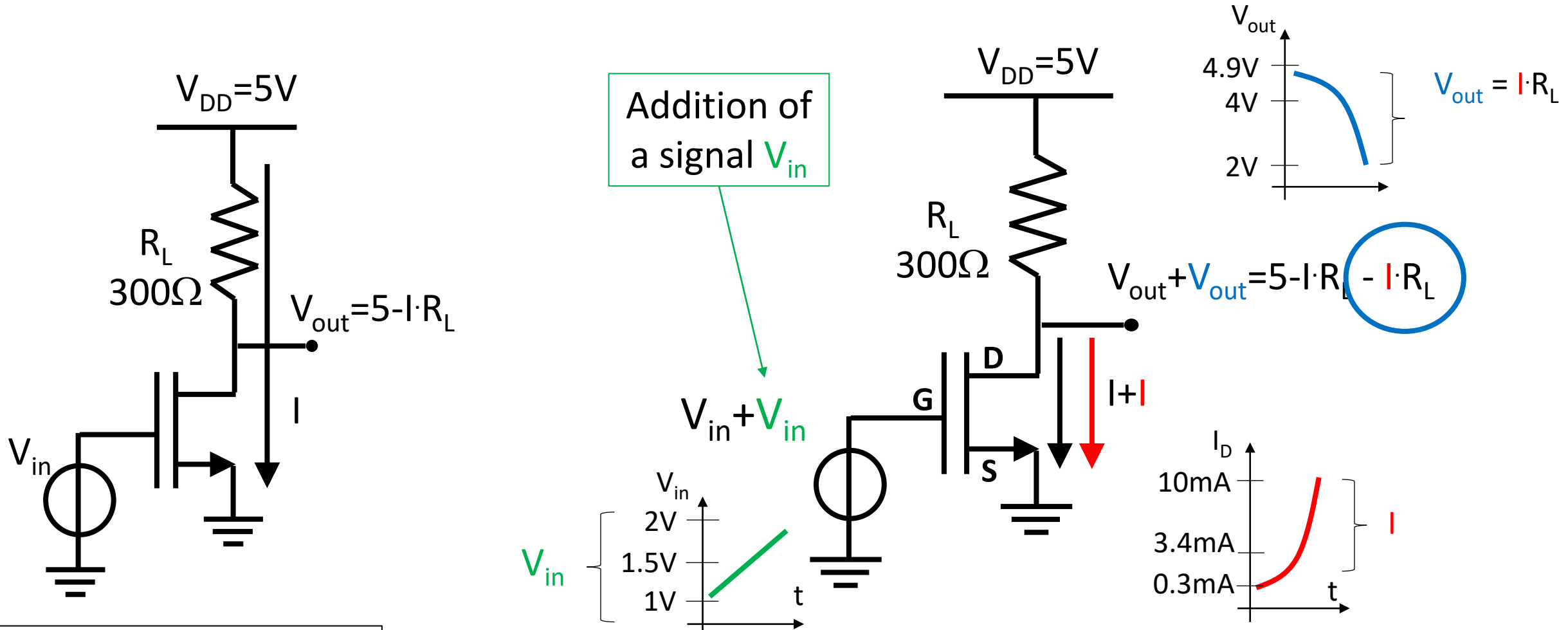
Polarisation and signal gain of an Amplifier



Starting condition
(Polarisation or Bias)

The information is contained in variations (color in the slide) with respect to the initial steady situation (black)

Tuning of the Gain of an amplifier

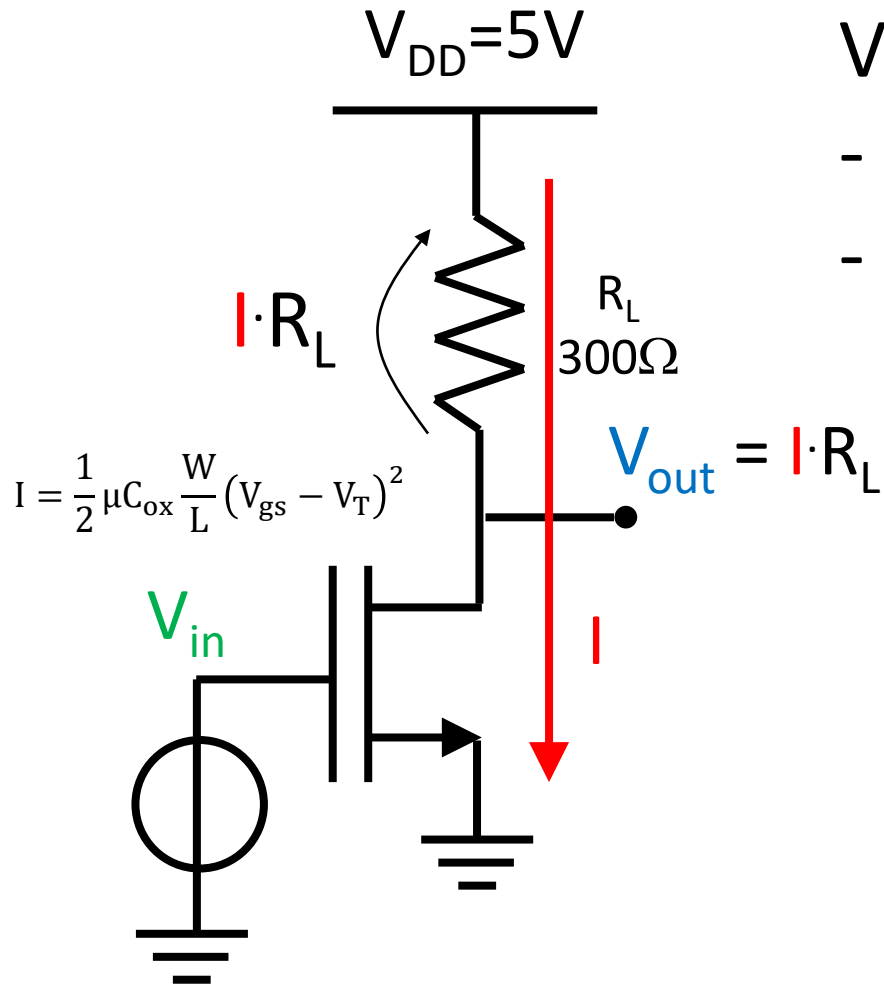


Voltage GAIN depends on :

- Transistor characteristics
- Value of R_L

Not very controllable
(change with technology,
with polarisation, with
temperature, etc. ...)


Multi-stage
Amplifier

$$G_{tot} = G_1 \times G_2$$

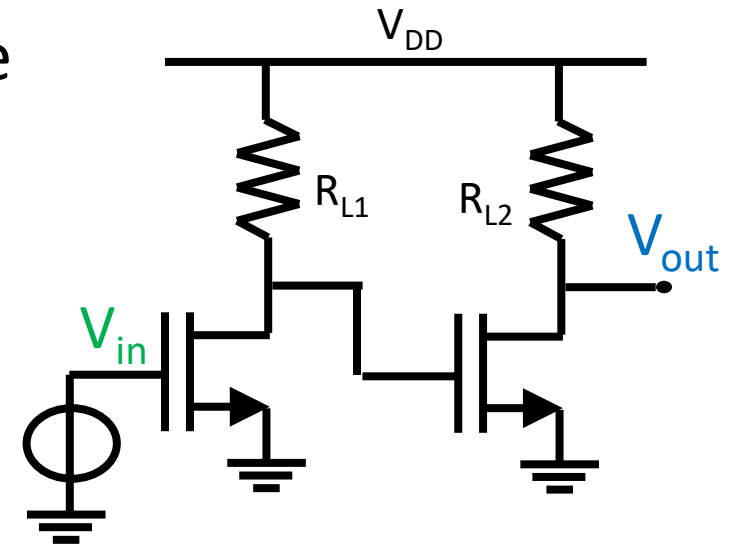



Very often the bias is not indicated (for simplicity)

Amplifier with very high gain

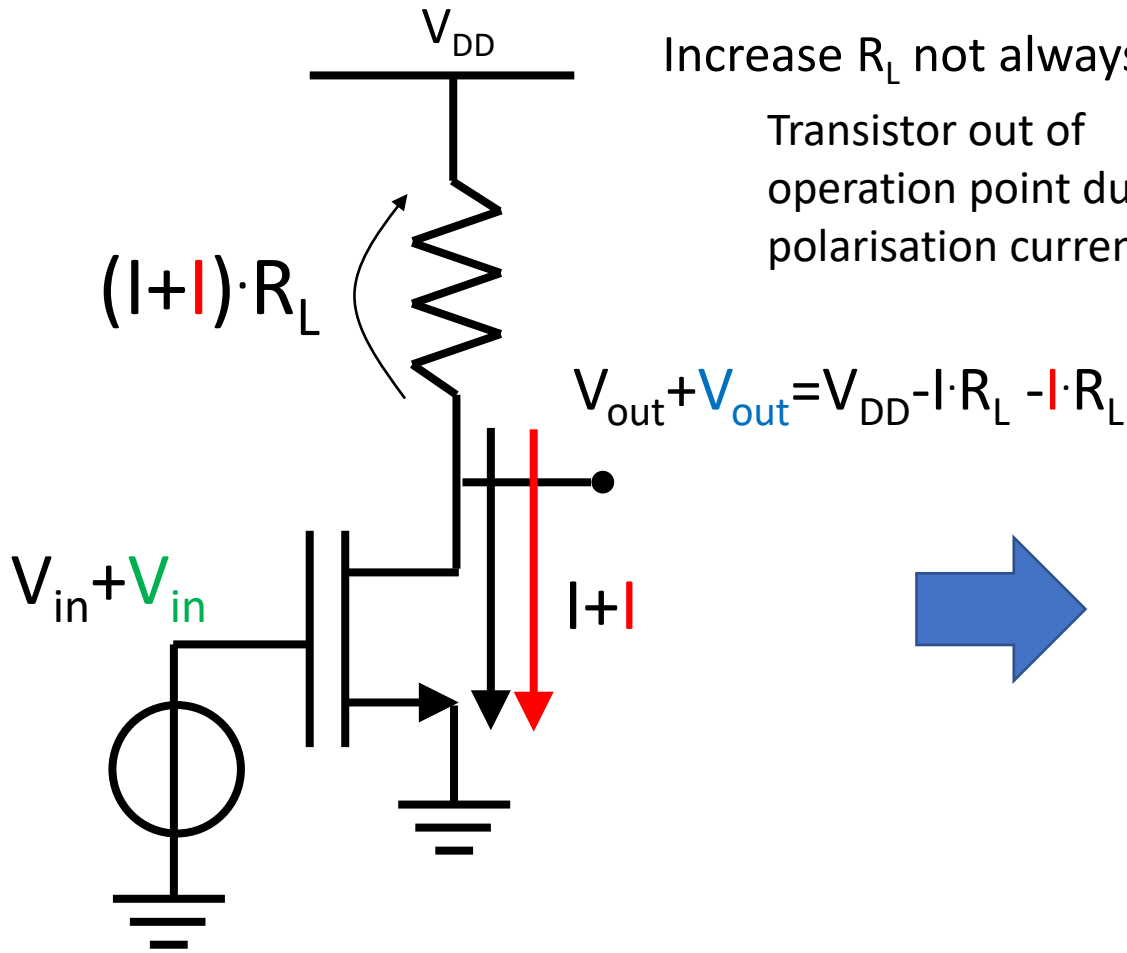

Increase R_L not always possible :

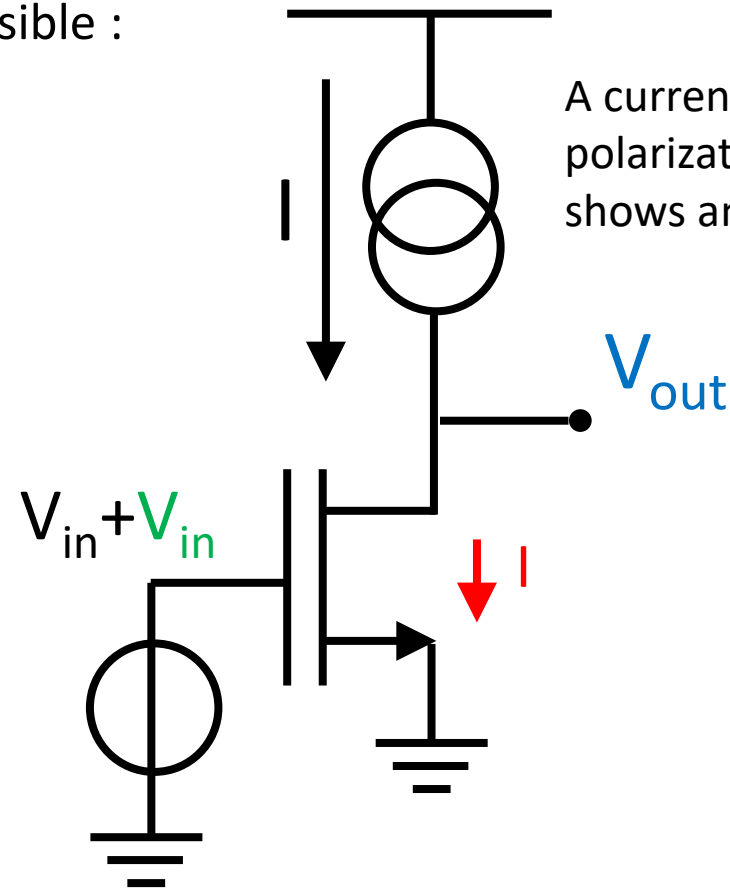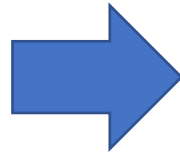Transistor out of operation point due to polarisation current I



A current generator sets polarization current and shows an ∞ resistance


$$G \approx -\infty$$

Close look on resistance of a Current generator

How to measure a resistance ?

Apply a voltage signal ...

ΔV

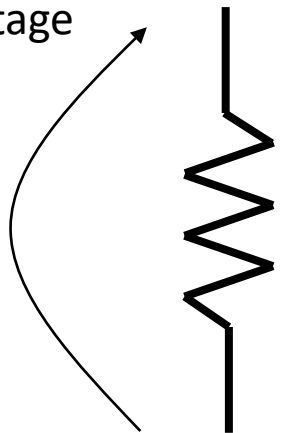


... and measure the corresponding current signal


ΔI

The ratio between the two gives the Resistance

$$R = \frac{\Delta V}{\Delta I}$$

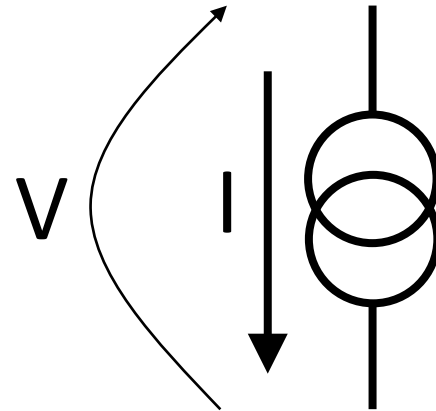


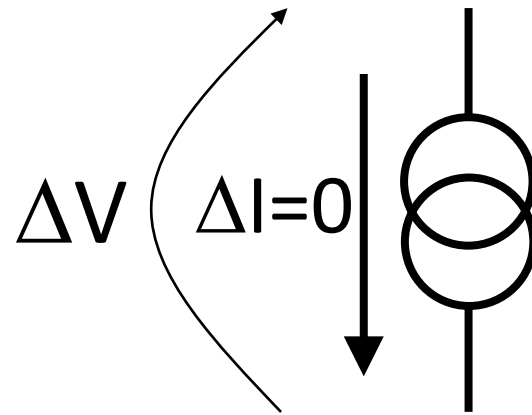A current generator sets the Current I independently of the Voltage V across



$$R = \frac{\Delta V}{\Delta I} = \frac{\Delta V}{0} = \infty$$


Compact symbol of an amplifier

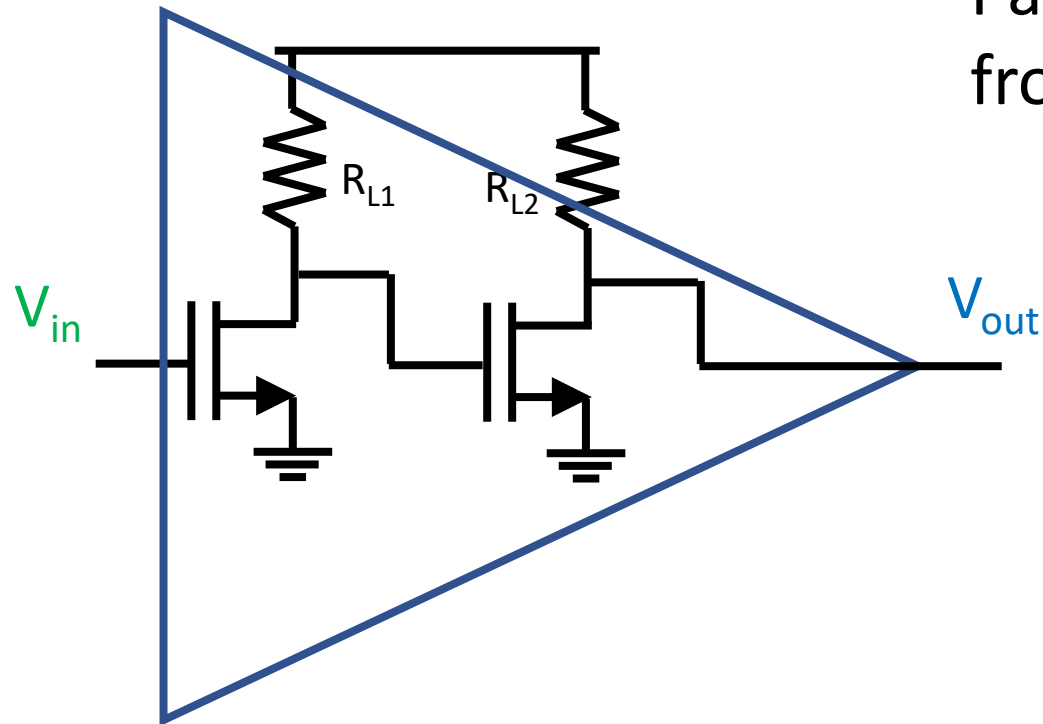

Parameters of amplifiers may change a lot from sample to sample (few % to 100 % !)


Gain changes
Distortion changes
Frequency response changes

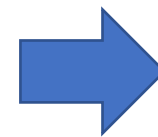Almost impossible to stabilize
an amplifier by design



Need a Game changer !

The idea of the FEEDBACK

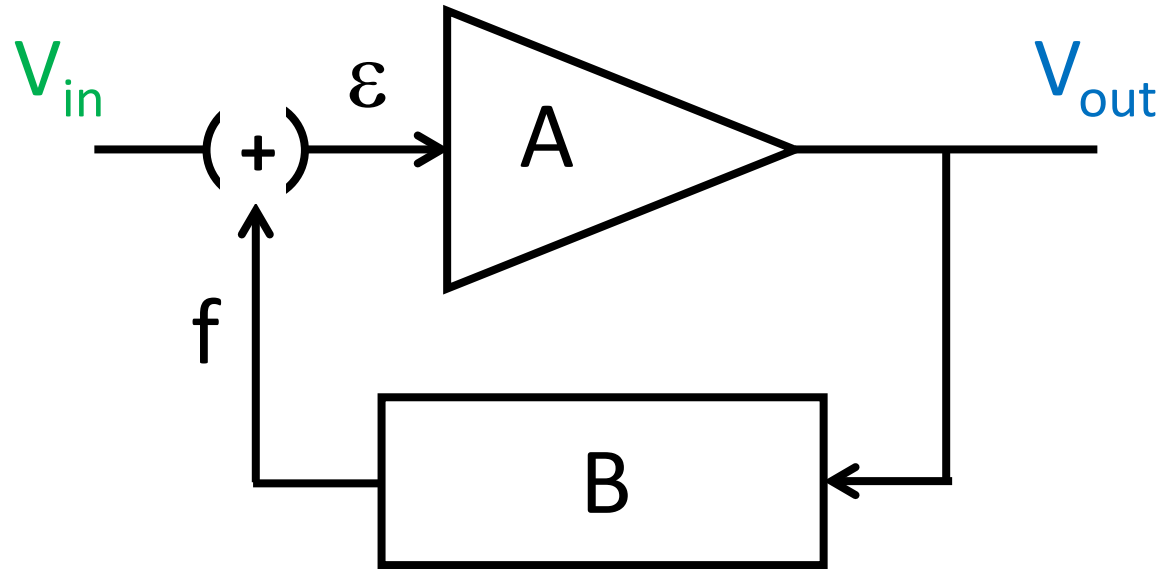

$$V_{out} = V_{in} \cdot A$$

Depends on the amplifier
(BAD)

$$V_{out} = V_{in} \cdot A + V_{out} \cdot A \cdot B$$

$$V_{out} = V_{in} \cdot \frac{A}{1 - A \cdot B}$$

$$V_{out} = \varepsilon \cdot A$$

$$\varepsilon = V_{in} + V_{out} \cdot B$$


$$\varepsilon = V_{in} + \varepsilon \cdot A \cdot B$$

$$\varepsilon = V_{in} \cdot \frac{1}{1 - A \cdot B}$$

$$V_{in} \cdot \frac{1}{1 - A \cdot B} = V_{in} + f$$

$$f = V_{in} \cdot \frac{A \cdot B}{1 - A \cdot B}$$

A closer look to the FEEDBACK

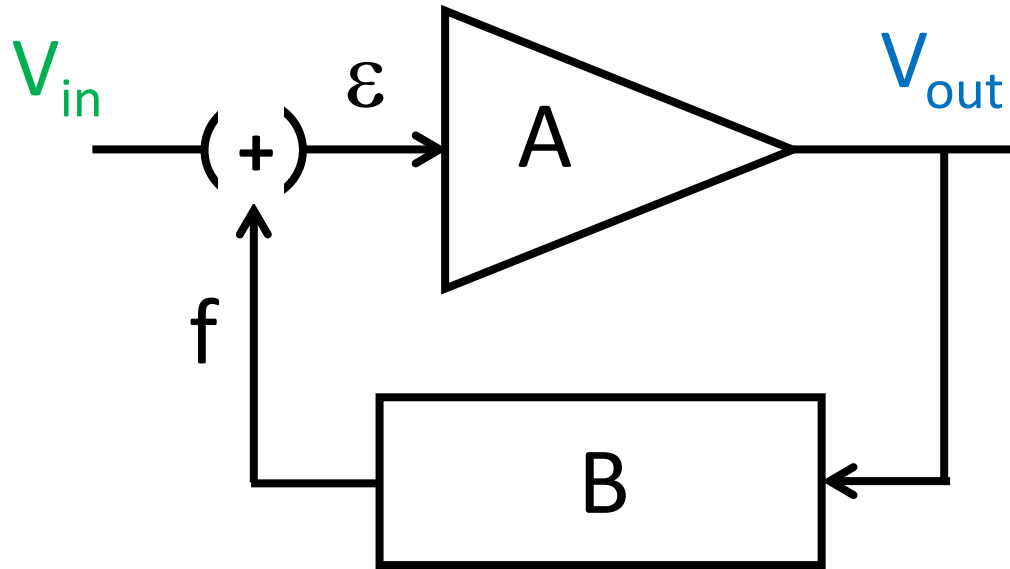

Suppose $A = -\infty$ (we know we can !)

« $A \cdot B$ » is the Loop Gain

The Gain does NOT depend on A
(Very GOOD)

$$V_{out} = V_{in} \cdot \frac{A}{1 - A \cdot B}$$

$$V_{out} = V_{in} \cdot \frac{1}{-B}$$

If B is stable and linear, also the Gain will be stable and linear (Very GOOD)

Practically no signal is applied to A (GOOD)

$$\varepsilon = V_{in} \cdot \frac{1}{1 - A \cdot B}$$



$$\varepsilon \cong 0$$

Practically all signal is available within the loop

$$f = V_{in} \cdot \frac{A \cdot B}{1 - A \cdot B}$$

$$f \cong -V_{in}$$

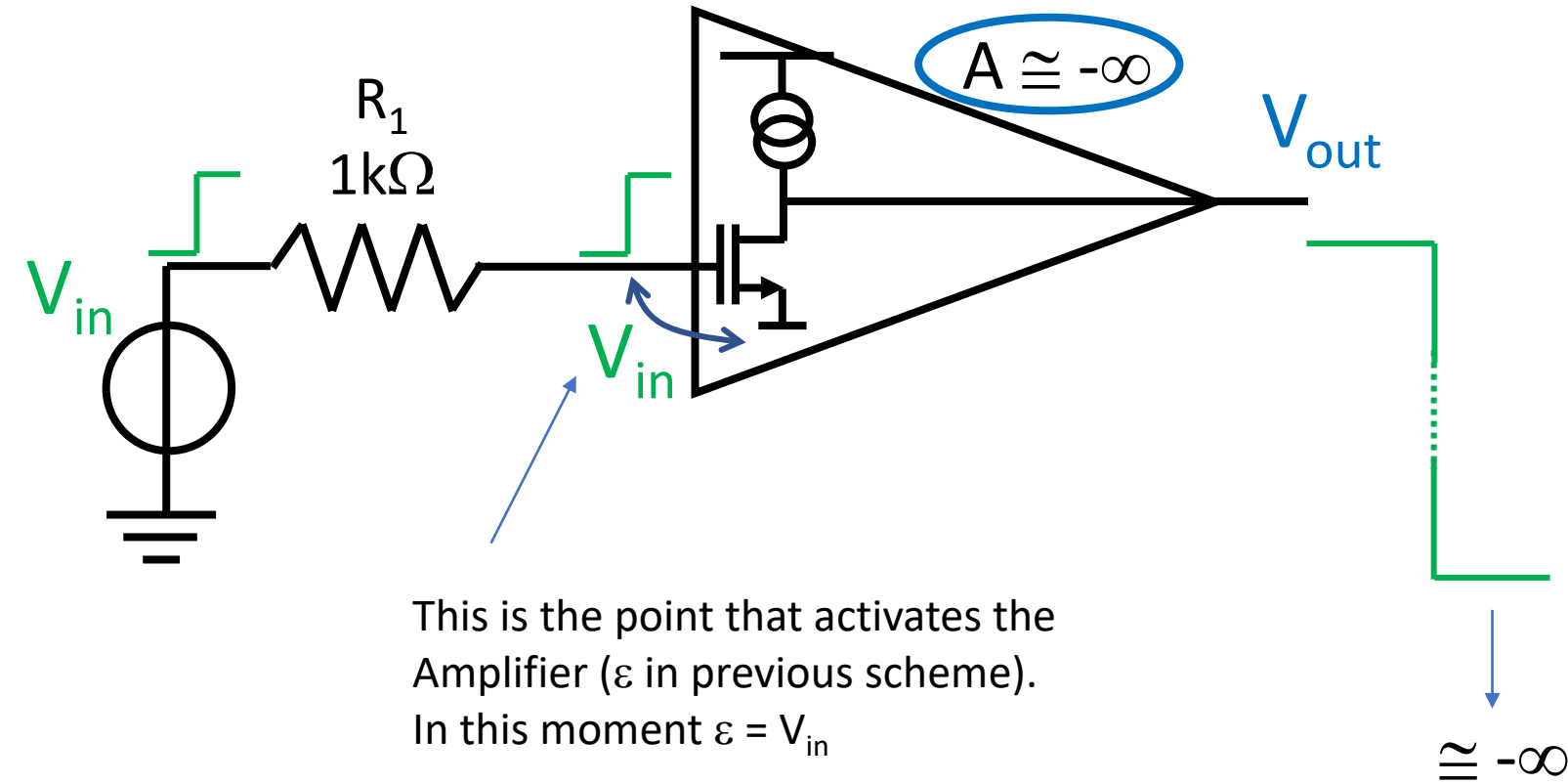
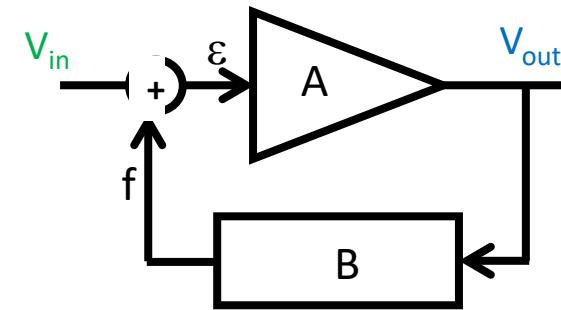
A practical example of Feedback circuit (1)



This is the point that activates the Amplifier (ϵ in previous scheme).
In this moment $\epsilon = V_{in}$



We have to use the output to reduce the voltage variation of point ϵ (ideally to $\epsilon \cong 0$)

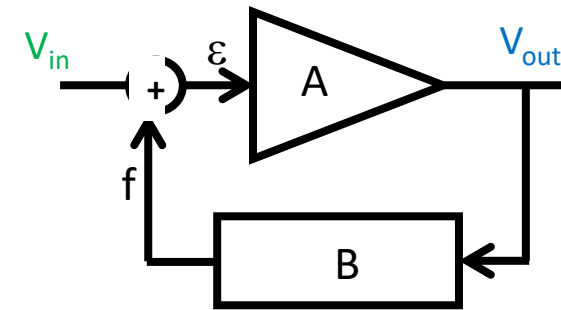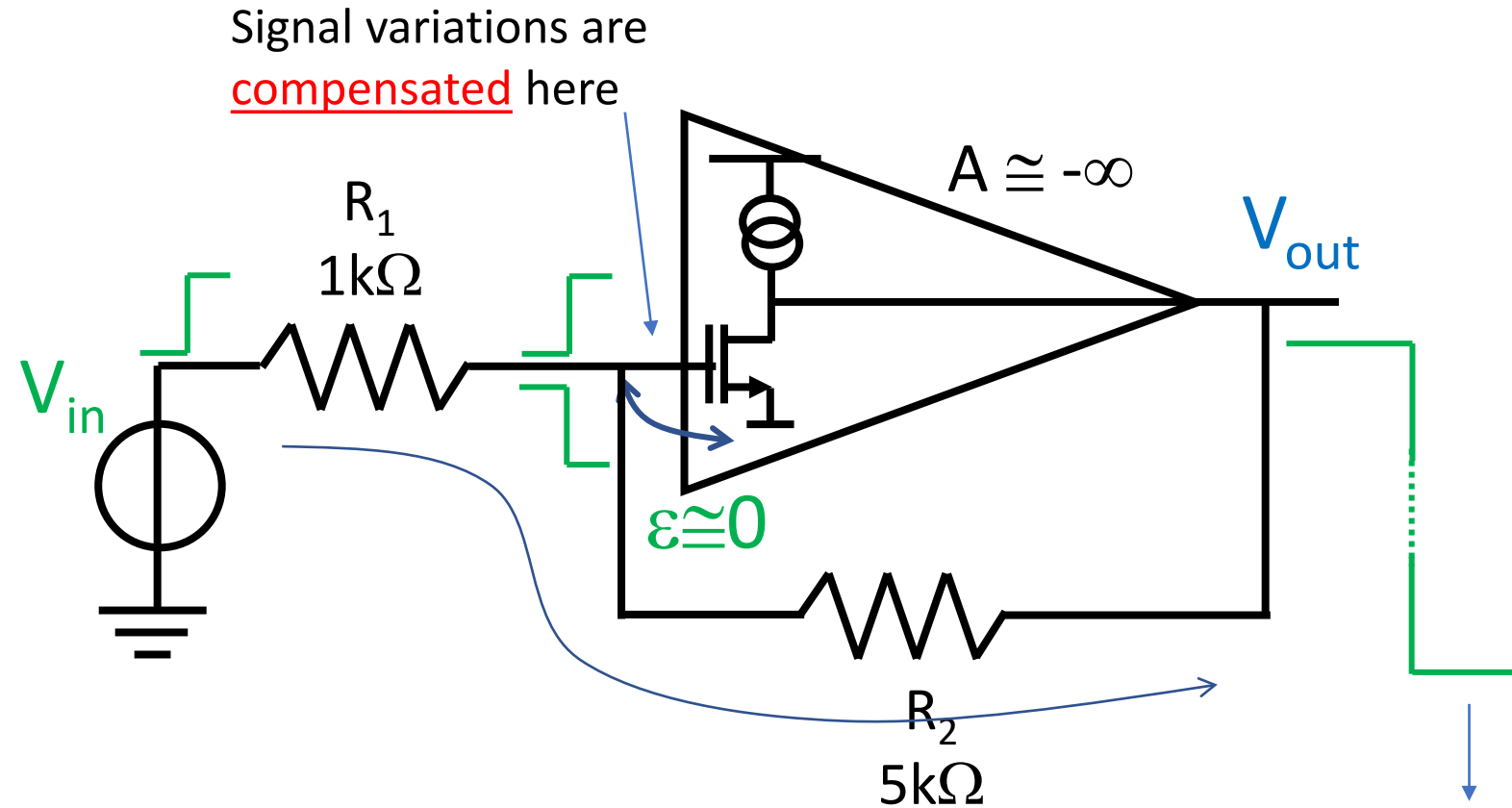A practical example of Feedback circuit (2)



The output voltage pulls down the voltage at input of amplifier (GOOD) . The maximum pulling down is equal to the initial V_{in} , reducing the voltage variation of point ε ideally to $\varepsilon \cong 0$.

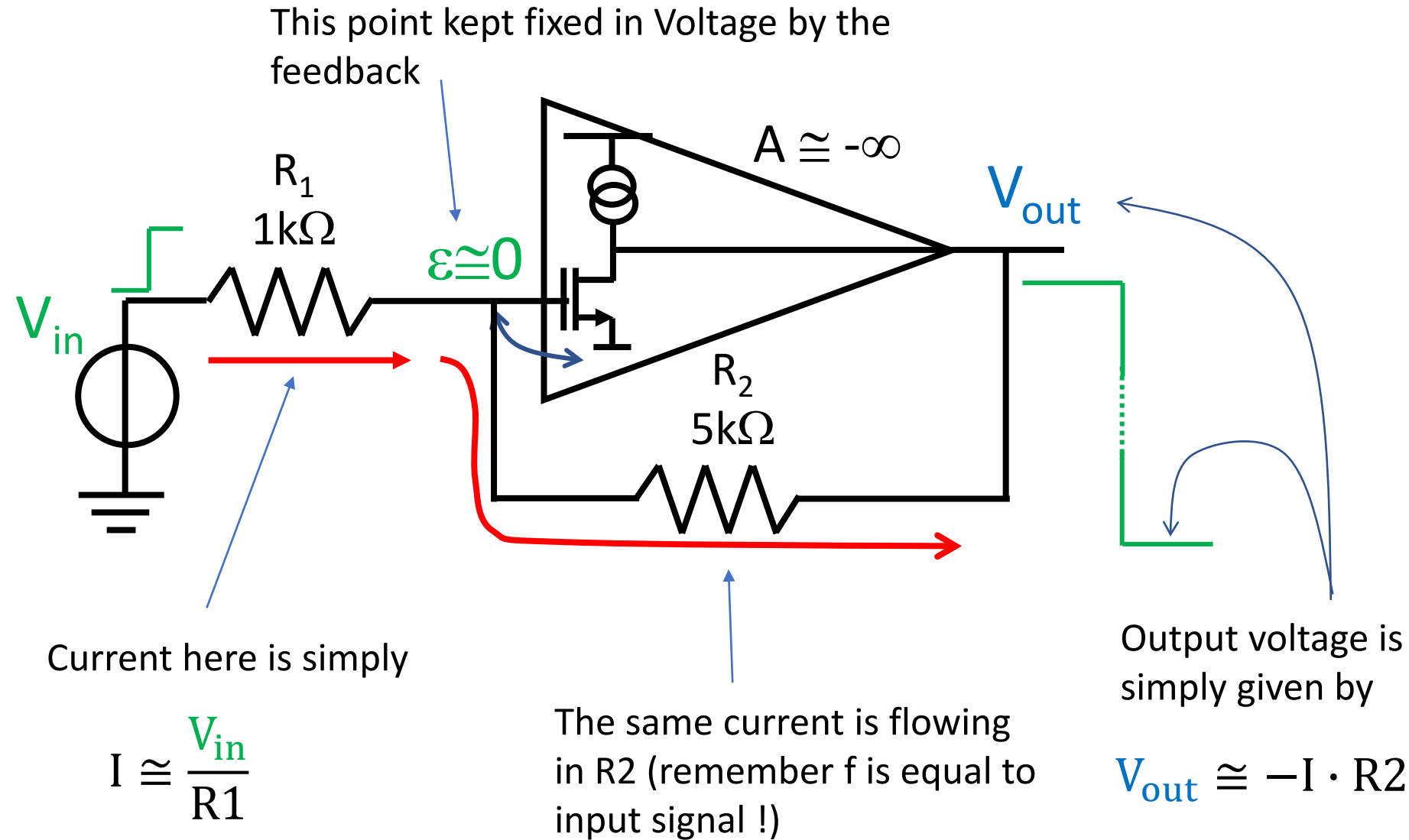
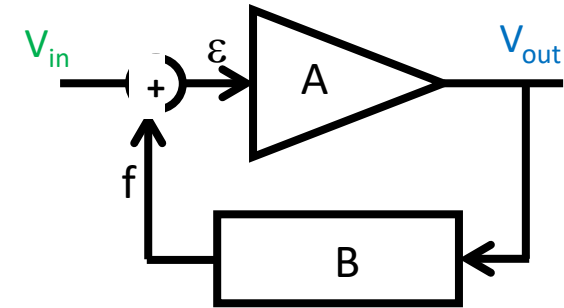
A practical example of Feedback circuit (3)



Amplifier A is NOT appearing in the Gain !

$$V_{out} \cong -\frac{V_{in}}{R_1} \cdot R_2$$

The ideal Gain of a Feedback circuit

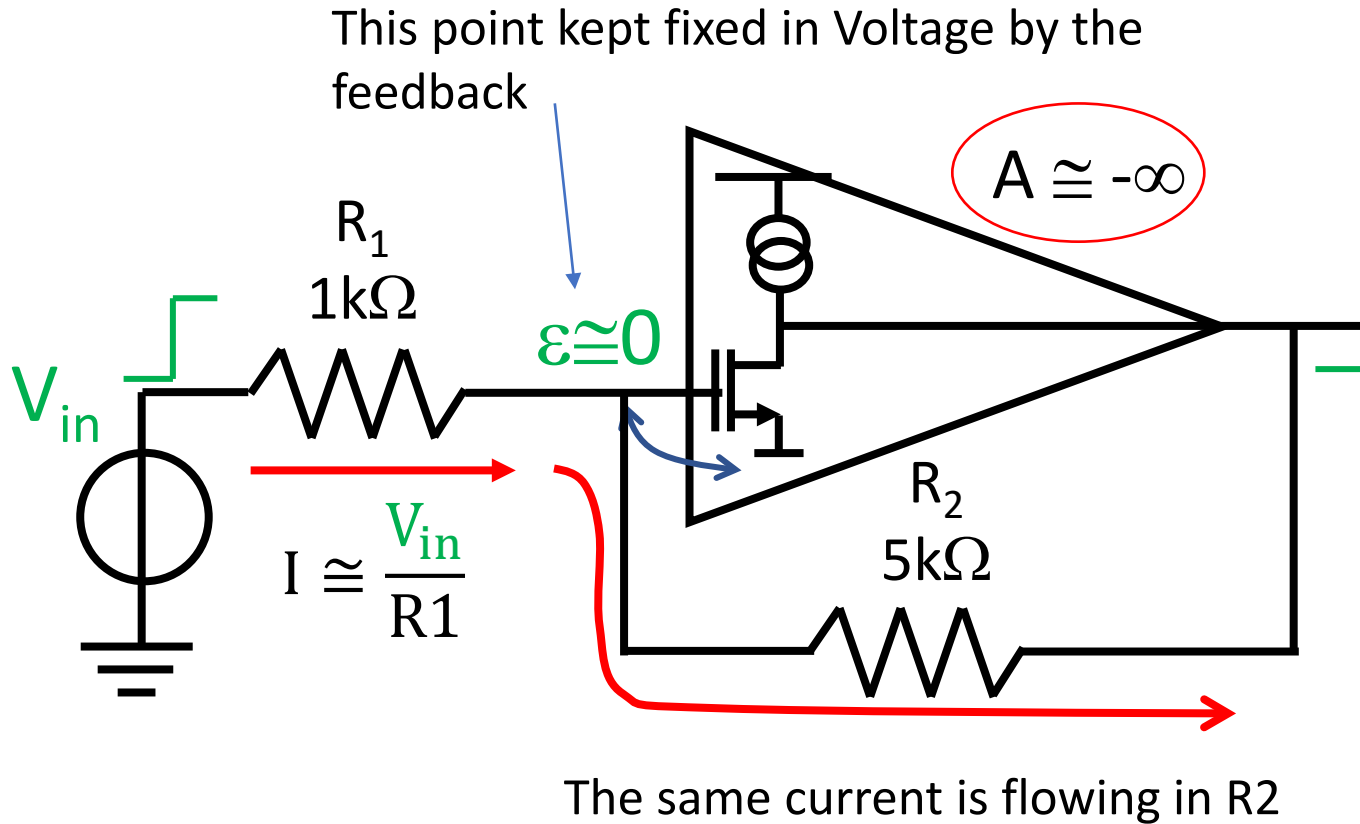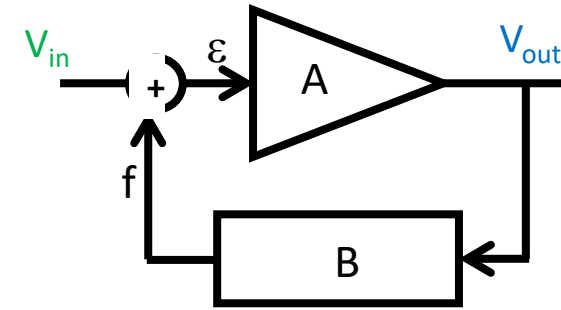

$$V_{out} = -\frac{V_{in}}{R_1} \cdot R_2$$





$$G_{id} = -\frac{R_2}{R_1} = -5$$

Ideal because $A = \infty$

The GAIN only depend on RESISTANCES :
Stable and Linear !

Negative and Positive Feedback

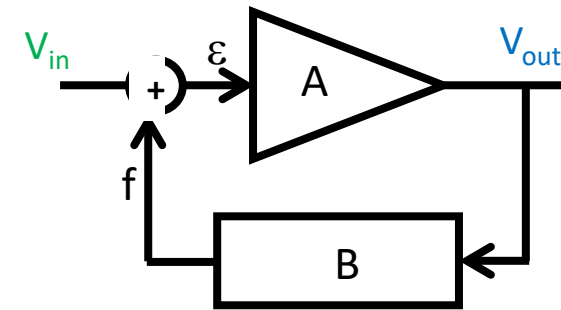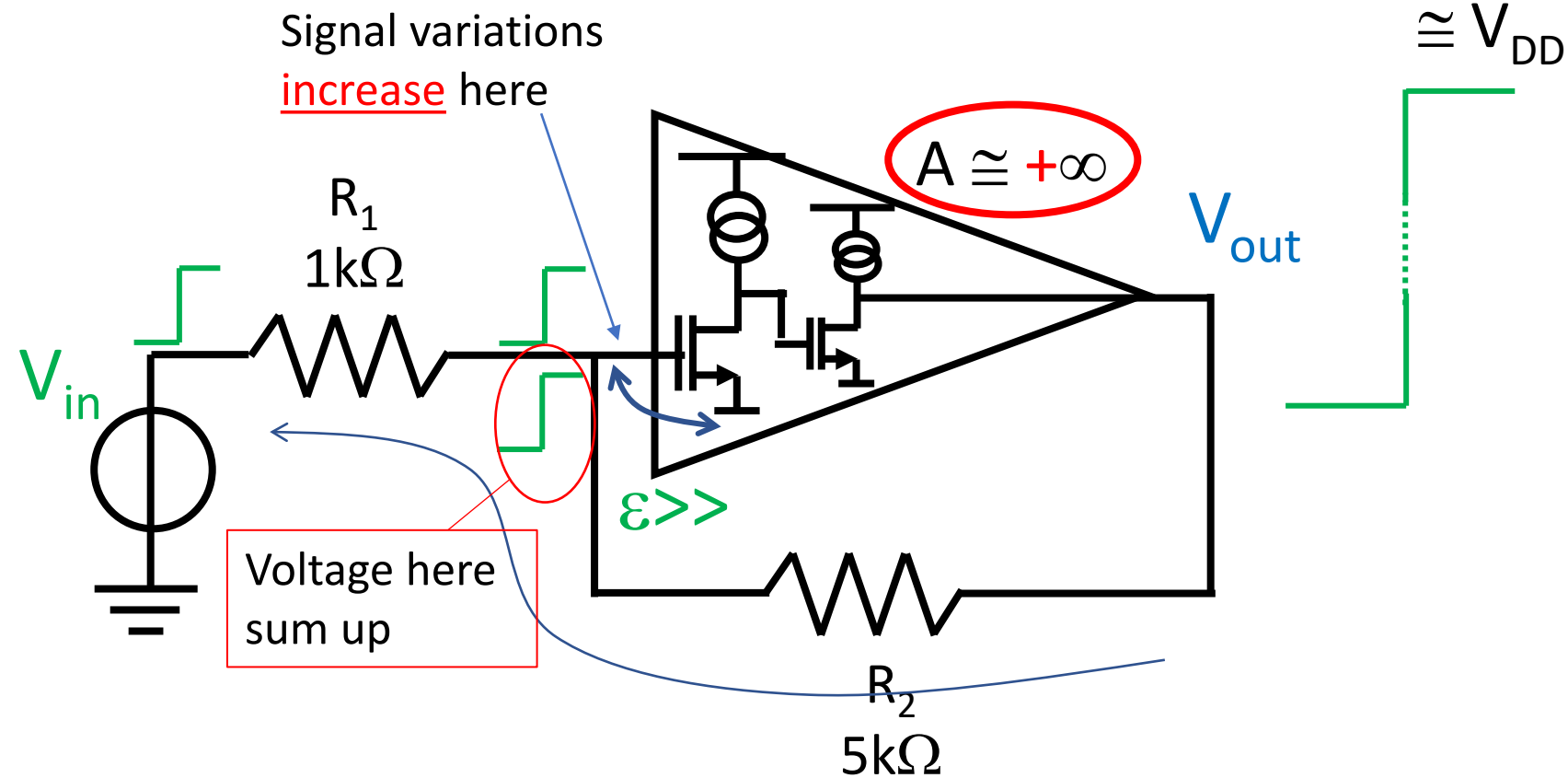

The output voltage pulls up the voltage at input of amplifier (ϵ increases, VERY BAD).

The output voltage will increase further. The system will only stop when V_{out} reaches V_{DD} .




**POSITIVE
FEEDBACK**

STABILITY is ensured only by NEGATIVE FEEDBACK

The inventor of the feedback : Harold S. Black

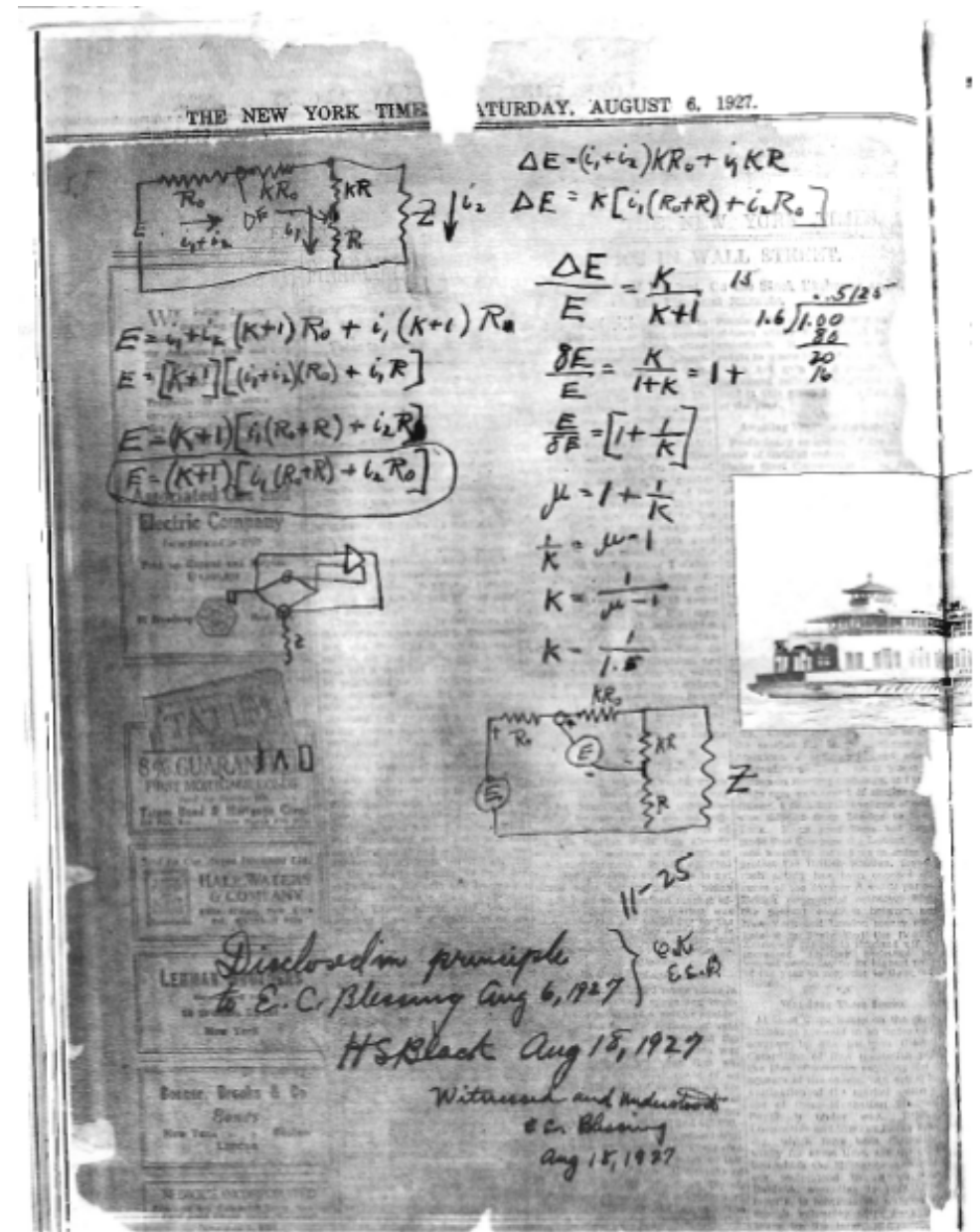It was a day in August 1927 when Harold S. Black, while crossing Hudson river on the Lackawanna boat to go to work in Manhattan, got the idea of the Feedback control to stabilize gain variations and reduce non-linearities. He was 29 years old and was working since six years at Bell Telephone Laboratories, a telephone company.



End of the lesson