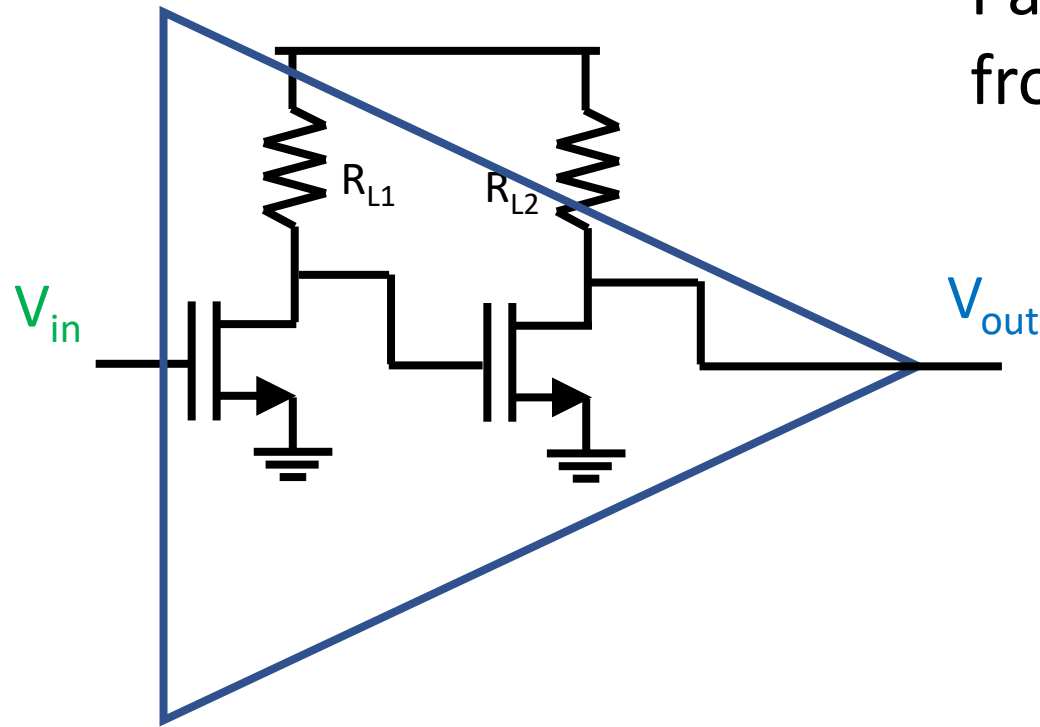



Recap : Open loop amplifiers very unpredictable



Parameters of amplifiers may change a lot from sample to sample (few % to 100 % !)


Gain changes
Distortion changes
Frequency response changes

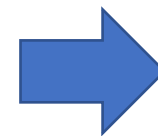Almost impossible to stabilize
an amplifier by design



Need a Game changer !

Recap : the FEEDBACK concept

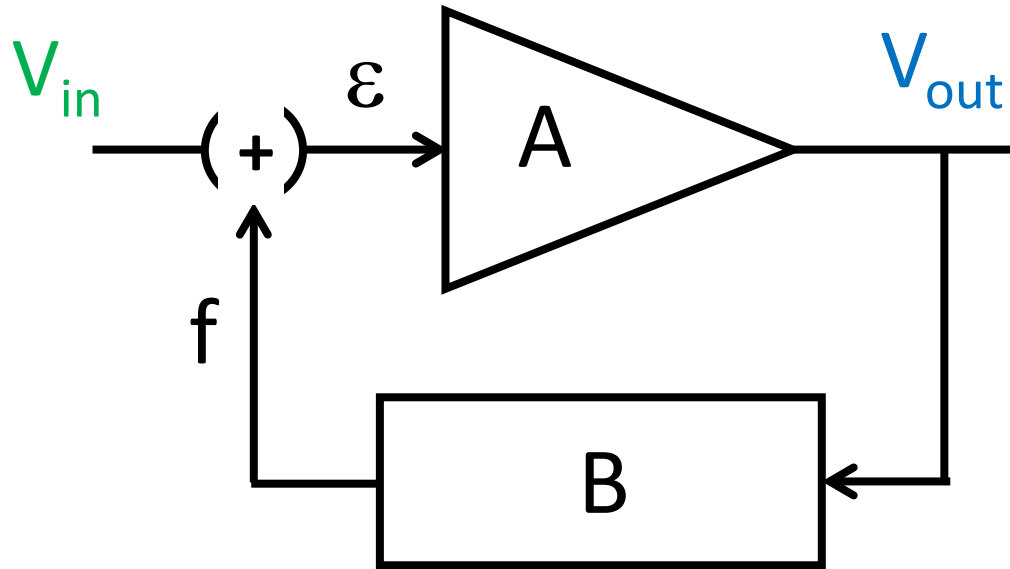

«A·B» is the Loop Gain

Suppose $A=-\infty$
(we know we can !)

The output does NOT depend on A
(Very GOOD)

$$V_{out} = V_{in} \cdot \frac{A}{1 - A \cdot B}$$

$$V_{out} = V_{in} \cdot \frac{1}{-B}$$

If B is stable and linear, also the Gain
will be stable and linear (Very GOOD)

Practically no signal is applied to A (Important)

$$\varepsilon = V_{in} \cdot \frac{1}{1 - A \cdot B}$$

$$\varepsilon \cong 0$$



Practically all signal is available within the loop

$$f = V_{in} \cdot \frac{A \cdot B}{1 - A \cdot B}$$

$$f \cong -V_{in}$$

Recap : the FEEDBACK in practice

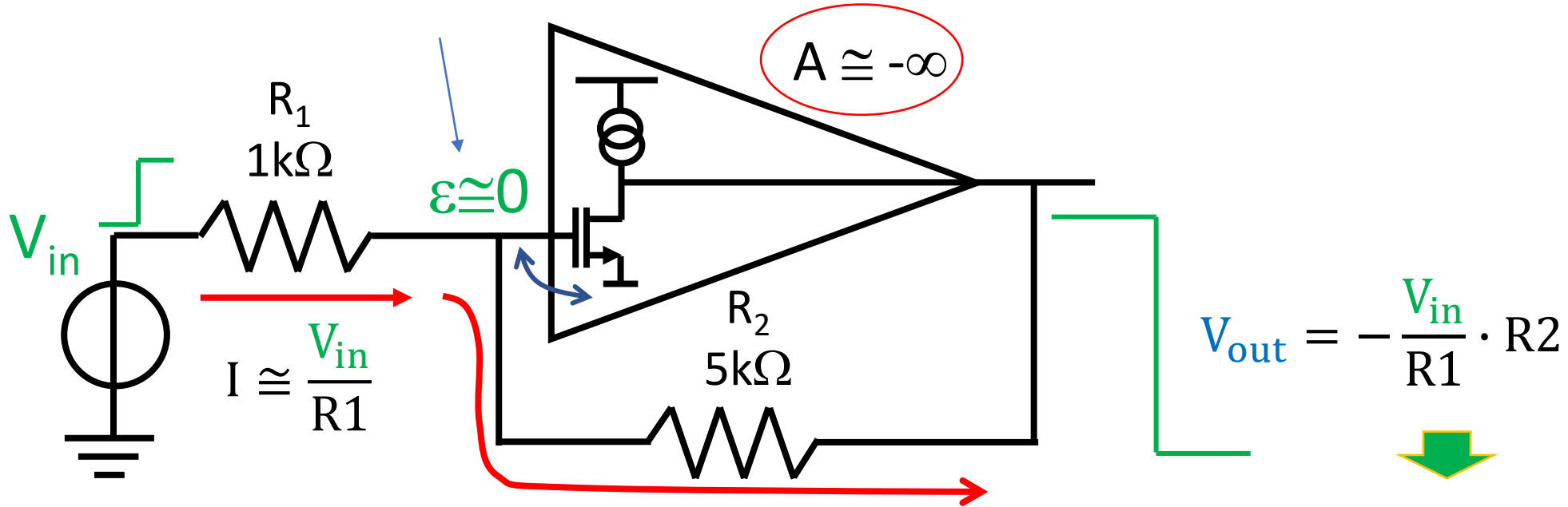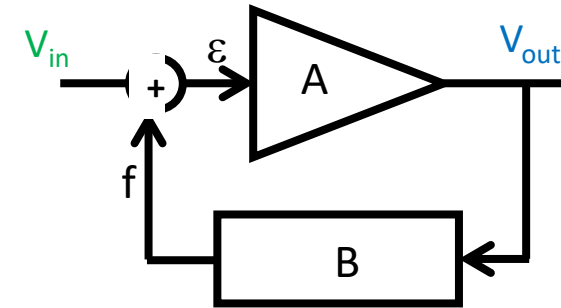This point is contrasted in its initial movement up,
by the feedback that pull it down.
At best it is NOT moving.



The same current is flowing in R2

Ideal because $A = -\infty$

$$G_{id} = -\frac{R2}{R1} = -5$$

GAIN only depends on RESISTANCES : Stable and Linear !

ELECTRONIC SYSTEMS and TECHNOLOGIES



Master in Management Engineering

Prof. Marco Sampietro

GROUND CONCEPTS ON ELECTRONICS

Feedback with Operational Amplifiers

About the Loop Gain

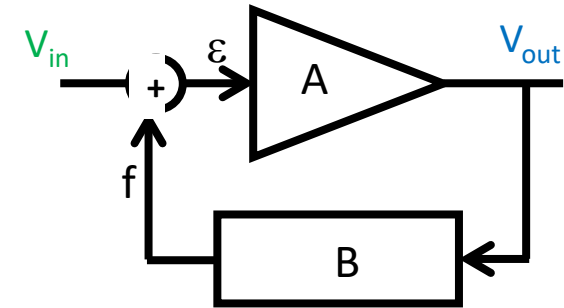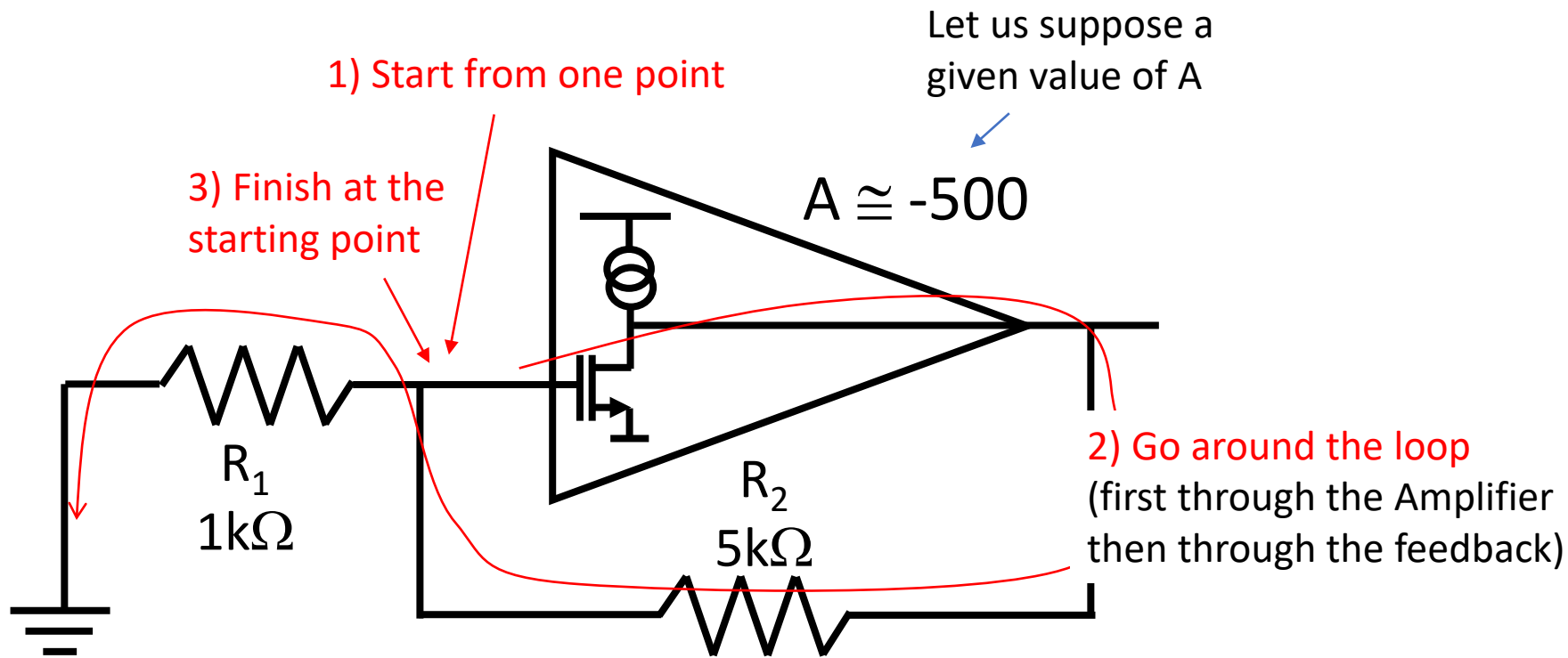



$$V_{out} = V_{in} \cdot \frac{A}{1 - A \cdot B}$$

Loop Gain

$$G_{loop} = -500 \frac{R_1}{R_1 + R_2} \cong -83$$

In negative Feedback circuits, the Loop Gain result negative (because the feedback always contrasts the initial variation !)

Ideal Gain and Real Gain

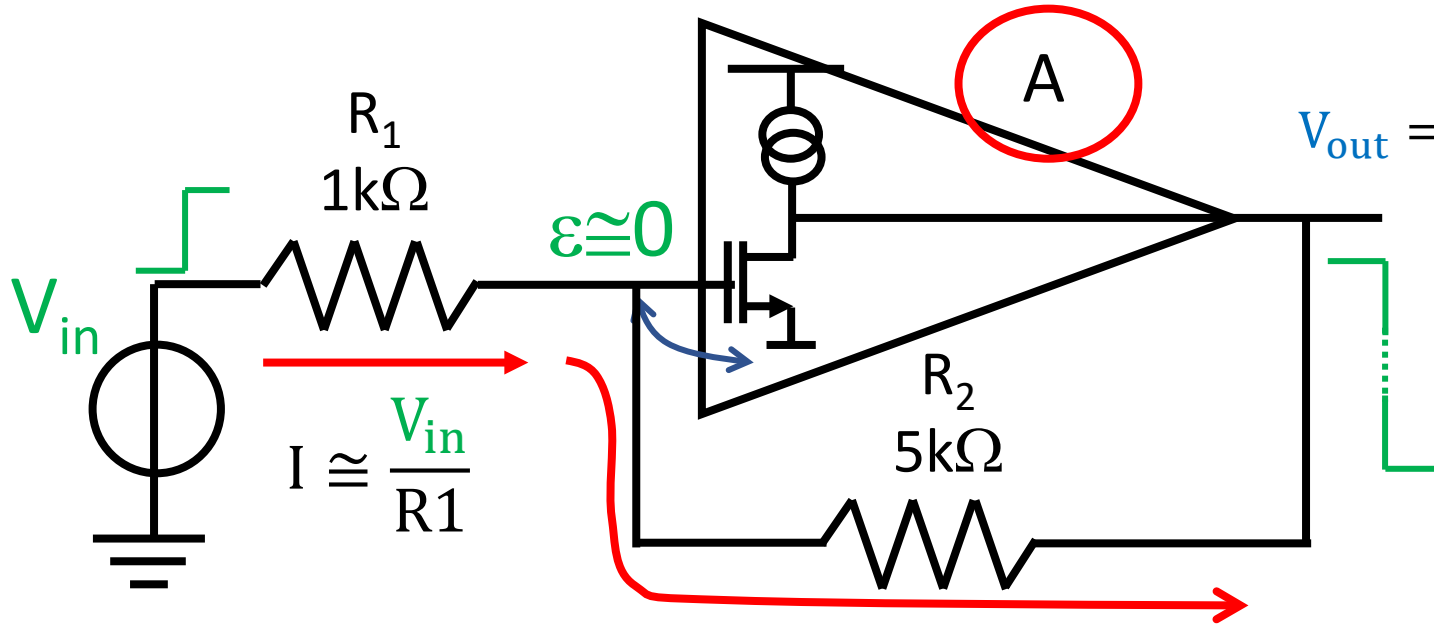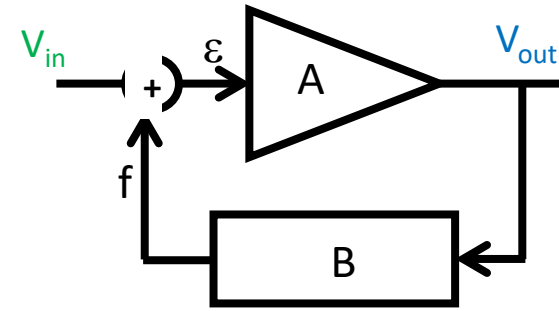

$$V_{out} = V_{in} \cdot \frac{A}{1 - A \cdot B}$$

The same current I is flowing in R2

If $A \cong -\infty \rightarrow V_{out} = V_{in} \cdot (-) \frac{1}{B}$

$$G_{id} = \frac{V_{out}}{V_{in}} = -\frac{1}{B} = -5$$

If $A \cong -500 \rightarrow V_{out} = V_{in} \cdot \frac{A}{1 - A \cdot B} \cdot \frac{B}{B} = V_{in} \cdot (-) \frac{1}{B} \cdot \frac{-A \cdot B}{1 - A \cdot B}$

$$G_{real} = \frac{V_{out}}{V_{in}} = G_{id} \cdot \frac{-G_{loop}}{1 - G_{loop}} = -5 \cdot \frac{83}{84} = -4.94$$

Only G_{id} and G_{loop} are necessary

Gain robustness

Given $G = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{A}{1 - A \cdot B}$

how is the variation of G when A varies ?
(We know that A is unpredictable !)

$$\frac{\partial G}{\partial A} = \frac{1}{1 - A \cdot B} + \frac{AB}{(1 - A \cdot B)^2} = \frac{1}{(1 - A \cdot B)^2} = \frac{1}{1 - A \cdot B} \cdot \frac{A}{1 - A \cdot B} \cdot \frac{1}{A} = \frac{1}{1 - A \cdot B} \cdot G \cdot \frac{1}{A}$$


$$\frac{\partial G}{G} = \frac{\partial A}{A} \cdot \frac{1}{1 - A \cdot B}$$

If A varies 50% and $G_{\text{loop}} = -100 \longrightarrow \frac{\partial G}{G} = 0.5\%$


If A varies 50% and $G_{\text{loop}} = -10 \longrightarrow \frac{\partial G}{G} = 5\%$

It is important to have big G_{loop} in order to be insensitive to variations of the gain of the amplifier A

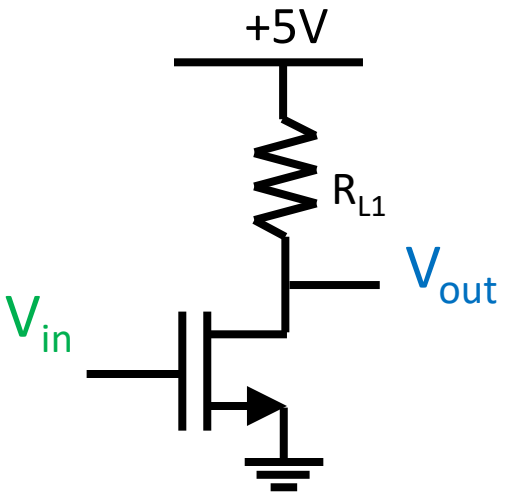
Amplifiers with 2 inputs : leveraging the difference



2 inputs

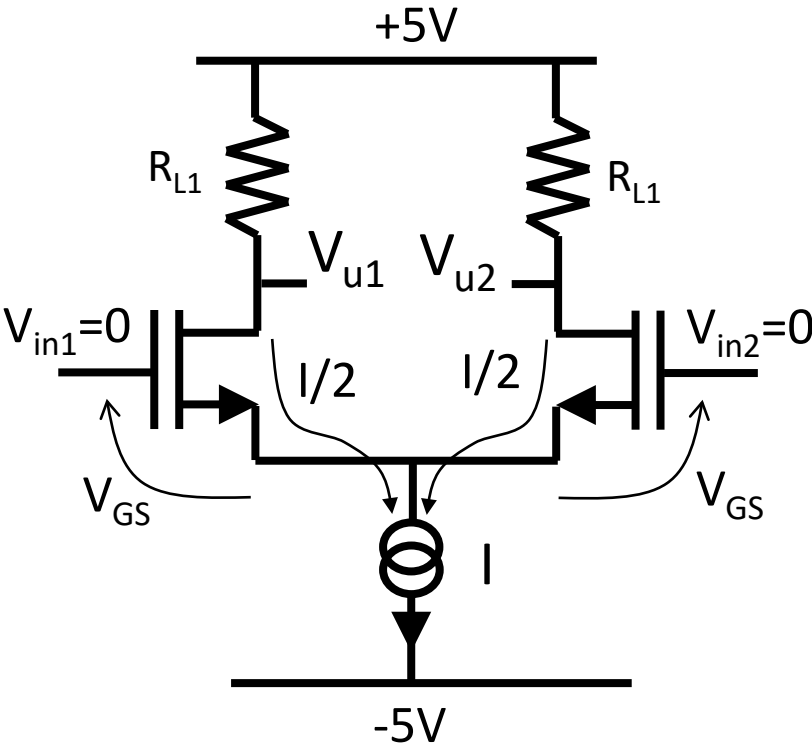


Example of Bias

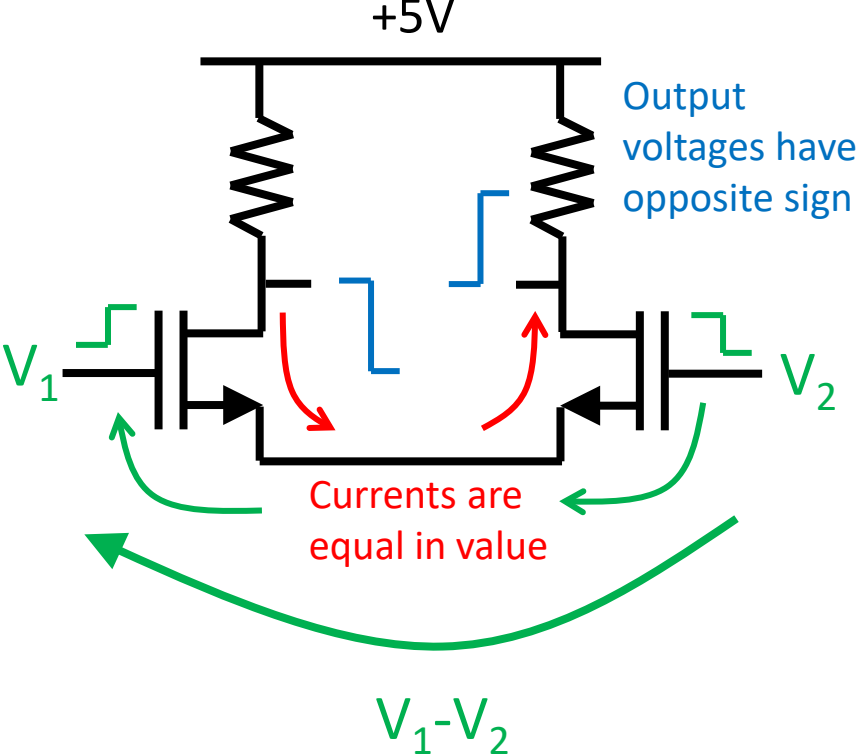


Behaviour with signal applied
 (only the signal is indicated)


The Operational Amplifier – OpAmp (1)

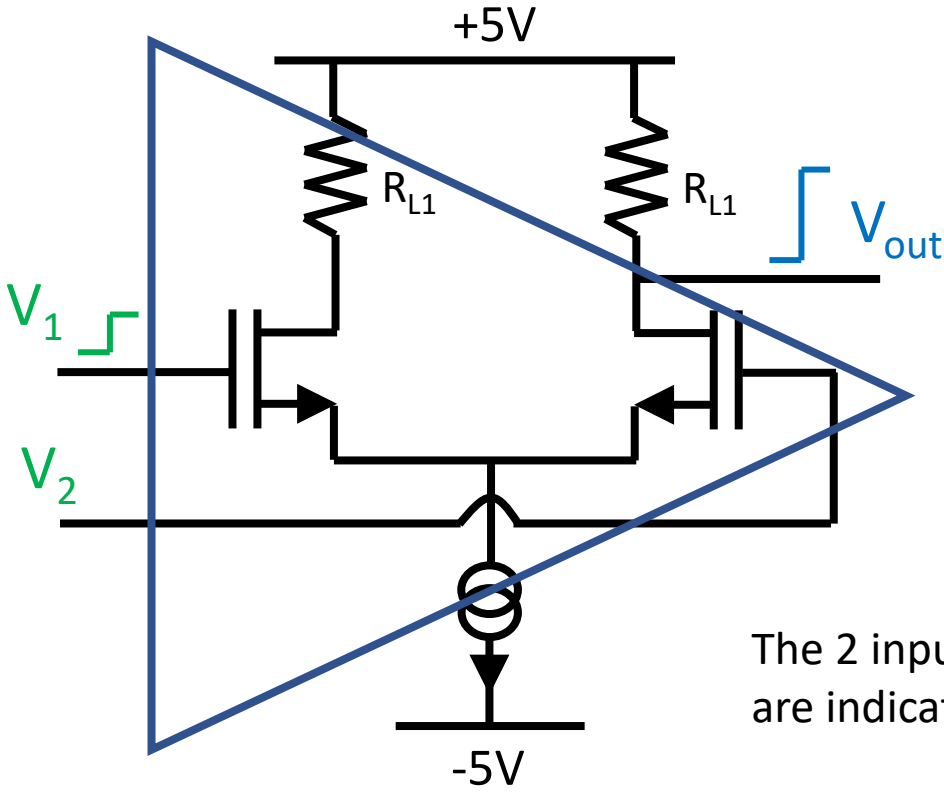

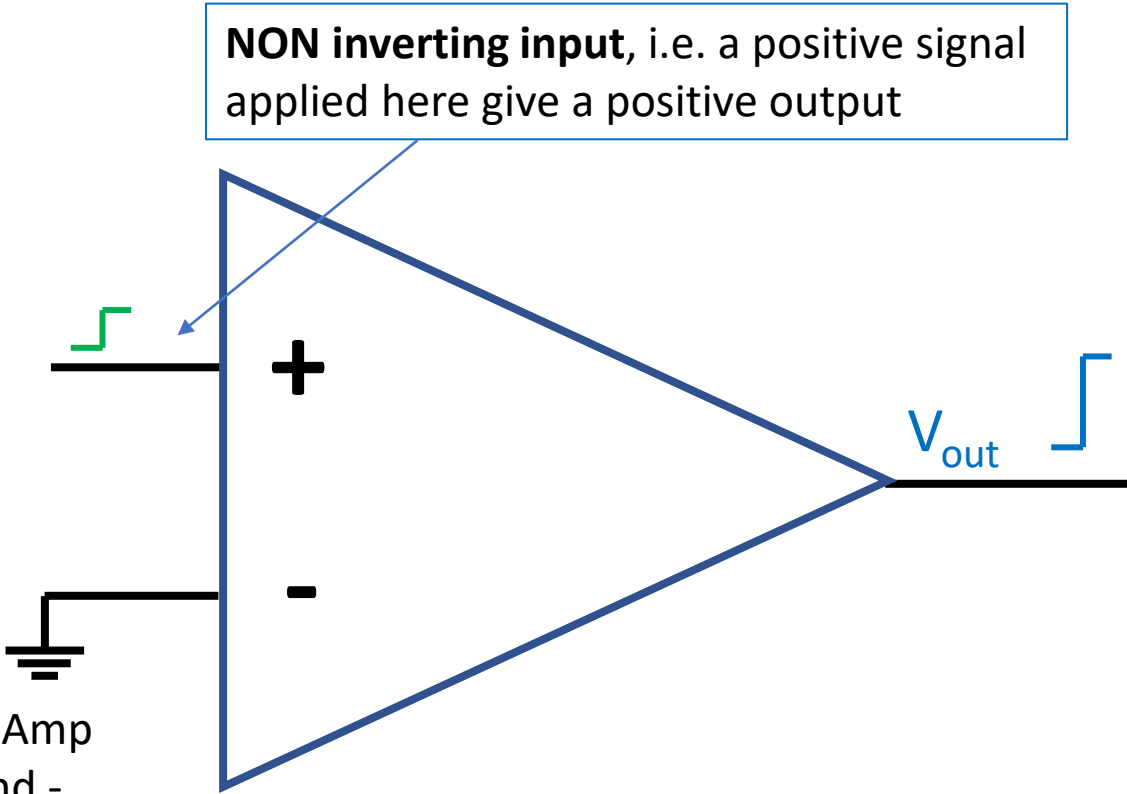
The 2 inputs of the OpAmp are indicated with + and -



The Operational Amplifier – OpAmp (2)

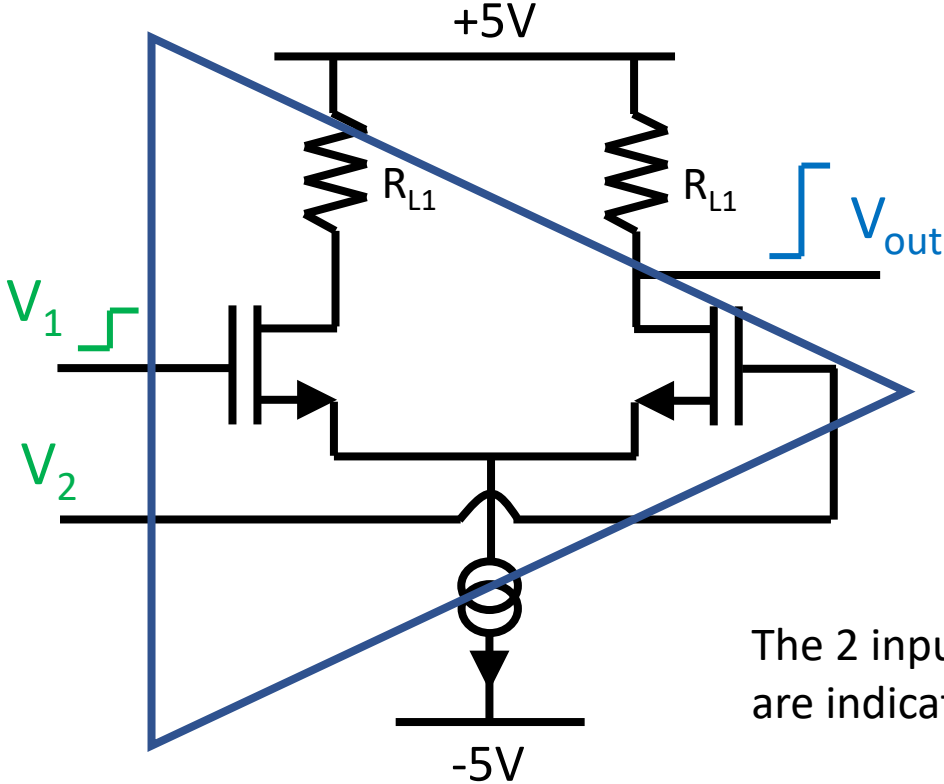


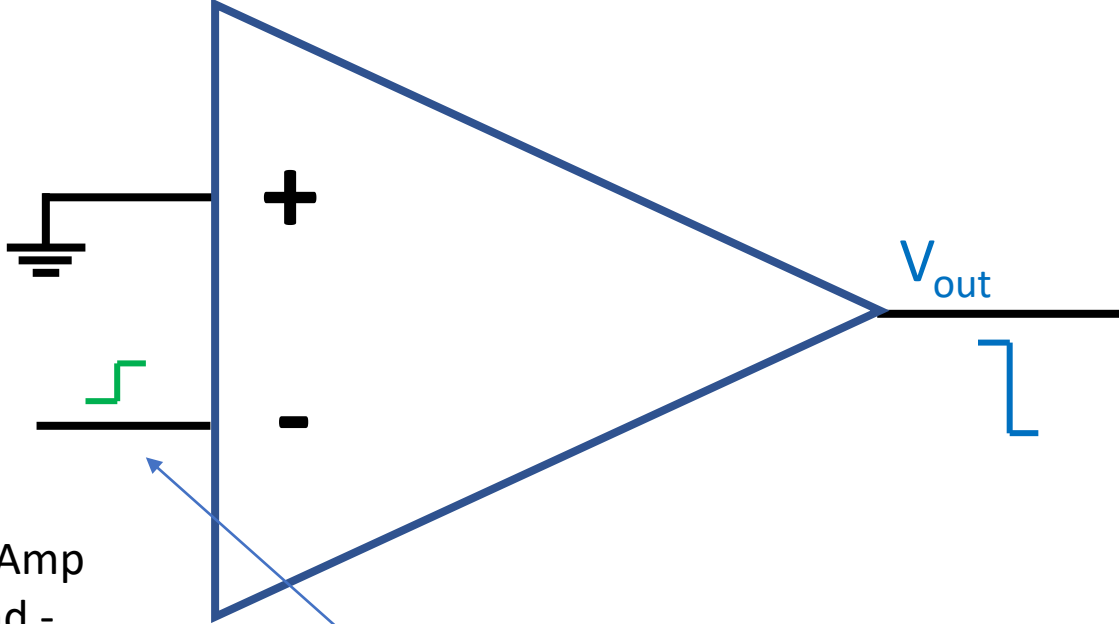The 2 inputs of the OpAmp are indicated with + and -




Inverting input, i.e. a positive signal applied here give a negative output

FEEDBACK using an OpAmp - review

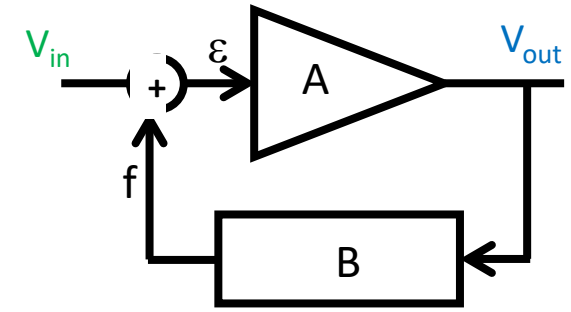

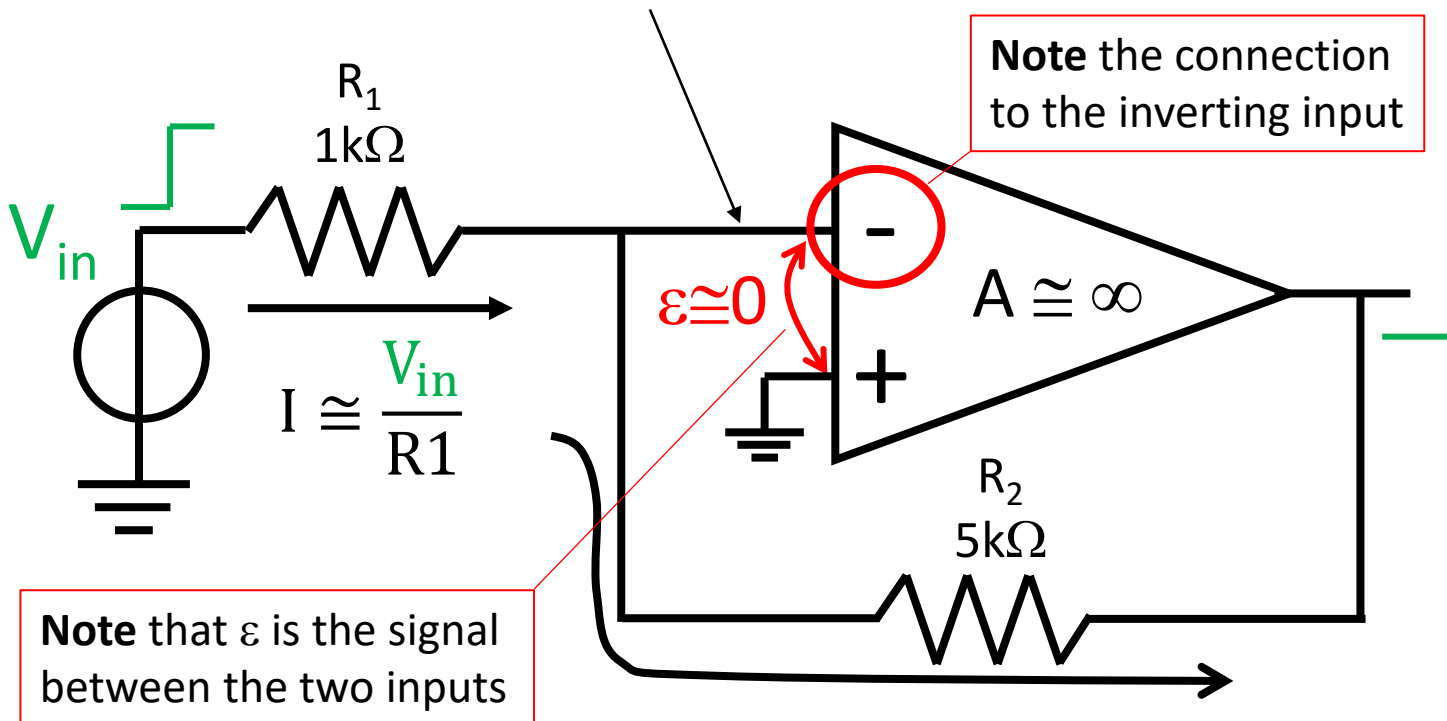This point is contrasted in its movement up by the feedback that pull it down. At best, it is kept fixed to the same voltage of the other input of the OpAmp (in this case to ground)





The same current is flowing in R2

$$V_{out} = -\frac{V_{in}}{R_1} \cdot R_2$$



$$G_{id} = -\frac{R_2}{R_1} = -5$$


Exercise on Feedback with OpAmp (1)

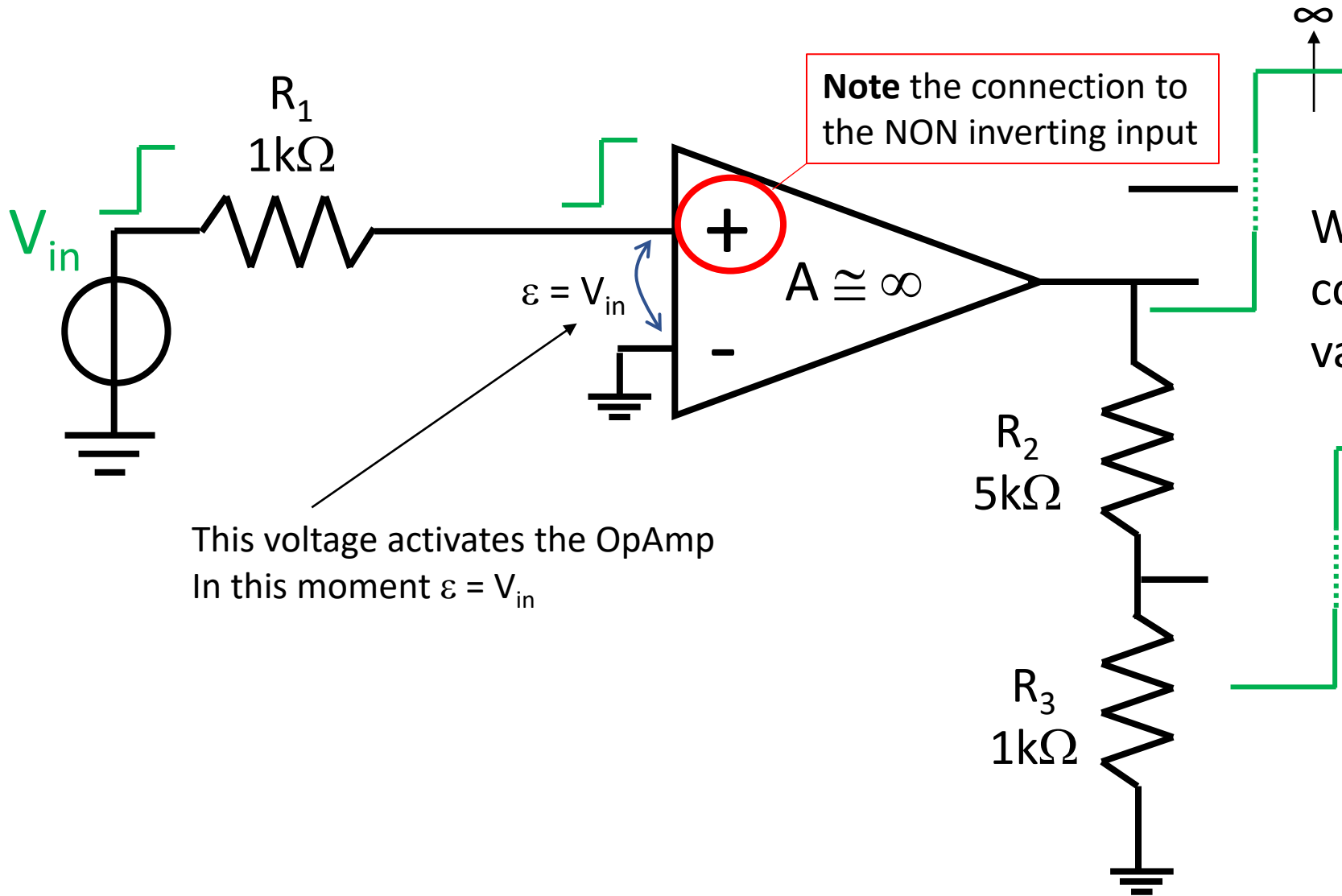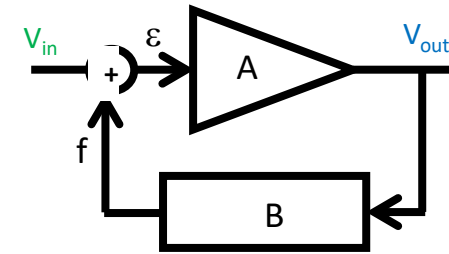

We have to use the output to compensate the voltage variation of ϵ (ideally to $\epsilon \cong 0$)


This voltage activates the OpAmp
In this moment $\epsilon = V_{in}$

Exercise on Feedback with OpAmp (2)


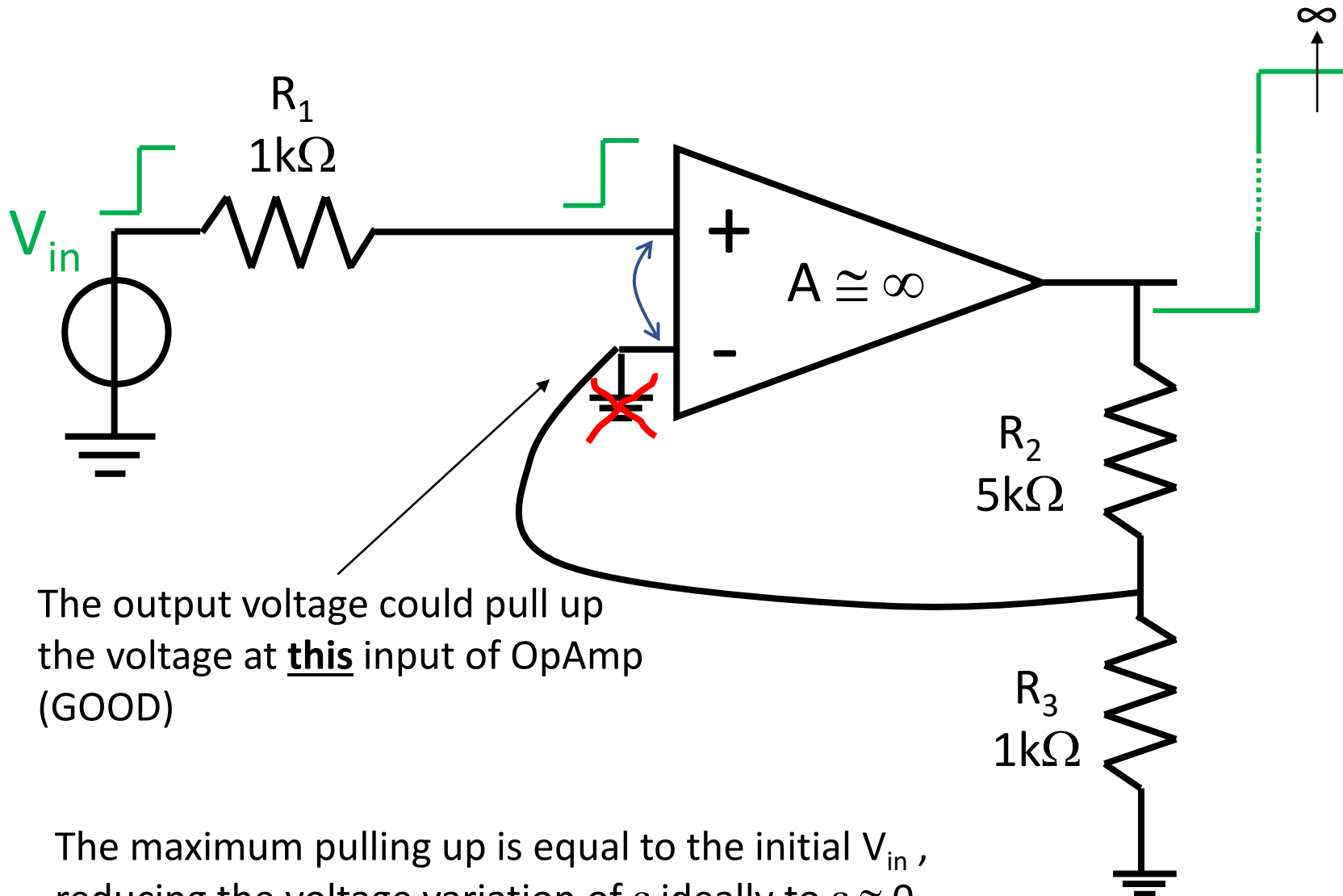


The output voltage could pull up the voltage at **this** input of OpAmp (GOOD)

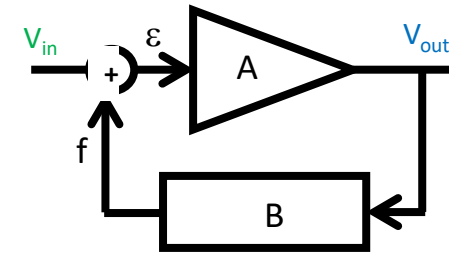The maximum pulling up is equal to the initial V_{in} , reducing the voltage variation of ε ideally to $\varepsilon \cong 0$.





Exercise on Feedback with OpAmp (3)

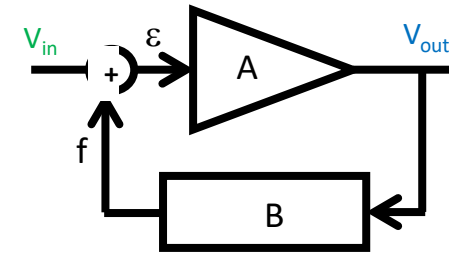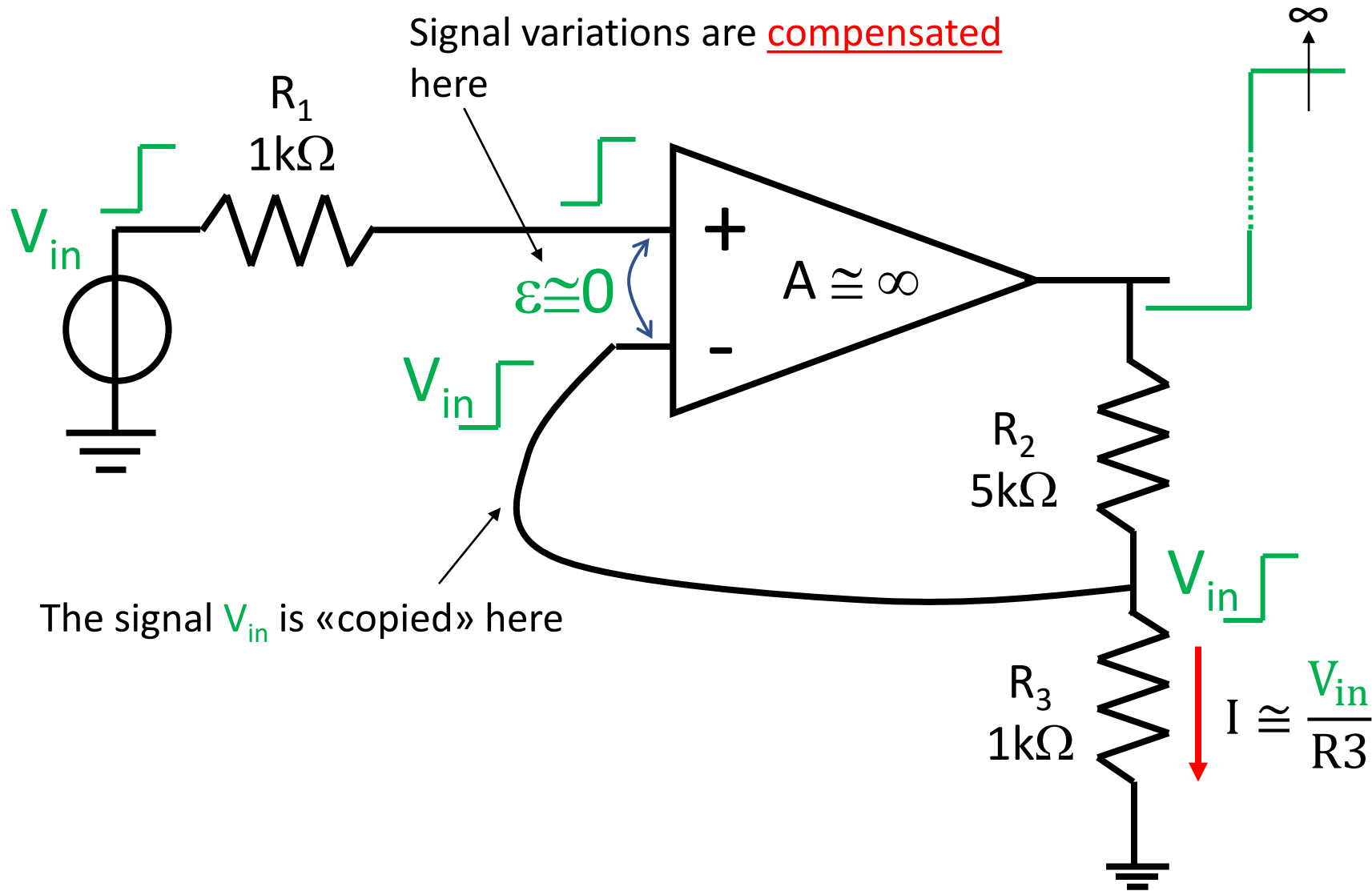

If this point moves up by V_{in}
the current in R_3 is defined

Exercise on Feedback with OpAmp (4)

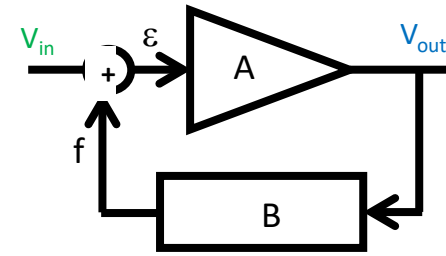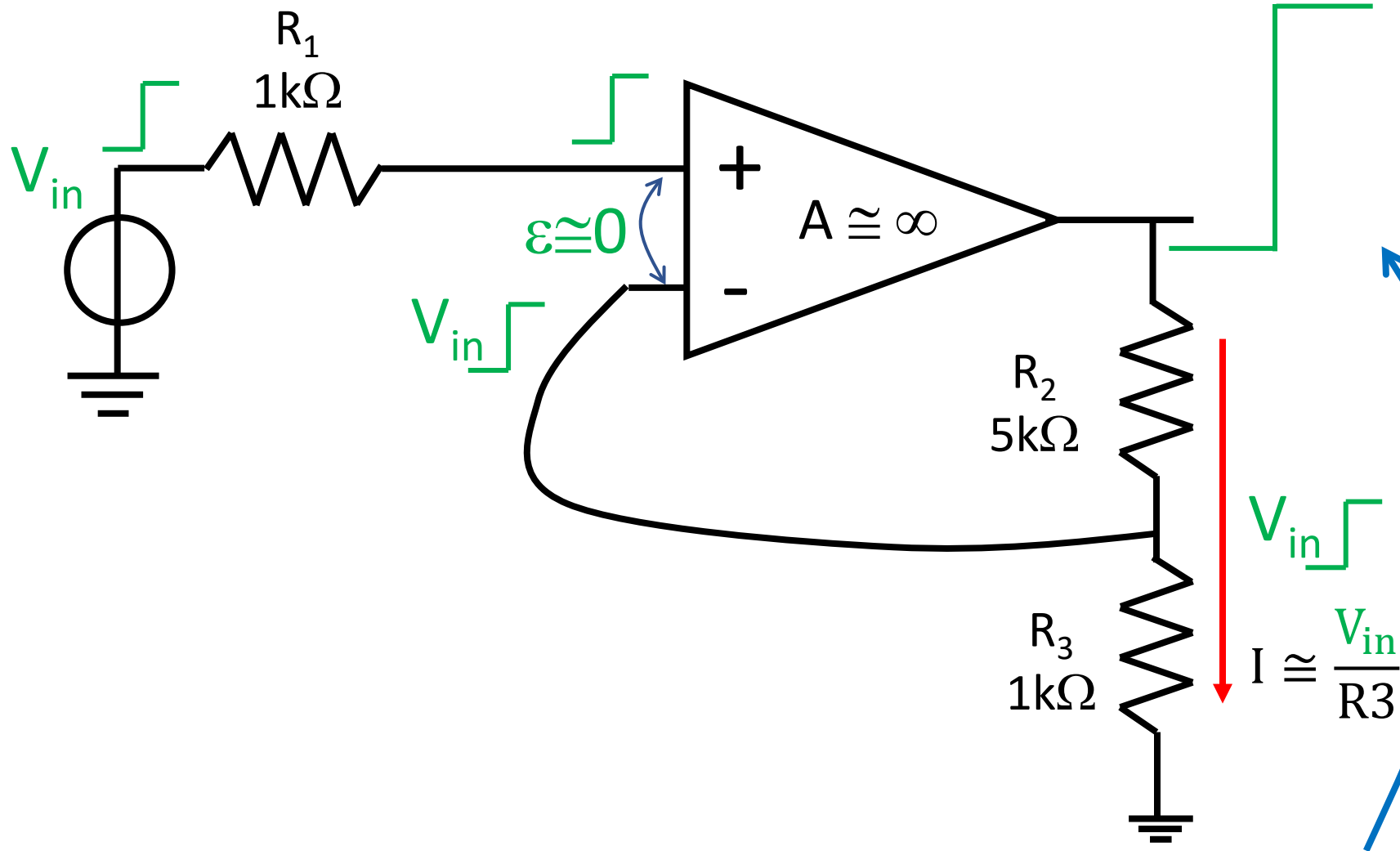

$$V_{out} \cong \frac{V_{in}}{R_3} \cdot (R_2 + R_3)$$



$$G_{id} = \frac{R_2 + R_3}{R_3} = 6$$

End of the lesson