
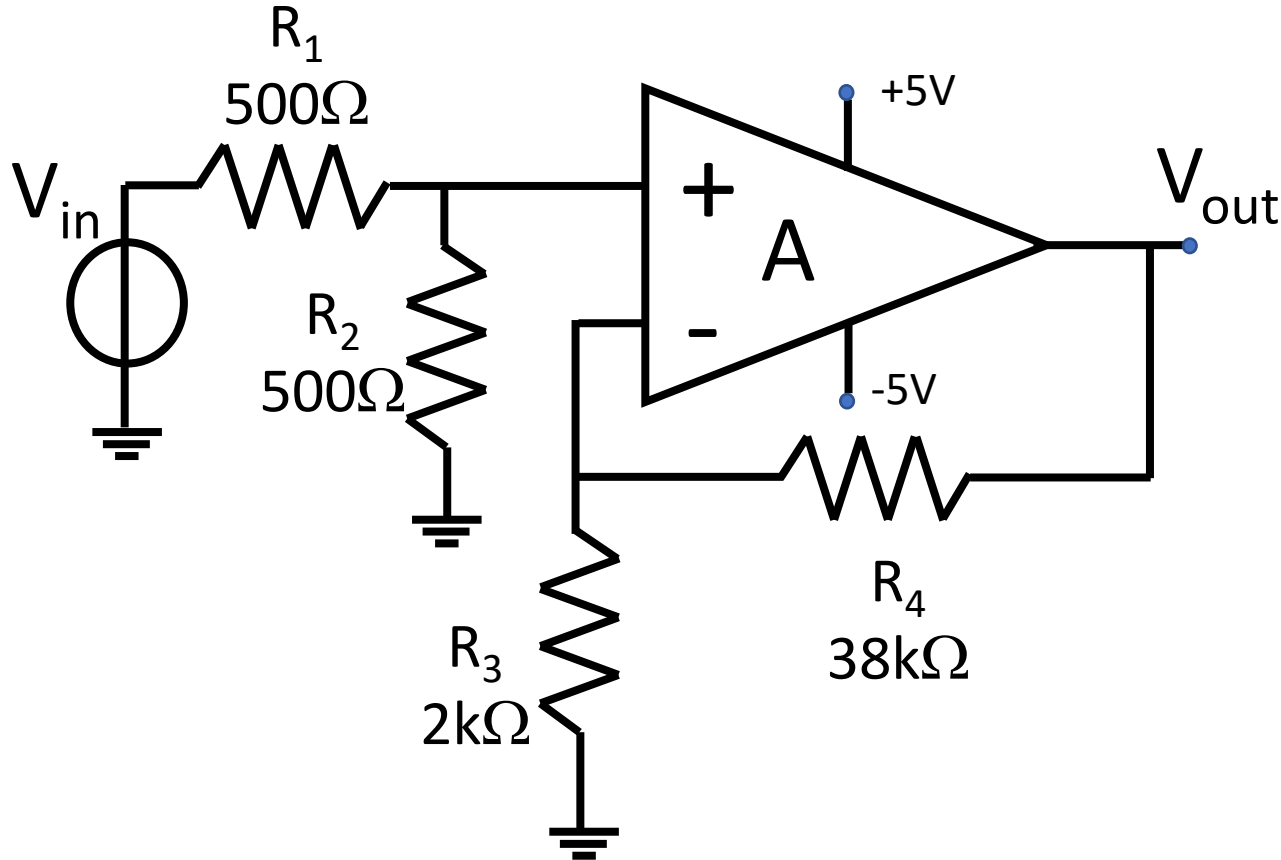


# Exercise (1)

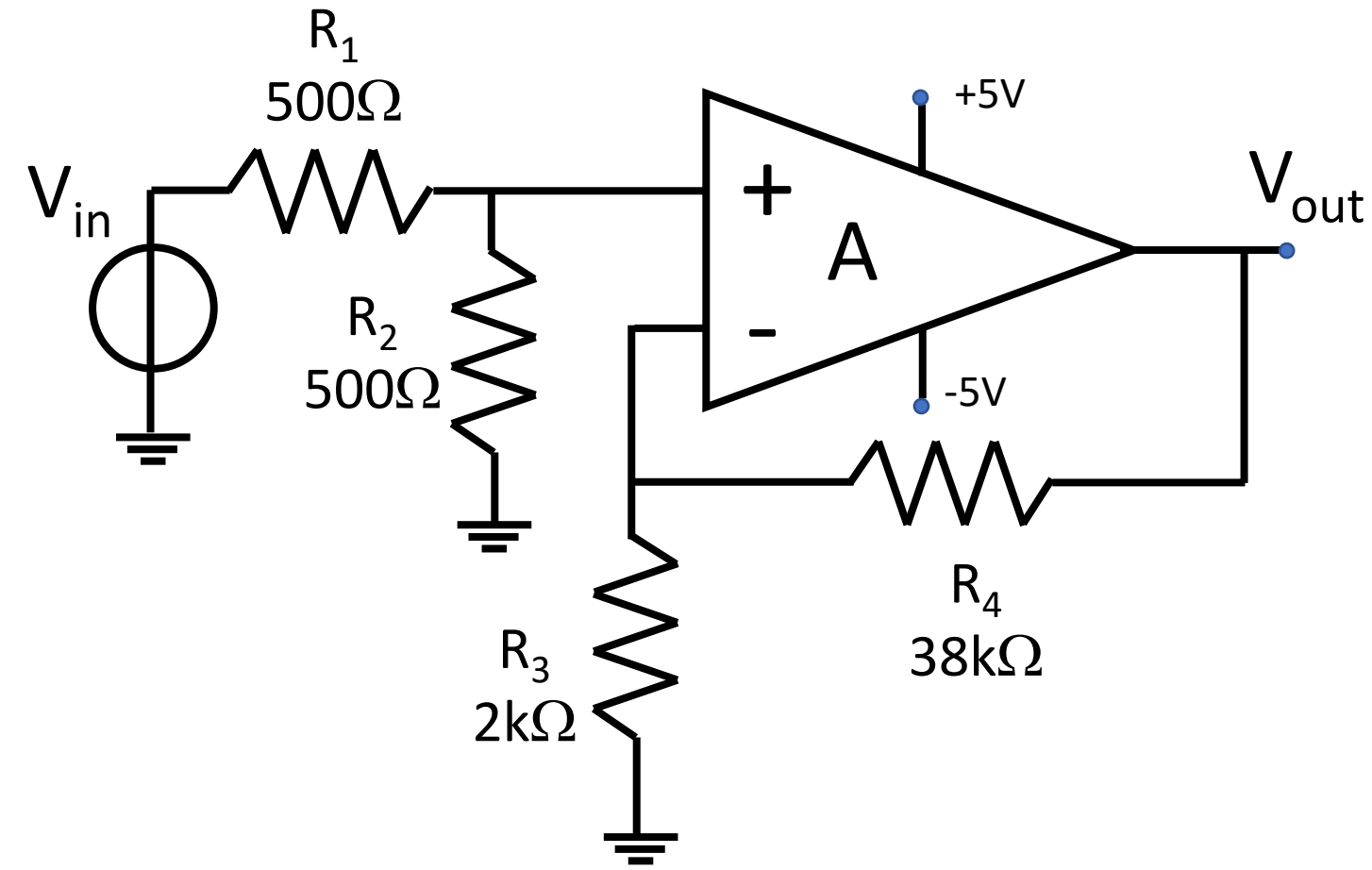


- What is the ideal Gain ( $A=\infty$ ) of the circuit ?
- What is the maximum amplitude of a sinusoid that can be applied to the input ?
- What is the actual Gain if  $A=8000$  ?
- If  $A$  is provided by the manufacturer with 40% of possible variations, what would be the distribution of performance of the produced amplifier ?


a) What is the ideal Gain ( $A=\infty$ ) of the circuit ?



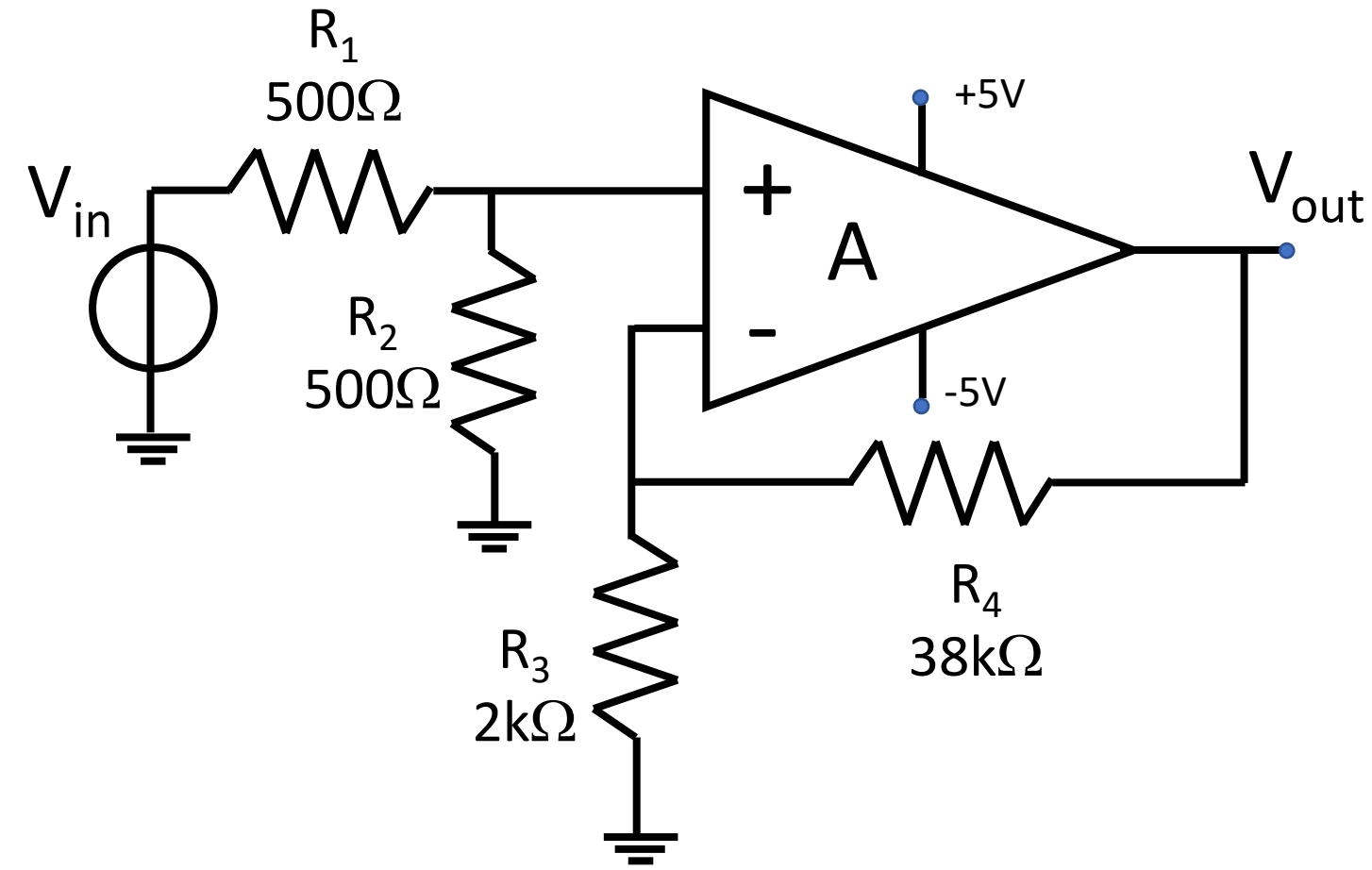
b) What is the maximum amplitude of a sinusoid that can be applied to the input ?



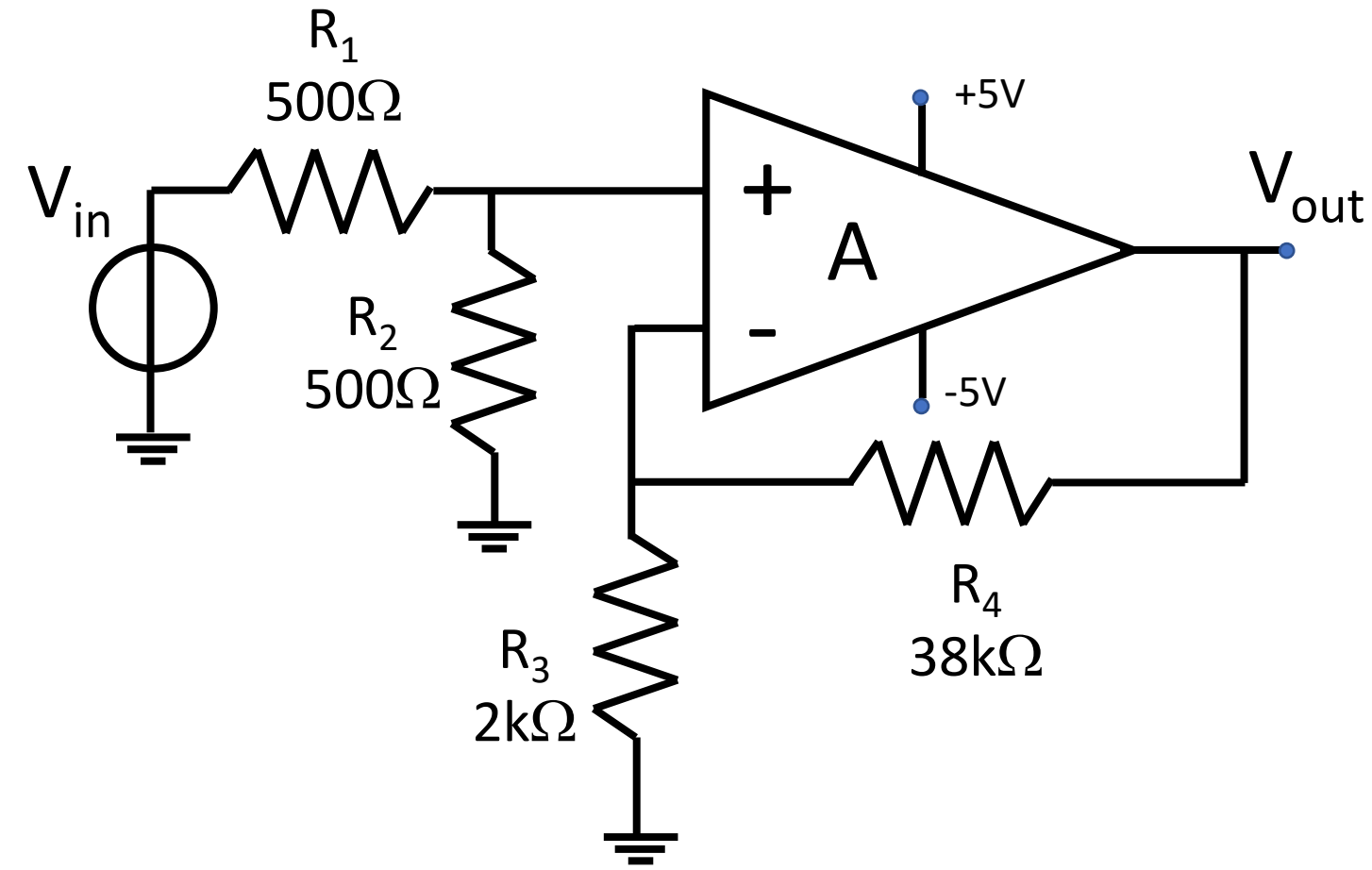
c) What is the actual Gain if  $A=8000$  ?



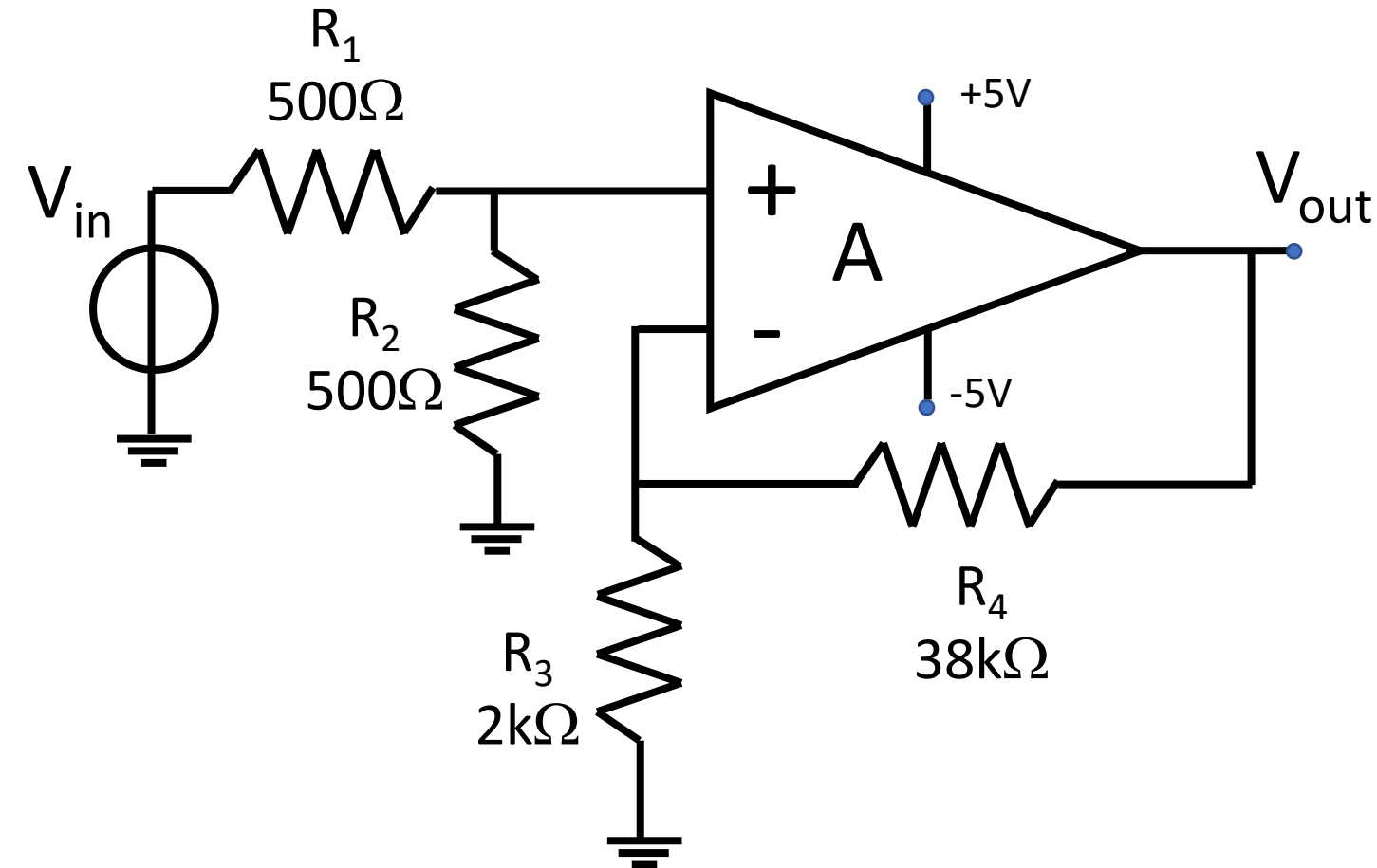d) If  $A$  is provided by the manufacturer with 40% of possible variations, what would be the distribution of performance of the produced amplifier ?




# Exercise (2)

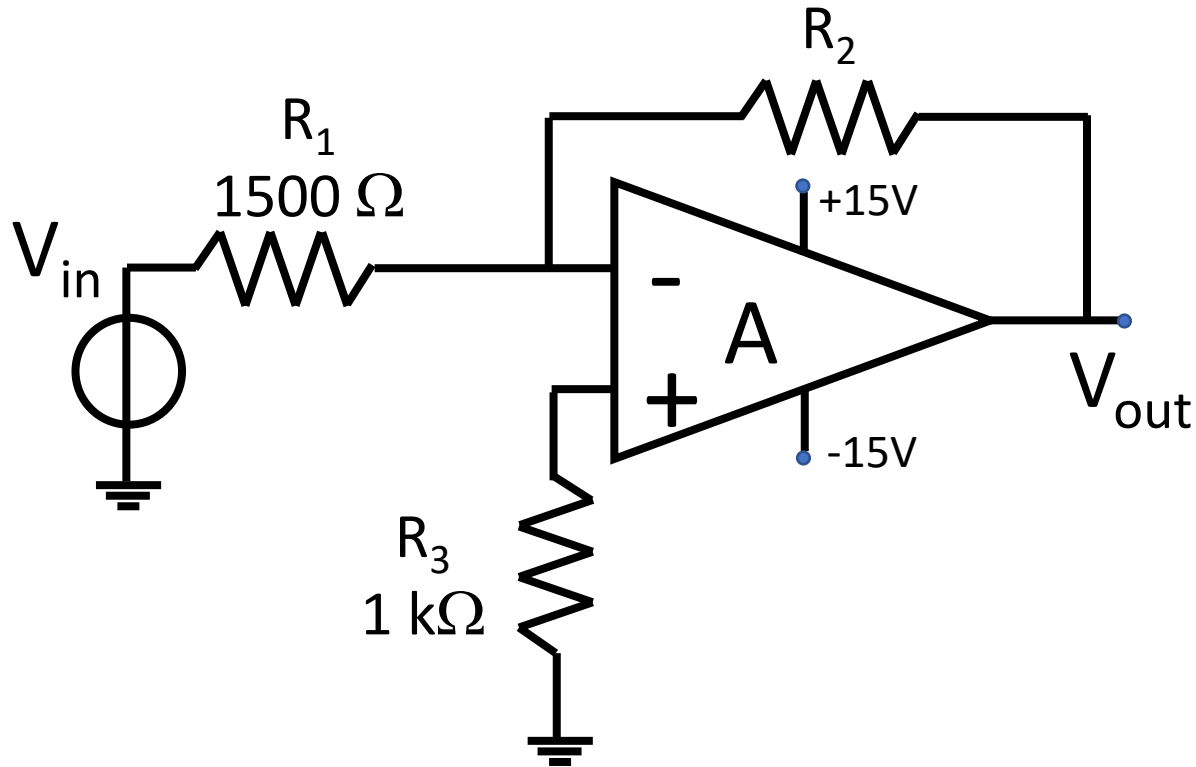


- Find the value of  $R_2$  in order to have an ideal Gain ( $A=\infty$ ) equal to  $G=-6$
- How does  $R_3$  play a role in the gain ?
- Find the loop gain of the circuit when the OpAmp that you have selected has  $A=750$  ?
- If  $A$  varies by 60%, what would be the variation in the gain of the amplifier ?

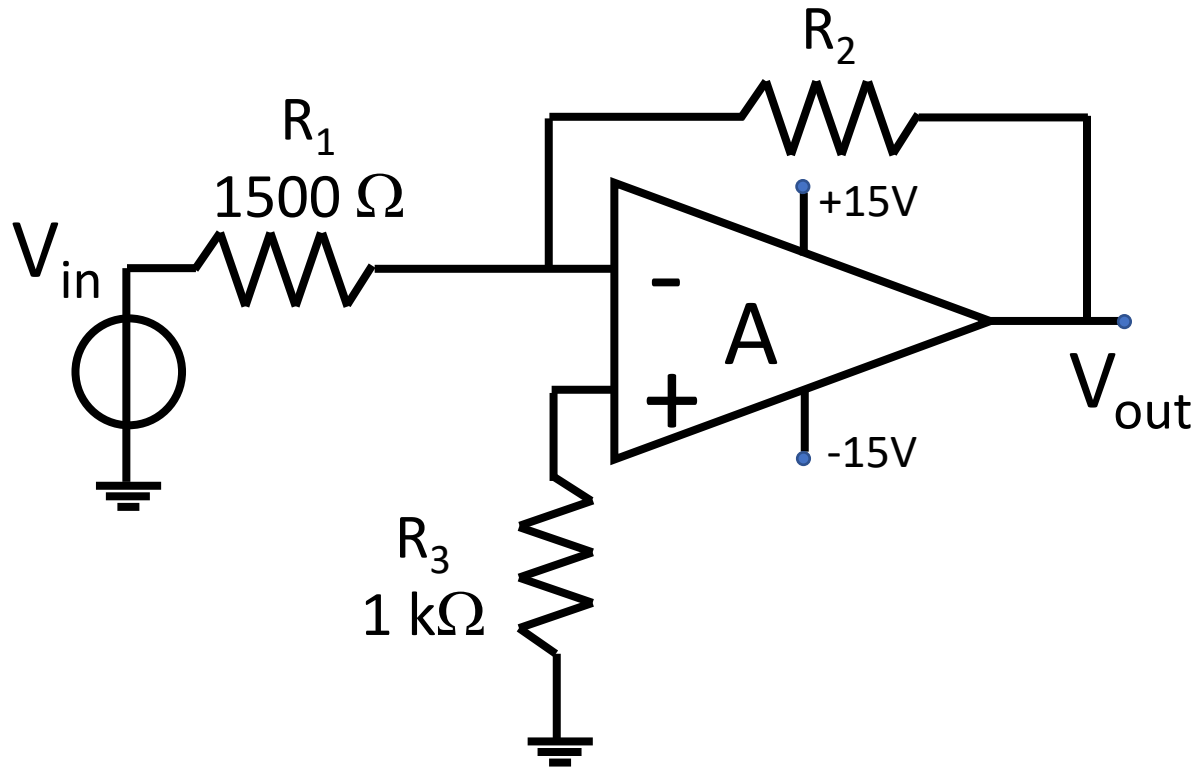a) Find the value of  $R_2$  in order to have an ideal Gain ( $A=\infty$ ) equal to  $G=-6$




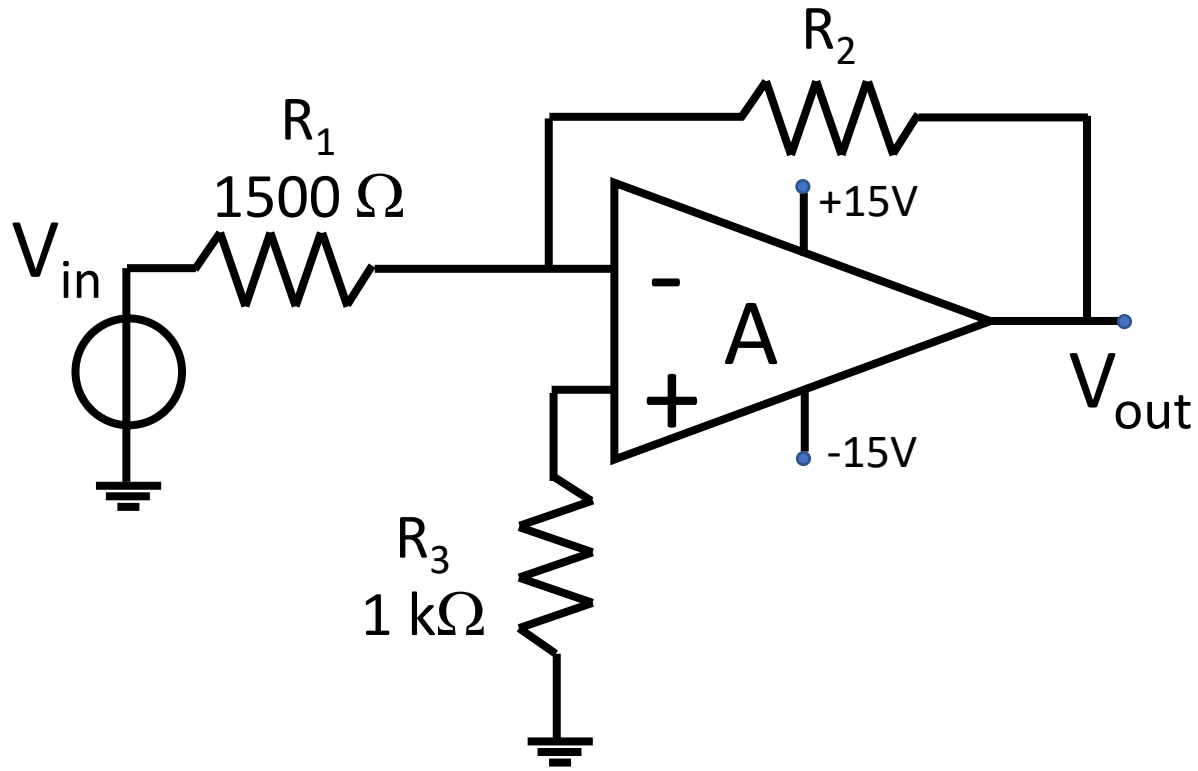b) How does  $R_3$  play a role in the gain ?






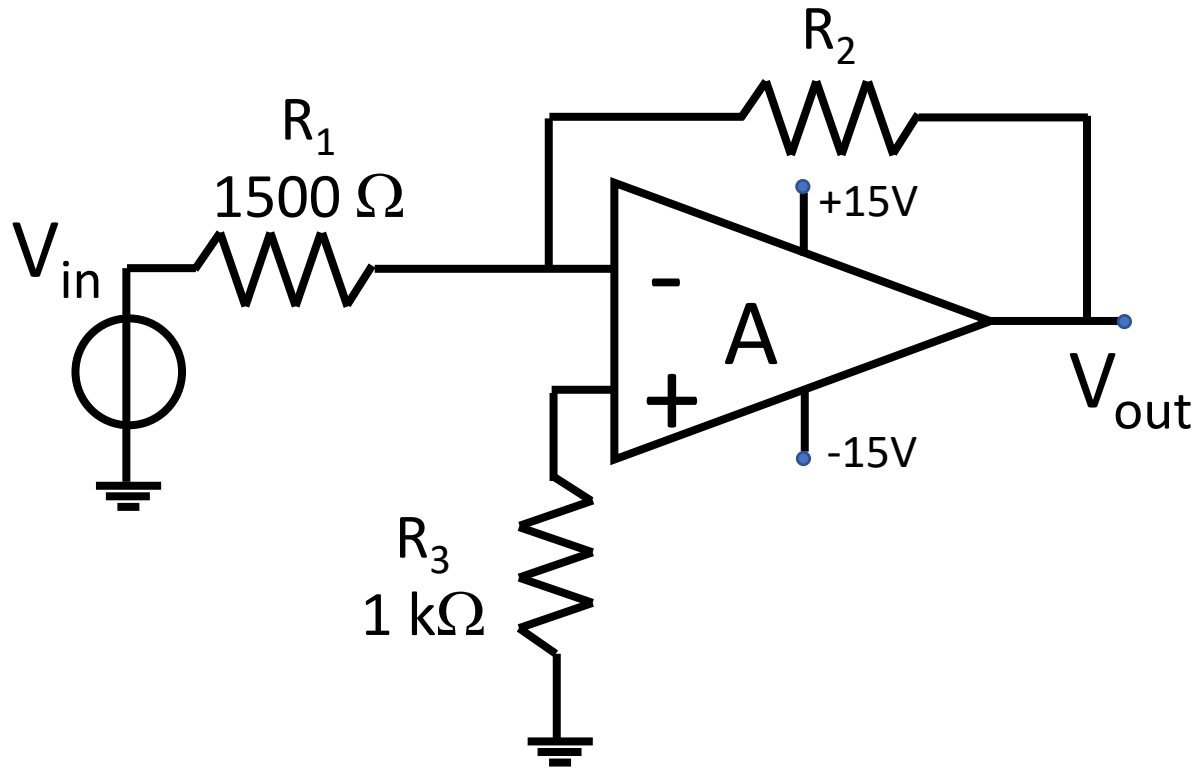
c) Find the loop gain of the circuit when the OpAmp that you have selected has  $A=750$  ?



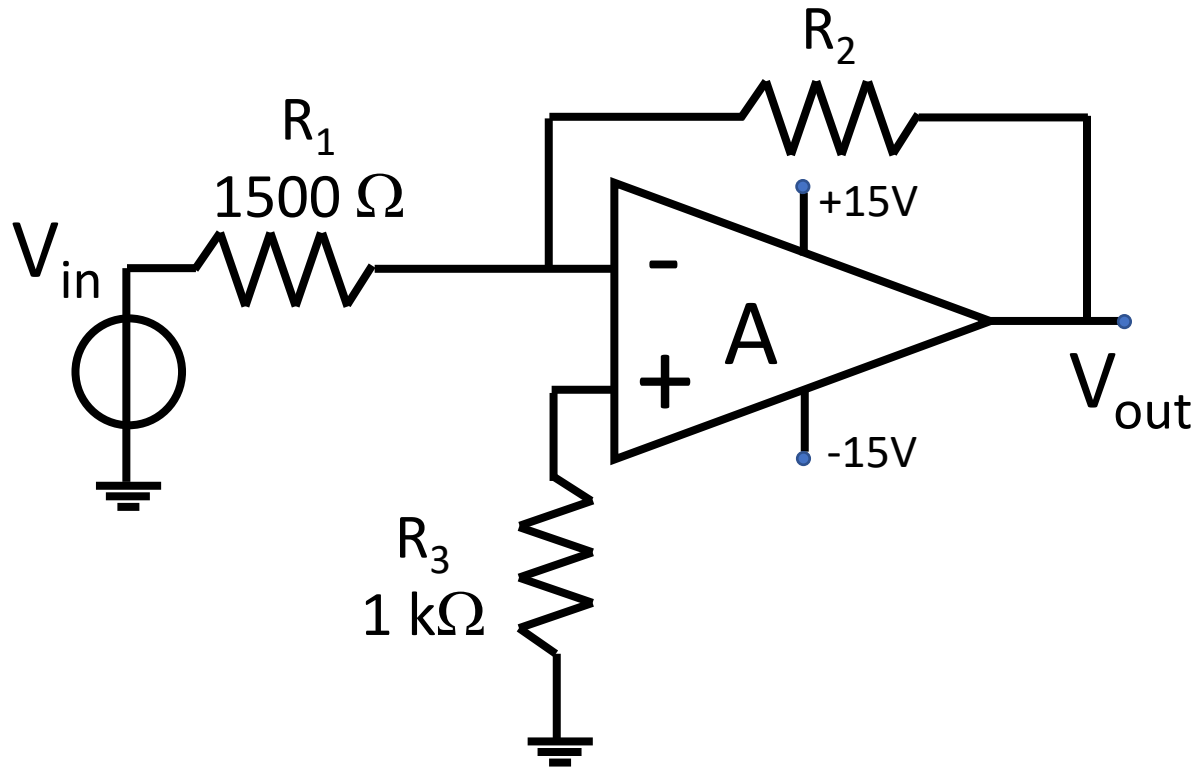d) If  $A$  varies by 60%, what would be the variation in the gain of the amplifier ?




# Exercise (3)

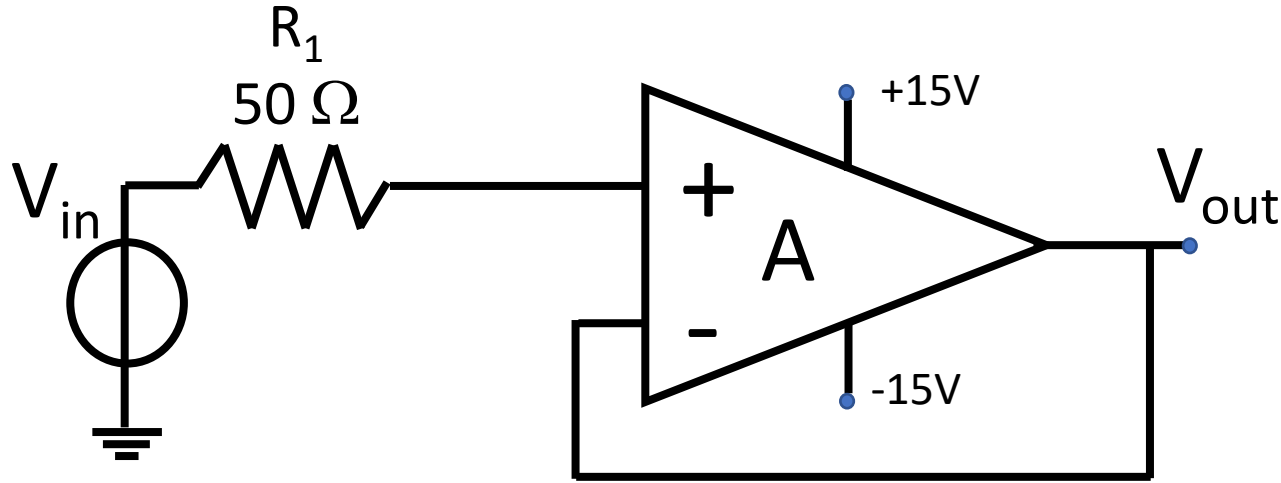

a) What is the ideal Gain ( $A=\infty$ ) of the circuit ?

b) What is the maximum amplitude of a sinusoid that can be applied to the input ?

# Exercise (4)

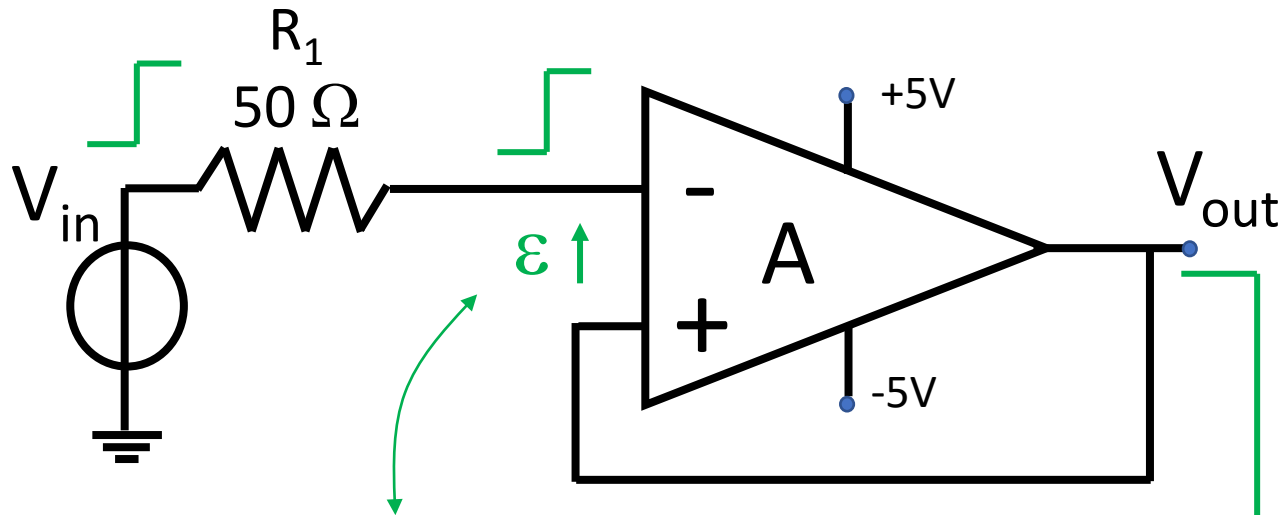

Difference would diverge toward bigger values.

If a signal of  $V_{in} = +10\text{mV}$  is applied to the input, what would be  $V_{out}$  ?

If  $A = \text{big}$ , then also the output tends to diverge negative, till **saturation to  $-5V$**

**ELECTRONIC SYSTEMS and TECHNOLOGIES**


**Master in Management Engineering**

*Prof. Marco Sampietro*

GROUND CONCEPTS ON ELECTRONICS

**Analog Operations with an OpAmp**

# Summing amplifier

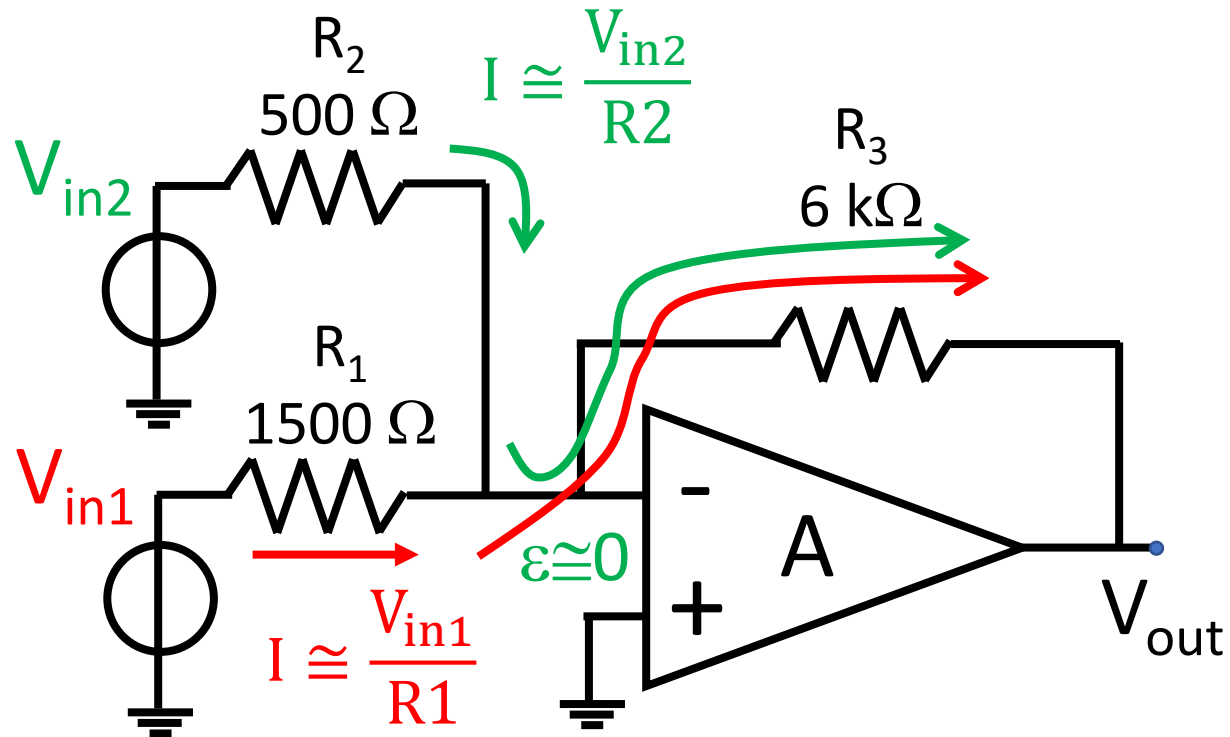


$$V_{out} = -\frac{V_{in1}}{R_1} \cdot R_3 - \frac{V_{in2}}{R_2} \cdot R_3$$


Ex. :  $V_{in1} = 80 \text{ mV}$  and  $V_{in2} = 248 \text{ mV}$   $\longrightarrow$   $V_{out} = ?$

Ex. :  $V_{in1} = -500 \text{ mV}$  and  $V_{in2} = 38 \text{ mV}$   $\longrightarrow$   $V_{out} = ?$

# Summing amplifier (positive sum)

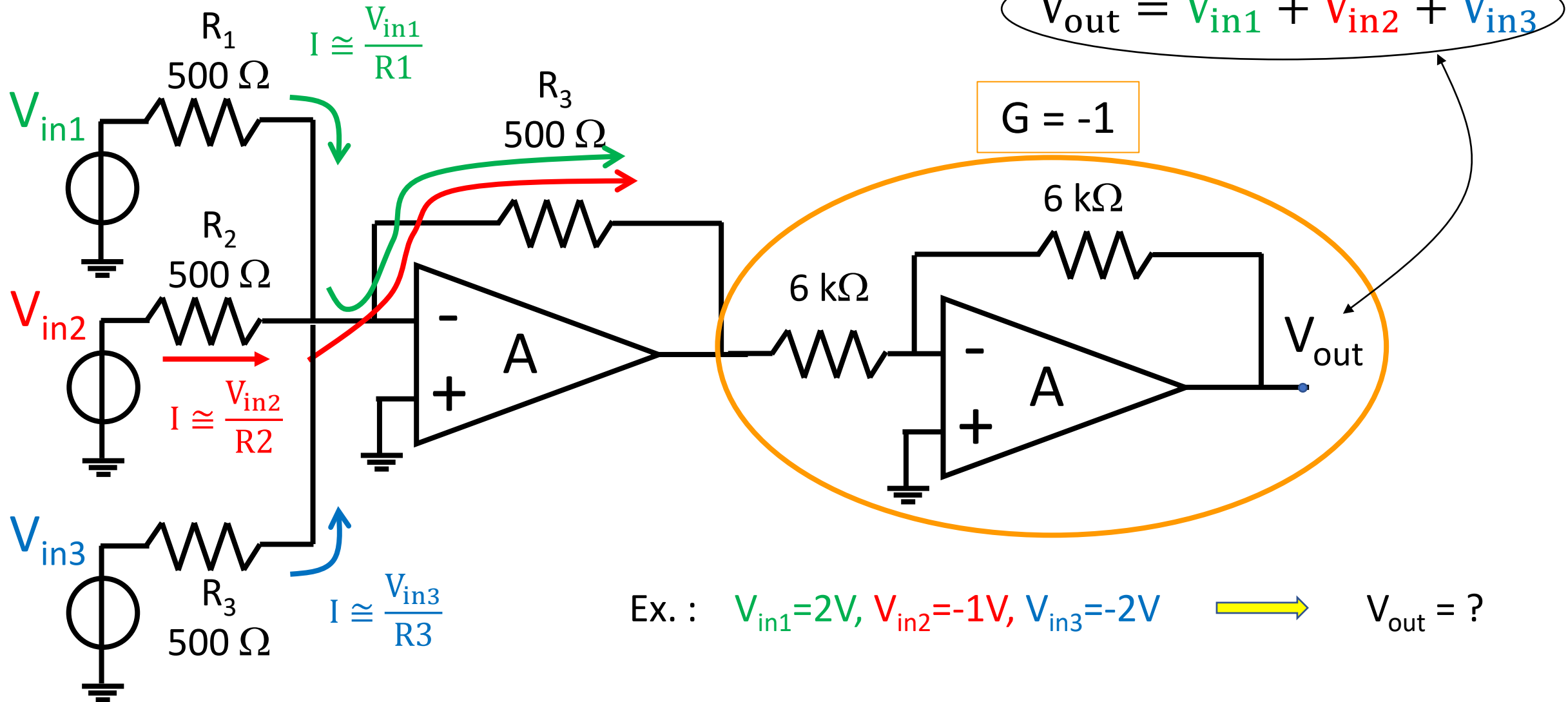


# Difference amplifier

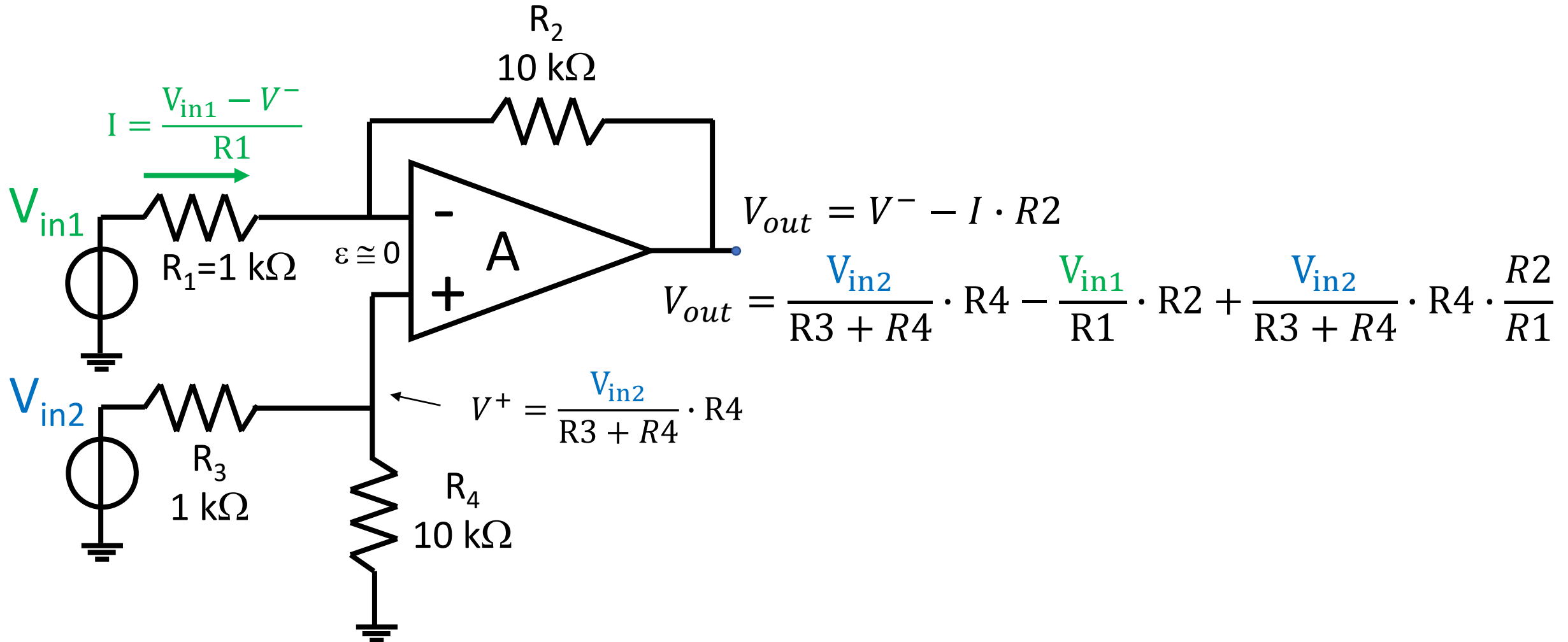



# Current to Voltage converter

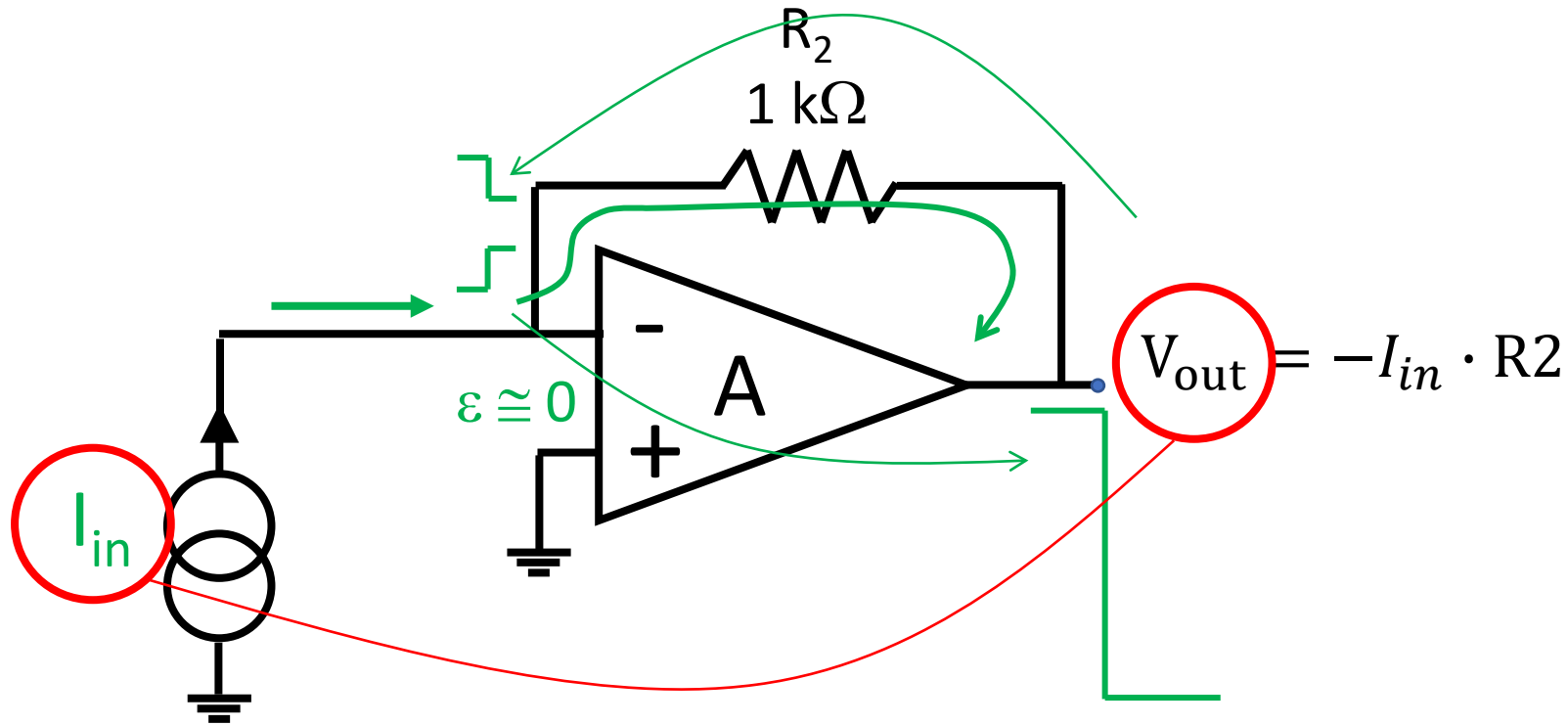


$$\frac{V_{out}}{I_{in}} = -R_2$$

It has the dimension  
of a resistance

TRANSRESISTANCE GAIN of  
the Transresistance Amplifier

Ex. :  $I_{in} = 1\text{ mA}$   $\longrightarrow$   $V_{out} = ?$

# Square root operator

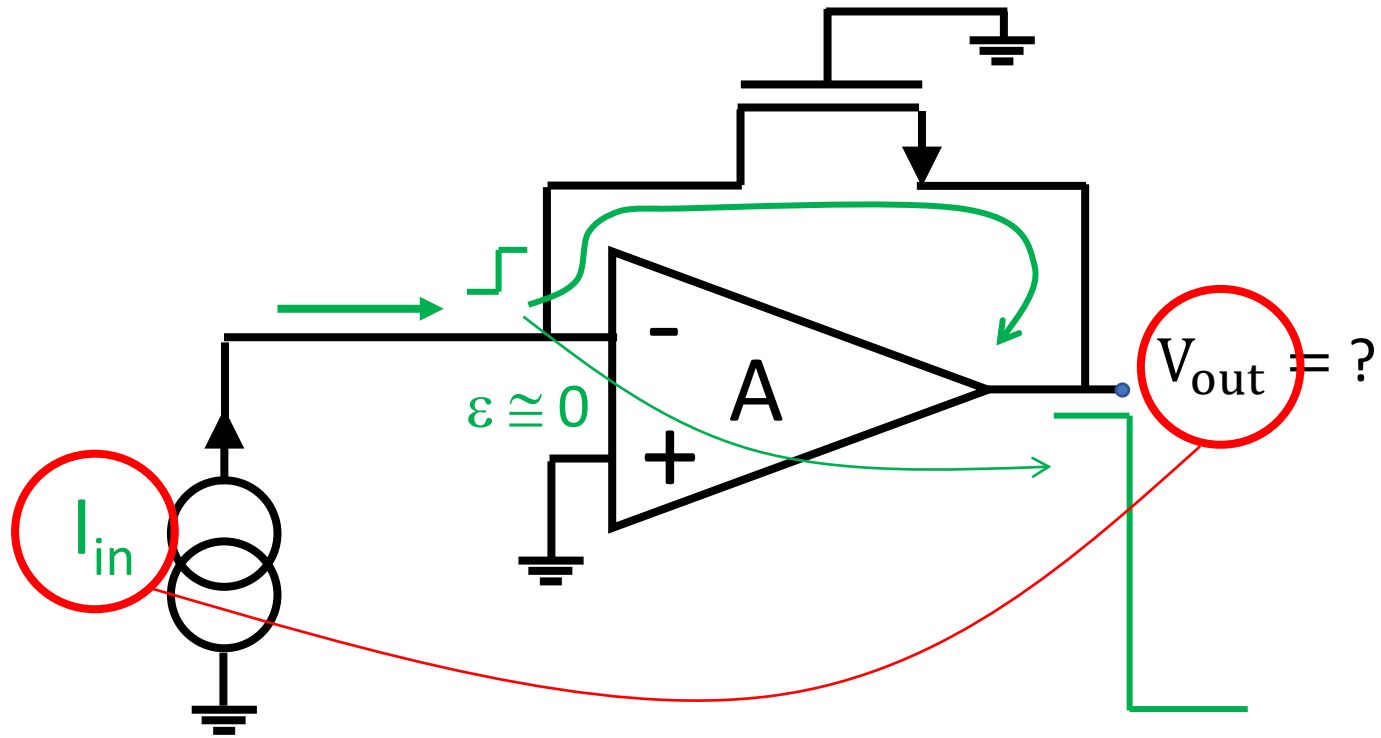

Ex. :  $I_{in} = 1\text{mA}$   $\longrightarrow$   $V_{out} = ?$

End of the lesson