
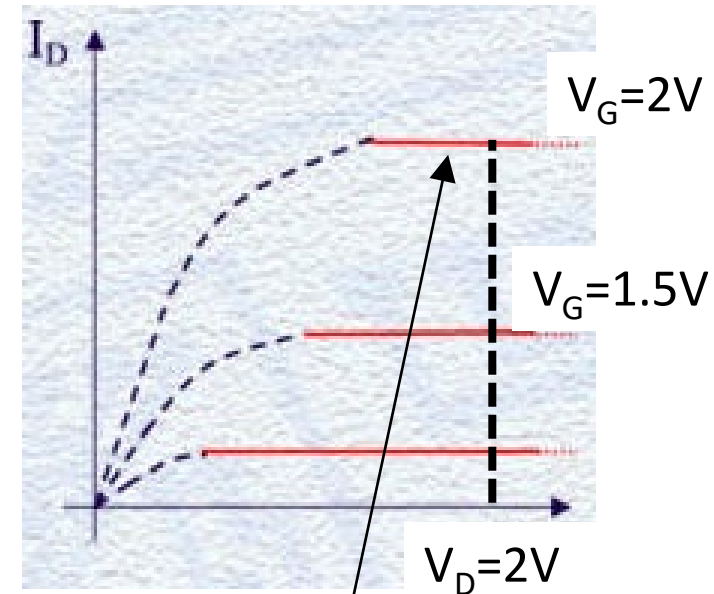


# Recap of previous lesson : Transistors

$$V_T = 0.8V$$

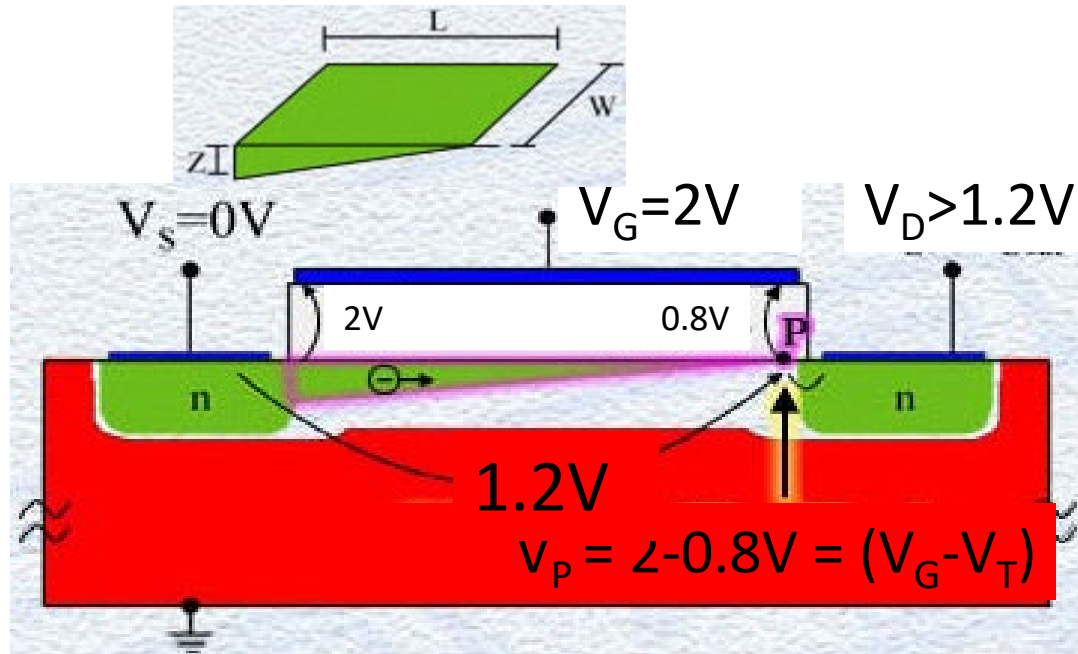


Costant current controlled by  $V_{Gate}$

$$I = k(V_G - V_T)^2$$

*A resistor below the oxide, whose voltage across is defined only by the Gate and whose current is delivered to a third contact*
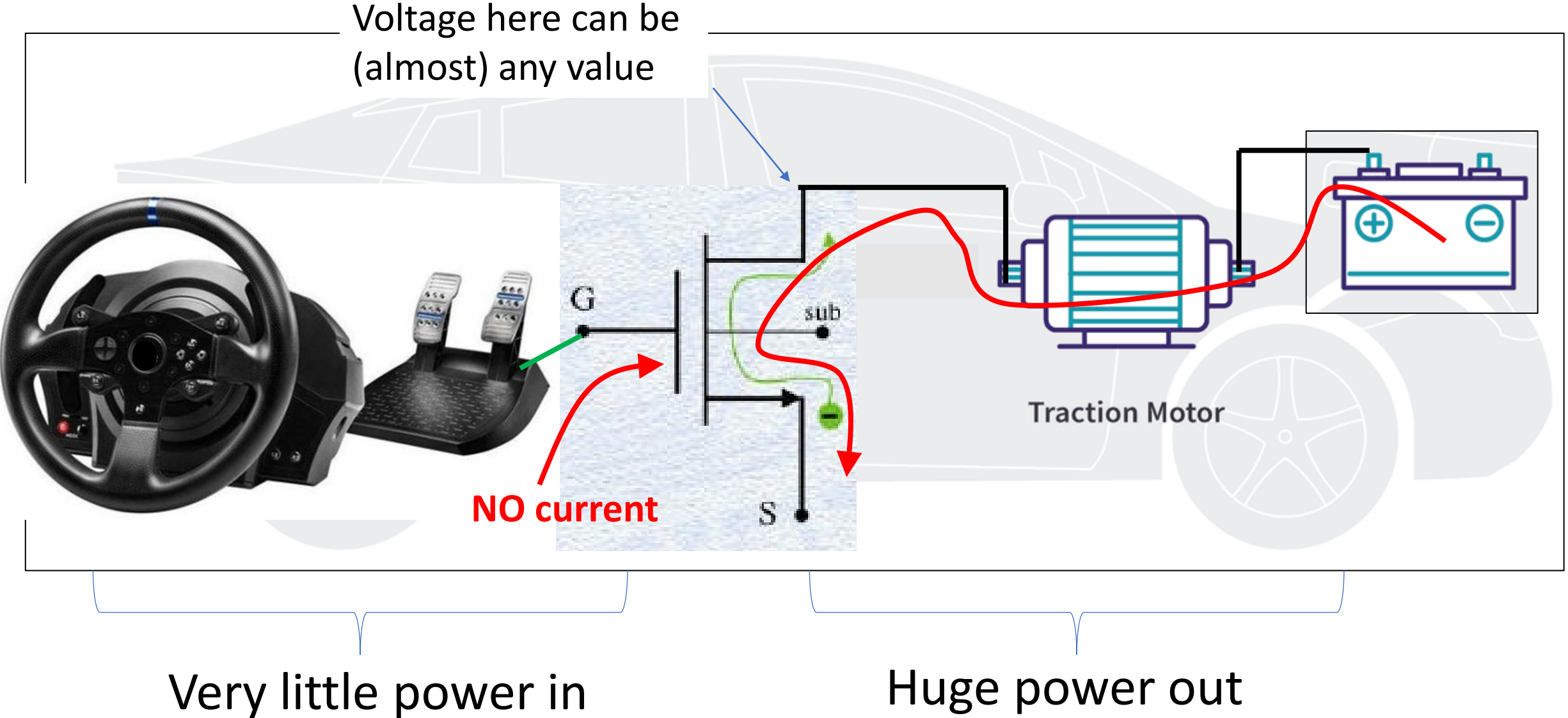
# Recap of previous lesson : Power amplification



**ELECTRONIC SYSTEMS and TECHNOLOGIES**


**Master in Management Engineering**

*Prof. Marco Sampietro*

GROUND CONCEPTS ON ELECTRONICS

**Signals, amplification & power**



# The use of a TRANSISTOR in a circuit

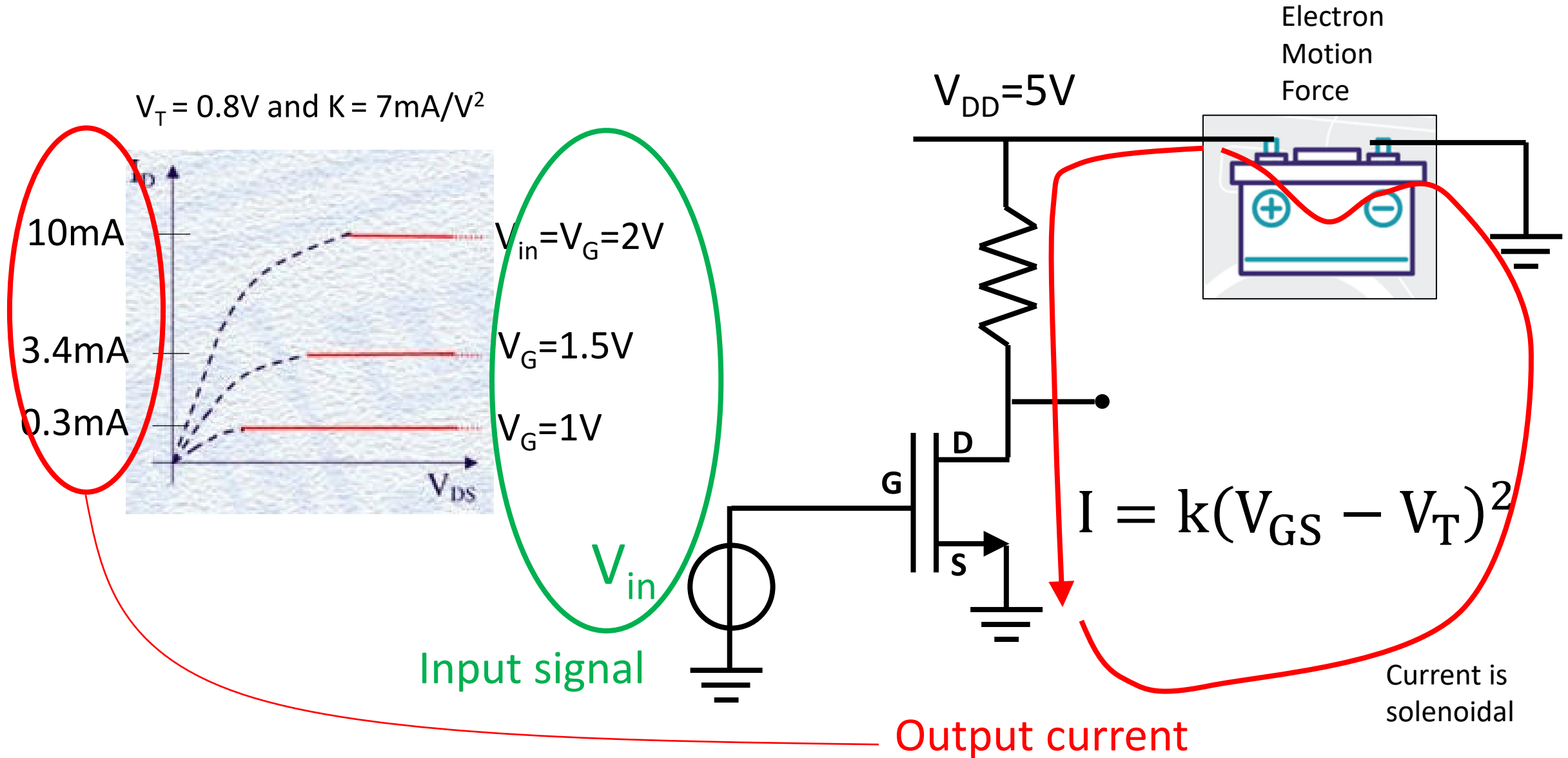

# Transfer of a Voltage from Gate to Drain


$V_T = 0.8V$  and  $K = 7mA/V^2$

$$I = k(V_{GS} - V_T)^2$$

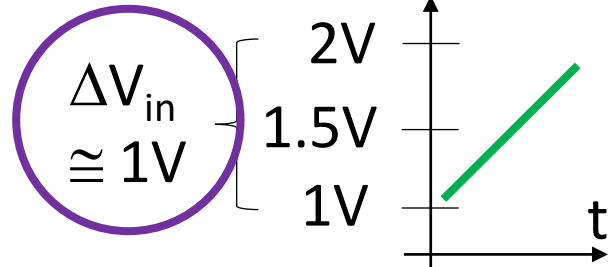
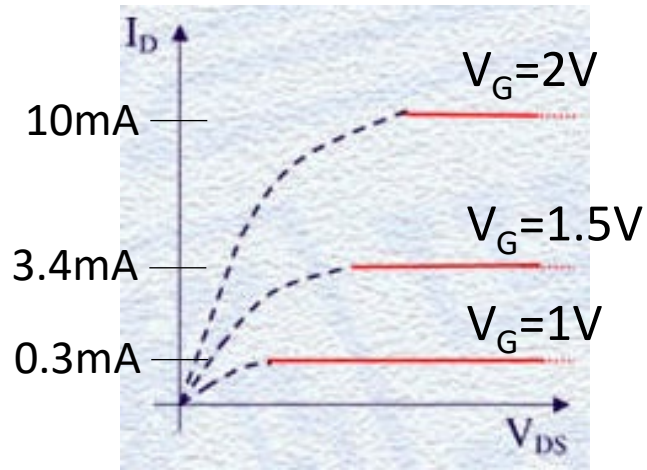


VOLTAGE GAIN
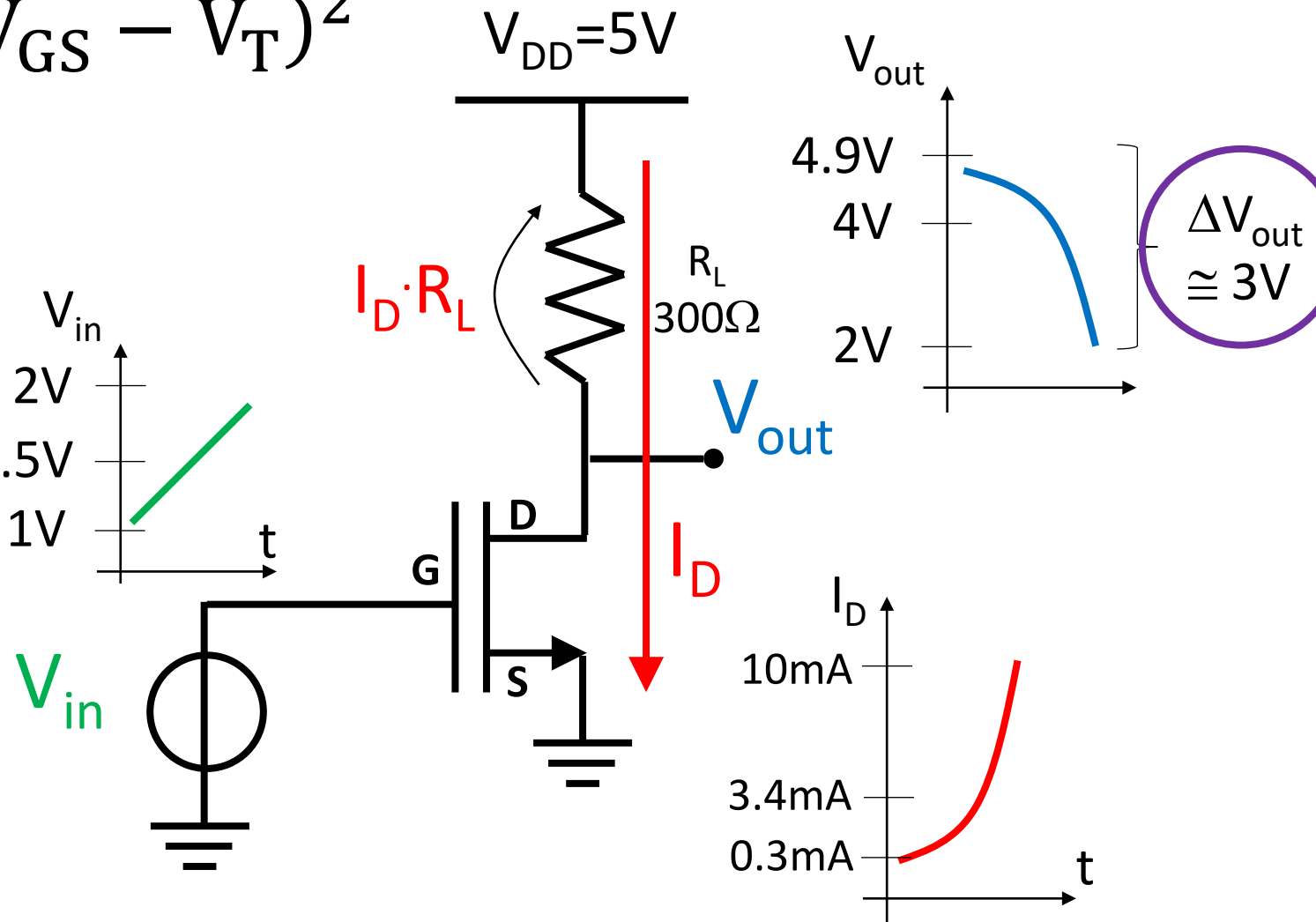
$$G = \frac{\Delta V_{out}}{\Delta V_{in}} \cong -3$$



# Polarisation and signal variations

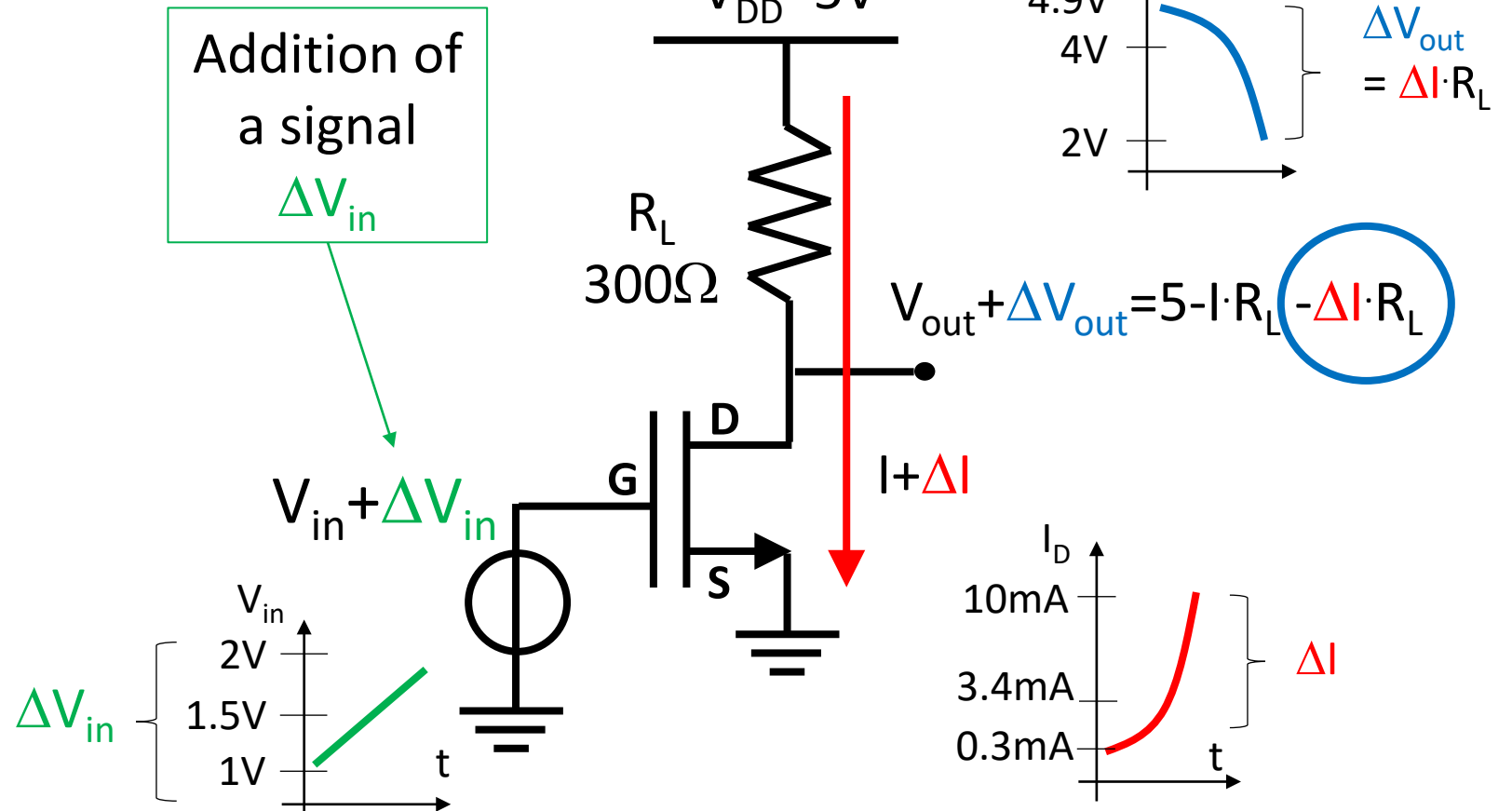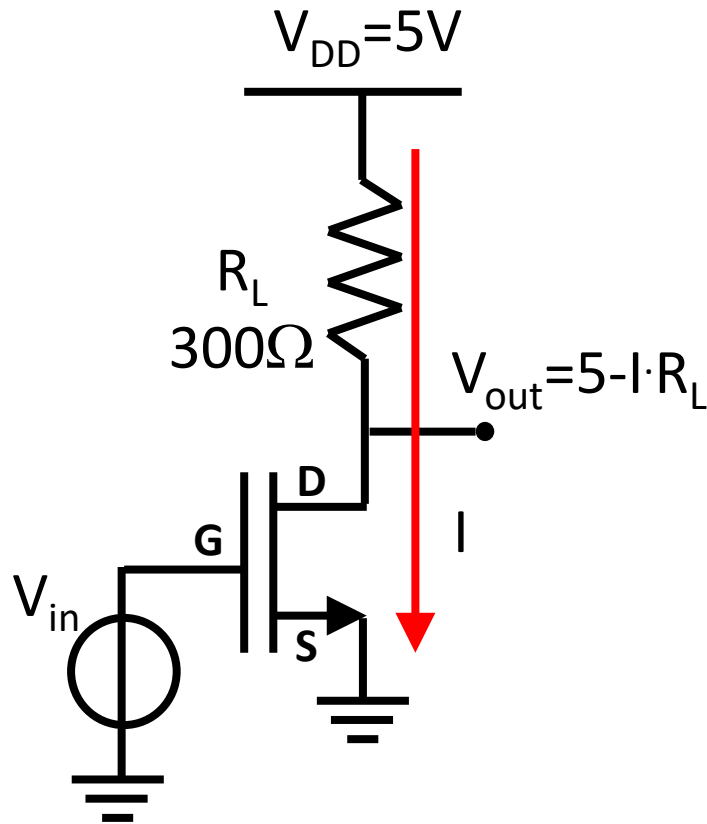

# Signal Gain and Power Gain


**Power gain**

$$\frac{\Delta P_{out}}{\Delta P_{in}} \cong \infty$$

$$\Delta P_{out} = \Delta V_{out} \cdot \Delta I_D$$

$$\cong 3V \cdot 9.7mA = 29mW$$




Power delivered to

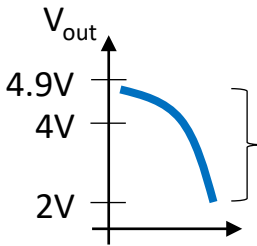

$$\Delta V_{out} = \Delta I_D \cdot R_L \cong 3V$$

$$\Delta P_{in} = \Delta V_{in} \cdot \Delta I_{in} \cong 0 W$$

$$\Delta V_{in} = 1V$$

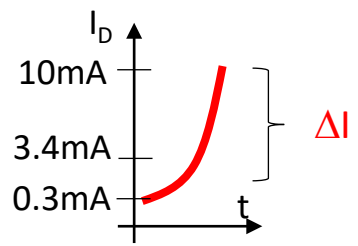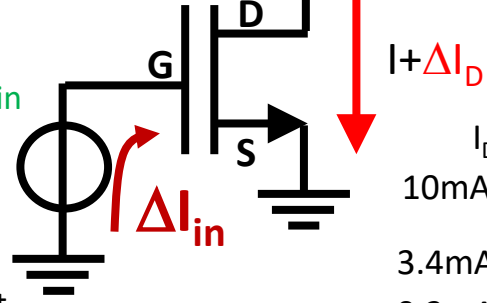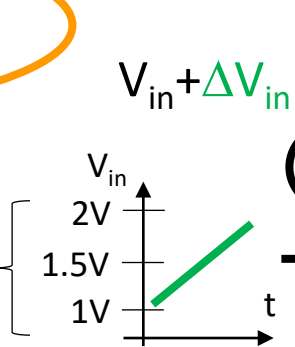

**Signal gain**

$$G = \frac{\Delta V_{out}}{\Delta V_{in}} \cong -3$$

# Power Delivered and Power Consumed


Power delivered to the load

$$\Delta P_{\text{out}} = \Delta V_{\text{out}} \cdot \Delta I_D$$

$$\cong 3V \cdot 9.7\text{mA} = 29\text{mW}$$

Power absorbed from the Power Supply
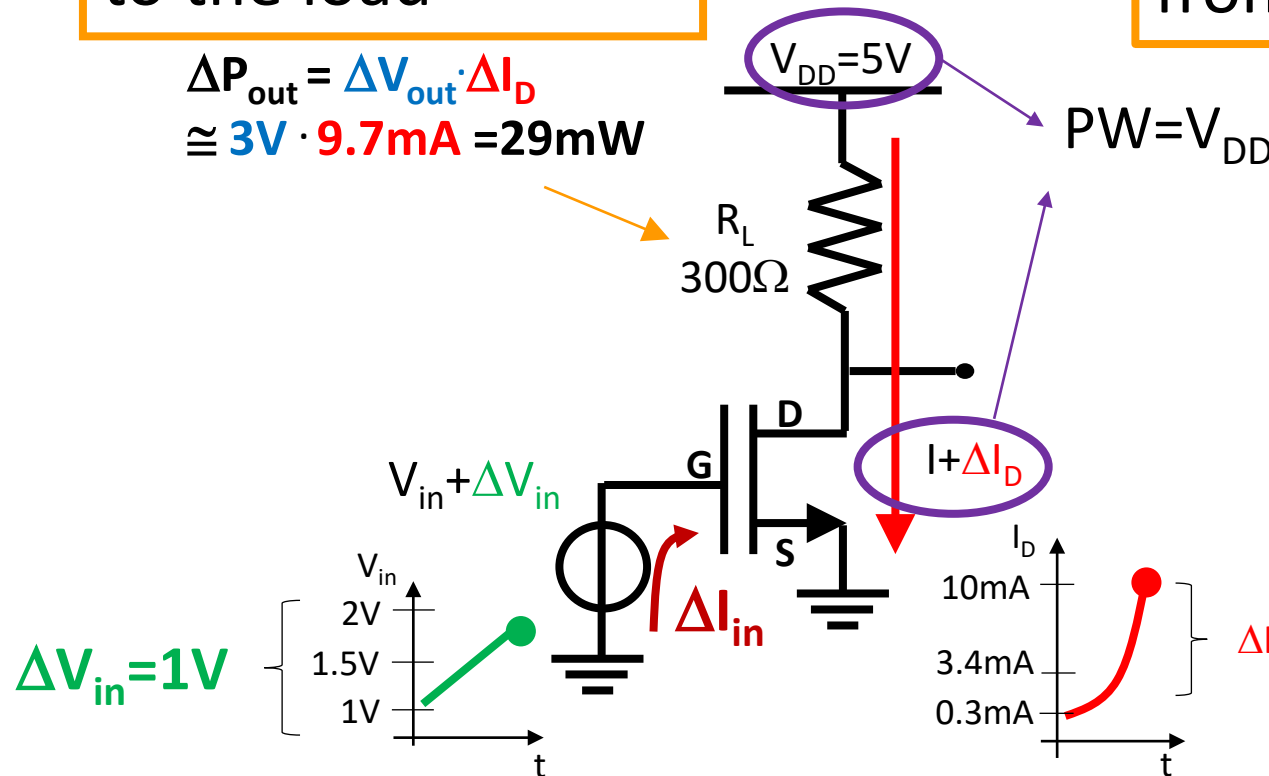
$$P_W = V_{DD} \cdot (I + \Delta I) \cong 5V \cdot 10\text{mA} = 50\text{mW}$$



- partly delivered to the Load (29mW)
- partly dissipated as Heat in the transistor (21mW)


The higher is  $V_{DD}$ , the higher is the consumption and the dissipation



# Charge consumption and battery capacity

The current is necessary for the telephone to function

3.8V

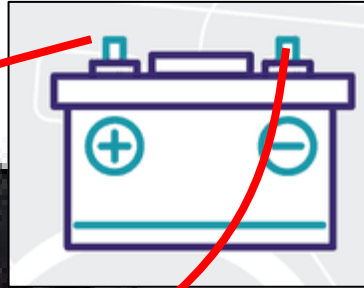

**1350mAh**

If you use a steady current of 1350 mA, the battery will last for 1 hour



## Exercise 1 :

*If the steady current consumption is 6mA, how long would the battery last ?*



## Exercise 2

You are the chief designer of the next generation of satellites for earth survey. Your team of mechanical engineers have designed a solar cell panel that is always (24h/day) directed toward the sun. They also defined the maximum area of the solar cell panel, of  $20\text{m}^2$ .



*Find how much electric power you will have available for all your electronic instrumentation and the transmission of data to the base station.*



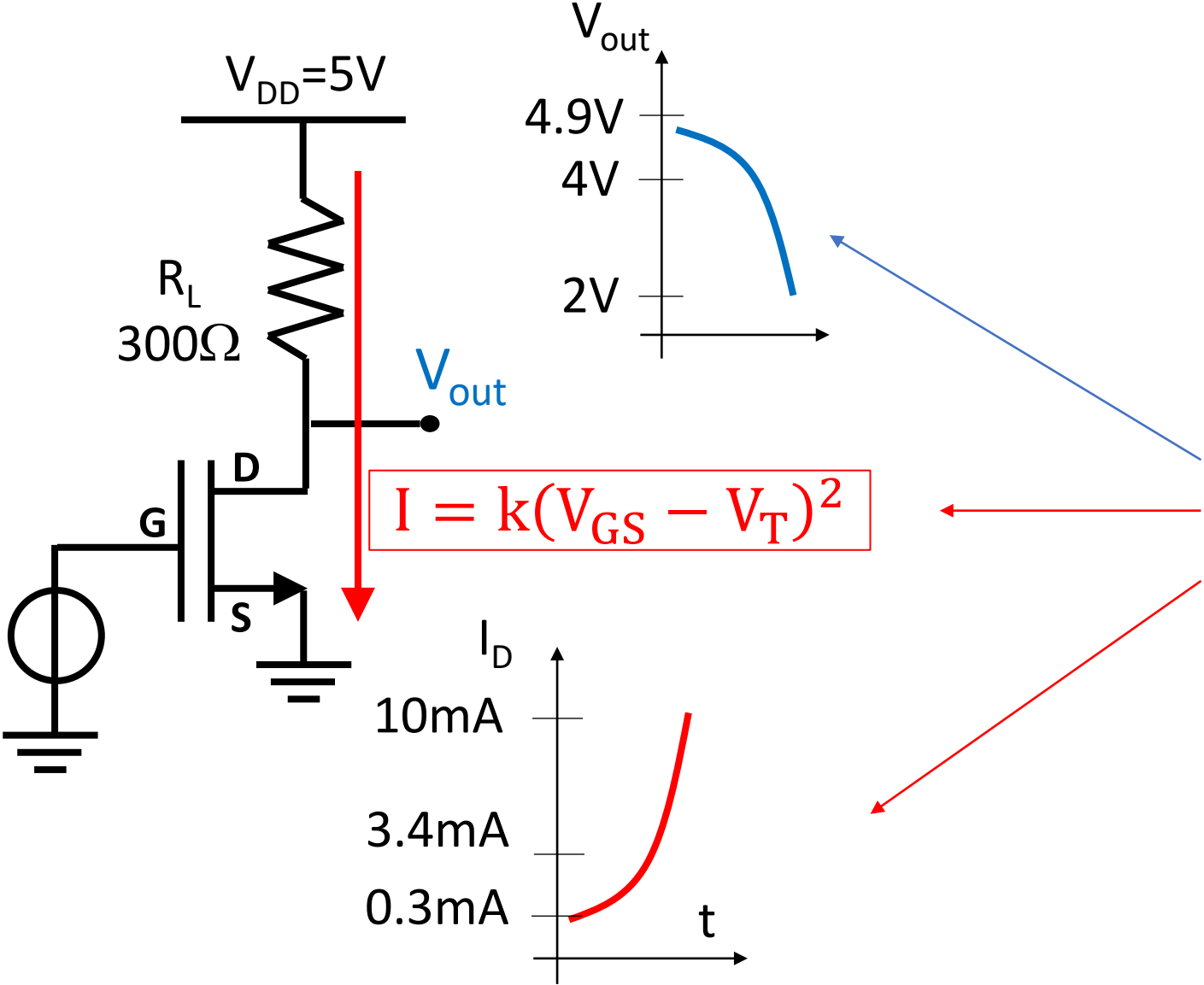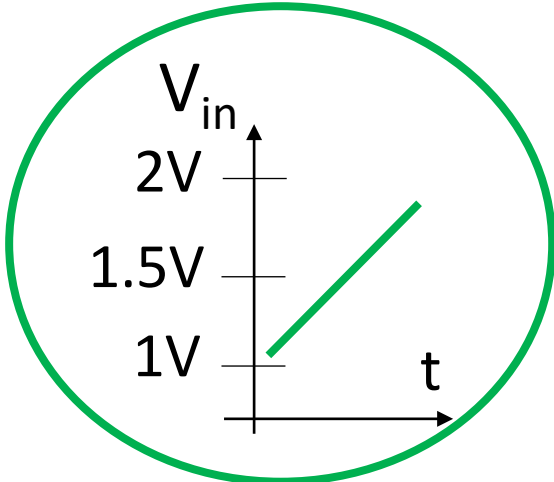
# NON-Linearity of the signal amplification




$$I = k(V_{GS} - V_T)^2$$

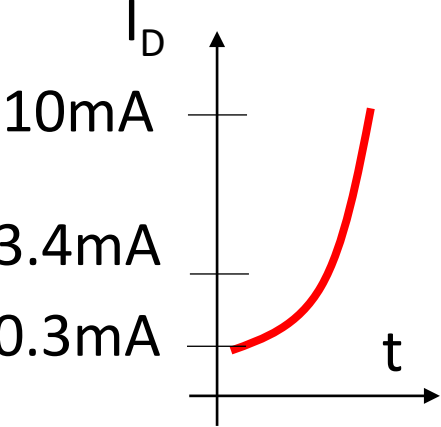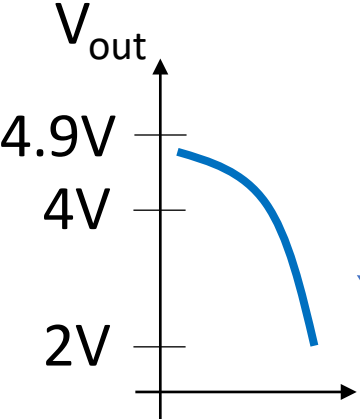
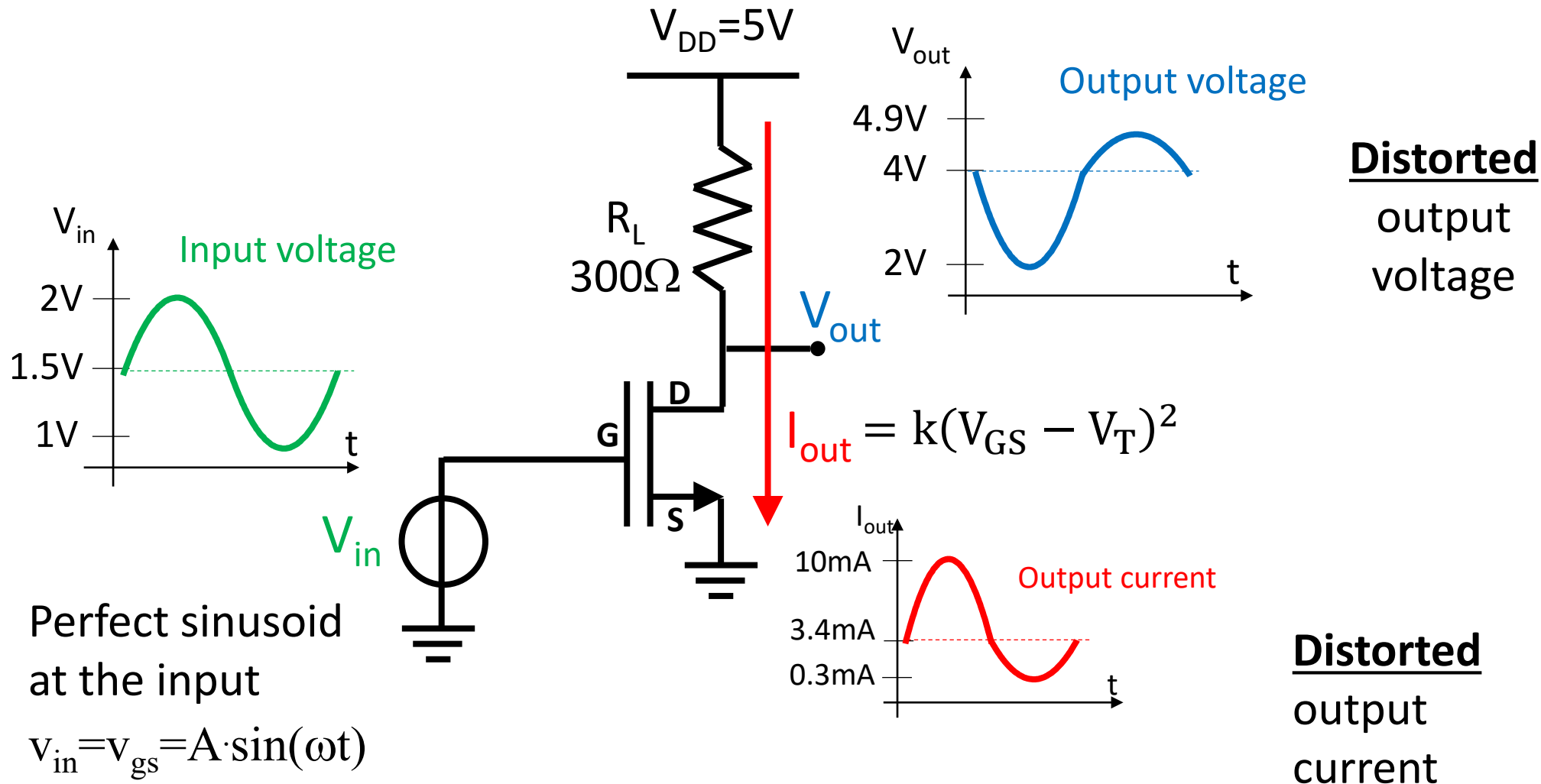
# Transfer of a SINUSOIDAL signal from Gate to Drain


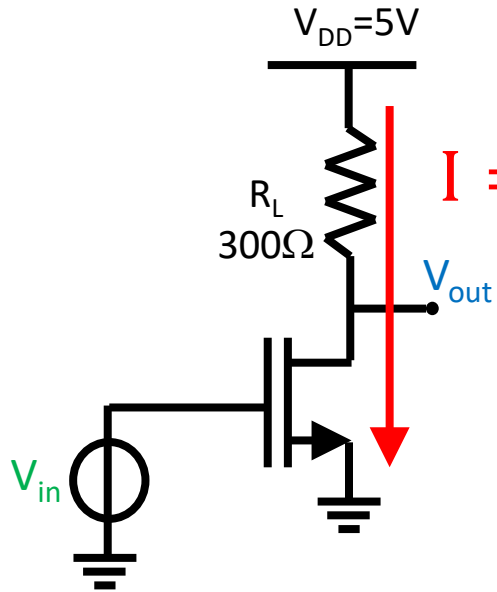
# Signal distortion and generation of harmonics



$$I = k(V_{GS} - V_T)^2$$

$$v_{in} = v_{gs} = A \cdot \sin(\omega t)$$



$$I = k(A \cdot \sin(\omega t) - V_T)^2$$

$$I = k[A^2 \sin^2(\omega t) + V_T^2 - 2AV_T \sin(\omega t)]$$


$$\sin^2 \omega t = \frac{1 - \cos 2\omega t}{2}$$

$$I = kV_T^2 + \frac{kA^2}{2} - 2kAV_T \sin(\omega t) - \frac{kA^2}{2} \cos(2\omega t)$$
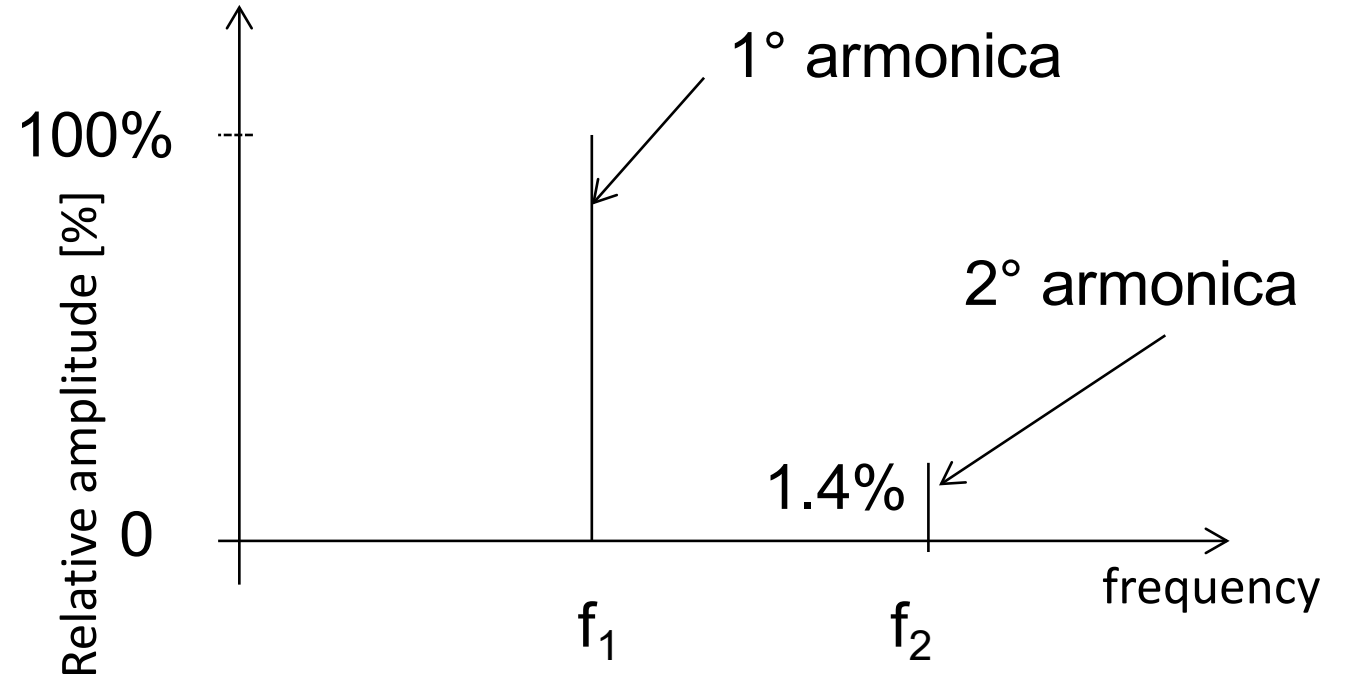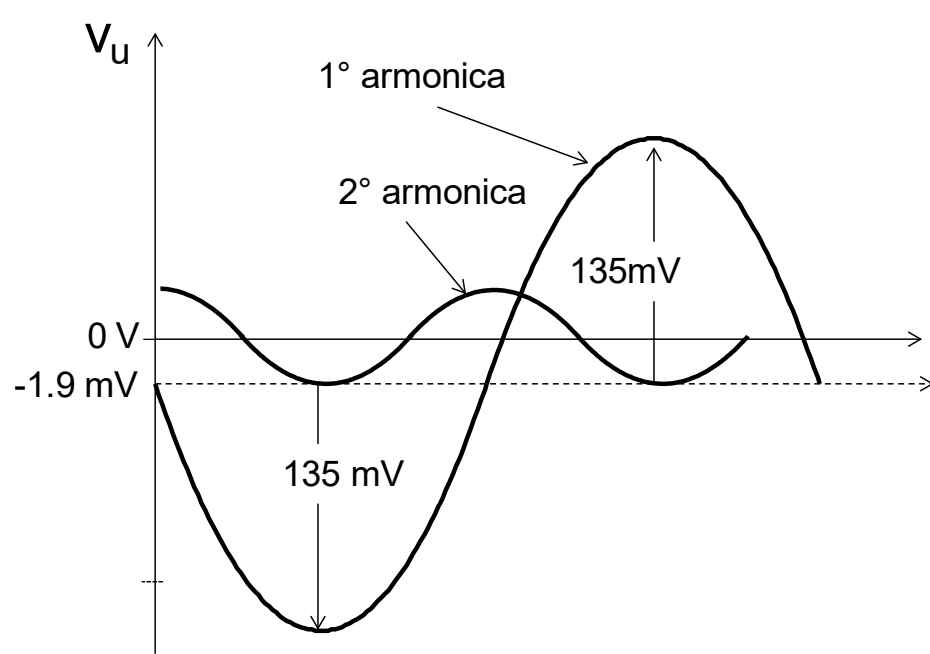
# Frequency spectrum : visualisation of harmonics


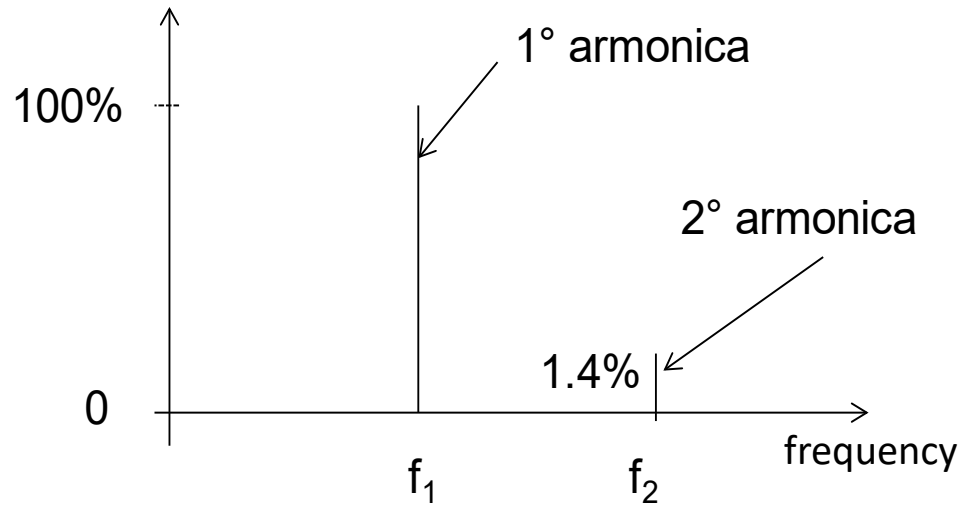
# Practical consequences of harmonics generation



↑  
Your  
communication  
channel

↑  
...produces signals also  
in adjacent channel



**POLITECNICO DI MILANO**

Piazza Leonardo da Vinci, 32 - 20133 Milano  
Tel. +39 02 2399.1 - <http://www.polimi.it>



## New generation chips, the factory of the future in Novara

Ing. Luca Moiraghi



**Friday, 4 March at 8.30, Building B12, Classroom L11,**  
**BOVISA CAMPUS**


The global microchip crisis continues to bite. Europe has begun to organize itself with the Chips Act which will move over 40 billion euros between public and private funds. Italy is answering with an investment of 300 million for a plant capable of producing 300 mm diameter silicon wafers, a key component in today microelectronic supply chain for making those chips used, for example, in consumer electronics, automotive and increasingly also in health diagnostics.

The talk will introduce MEMC Electronic Materials Spa, a GlobalWafers company, an Italian excellence in the core materials for the electronic industry. The talk will start with a company description and then it will overview the fabrication process flow from crystal pulling to finished wafer shipment. The manufacturing strategies to deliver a steady supply of exceptionally pure silicon that meet customer requirements all over the world will end the seminar.

*The seminar is open to public.*

*It is also part of the "ELECTRONIC SYSTEMS and TECHNOLOGIES" course in the Master of Management Engineering.*

# Friday talk

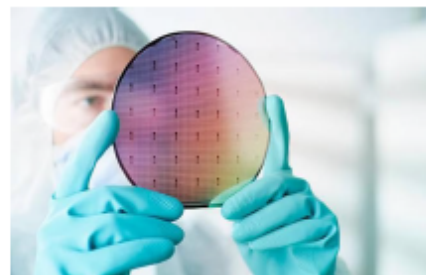



End of the lesson