

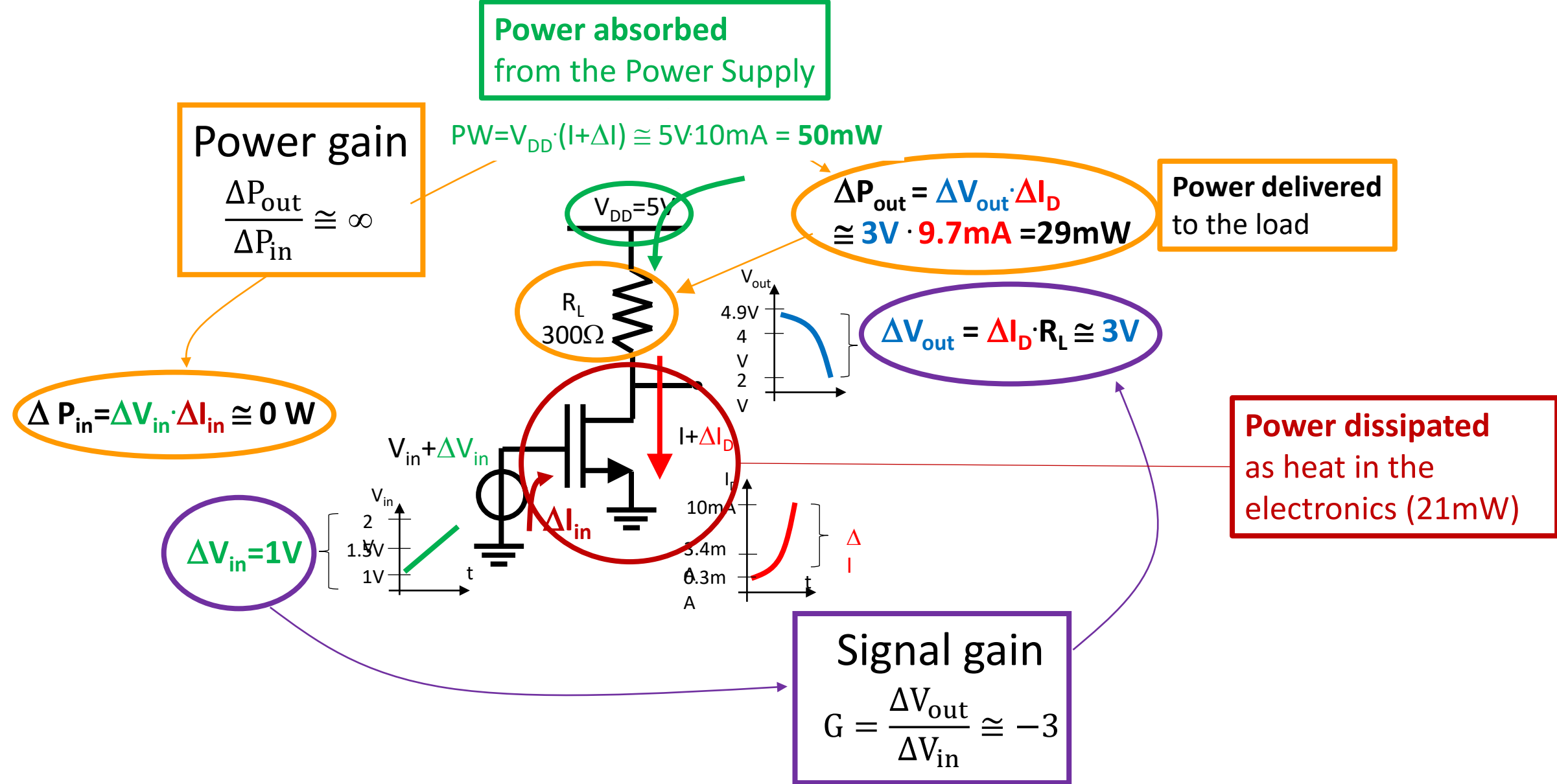


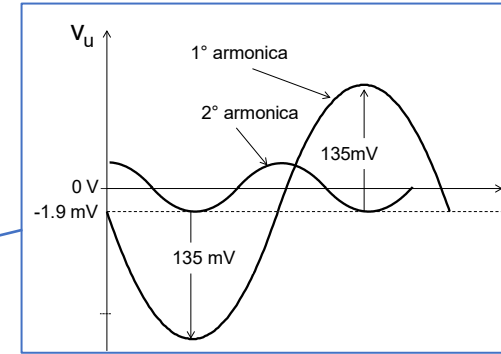
Recap : Signal Gain, Power Gain and Power consumption



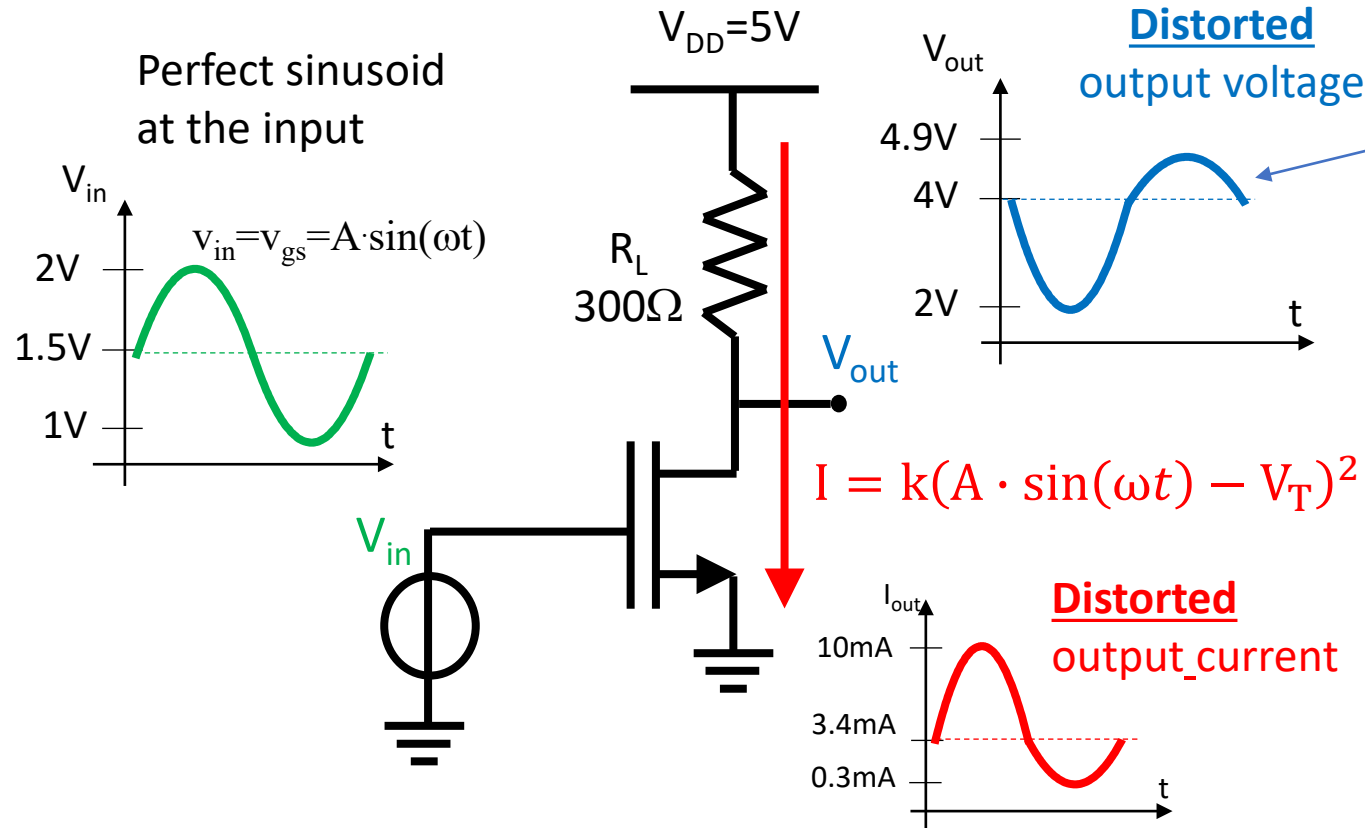Recap : signal Distortion and Harmonics generation



$$I = k(A \cdot \sin(\omega t) - V_T)^2 = kV_T^2 + \frac{kA^2}{2} - 2kAV_T \sin(\omega t) - \frac{kA^2}{2} \cos(2\omega t)$$

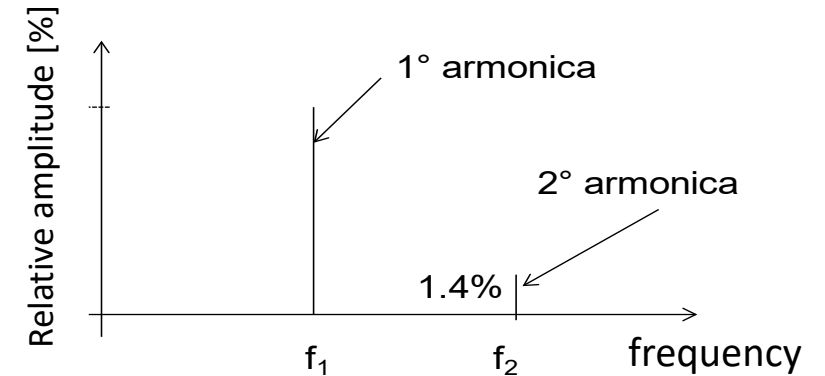

Exercise 2

You are the chief designer of the next generation of satellites for earth survey. Your team of mechanical engineers have designed a solar cell panel that is always (24h/day) directed toward the sun. They also defined the maximum area of the solar cell panel, of 20m^2 .

Find how much electric power you will have available for all your electronic instrumentation and the transmission of data to the base station.



ELECTRONIC SYSTEMS and TECHNOLOGIES

Master in Management Engineering

Prof. Marco Sampietro



GROUND CONCEPTS ON ELECTRONICS

CMOS and the Digital world

nMOSFET and pMOSFET circuits

Electrons travels from S to D

Holes travels from S to D

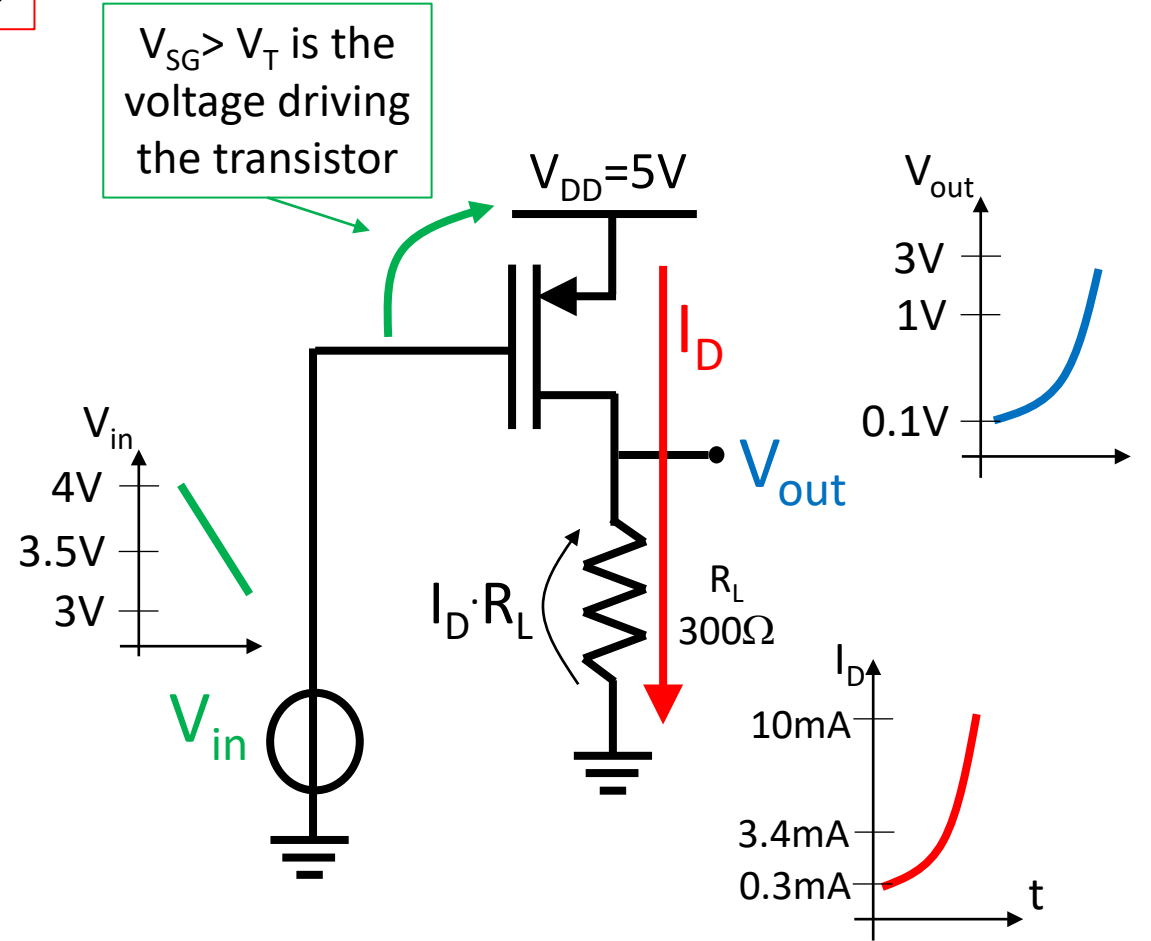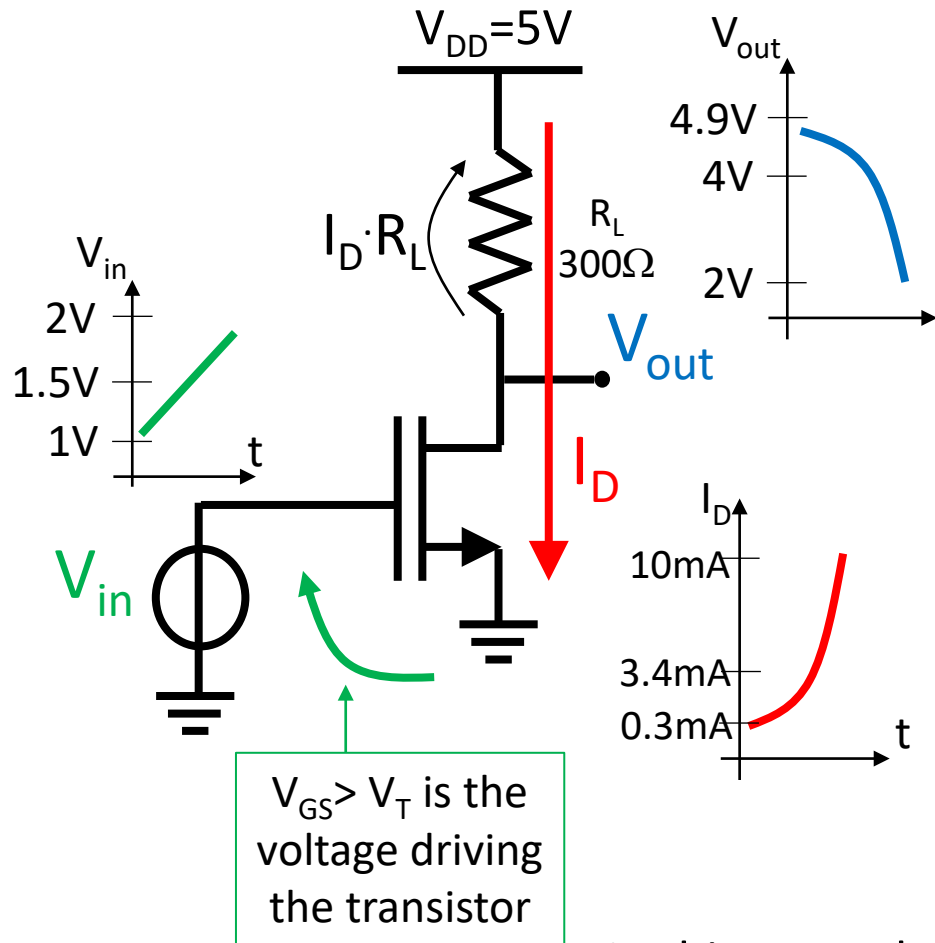

In this example $V_T = 0.8V$ and $K = 7mA/V^2$ for both type of transistors


ANALOG vs DIGITAL signals

Signals assume any value in a continuous time

Digital Input Signal


Logic «0» -> 0V

Logic «1» -> 5V

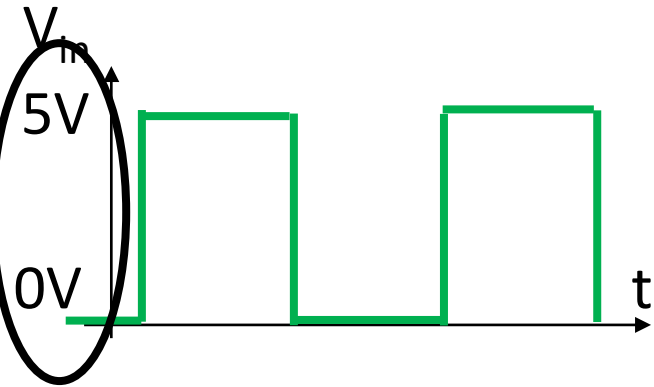

Rail-to-rail

(from the voltage supply to ground)

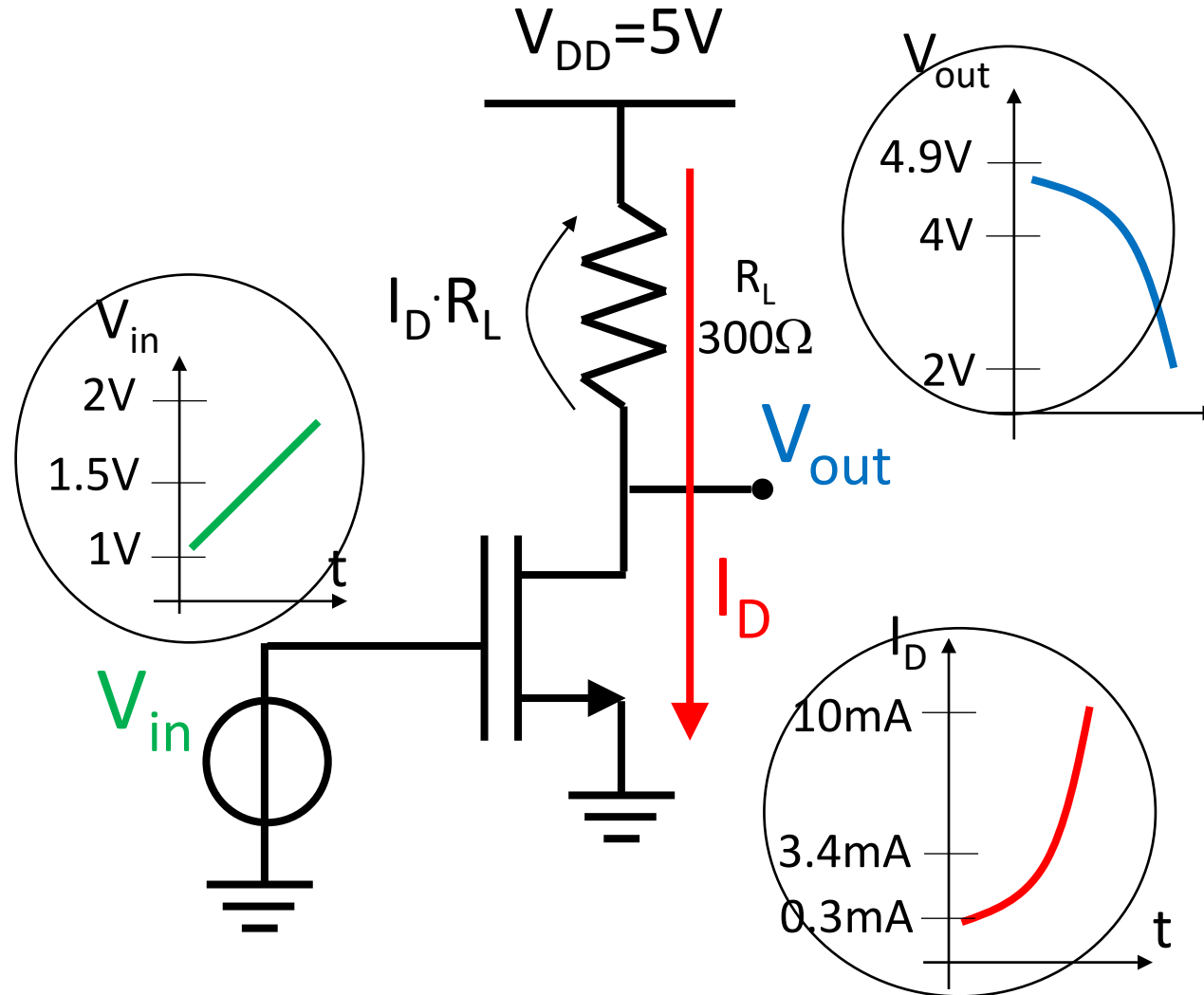



$V_T = 0.8V$ and $K = 7mA/V^2$

?


?

Response to a digital input signal low (0V)

$V_T=0.8V$ and $K=7mA/V^2$

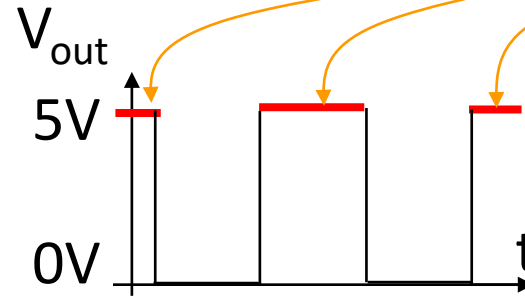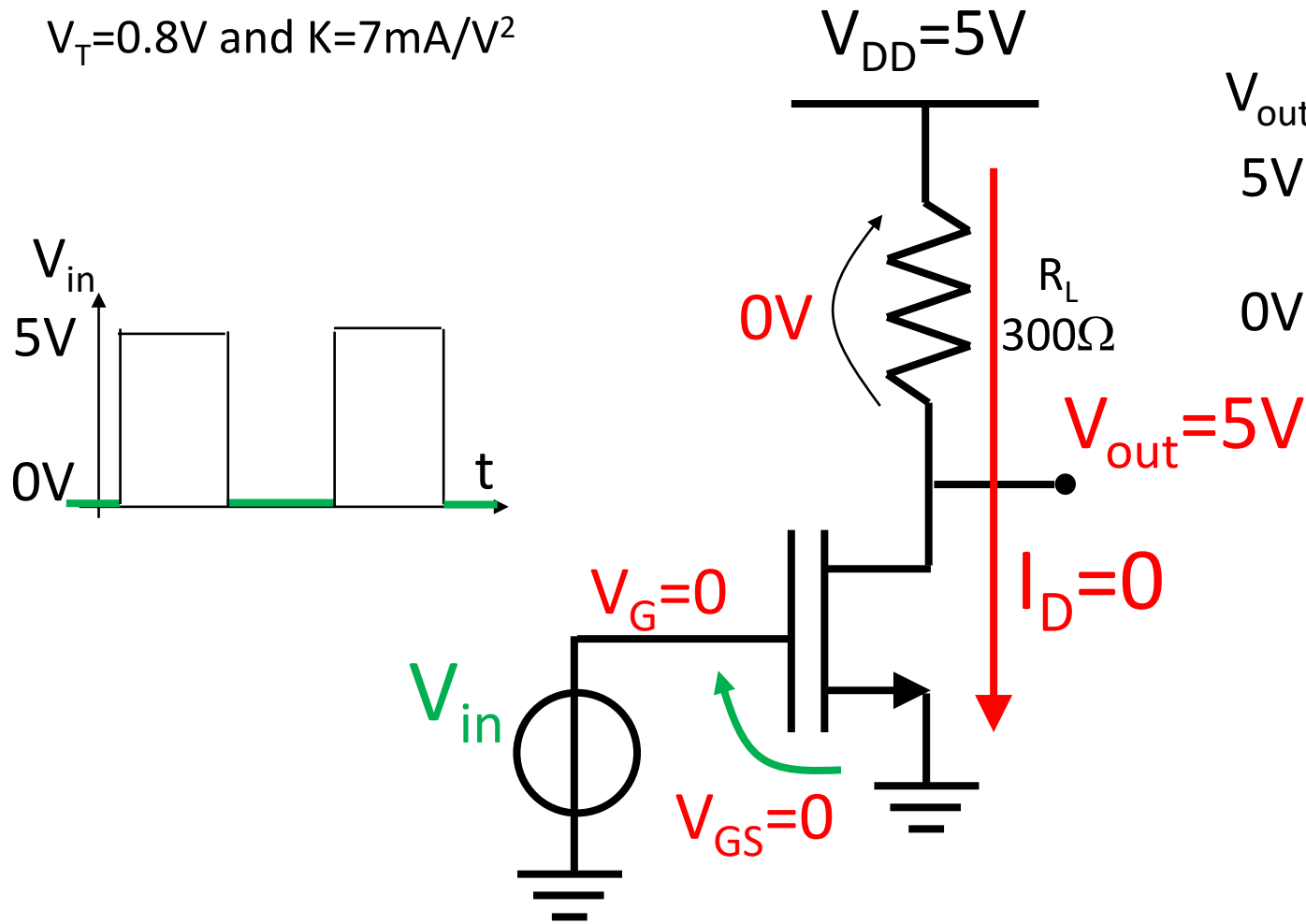

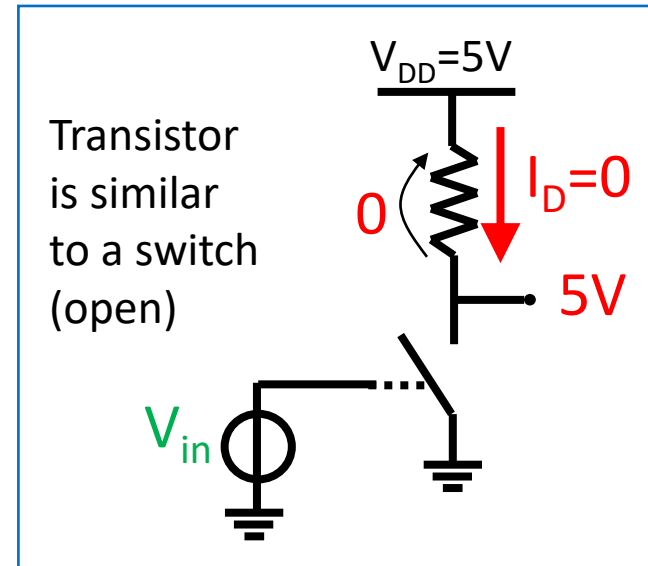
NO power consumption
 $P = V_{DD} \cdot I_D = 0$




MOSFET operates below threshold : $V_{GS} < V_T \rightarrow I_D = 0 \rightarrow V_u = +5V$

Response to a digital input signal high (5V)


$V_T = 0.8V$ and $K = 7mA/V^2$

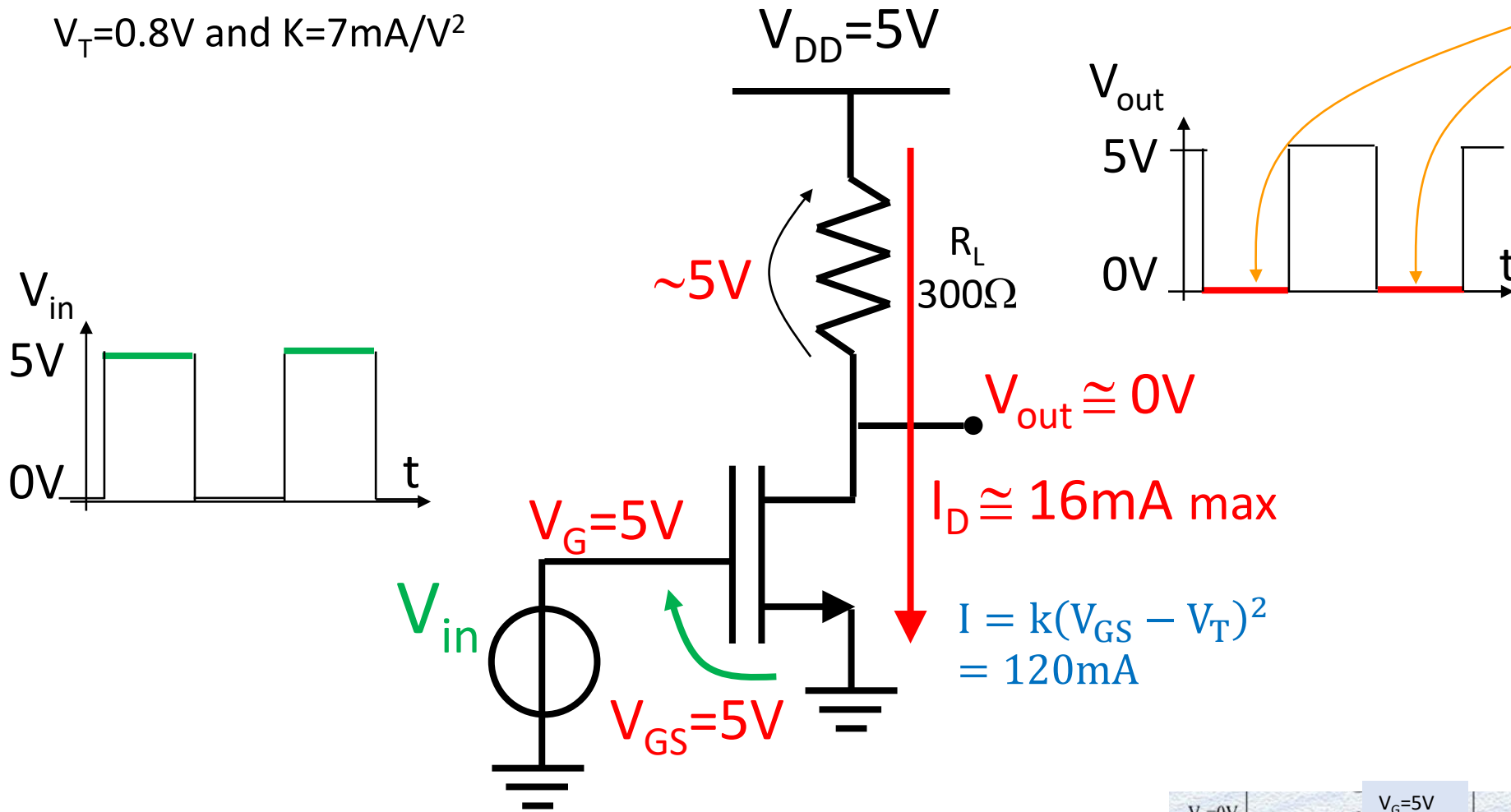

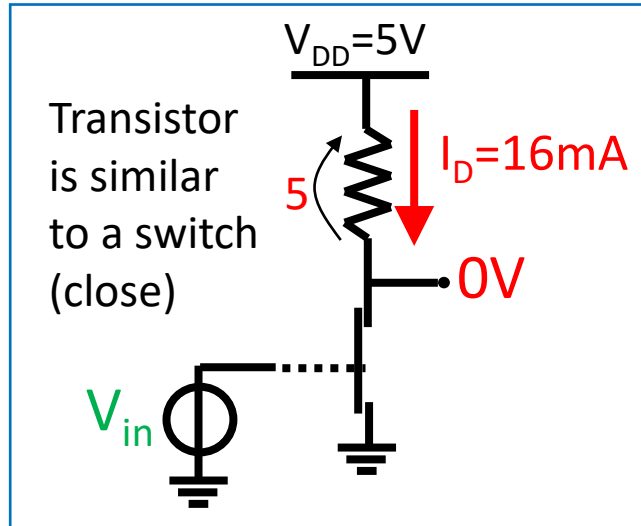HIGH power consumption
 $P = V_{DD} \cdot I_D = 80mW$



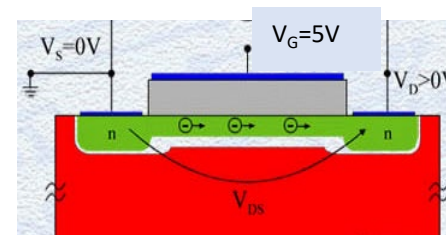MOSFET operates as a resistor (of low value):




The Digital Inverter

$V_T = 0.8V$ and $K = 7mA/V^2$




$$V_{in} = 0V(0) \rightarrow V_U = 5V(1)$$

$$V_{in} = 5V(1) \rightarrow V_U = 0V(0)$$

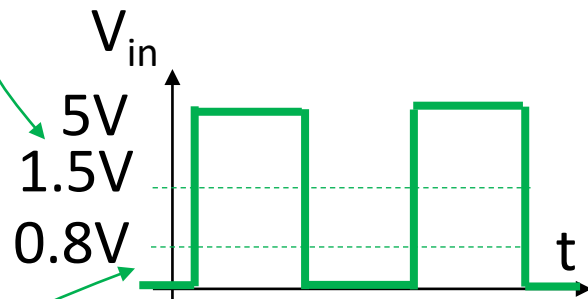Input values above 1.5V
($I > 16mA$) surely give $V_{out} = 0V$



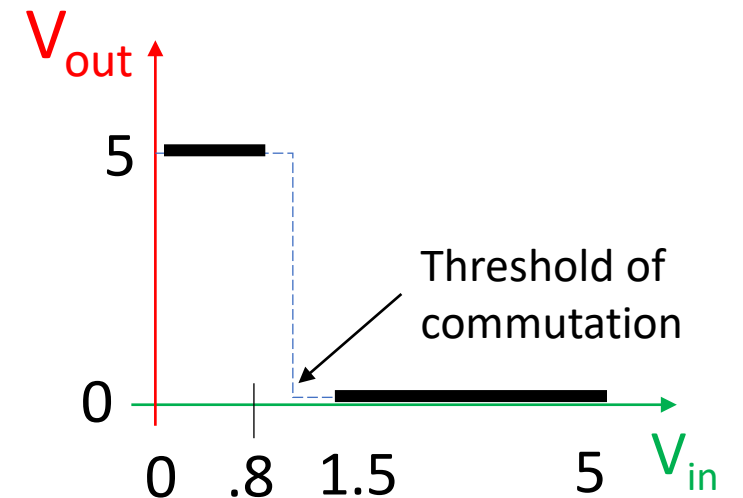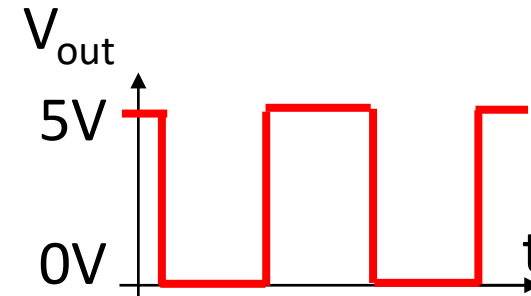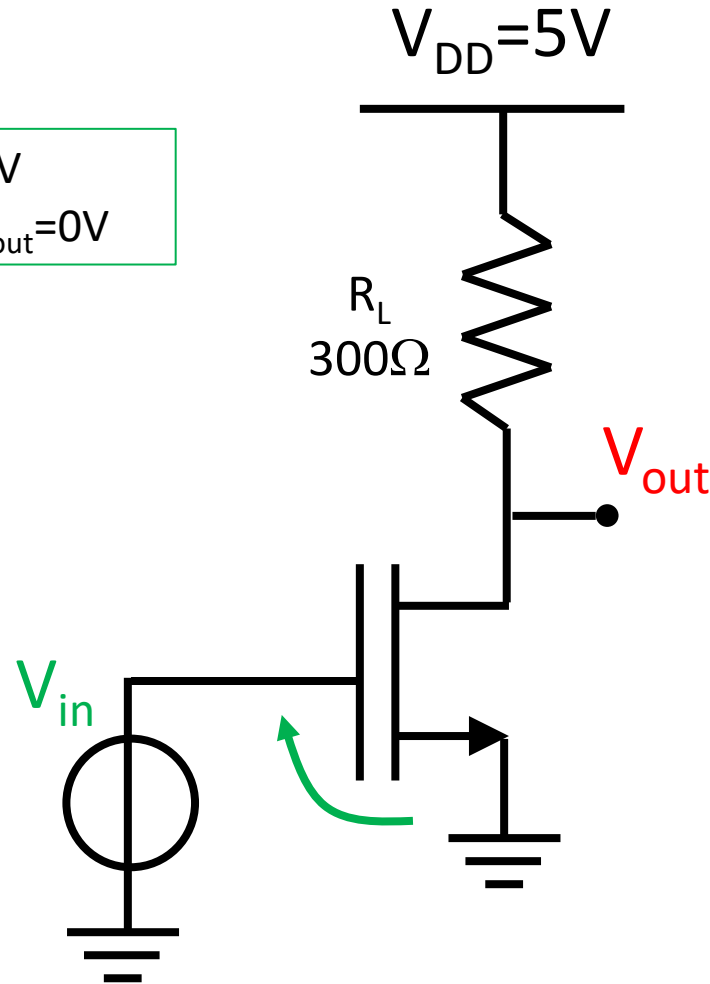
Input values below 0.8V
surely give $V_{out} = 5V$



Immunity to disturbances of a digital circuit

The threshold characteristic of the inverter allows, in many cases, a correct interpretation of the sequence even in the presence of a significant noise level.



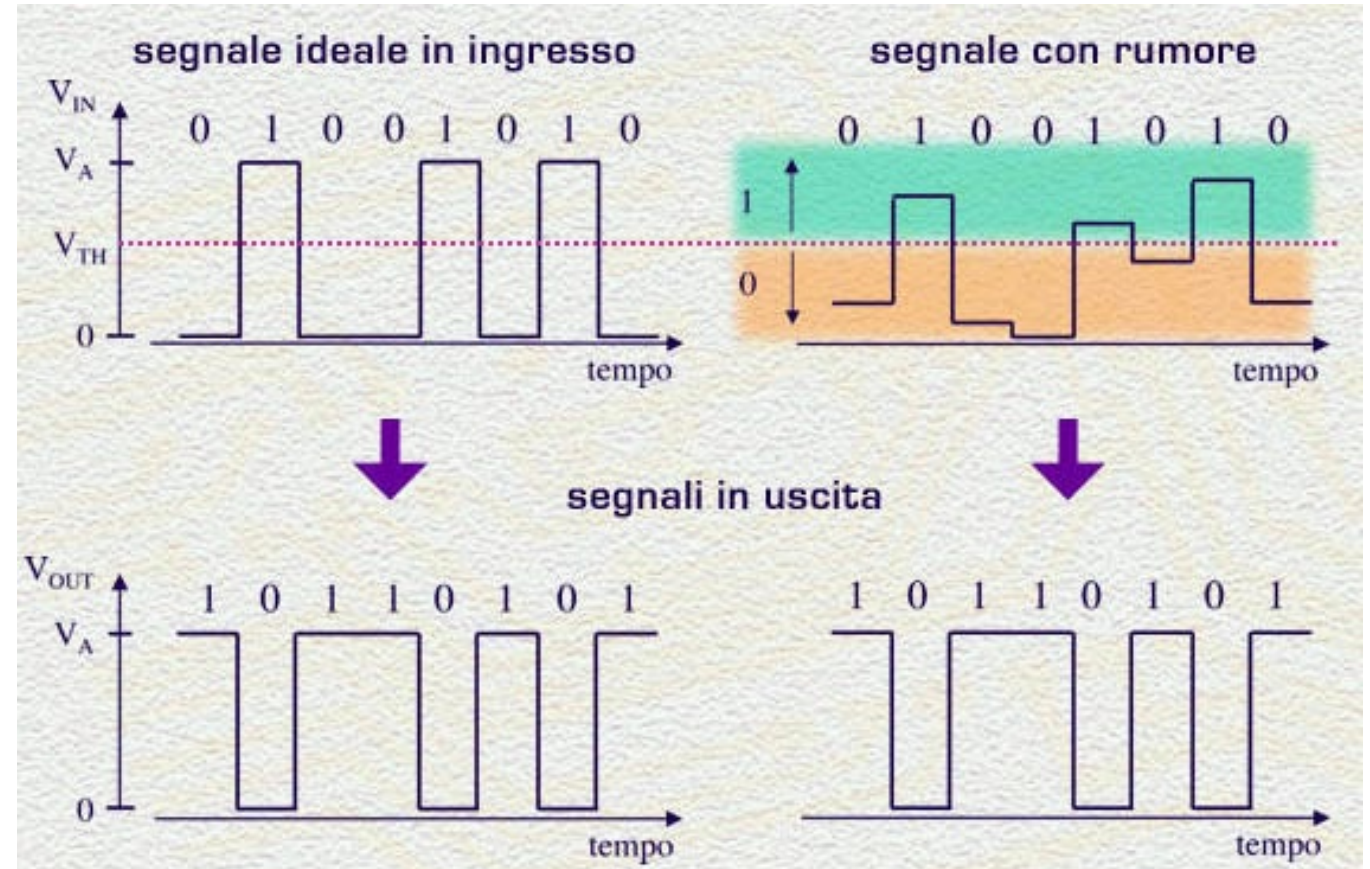
Note also that the inverter has reset the logic levels to 0 volts and 5 volts !



This feature is fundamental of digital systems and it provides «high degree of immunity to disturbances».



Digital input signal low (0V) - adding a pMOSFET

$V_T=0.8V$ and $K=7mA/V^2$

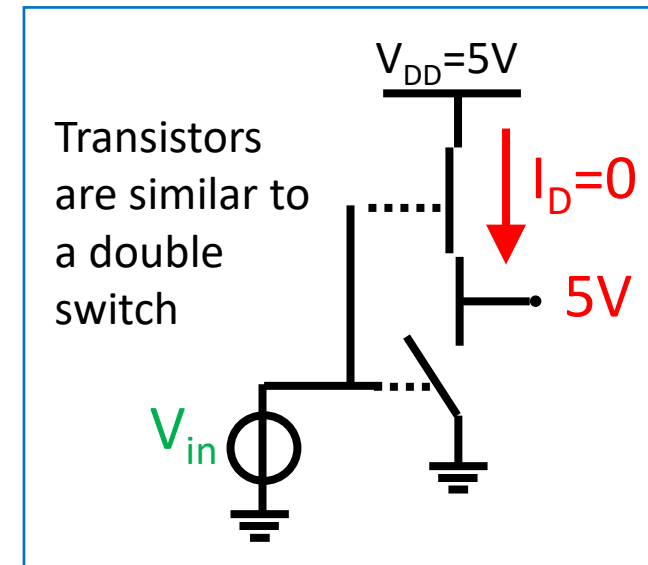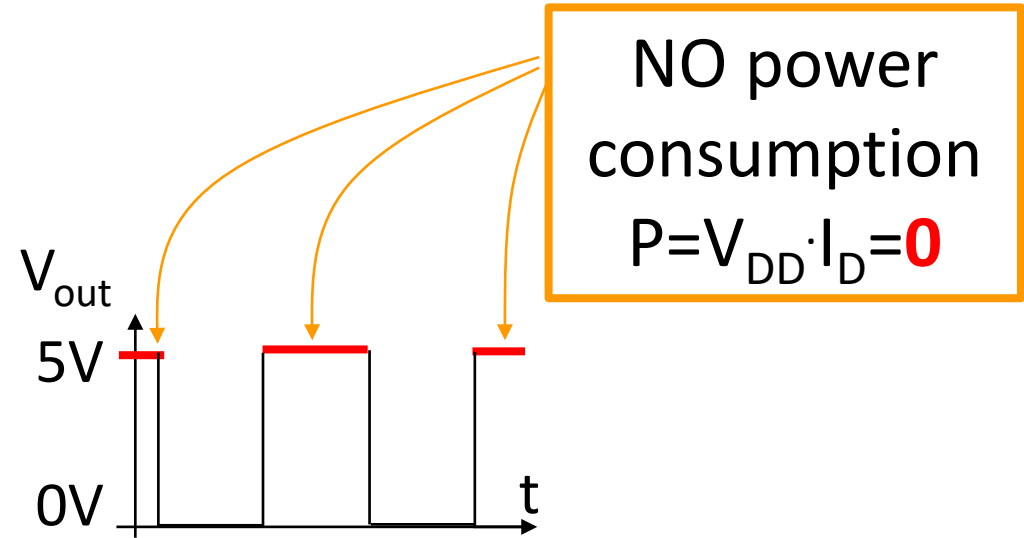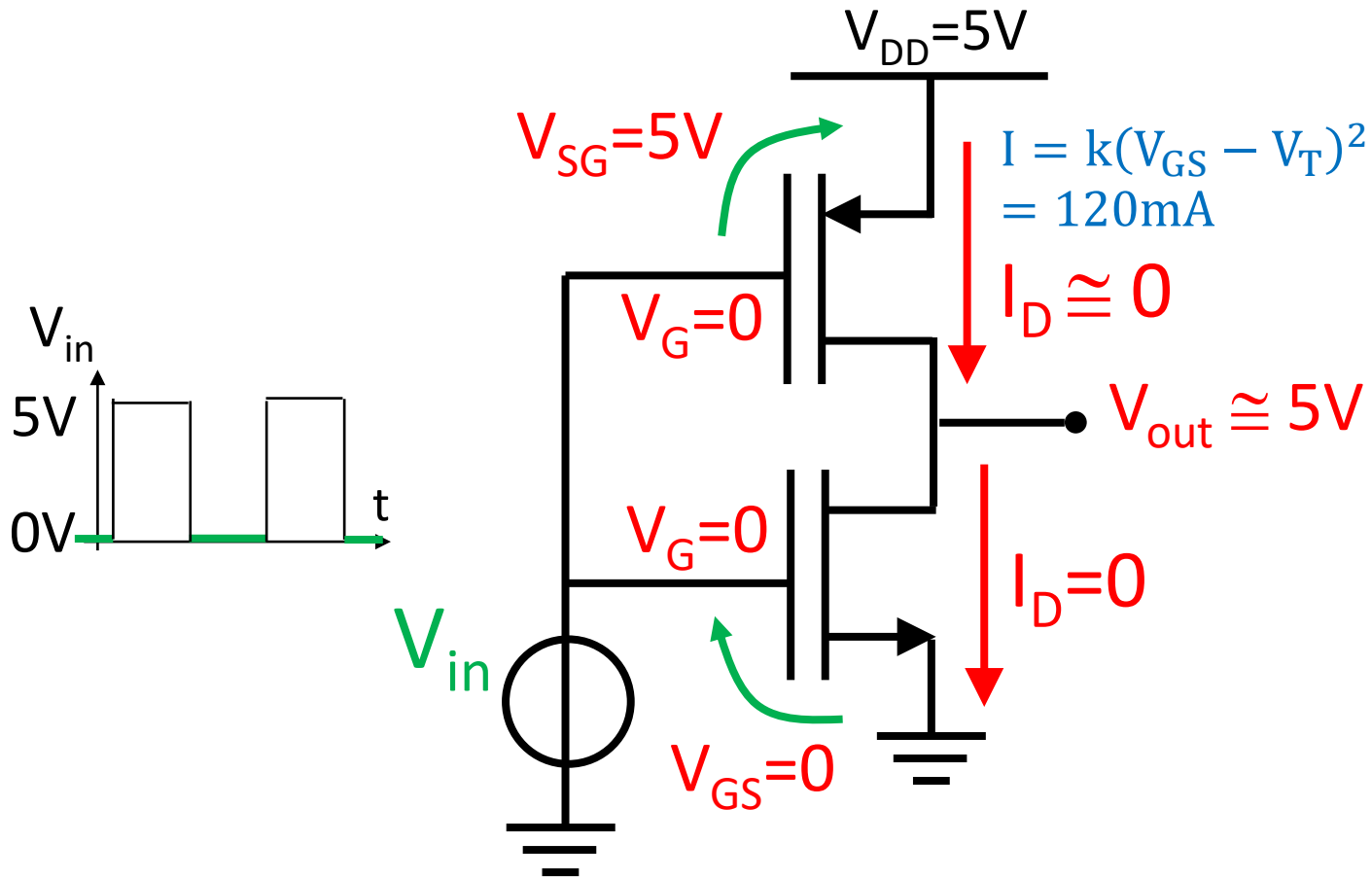



Digital input signal high (5V) - adding a pMOSFET

$V_T=0.8V$ and $K=7mA/V^2$

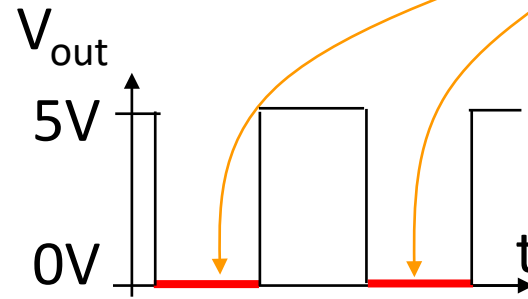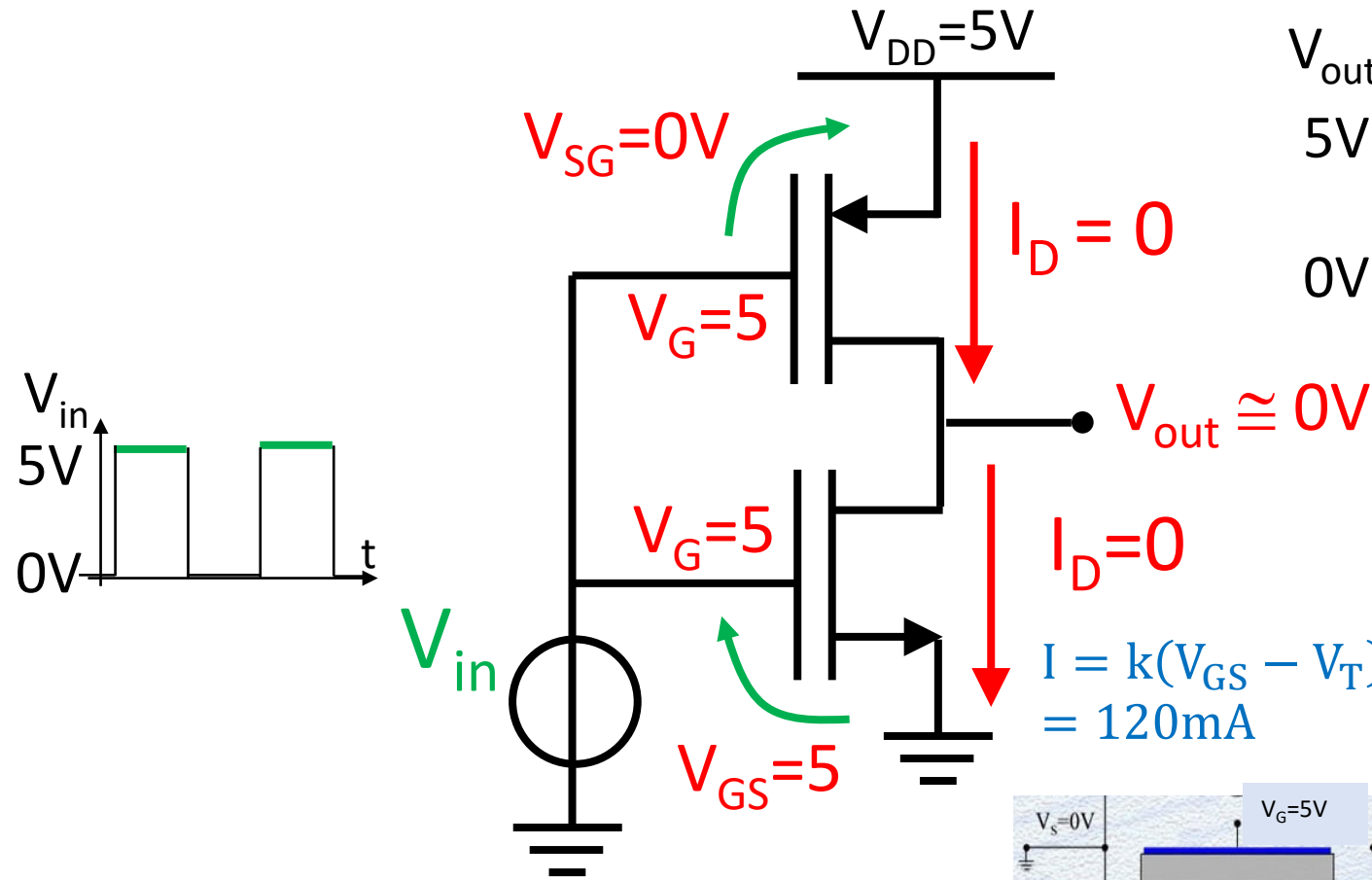


NO static power consumption
 $P=V_{DD} \cdot I_D=0$

$I = k(V_{GS} - V_T)^2$
 $= 120mA$

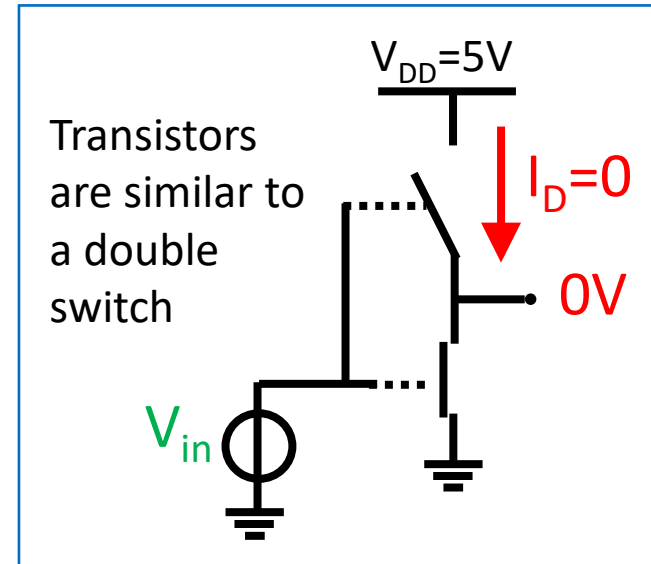
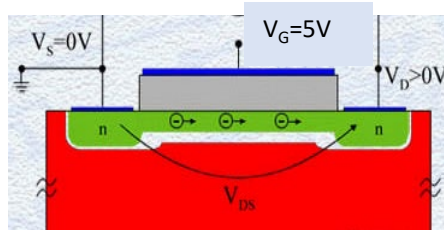


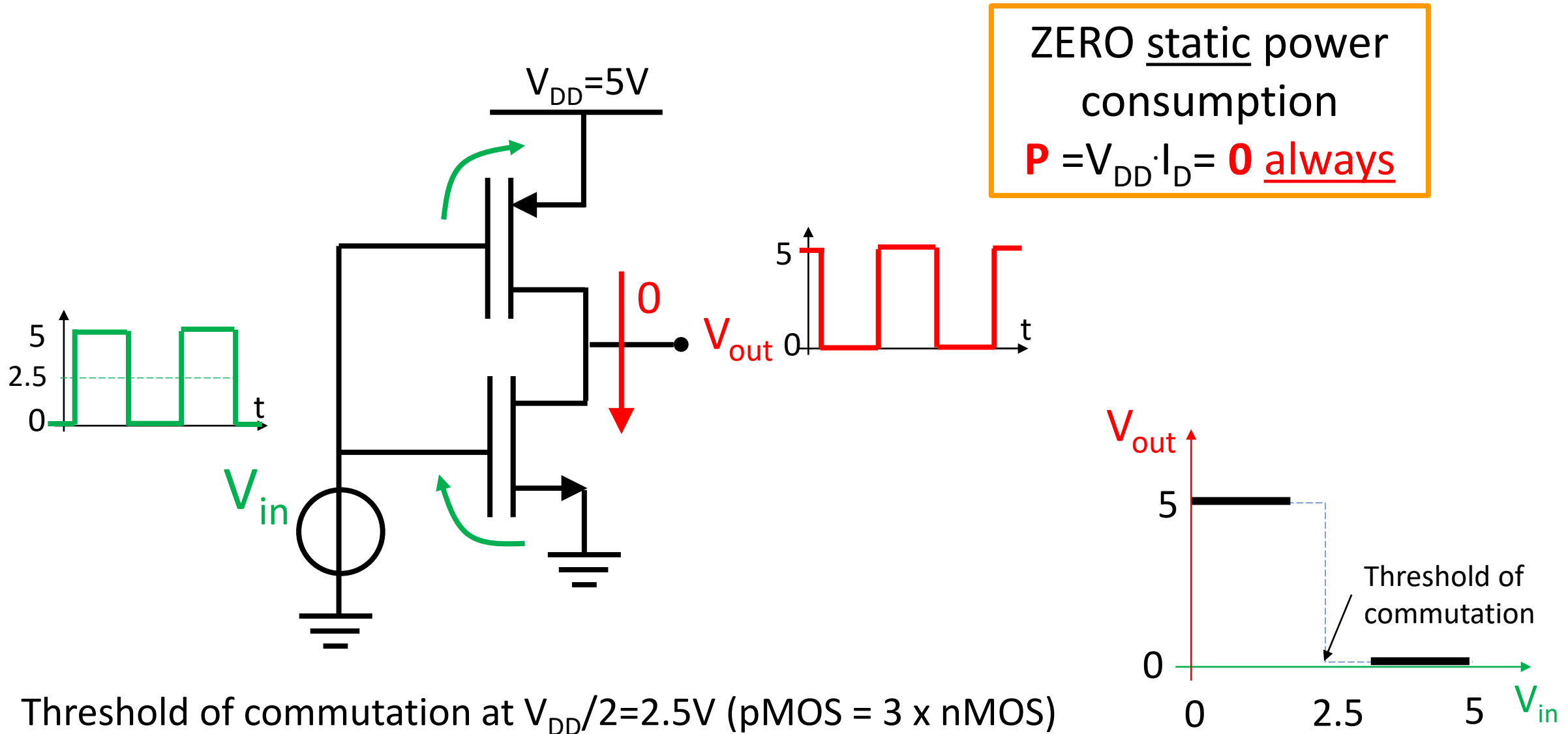The Complementary MOSFETs architecture : CMOS



The CMOS in the planar technology

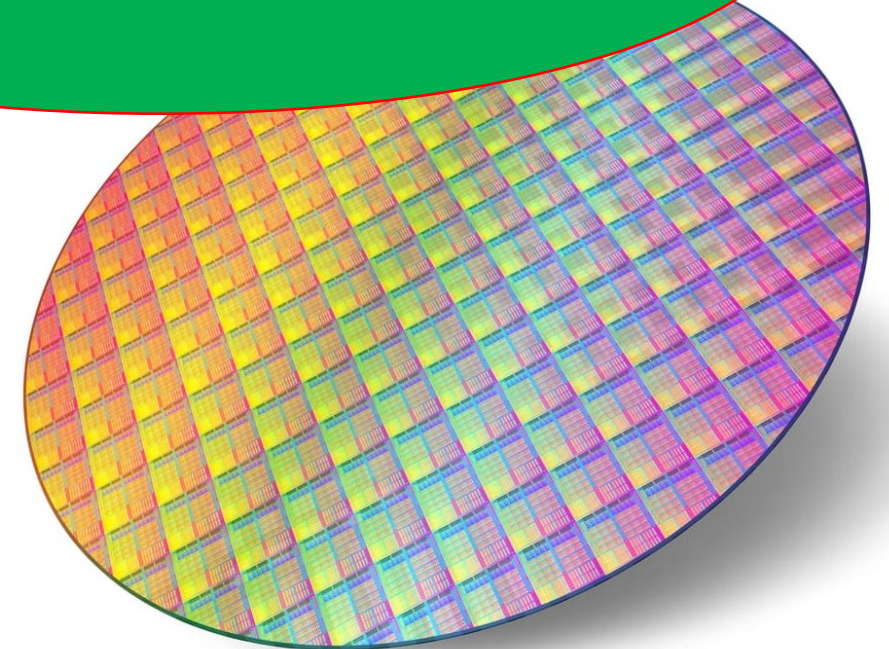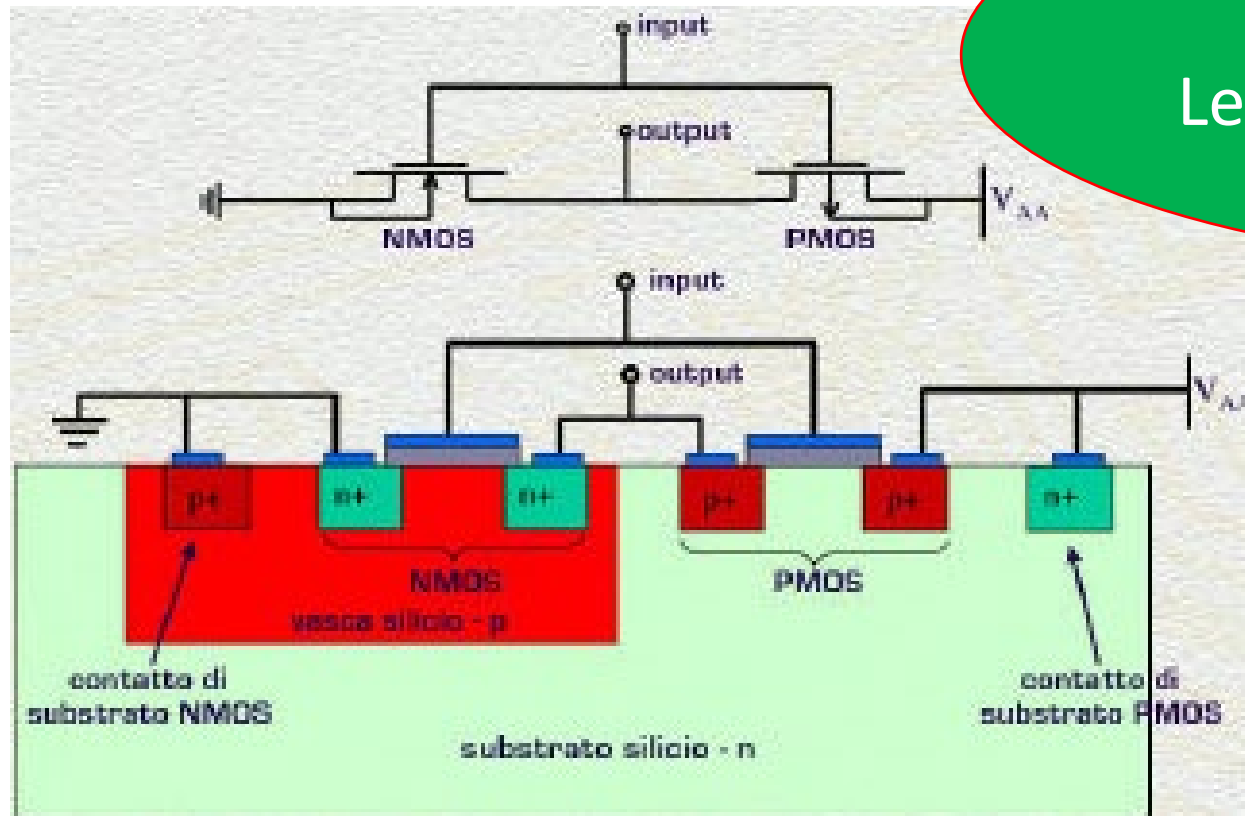Tuesday, March 15
Lesson on Planar Technology



Boolean variables and logic operations


Boolean variables
(a two values variable)

True or False
1 or 0
High or Low


Boolean Operations

negation operation (NOT)
logical product (AND) of two or more variables.
logical sum (OR) of two or more variables.

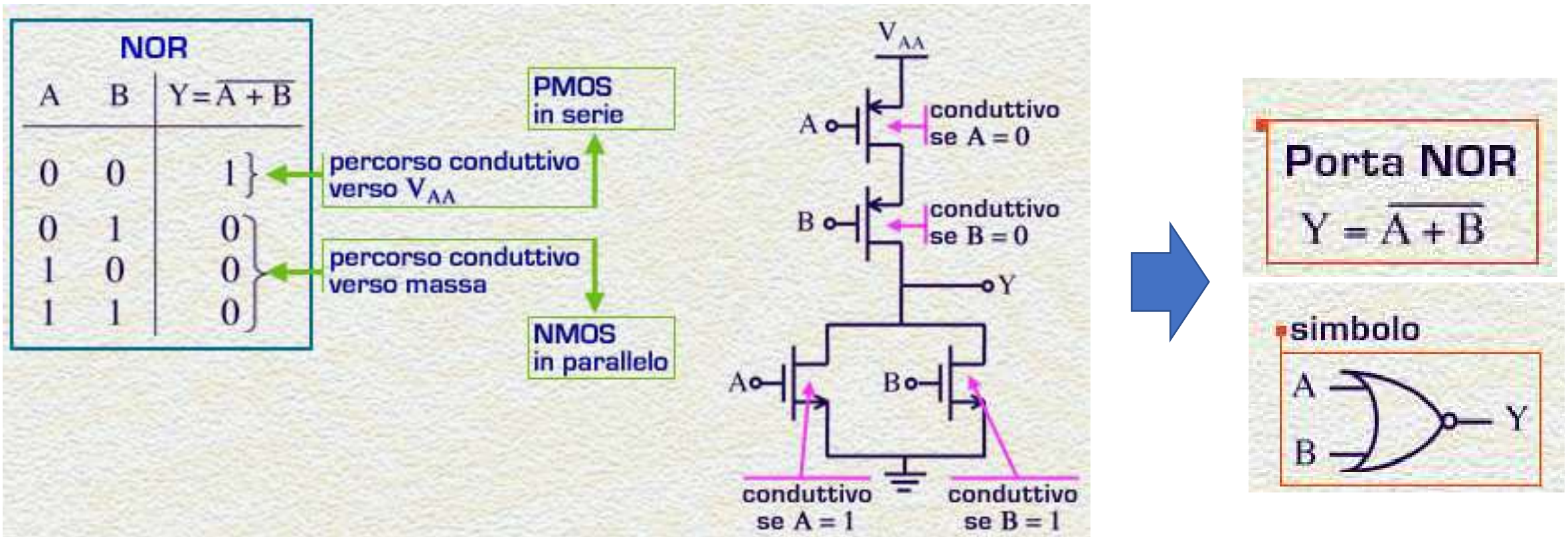
Multiple inputs Logic Gates : the NOR operation



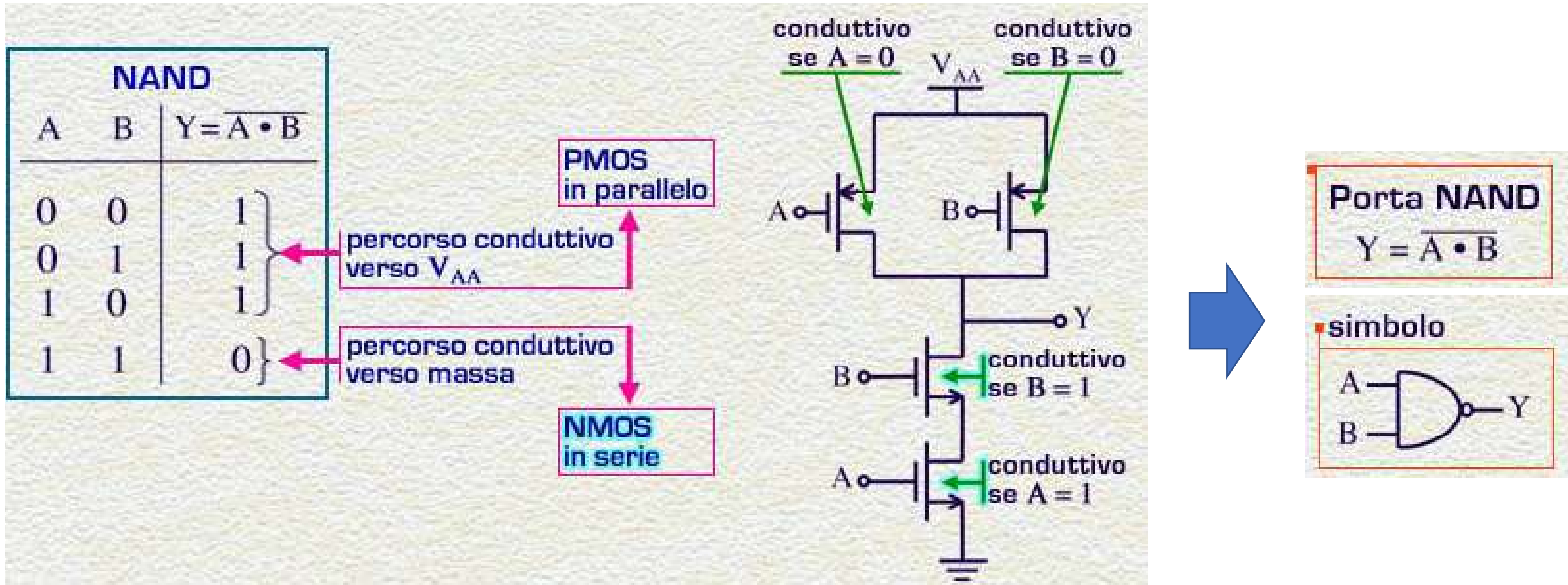Multiple inputs Logic Gates : the NAND operation



Digital Signal Processing

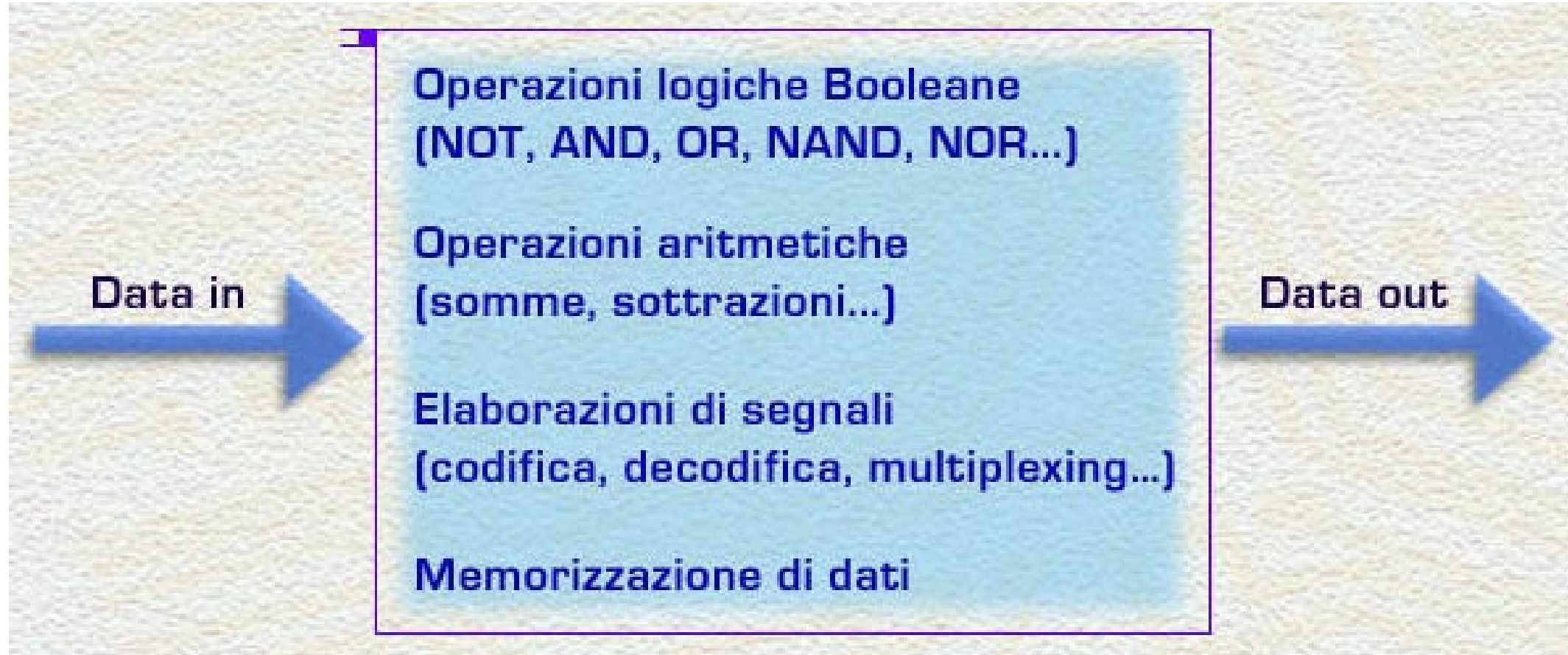

Possible subjects for Oral Presentations

European Chips Act

Chips shortage

The Silicon Valley : a case study

Comparison btwn European (STm)
and Korean (Samsung) company

The evolution of electronics in a car

The technology of electronic boards

Examples of flexible electronics

End of the lesson