

 
 


Recap : The CMOS architecture

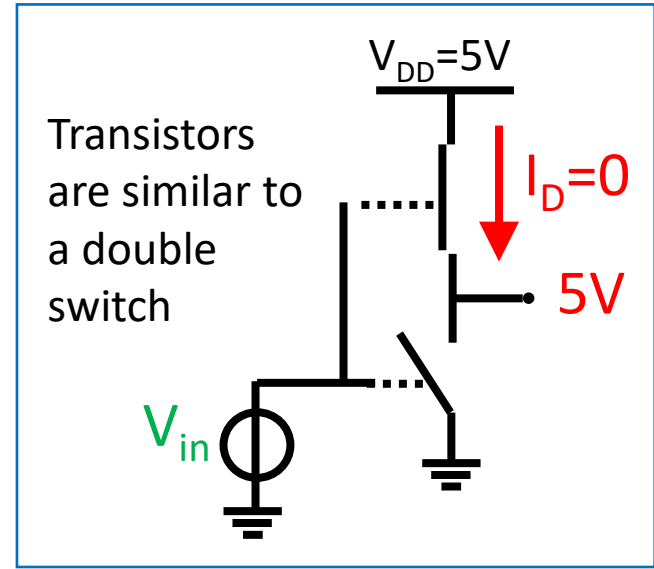

ZERO static power consumption
 $P = V_{DD} \cdot I_D = 0$

Current always = 0

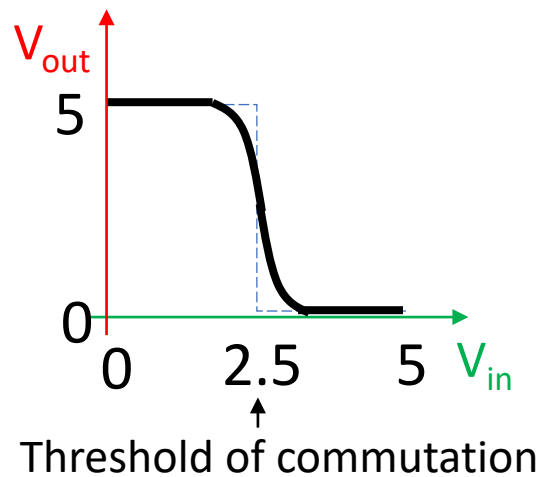


Transistors are similar to a double switch

Recap : Immunity to disturbances & reconditioning


Correct interpretation of the sequence even in the presence of a significant noise level.

High degree of immunity to disturbances

 Reconstruction of the logic levels at output to 0 volts and 5 volts !



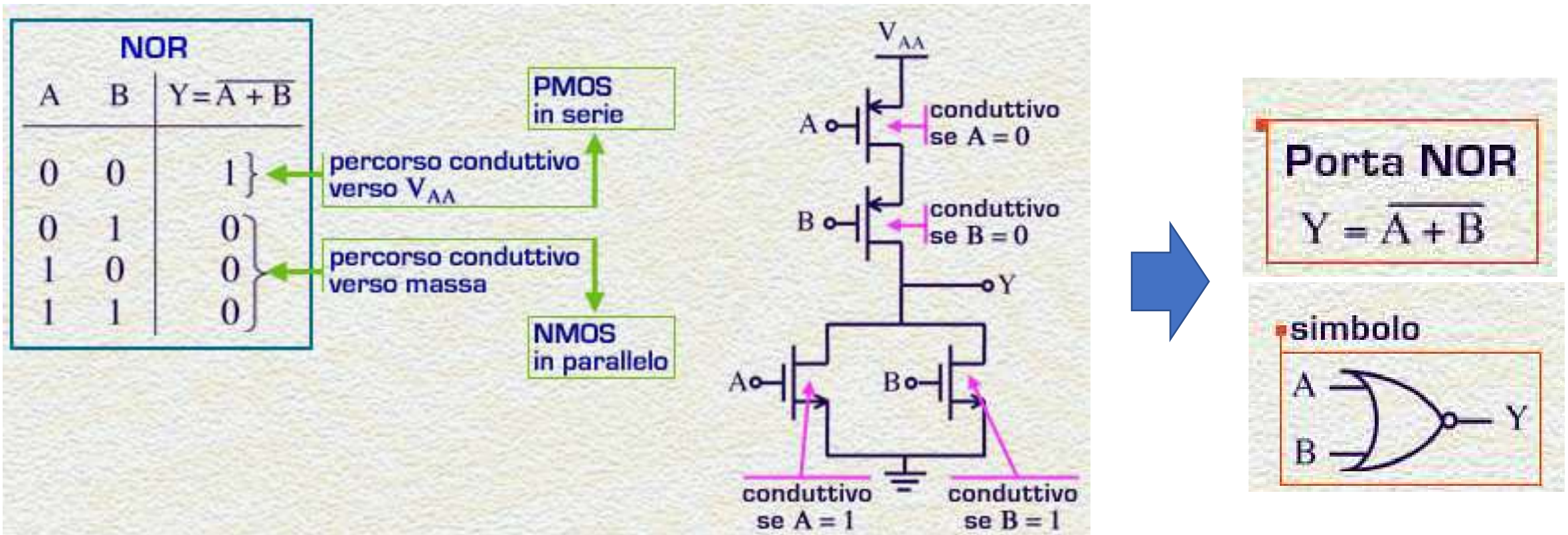CMOS gate as a building block for any Logic Circuit



ELECTRONIC SYSTEMS and TECHNOLOGIES

Master in Management Engineering

Prof. Marco Sampietro

GROUND CONCEPTS ON ELECTRONICS


Dynamics of Digital Circuits

Cascading many CMOS inverters

Output of this stage drives the following stage


ZERO static power consumption
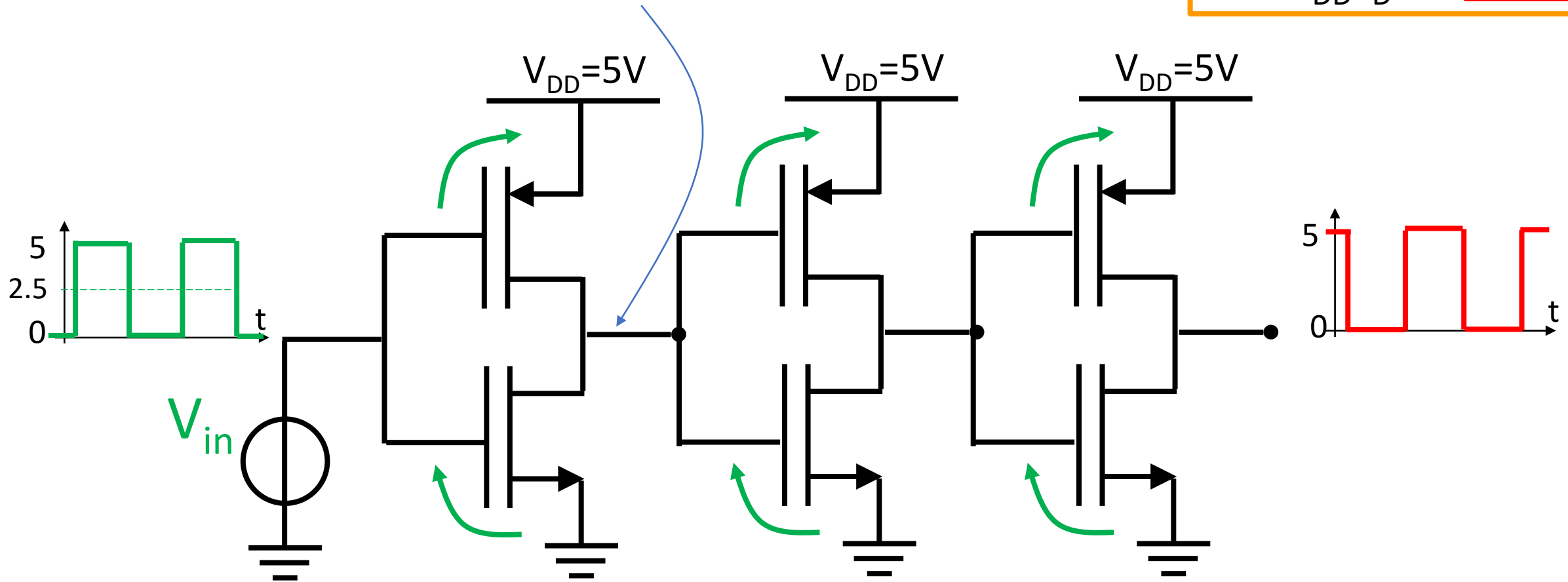
$$P = V_{DD} \cdot I_D = \mathbf{0 \text{ always}}$$





Each CMOS inverter sequentially switch to the new logical state

 A closer look to the Gate of a transistor



  The Gate of the transistor behaves like a **capacitor**




$$C = \frac{\epsilon_0 \cdot \epsilon_r}{X_{ox}} \cdot W \cdot L$$

X_{ox} is the oxide thickness


Vacuum permittivity, $\epsilon_0 = 8.854 \cdot 10^{-12} \left[\frac{Q}{V \cdot m} \right]$

SiO₂ relative permittivity, $\epsilon_r = 3.9$

 
Connections among transistors are also capacitors



 
Any metal wire is like a plate of a capacitor, the other plate being another metal around or the ground somewhere



Capacitive load of a CMOS inverter

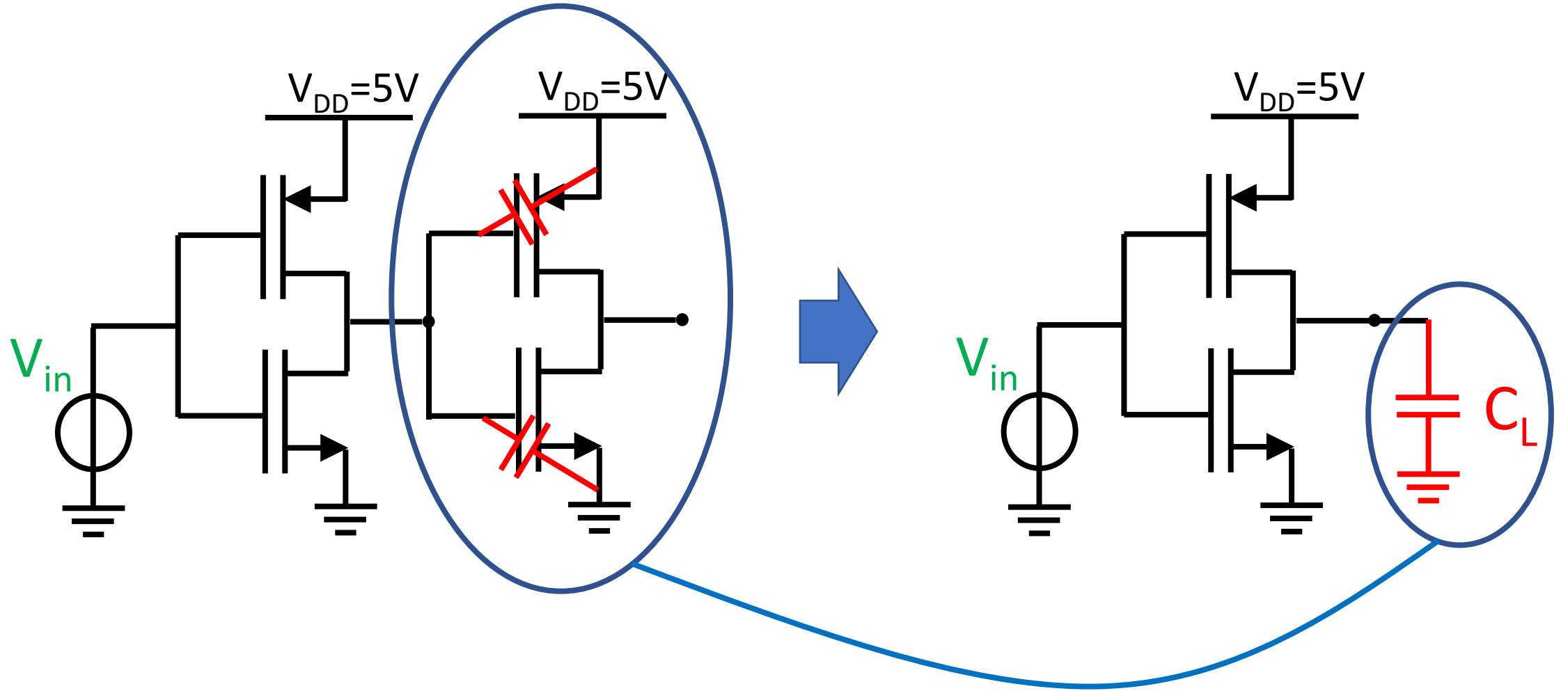

Charge-Voltage relation on a Capacitor




 


Charge Q is delivered by the current


Any node in an electronic circuit can change its voltage only when a charge is provided or removed

Dynamics of the CMOS inverter


$$V = \frac{Q}{C}$$

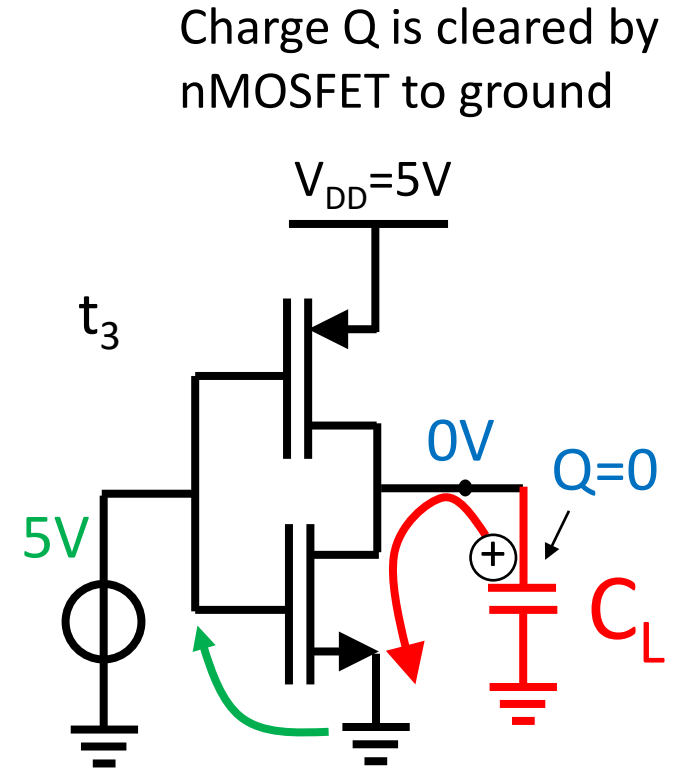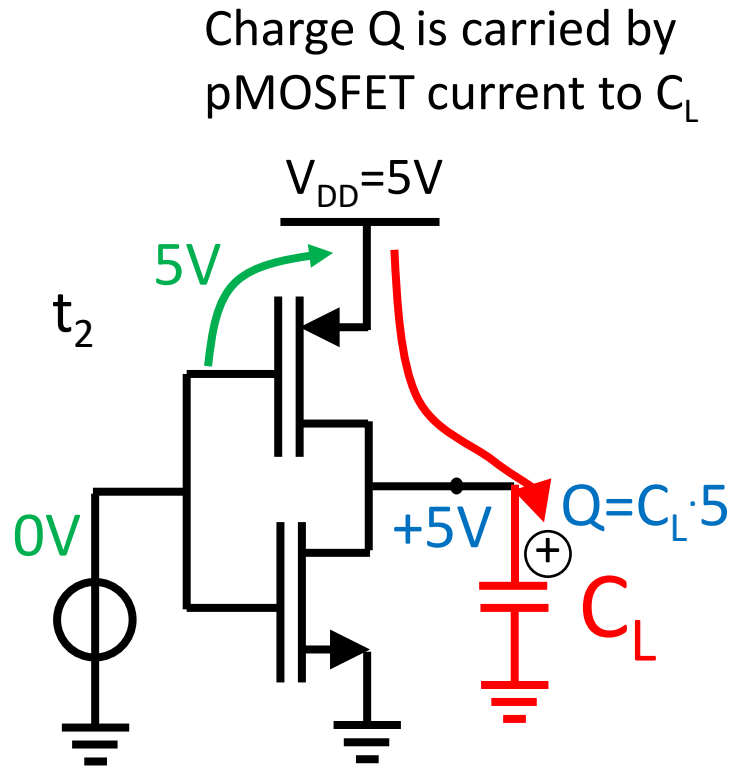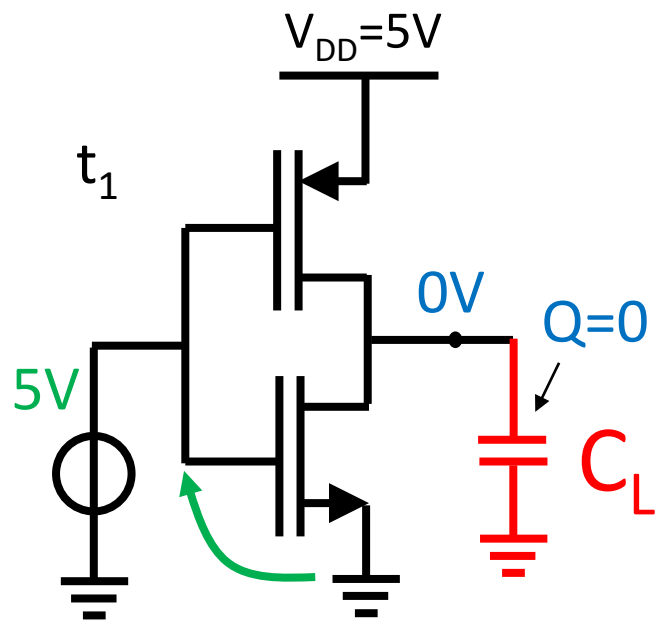 

Dinamic Power consumption of a CMOS

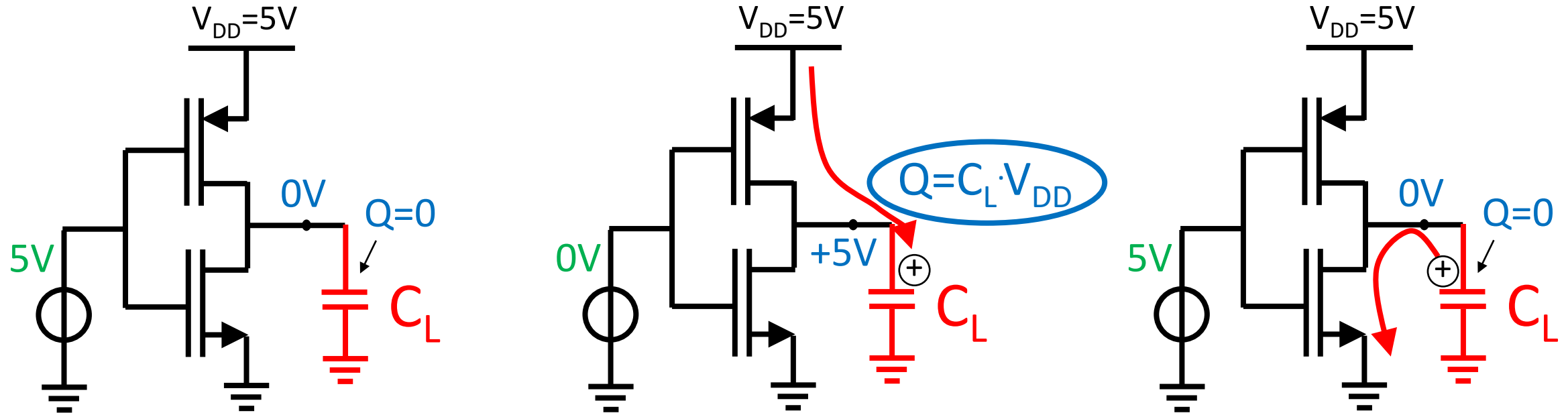

 
Charge Q started at $V_{DD}=+5V$ and finished to ground in the time of a period T_p



$$P|_{T_p} = V_{DD} \cdot \frac{Q}{T_p} = V_{DD} \cdot C \cdot V_{DD} \cdot \frac{1}{T_p} = V_{DD}^2 \cdot C \cdot f$$

How many times in 1 second? $f = \frac{1}{T_p}$

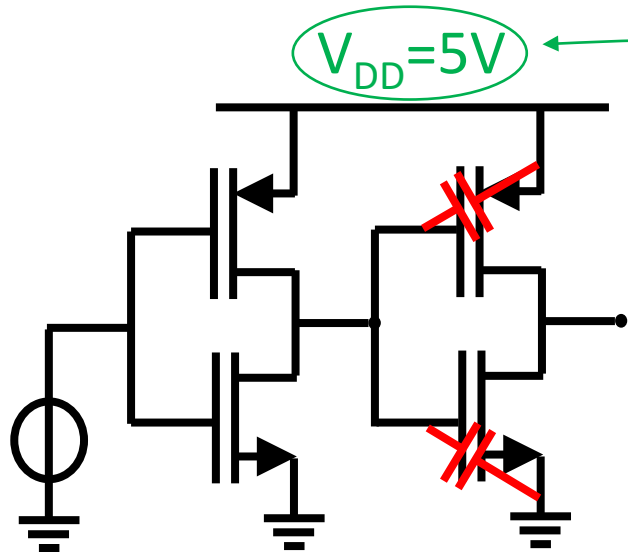Design considerations to manage Power consumption



$$P|_{T_p} = V_{DD}^2 \cdot C \cdot f$$

Big advantage in reducing Voltage Supply
5V → 3.3V → 1.9V → ...

BUT :
Reduces Noise margin
(see previous lesson)

and (see next)

CMOS with minimum dimensions
90nm → 26nm → 11nm → ...


Connections btwn CMOS
as short as possible

The total capacitance at
the Drain node to ground
is important

Linearly increase with
frequency of operation
(today 3.7GHz).

In portable computer
clock frequency can be
reduced to save power.

A trade btwn Frequency
and Power

 

Example 1

My desktop computer is more than 10 years old and uses a CPU manufactured with a 32nm technology (minimum feature size) on an oxide thickness $x_{ox}=8\text{nm}$. The CPU is powered at a Voltage Supply $V_{DD}=3.3\text{V}$ and operated at a clock frequency of $f=2.6\text{GHz}$. Find the power consumption of one single CMOS inverter.

If the CPU dissipates about 100W, how many CMOS inverters are operating at the same time ?


Example 2

Computers have not increased much the clock frequency through the years, being steady around $f_{ck}=3.8\text{GHz}$. Instead, feature size has diminished a lot, down to 6nm (with $x_{ox}=2\text{nm}$) and voltage supply is 0.9V.


How much power would consume 400 millions of digital inverters ?

Propagation time (Delay) of a logic gate

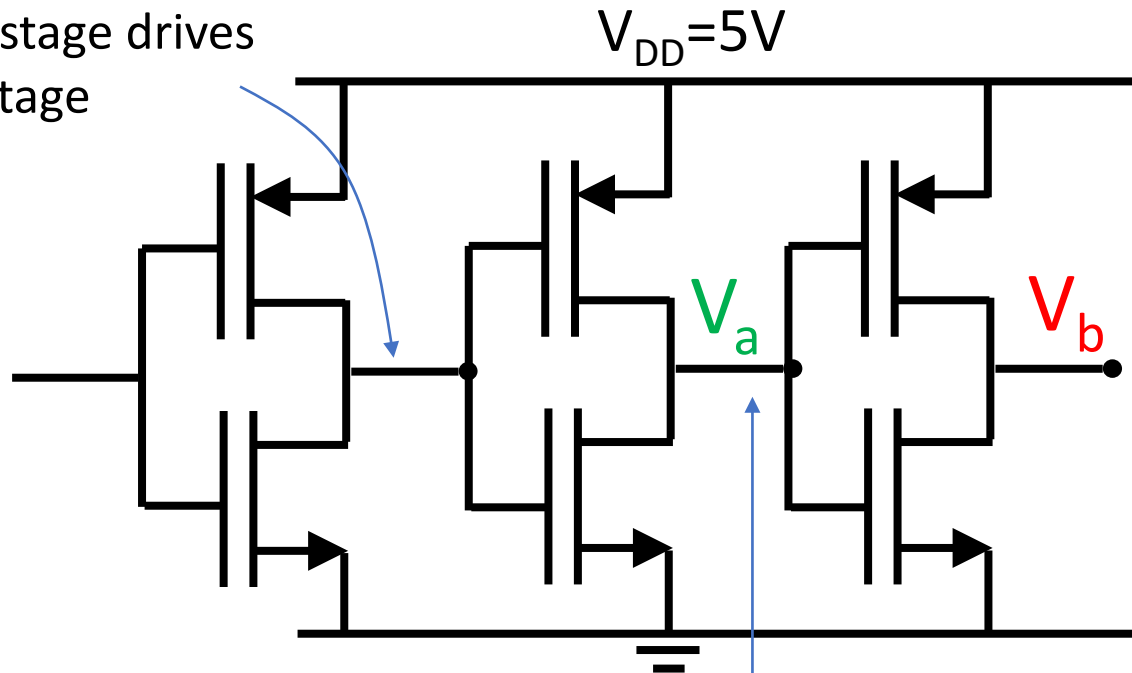Output of one stage drives the following stage





 
When $V_{DD}/2$ is reached, the next inverter has switched



Delay time t_d of the inverter

How fast is the switching ?

$$I = \frac{Q}{t}$$

 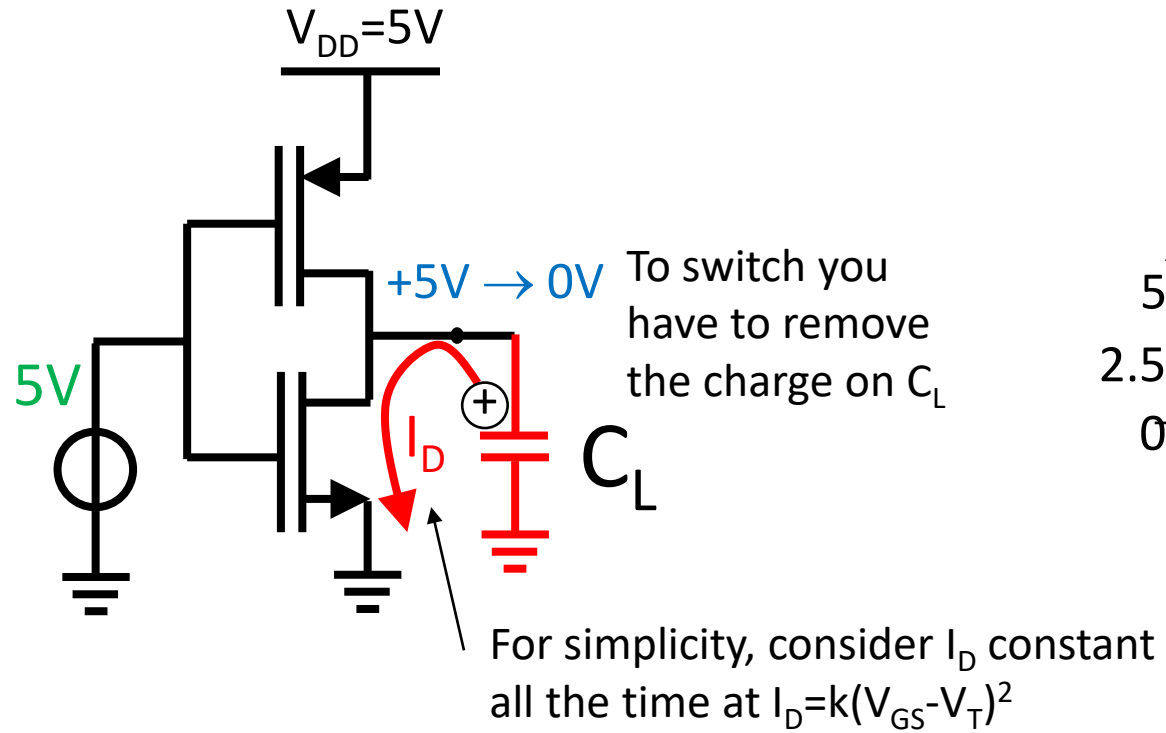 

$$t_{sw} = \frac{Q}{I_D} \approx \frac{C_L \cdot V_{DD}}{k(V_{GS} - V_T)^2} = \frac{\frac{\epsilon_{ox}}{x_{ox}} W \cdot L \cdot V_{DD}}{\frac{1}{2} \mu \frac{\epsilon_{ox}}{x_{ox}} \frac{W}{L} (V_{DD} - V_T)^2} = \frac{L^2 \cdot V_{DD}}{\frac{1}{2} \mu (V_{DD} - V_T)^2}$$

Small transistors (again)


Voltage supply NOT too small

Example 3

Let us consider again a very advanced computer having a CPU with 6nm technology (with $x_{ox}=2\text{nm}$), transistors with a threshold voltage $V_T=0.45\text{V}$ and voltage supply of 0.9V .

Estimate the switching time, t_{sw} , of each CMOS gate.
 
$$t_{sw} = \frac{Q}{I_D} = \frac{L^2 \cdot V_{DD}}{\frac{1}{2}\mu(V_{DD} - V_T)^2}$$



End of the lesson